

Verilog RTL programming self-learning text material

Logic Design Workshop

Verilog RTL programming practice

Mar. 2012

v2r04

Dr. Keijiro Hayashi


This text material covers the very basics of Verilog RTL programming.

You will be able to write RTL code by yourself after you finish this text material.

However, while you study basics of what RTL is and how to write RTL code through this text material, **you must read “Logic Design Workshop part I” to review your understandings are correct and to know details about Verilog RTL design.**

Do not think that you have got enough knowledge to design logics in RTL before you completed “Logic Design Workshop part I” .


Throughout this text material

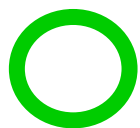

and



mean good and recommended.

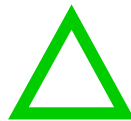

means not recommended but
allowed in certain cases.



means bad/wrong and must not be used.

RTL programming practice

———— Index ————

1. Verilog RTL

- 1.1. What is RTL
- 1.2. Simulation and synthesis
- 1.3. RTL source code structure

2. Generate arbitrary signal and observe it

- Exercise 2.1 1-bit waveform and initial
- Exercise 2.2 Procedure and racing
- Exercise 2.3 Vector waveform and initial
- Exercise 2.4 Repeated waveform and always
- Exercise 2.5 Repeated waveform and task
- Exercise 2.6 How to use implicit event
- Exercise 2.7 How to use named event
- Exercise 2.8 Observe signals periodically
- Exercise 2.9 Signals synchronized to clock
- Exercise 2.10 Clock and signal timing

3. Combinational logic and test bench

- Exercise 3.1 All-in-one module for testing 4-bit AND
- Exercise 3.2 Test bench and target module
- Exercise 3.3 Using two instances of one module
- Exercise 3.4 How to use function
- Exercise 3.5 Parameterize bit width
- Exercise 3.6 Assign for combinational logic
- Exercise 3.7 Always for combinational logic
- Exercise 3.8 Sign bit and Concatenating operator
- Exercise 3.9 Missing case item and latching
- Exercise 3.10 Compare signed data in Verilog1995
- Exercise 3.11 Arithmetic operation in Verilog1995
- Exercise 3.12 Test bench and coverage

RTL programming practice

———— Index ————

4. Flip-flops and sequential logic

- Exercise 4.1 Sequential lamps
- Exercise 4.2 Counter with limiter
- Exercise 4.3 Up down counter and STT
- Exercise 4.4 Sequential accumulator with
overflow checker
- Exercise 4.5 Automatic test bench
- Exercise 4.6 Serial bit pattern detector
- Exercise 4.7 Data change range checker
- Exercise 4.8 One byte data buffer
- Exercise 4.9 Average of sequential four
4-bit data
- Exercise 4.10 6-stage bound flasher

5. RTL coding style suitable for optimization


- Exercise 5.1 For-loop and if statement
- Exercise 5.2 On-bit-block counter

6. Advanced exercises

- Exercise 6.1 Snake game
- Exercise 6.2 LRU algorithm
- Exercise 6.3 Two ring flasher
- Exercise 6.4 Elevator
- Exercise 6.5 Asynchronous data transfer
- Exercise 6.6 Cyclic FIFO buffer

Chapter 1. Verilog RTL

1.1. What is RTL

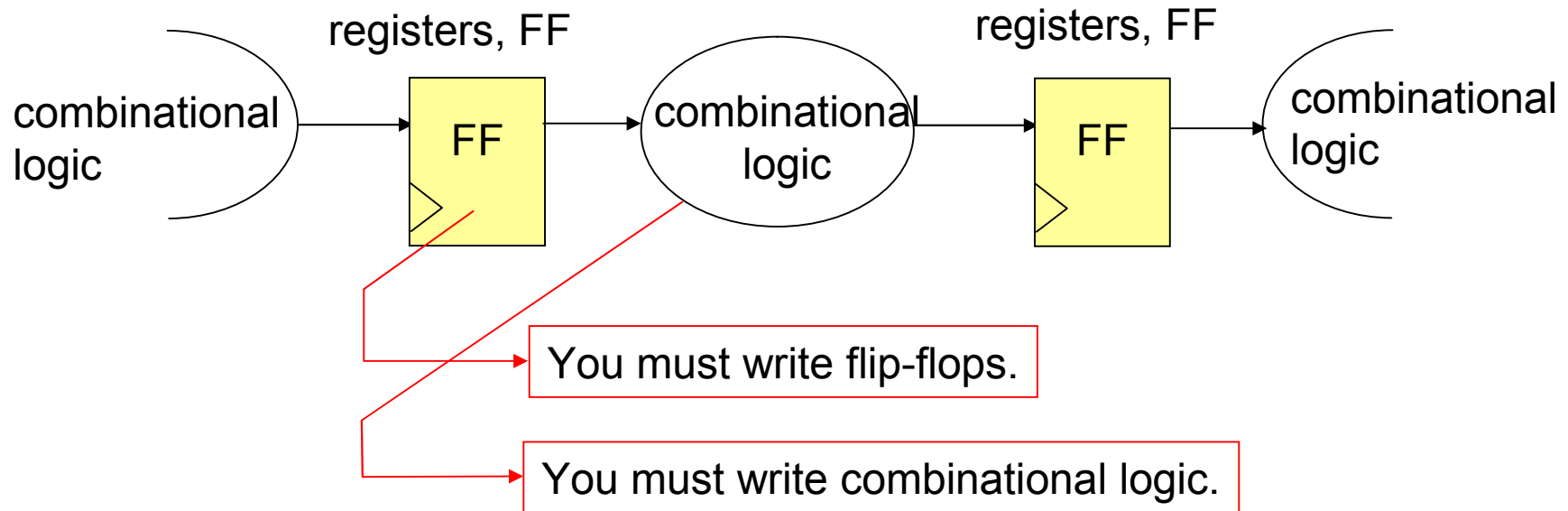


In RTL design, registers (usually they are flip-flops) and combinational logic are two major logic elements.


You have to describe them explicitly by using Verilog programming language.

The description must be written in a module as shown on the next page.

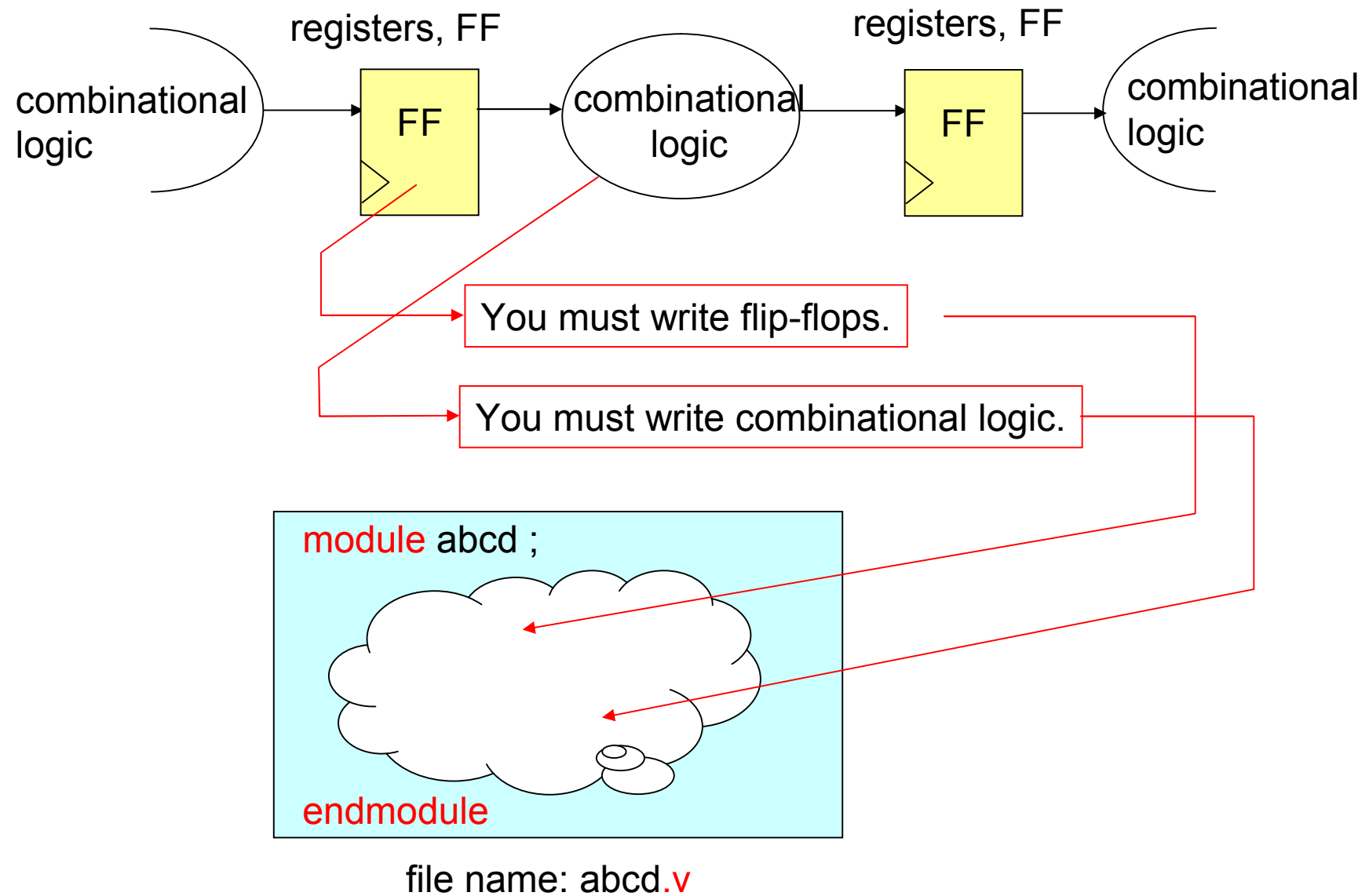RTL: Register Transfer Level
FF: Flip-Flop



1.2. Simulation and synthesis

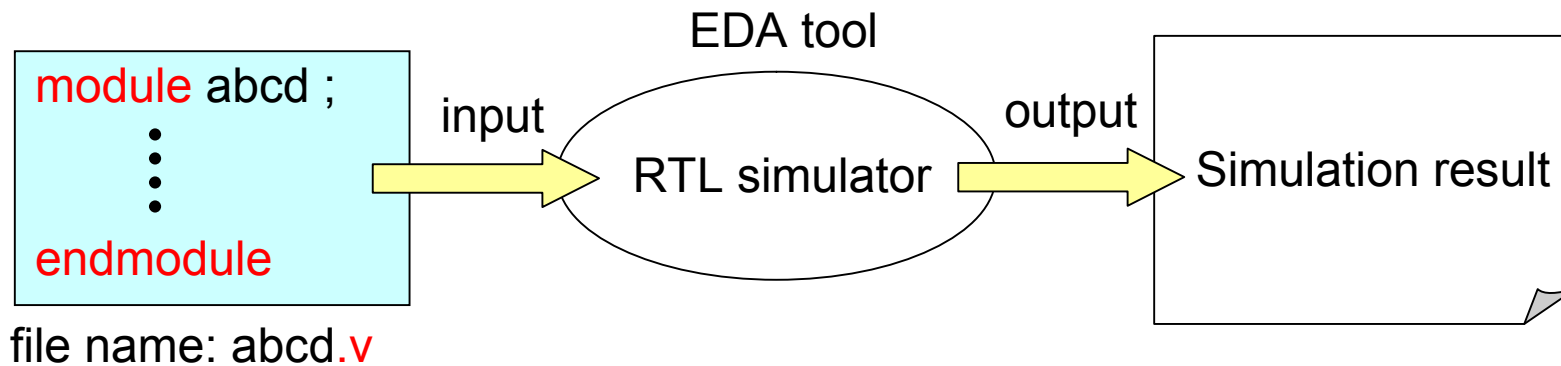

A file containing modules can be an input to an RTL simulator.

In general it is recommended to use a file name "abcd.v" for a file whose contents is a module named "abcd". If there are several modules in one file, use the module name appearing at the top of the file.

There is no concept such as "main program in C language". A simulator can automatically find out which module to execute first.

EDA: Electronic Design Automation

To run a Verilog simulation, input the file abcd.v to an RTL simulator.

Verilog RTL source file


```
module abcd ;
```

.....

```
endmodule
```

file name: **abcd.v**

Input the file to
an RTL simulator

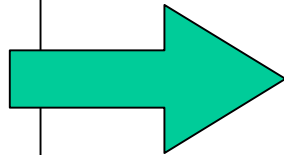

In Renesas developing environment;

```
> bs -source,,,, vcs -R abcd.v
```

VCS activating command

When using a free RTL simulator, cver ;

```
> cver abcd.v
```

cver activating command

VCS: Verilog simulator made by Synopsys

RTL programming rules

(1) Give everything a **meaningful name**. Do not give name such as temp1, temp2, ..., ST1, ST2, ..., etc. Use names such as mem_rd_strb.


(2) If a module in a file has a name **abcd**, the file name must be **abcd.v**.


If there are several modules in a file, name the file using the module's name which appears at the top of the file.

(3) Do not append version/revision number to a module name. Version/revision number can be given in a file name.

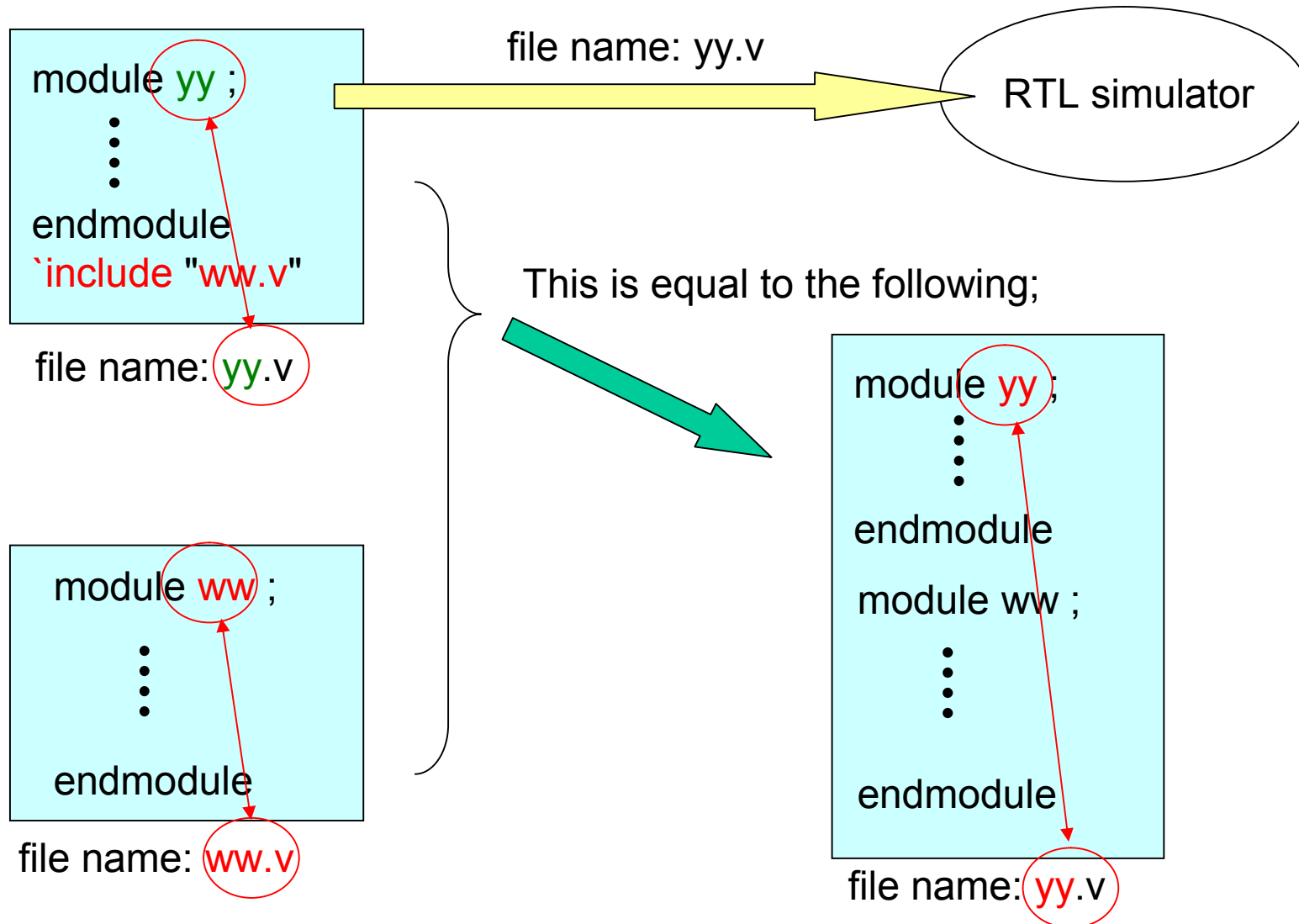
Example; module name abcd, file name abcd_v1r3.v

We can use compiler directive, ``include`, where ``` is a grave accent, to incorporate other files as shown below.



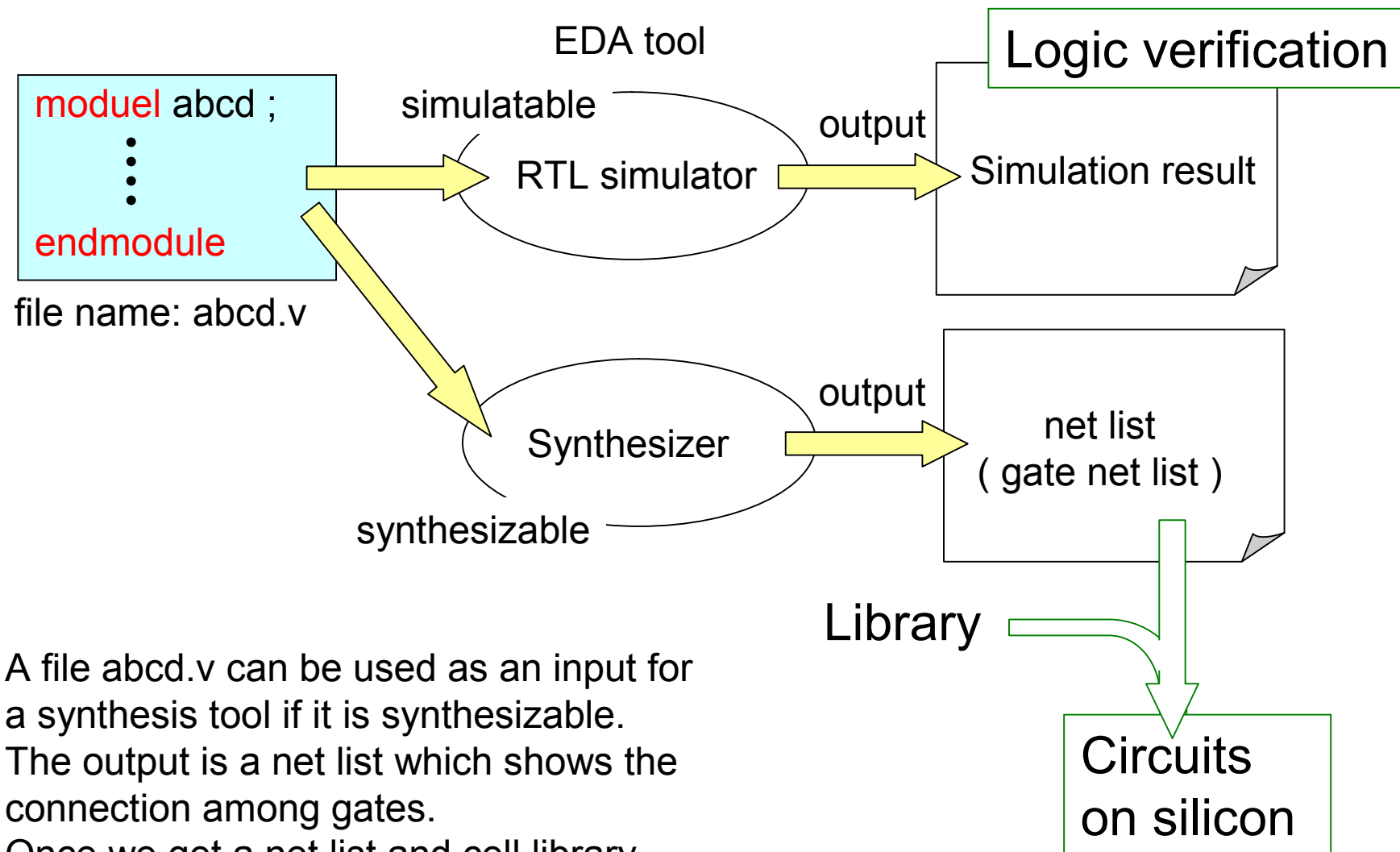

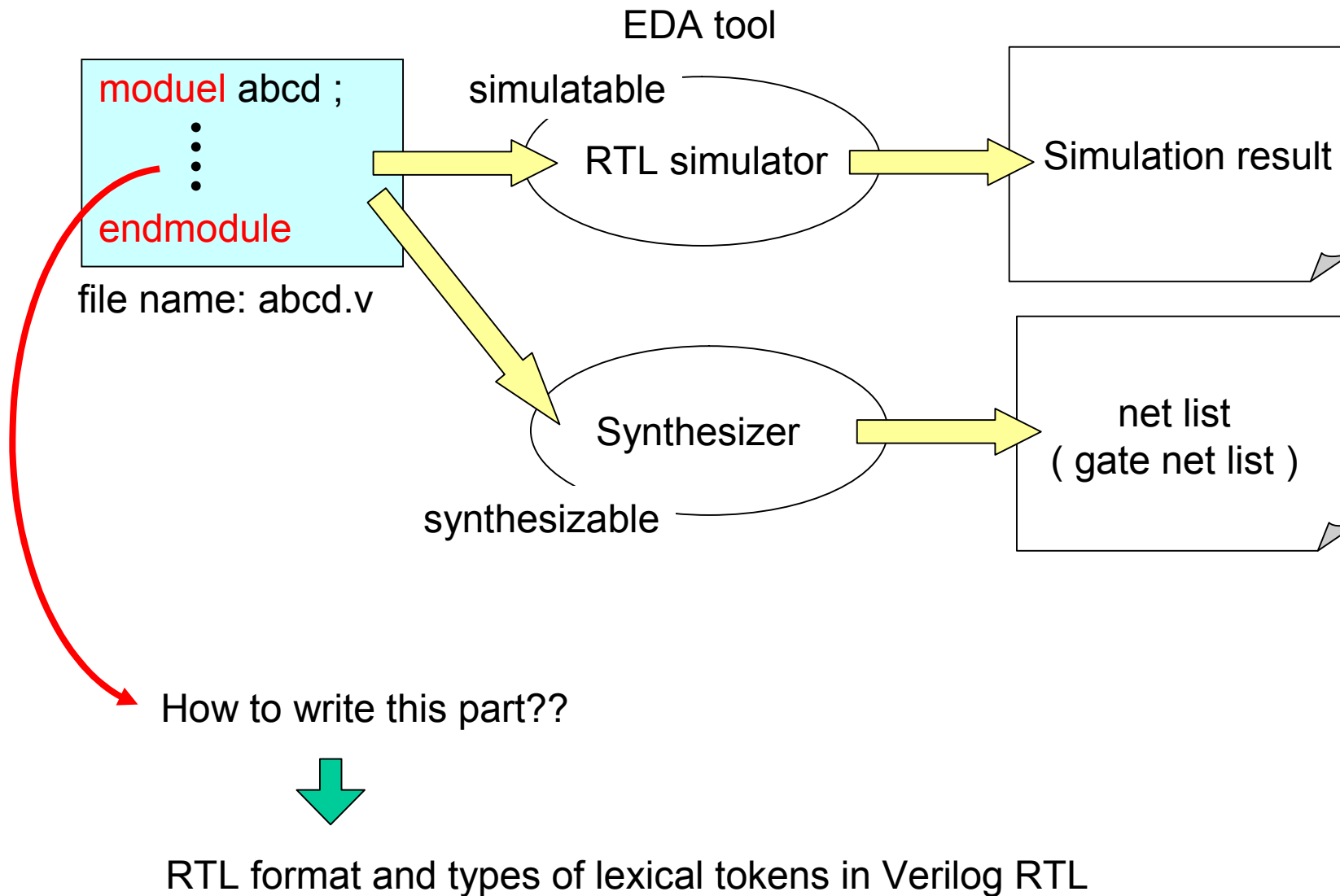A file abcd.v can be used as an input for a synthesis tool if it is synthesizable. The output is a net list which shows the connection among gates. Once we get a net list and cell library data, we can create a mask pattern for the module abcd.




1.3. RTL source code structure

An RTL source code consists of sequence of tokens.

Format: **free format**

Position has no meaning.


$a = b ;$
 $a = \quad b ;$

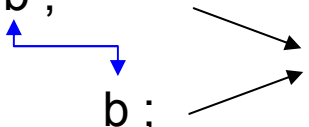

same


Sequence matters.

$a = b ;$
 $b = \quad a ;$

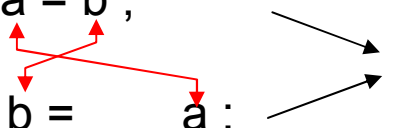

different

$a = b + c ;$

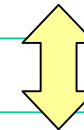

equivalent


c
 $a ; = b +$

The types of lexical tokens:

Identifier, comment, space, numbers, etc.


The types of lexical tokens:

Type	description	comment
White space	Characters for spaces, tabs, newlines, and formfeeds. These characters shall be ignored except when they serve to separate other lexical tokens.	Blanks and tabs shall be considered significant characters in strings.
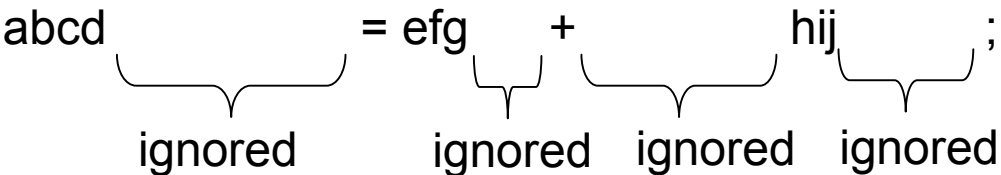
`abcd = efg + hij ;`


This sentence can be disintegrated into abcd, =, efg, +, hij, and ; using lexical tokens, =, +, and ;.

For this line, spaces are not needed to separate abcd, efg, and hij.
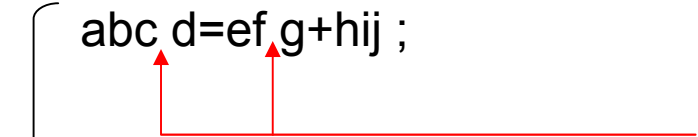
`abc d=ef g+hij ;`


These spaces are not ignored.
Therefore, this statement is illegal.

different

`abcd=efg+hij ;`

The types of lexical tokens:

Type	description	comment
Comment	A one-line comment shall start with the two characters // and end with a newline. A block comment shall start with /* and end with */. Block comments shall not be nested.	Do not use a block comment.

/* do not use
this block comment because
it is not clear that this line is a comment or not

*/

// this is comment line
// use one-line comment is recommended
// because it is very clear that this line is a comment

The types of lexical tokens:

Type	description	comment
Operator	Perform specific manipulation over the operand(s).	Operators are single-, double-, or triple-character sequences.

sig_a = yy **+** in_a ; add operator

if (a **==** b) begin equality operator

>>> arithmetic shift right operator

The types of lexical tokens:

Type	description	comment
Number	Constant numbers can be specified as integer constants or real constants.	

64	integer, signed
2.3	real
16'hFF05	16-bit hexa, unsigned
8'b0101_1100 ;	8-bit binary, unsigned
4'sb1101	4-bit binary, signed This is equal to decimal -3.

The types of lexical tokens:

Type	description	comment
String	A string is a sequence of characters enclosed by double quotes (" ") and contained on a single line.	Strings used as operands shall be treated as unsigned integer constants represented by a sequence of 8-bit ASCII values.

"abcd efg" ← OK

"abcd
efg" ← NG

Use `\n` as shown below if you want to make it appear as two lines.

"abcd `\n` efg"

Note: `\` is the same to back slash (\).

sig_y = sig_w + "ab" ;



sig_y = sig_w + 16'h6162 ;

ASCII: American Standard Code for Information Interchange

The types of lexical tokens:

Type	description	comment
Identifier	An identifier is used to give an object a unique name so it can be referenced. An identifier is either a simple identifier or an escaped identifier. A simple identifier shall be any sequence of letters, digits, dollar signs (\$), and underscore characters (_).	The first character of a simple identifier shall not be a digit or \$; it can be a letter or an underscore. Identifiers shall be case sensitive.

sig_abc ————— simple identifier

\sig_abc
 }
 \ab+cd ————— escaped identifier

~~\$sig_abc~~

~~8to4converter~~

converter8to4

Do not use escaped identifier.


About escape

Do not use escaped identifier.

abcd+efgh ← This can not be an identifier because
“+” is a Verilog keyword.


\abcd+efgh ← This can be an identifier because escape
character is attached at the beginning.

\abcd+efgh = abcd+efgh; space



The signal named abcd+efgh is equal to abcd + efgh.

\abcd+efgh=abcd+efgh; No space



This is a signal named abcd+efgh=abcd+efgh; .

The types of lexical tokens:

Type	description	comment
Keyword	Keywords are predefined nonescaped identifiers that are used to define the language constructs.	A Verilog HDL keyword preceded by an escape character is not interpreted as a keyword.

Keywords are shown on the next page.

They are reserved to define the language constructs therefore we can not use them in the other context than they are supposed to be used.

HDL: Hardware Description Language


Verilog2001 (keywords)

always, and, assign, automatic,
begin, buf, bufif0, bufif1,
case, casex, casez, cell, cmos, config,
deassign, default, defparam, design, disable,
edge, else, end, endcase, endconfig, endfunction, endgenerate, endmodule,
endprimitive, endspecify, endtable, endtask, event,
for, force, forever, fork, function,
generate, genvar,
highz0, highz1,
if, ifnone, incdir, include, initial, inout, input, instance, integer,
join, large,
liblist, library, localparam,
macromodule, medium, module,
nand, negedge, nmos, nor, noshowcancelled, not, notif0, notif1,
or, output,
parameter, pmos, posedge, primitive, pull0, pull1, pulldown, pullup,
pulsestyle_oneevent, pulsestyle_ondetect,
rcmos, real, realtime, reg, release, repeat, rmos, rpmos, rtran, rtranif0, rtranif1,
scalared, showcancelled, signed, small, specify, specparam,
strong0, strong1, supply0, supply1,
table, task, time, tran, tranif0, tranif1, tri, tri0, tri1, triand, trior, trireg,
unsigned, use, uwire,
vectored,
wait, wand, weak0, weak1, while, wire, wor,
xnor, xor

RTL programming rules

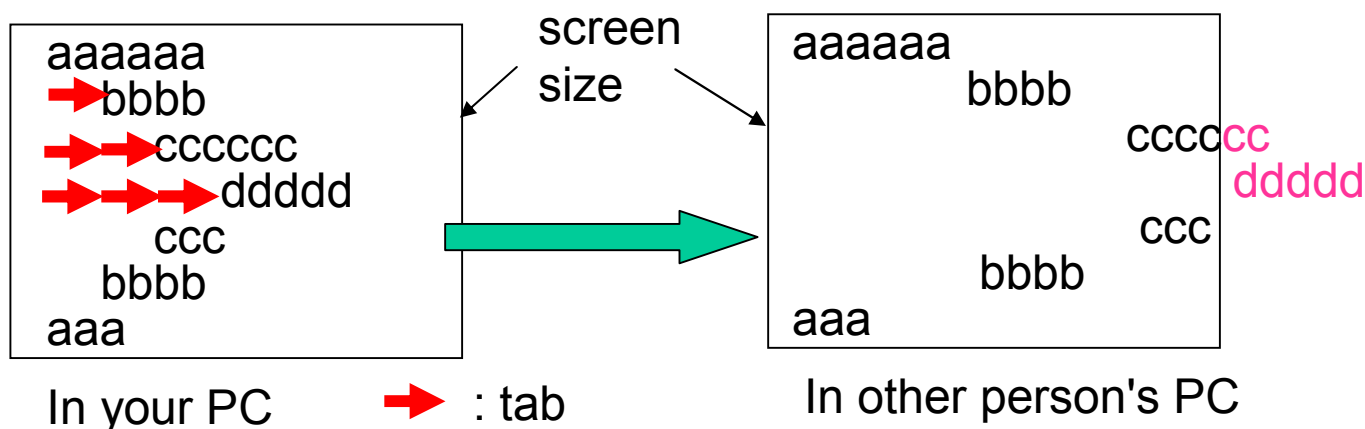- (1) Do not use tab for indentation. **Use 2 spaces for indentation.**
- (2) Write **header information** to show general description of the module, author name, creation date, updated date and reasons, etc.
- (3) Give comments using one line comment (//) so that other engineers can easily understand the code.
- (4) Write a related code lines in one place. Do not scatter them in different places.

Tab settings are different from PC to PC. Even if your code using tabs looks beautiful in you PC, it may be very hard to see in other's PC.



module

```
module xxx ( , , , );
```

```
port declaration
```

```
data type declaration
```

```
m_abc m_abc_01( , , , );
```

```
assign , , , = , , , ;
```

```
function xxx ;  
endfunction
```

```
assign , , , = , , , ;
```

```
always , , , , begin  
end
```

```
assign , , , = , , , ;
```

```
assign , , , = , , , ;
```

```
m_efg m_efg_01( , , , );
```

```
always , , , , begin  
end
```

```
m_abc m_abc_02( , , , );
```

```
task xxx ;  
endtask
```

```
assign , , , = , , , ;
```

```
initial begin  
end
```

```
always , , , , begin  
end
```

```
endmodule
```

```
module xxx ( , , , );
```

```
port declaration
```

```
data type declaration
```

```
assign , , , = , , , ;
```

```
always , , , , begin  
end
```

```
assign , , , = , , , ;
```

```
m_abc m_abc_01( , , , );
```

```
m_abc m_abc_02( , , , );
```

```
always , , , , begin  
end
```

```
m_efg m_efg_01( , , , );
```

```
assign , , , = , , , ;
```

```
task xxx ;  
endtask
```

```
assign , , , = , , , ;
```

```
function xxx ;  
endfunction
```


assign, function, task, always, and initial can go to any place in a module. However, do not scatter them randomly. Code lines doing similar job must be placed near by each other.

RTL programming rules


assign, function, task, always, and initial can go to any place in a module but the following places **are not allowed**.

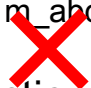- (1) procedures can not be declared in a procedure,
- (2) modules can not be instantiated in a procedure,
- (3) continuous assign, except procedural continuous assign, must not appear in procedures.


```
always ,,,, begin
  always ,,,, begin
  end
end
```




```
function xxx ;
  m_abc m_abc_01( ,,, ) ;
endfunction
```



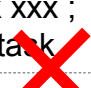
```
initial ,,,, begin
  task xxx ;
  endtask
end
```



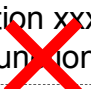
```
always ,,,, begin
  function xxx ;
  endfunction
end
```




```
function xxx ;
  assign ,,, = ,,,, ;
endfunction
```



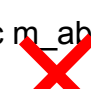
```
initial ,,,, begin
  m_abc m_abc_02( ,,, ) ;
end
```




```
always ,,,, begin
  m_abc m_abc_01( ,,, ) ;
end
```



```
task xxx ;
  always ,,,, begin
  end
endtask
```



```
module ,,,, ;
  module xxx ;
  endmodule
endmodule
```

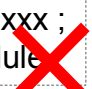

Chapter 2. Generate arbitrary signal and observe it

To verify Verilog RTL code using an RTL simulator, we need to input signals to the module under test and observe the output of the module to check if the code works correctly.

In this chapter, we will learn how to write RTL code to generate arbitrary signals and techniques to observe those signals. We do not care if the code is synthesizable or not because it does not go into silicon.

Verilog world has only 1 and 0 (and Hi-z) therefore we can not generate a waveform shown in Fig.1. We can only generate a waveform shown in Fig. 2.

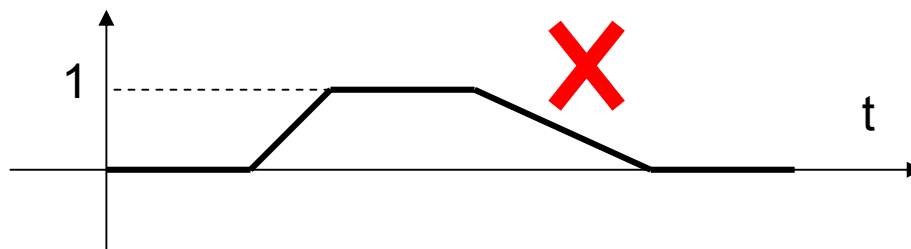


Fig.1 Waveform unable to generate


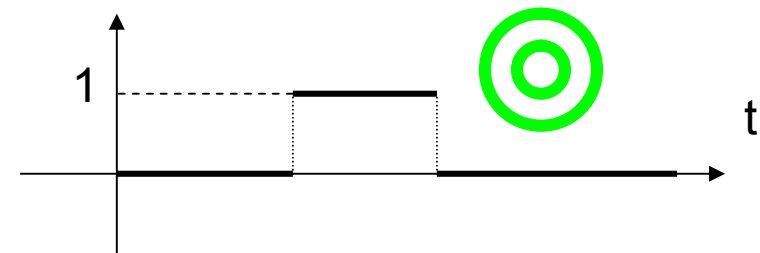



Fig.2 Waveform possible to generate

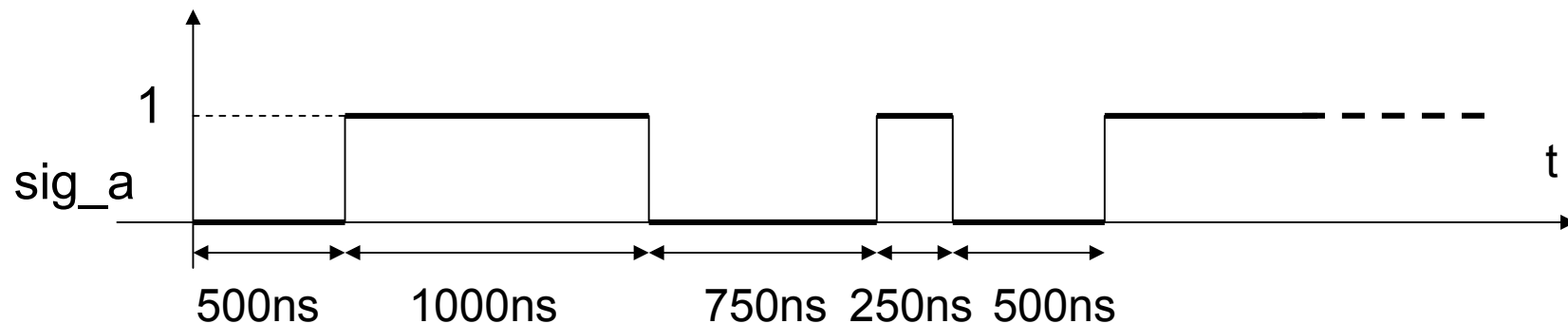Ex 2-1. 1-bit waveform and initial: Write a logic block to generate and observe a signal (sig_a) of which waveform is shown below.



To create a signal which does not repeat the same pattern, we can use **initial construct** which is **executed only once** by a simulator. To observe signals and display the values of them on a terminal, we can use a system task **\$monitor**. It watches signals once it is activated, and if any change of watching signals are detected, it output message onto a terminal screen.

To set initial values, we can use “**initial construct**” as below.
In RTL simulation, an initial construct is **executed only once at time 0**.
And if there are several initial constructs, they are all executed at time 0.



```
initial sig_a = 0 ; // in_a becomes 0 at time 0
initial sig_b = 1 ; // in_b becomes 1 at time 0
```


Executed only once at time 0.

The value of sig_a, before it is given the value 0, is x (unknown).

By using **delay**, specified by **#**, we can delay the execution of the assignment as below;


```
initial #10 sig_a = 0 ; // in_a becomes 0 at time 10
initial #20 sig_b = 1 ; // in_b becomes 1 at time 20
```

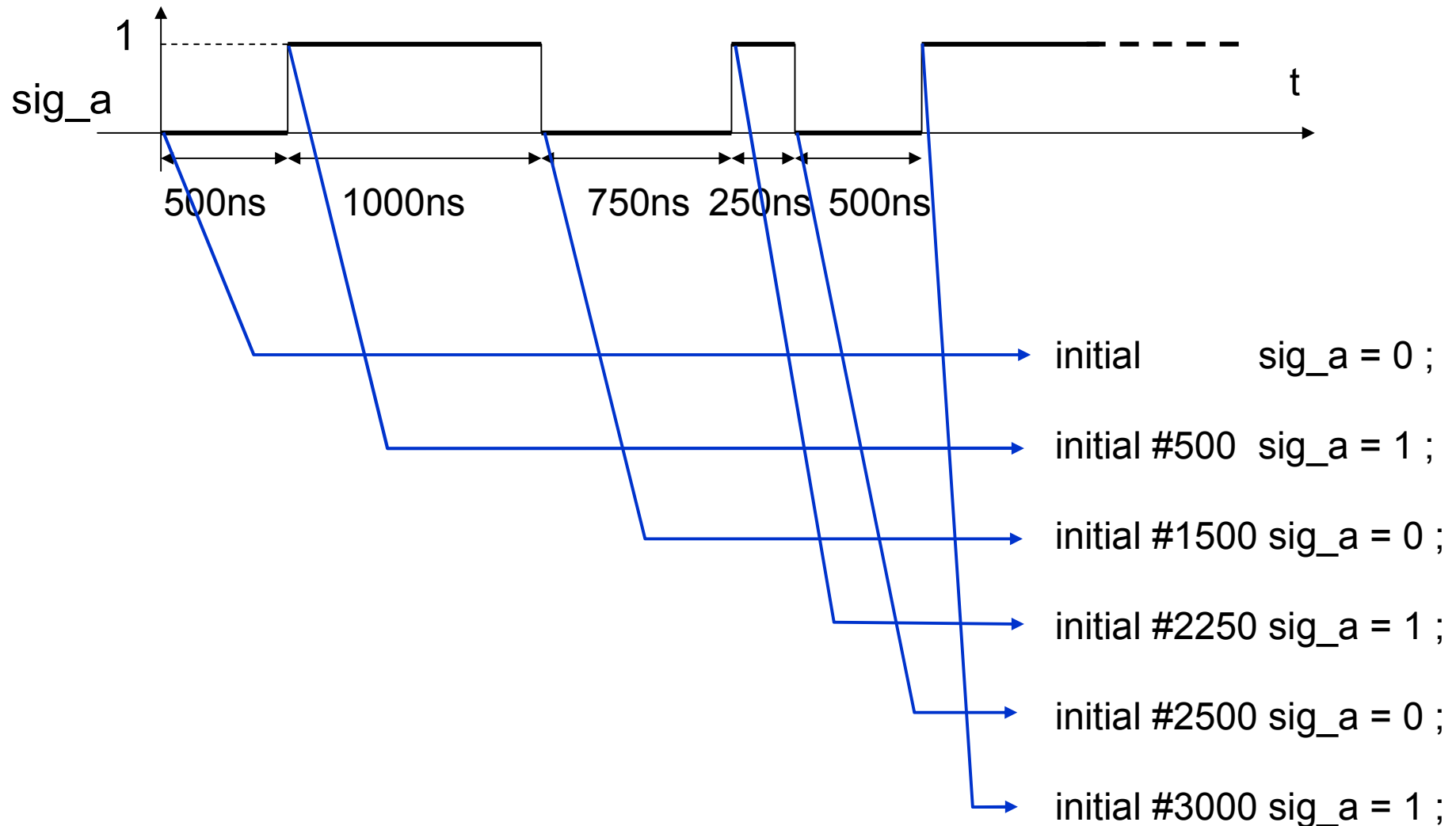By 6 initial constructs shown below, a simulator will generate a wave form of sig_a.



Because initial constructs are all executed at time 0, two code blocks below will create the same wave form of sig_a.
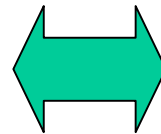
```
initial      sig_a = 0 ;  
initial #500  sig_a = 1 ;  
initial #1500 sig_a = 0 ;  
initial #2250 sig_a = 1 ;  
initial #2500 sig_a = 0 ;  
initial #3000 sig_a = 1 ;
```




```
initial #2500 sig_a = 0 ;  
initial      sig_a = 0 ;  
initial #3000 sig_a = 1 ;  
initial #500  sig_a = 1 ;  
initial #2250 sig_a = 1 ;  
initial #1500 sig_a = 0 ;
```



However, the above sequences of initial constructs are not easy to understand what is done as a whole.

Using begin end block, sequential block, is suitable to show which is executed after which because **in a sequential block all sentences are executed in serial.**

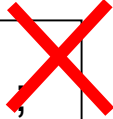The code block on the left can be written as the code block on the right by using begin end block, sequential block. Note the difference of delay times.



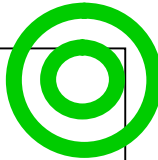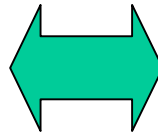
```
initial    sig_a = 0 ;
initial #500 sig_a = 1 ;
initial #1500 sig_a = 0 ;
initial #2250 sig_a = 1 ;
initial #2500 sig_a = 0 ;
initial #3000 sig_a = 1 ;
```



```
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
```


Do not use a programming style on the left.
The right one is a common style.

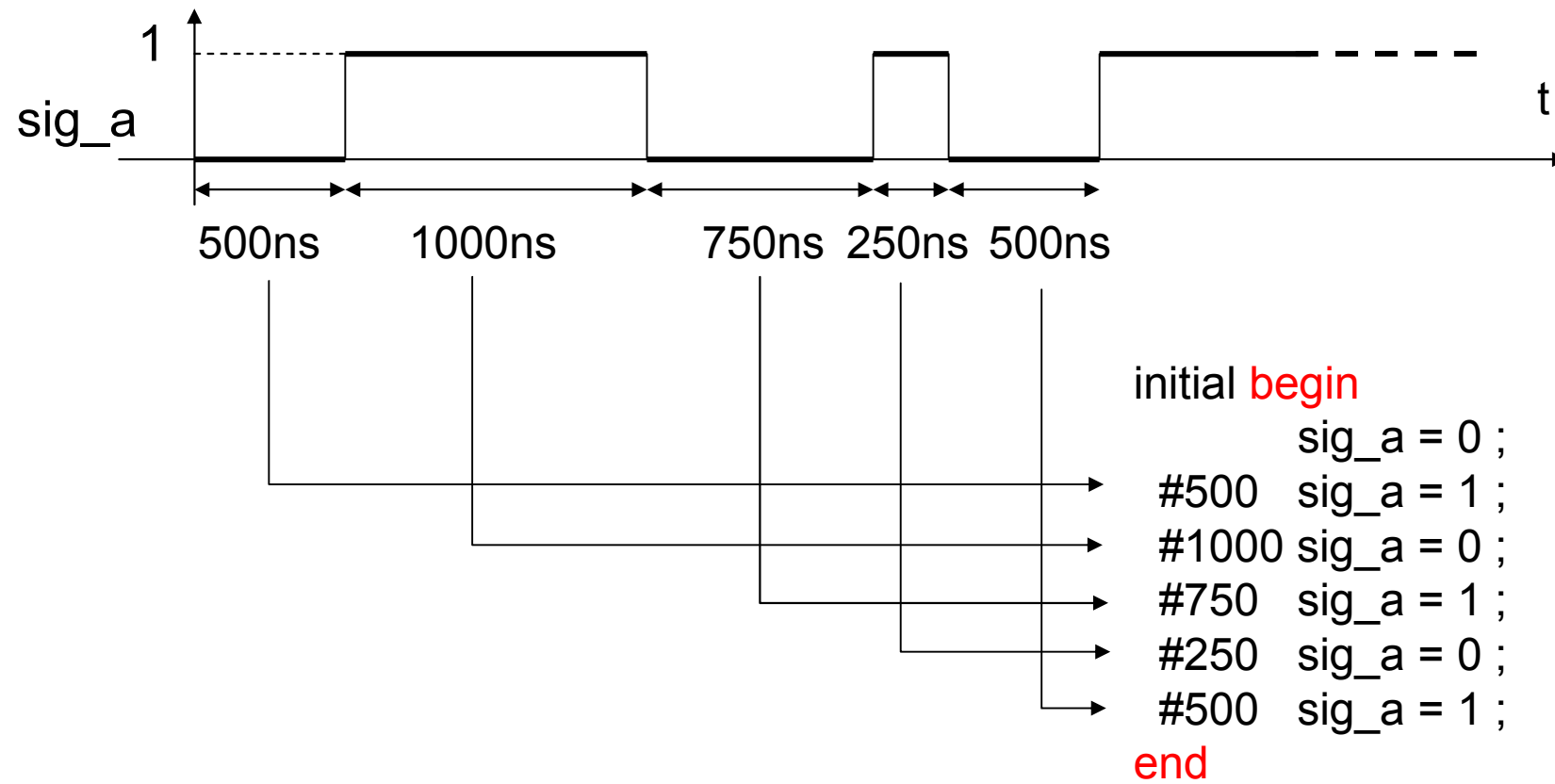Sentences in a sequential block are executed one by one. A sentence is executed only after the preceding sentence completed.



To observe values, we can use “\$monitor system task” as below.

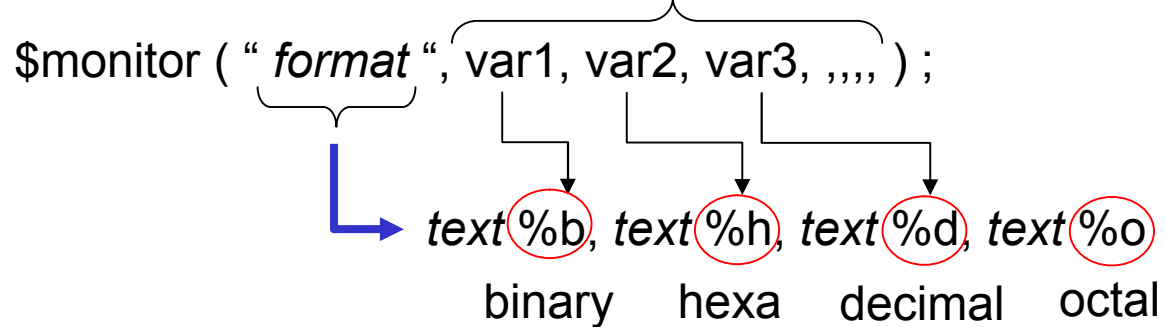After invoked, \$monitor keep watching these signals.
Whenever there is a change, it outputs a message on a terminal window.



```
$monitor ( "format", var1, var2, var3, ..., );
```

`text %b`, `text %h`, `text %d`, `text %o`
 binary hexa decimal octal

An example:

```
$monitor ( "time=%d, in_a = %b, in_b = %b, out_y = %b",  
          $stime, in_a,    in_b,    out_y );
```

A system function to return simulation time.

RTL programming rules

- (1) Only **variable data** type is allowed as **LHS, Left Hans Side, in a procedure**. Variable data type can be declared by **reg** keyword.
- (2) Initial construct is a procedure (*1). Therefore the rule says "sig_a must be declared by **reg** keyword."

```

initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end

```


*1: In Verilog, there are 4 procedures. They are initial construct, always construct, function, and task.

Items written on the Left Hand Side, LHS, of procedural assignment must be declared as **reg** or integer as below;

```

reg sig_a ; // this data type declaration
              // makes sig_a's data type "variable".

```

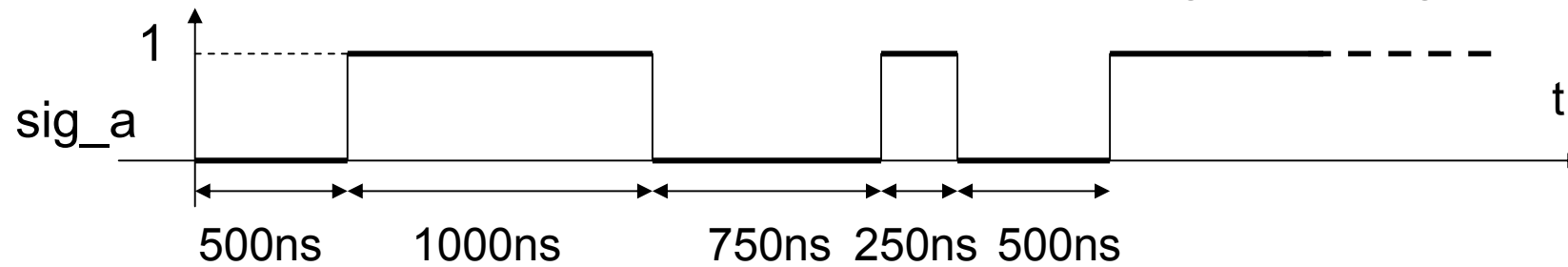


```

`timescale 1ns/100ps
module arbit_binary_sig ;
  reg sig_a ; // non-FF, 1-bit signal
  initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
  end
  initial begin
    $monitor("time=%d, sig_a=%b",
             $stime, sig_a ) ;
    #4000 $finish ; ←
  end
endmodule

```

Coding example.

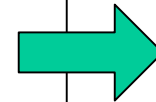

The result of
a simulation

```

time=      0, sig_a=0
time=     500, sig_a=1
time=    1500, sig_a=0
time=    2250, sig_a=1
time=    2500, sig_a=0
time=    3000, sig_a=1
Halted at location
**arbit_binary_sig.v(15) time
4000000 ps from call to $finish

```

`$finish` is a system task to terminate the simulation. This sentence is needed to terminate the simulation.

file name: `arbit_binary_sig.v`

Ex 2-2. Procedure and racing: Run the following two sequence of initial constructs and see the difference of the results. (Racing and "must not do" in RTL programming)

```
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end
```

```
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end
```

```
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end
```

```
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end
```

Initial construct and always construct are called "procedure" in Verilog. When there are several procedures in a simulation target, depending on tools or tool vendors, which procedure shall be executed first is different. Verilog standard does not define any rule for the execution order. Therefore, the code block above has "**racing**" problem. Use **`define compiler directive** to write two alternative source code blocks in one file.

```

`define CASE1
module test_racing ;
reg sig_a ;
`ifdef CASE1
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end
`else
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end
`endif

```

(A)

(B)

```

initial begin
    $monitor(
        "t=%d, sig_a=%b",
        $stime, sig_a
    );
    #600 $finish ;
end

endmodule

```

Depending on CASE1
is defined or not, a
compiler select either
one of (A) or (B).

file name: test_racing.v

```

module test_racing ;
reg sig_a ;
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end

```

(B)

```

`define CASE1
module test_racing ;
reg sig_a ;
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
end
initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
end

```

(A)

Run this file two times,
one with "`define CASE1"
and another without it.

The result shall be different depending on `define CASE1 is written in the source code or not;

```
t=      0, sig_a=1
t=      500, sig_a=0
Halted at location ,,,,
```

Note the difference.
This is called **racing**.

and

```
t=      0, sig_a=0
t=      500, sig_a=1
Halted at location ,,,,
```

Depending on which initial is written first, the results are different.

This means that the same code may have different result if use a tool from a different vendors.



Racing problem

```
module test_racing ;
  reg sig_a;

  initial begin
    sig_a = 1 ;
    #500 sig_a = 0 ;
  end

  initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
  end

  initial begin // observe sig_a
    $monitor ("t= %d, sig_a=%b",
              $stime, sig_a ) ;

    #1000 ;
    $finish ;
  end
endmodule
```

RTL programming rules


(1) Do not write the same variable on LHS, Left Hand Side, of the different initial constructs to avoid possible racing problem. The **same variable must not appear on LHS of other structured procedures.**

The same variable, sig_a, appearing in LHS of different initial constructs.

```
initial begin
    sig_a = 0 ;
#500 sig_a = 1 ;
end

initial begin
    sig_a = 1 ;
#500 sig_a = 0 ;
end
```

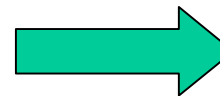Write one variable in LHS of one initial construct.



```
initial begin
    sig_a = 0 ;
    sig_a = 1 ;
#500 sig_a = 1 ;
    sig_a = 0 ;
end
```

This will not cause a racing problem.

```
initial begin
```

```
    sig_a = 0 ;
```

```
    sig_a = 1 ;
```

```
    #500 sig_a = 1 ;
```

```
    sig_a = 0 ;
```


```
end
```



sig_a will be given value 1 by the next sentence, therefore this may better be deleted.

sig_a will be given value 0 by the next sentence, therefore this may better be deleted.

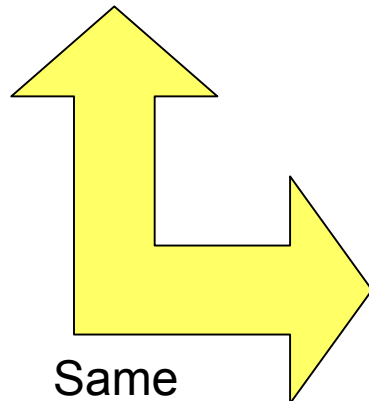This is **not a recommended coding style** because it assign different values to the same variable at the same time.




Same

```
initial begin
```

```
    sig_a = 1 ;
```


```
    #500 sig_a = 0 ;
```

```
end
```

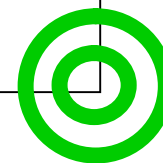


Ex 2-3. Vector waveform and initial: Write a logic block to generate and observe an 8-bit signal (sig_w) of which waveform is shown below.

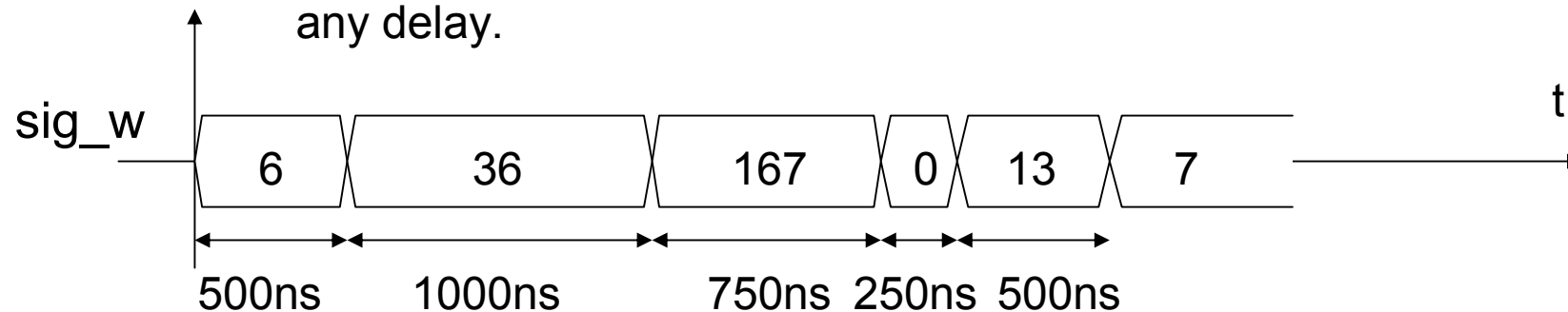Although the waveform shows transient time of change from 6 to 36, etc. RTL code does not have to take care of such transient (zero delay simulation). The signal may change from 6 to 36 at once, without any delay.



We can apply almost the same logic to the previous exercise. The only difference is the bit width of the signal. This time, the bit width is not 1 but 8.

Zero delay simulation

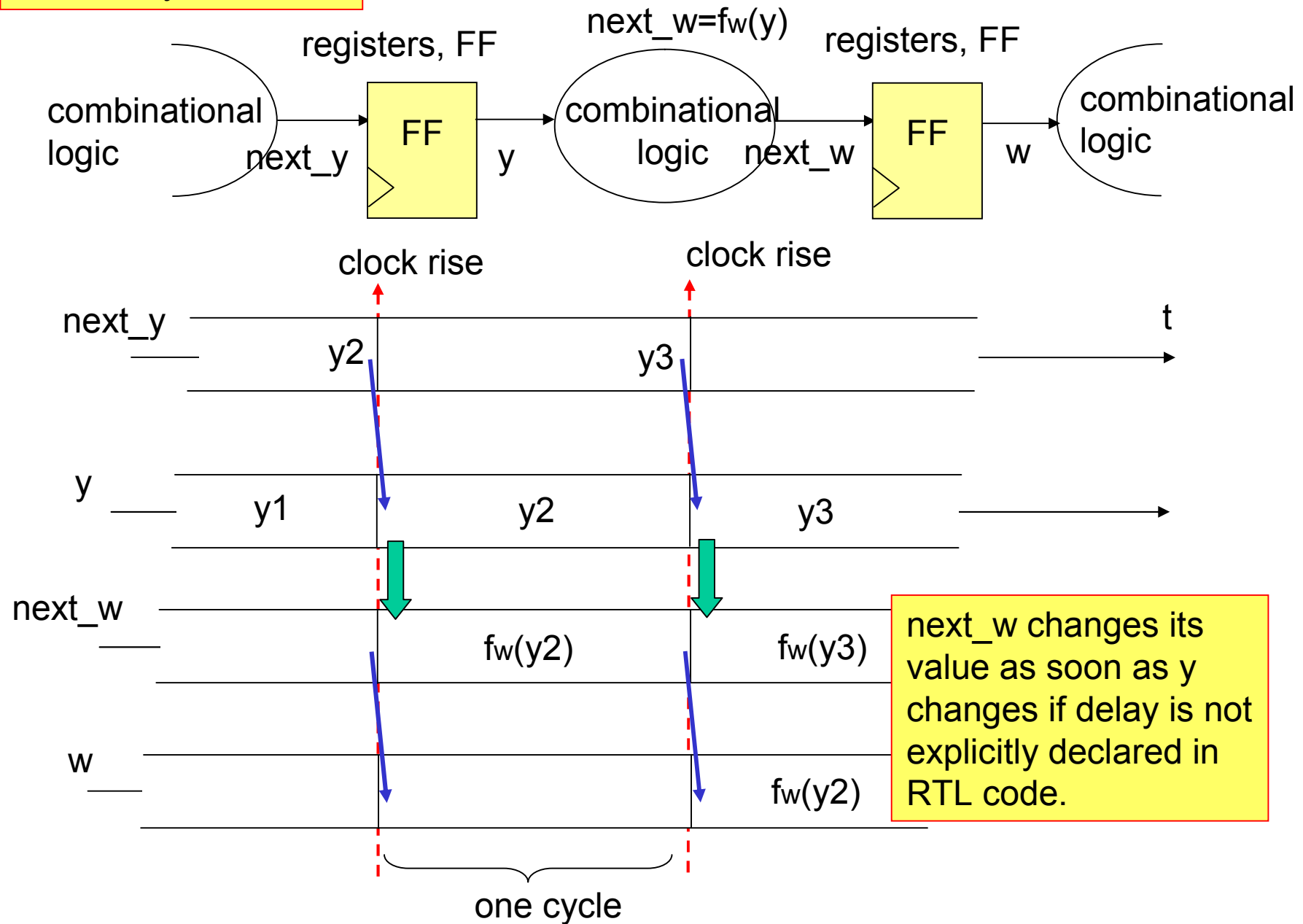


RTL programming rules

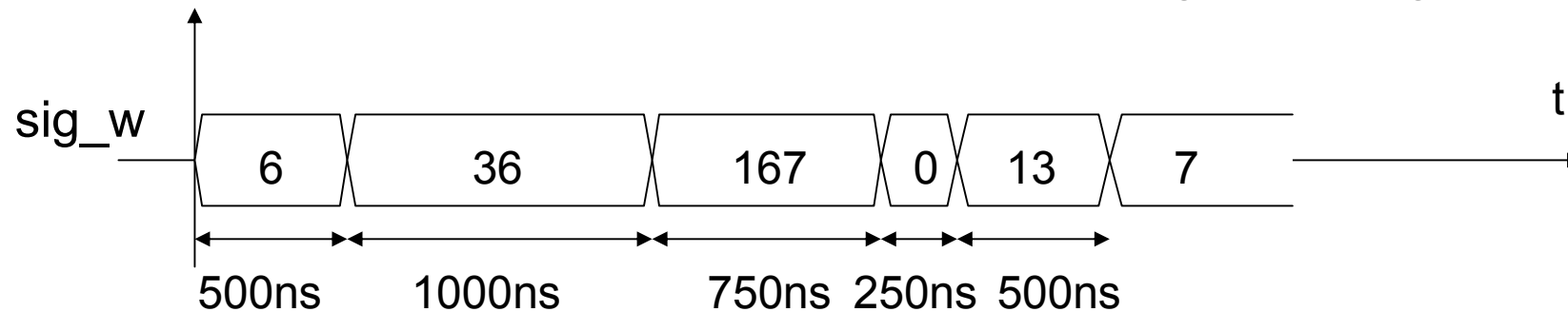(1) Multi-bit signal, vector, must declare its bit size by **range specification**. The range specification is given by [MSB : LSB] where MSB is a bit number of Most Significant Bit and LSB is that of Least Significant Bit.

If the bit width is 8, then declare the range by [7:0].

MSB: Most Significant Bit
LSB: Least Significant Bit




```

`timescale 1ns/100ps
module arbit_8bit_sig ;
reg [7:0] sig_w ; // non-FF, 8-bit signal
initial begin
    sig_w = 6 ;
    #500 sig_w = 36 ;
    #1000 sig_w = 167 ;
    #750 sig_w = 0 ;
    #250 sig_w = 13 ;
    #500 sig_w = 7 ;
end
initial begin
    $monitor("time=%d, sig_w=%d",
            $stime, sig_w ) ;
    #4000 $finish ;
end
endmodule

```

Coding example.

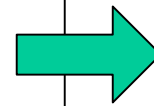

The result of
a simulation


```

time=      0, sig_w=  6
time=     500, sig_w= 36
time=    1500, sig_w=167
time=    2250, sig_w=  0
time=    2500, sig_w= 13
time=    3000, sig_w=  7
Halted at location
**arbit_binary_sig.v(15) time
4000000 ps from call to $finish

```


file name: arbit_8bit_sig.v

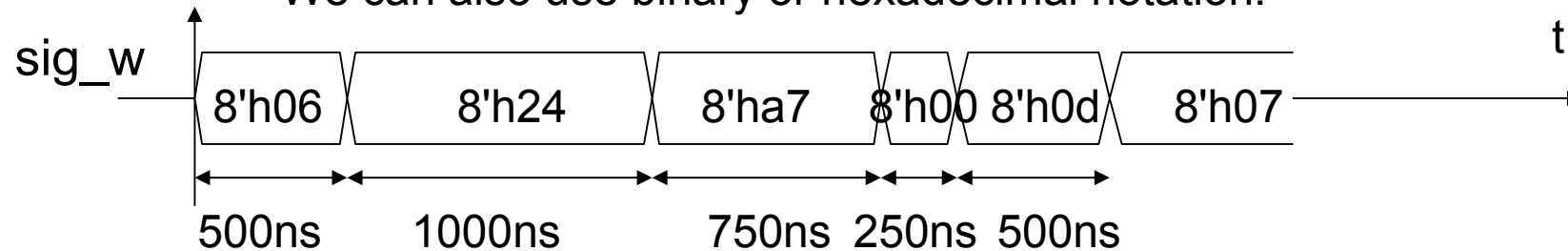We can also use binary or hexadecimal notation.



```
`timescale 1ns/100ps
module arbit_8bit_hex ;
reg [7:0] sig_w ; // non-FF, 8-bit signal
initial begin
    sig_w = 8'h06 ;
    #500 sig_w = 8'h24 ;
    #1000 sig_w = 8'ha7 ;
    #750 sig_w = 8'h00 ;
    #250 sig_w = 8'h0d ;
    #500 sig_w = 8'h07 ;
end
initial begin
    $monitor("time=%d, sig_w=%h",
            $stime, sig_w ) ;
    #4000 $finish ;
end
endmodule
```

Coding example.

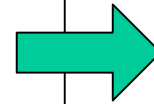


The result of
a simulation

```
time=      0, sig_w=06
time=     500, sig_w=24
time=    1500, sig_w=a7
time=    2250, sig_w=00
time=    2500, sig_w=0d
time=    3000, sig_w=07
Halted at location
**arbit_8bit_hex.v(15) time
4000000 ps from call to $finish.
```

file name: arbit_8bit_hex.v

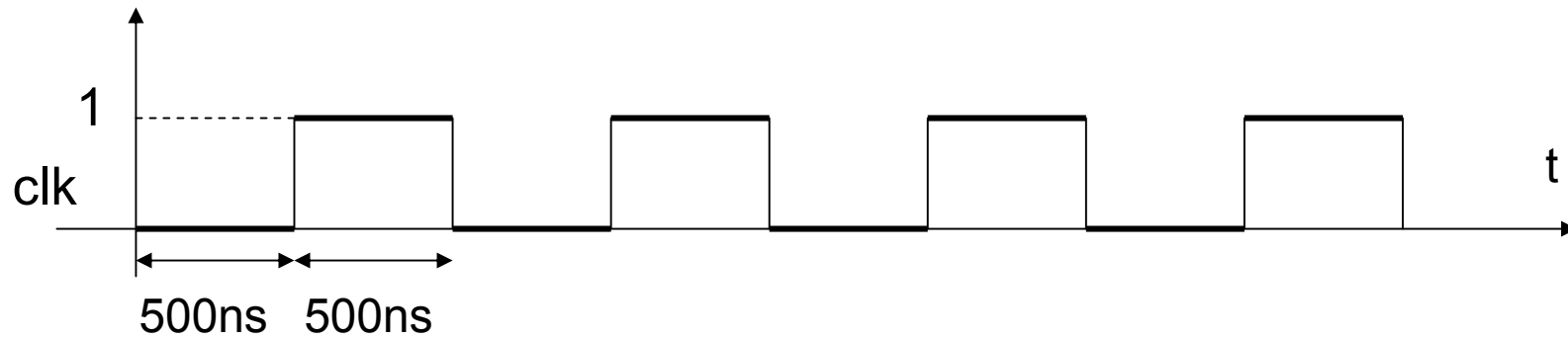Ex 2-4. Repeated waveform and always: Write a logic block to generate and observe a clock signal (clk) of which waveform is shown below.



To generate repeating forever signal, we can use **always construct** which is activated at time 0 and run repeatedly by a simulator.

To do something repeatedly forever, we can use “**always construct**” as below. In RTL simulation, an always construct is **executed at time 0 and repeated forever**.

And if there are several always constructs, they are all executed at time 0.

```
always sig_a = 0 ; // sig_a is given value 0 at time 0  
                // and repeatedly given 0 forever.
```




This code will hang up a simulator.

By using delay, or wait, specified by @, we can use always construct without making a simulator hung-up.

RTL programming rules

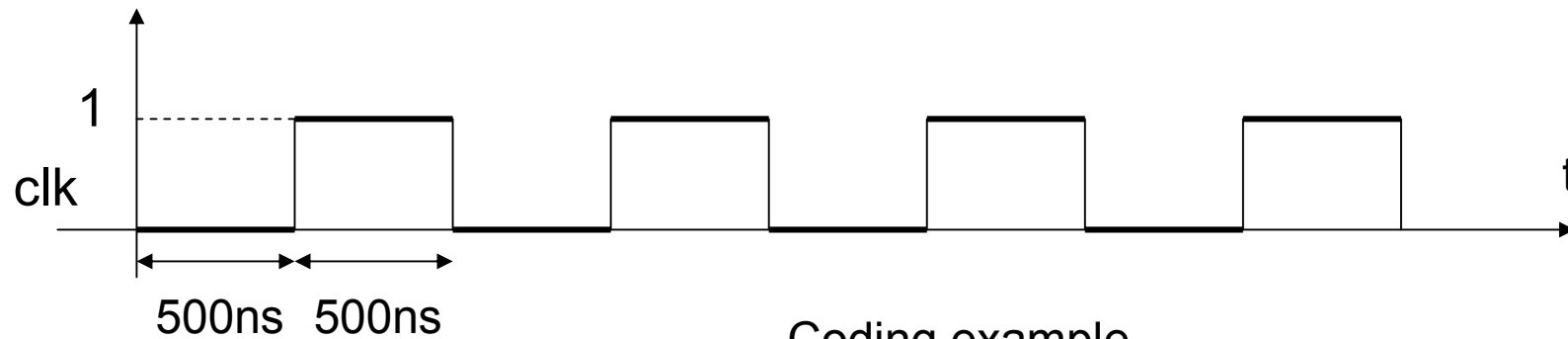(1) **# and @ are mandatory in always construct.**

Because always construct is executed forever, there must be some delay or wait written in the always construct. If there is no delay or wait, a simulator program will hang up in infinite loop to execute the always construct and can do nothing else.



Coding example.

```
`timescale 1ns/100ps
module clk_sig ;
reg clk ; // non-FF, clock signal
always begin
  clk = 0 ; #500 ;
  clk = 1 ; #500 ;
end
initial begin
  $monitor("time=%d, clk=%b", $stime, clk ) ;
  #5000 $finish ;
end
endmodule
```

file name: clk_sig.v

The result of
a simulation

```
time=      0, clk0
time=     500, clk1
time=    1000, clk0
time=    1500, clk1
time=    2000, clk0
time=    2500, clk1
time=    3000, clk0
time=    3500, clk1
time=    4000, clk0
time=    4500, clk1
Halted at location
**clk_sig.v(10) time 5000000 ps
from call to $finish.
```


The code on the previous page is not convenient for changing the cycle time. It is recommended to use parameter for such may-be-changed-often value as shown below.

```
`timescale 1ns/100ps
module clk_sig_para ;
parameter HF_CYCL=500 ;
reg clk ; // non-FF, clock signal
always begin
  clk = 0 ; #HF_CYCL ;
  clk = 1 ; #HF_CYCL ;
end
initial begin
  $monitor("time=%d, clk=%b", $stime, clk ) ;
  #(HF_CYCL*10) $finish ;
end
endmodule
```

file name: clk_sig_para.v

Coding example.


The result of
a simulation

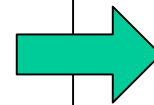


```
time=      0, clk0
time=     500, clk1
time=    1000, clk0
time=    1500, clk1
time=    2000, clk0
time=    2500, clk1
time=    3000, clk0
time=    3500, clk1
time=    4000, clk0
time=    4500, clk1
Halted at location
**clk_sig_para.v(11) time
5000000 ps from call to $finish.
```

Run with different
parameter values.

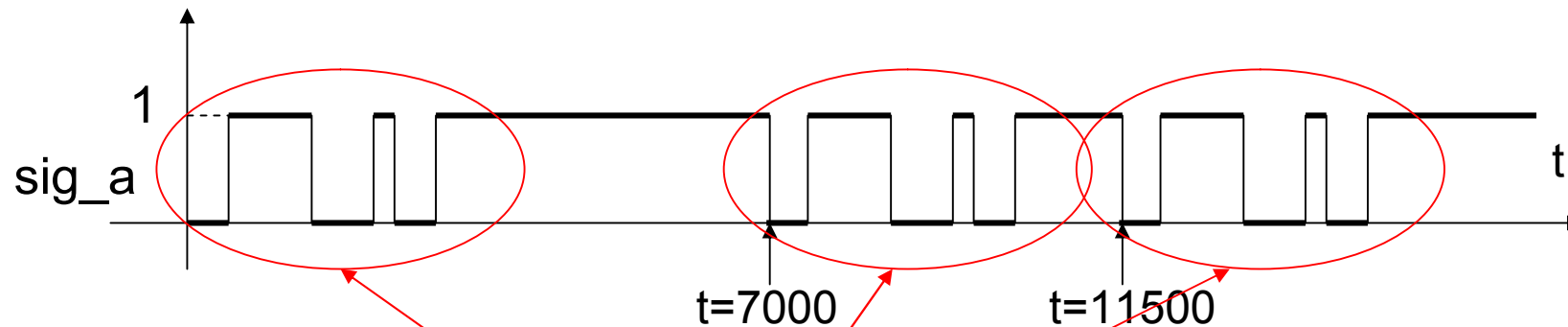Ex 2-5. Repeated waveform and task: Write a logic block to generate and observe a signal (sig_a) of which waveform is shown below.




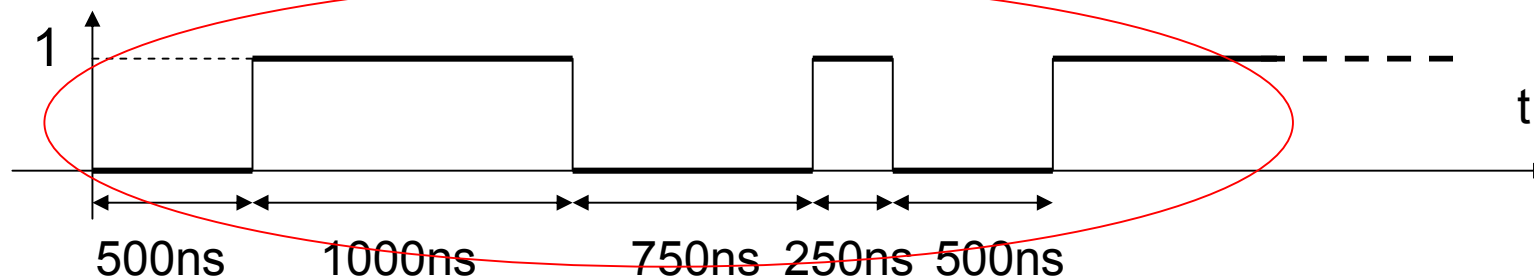Repeating the same pattern from time 0, 7000, and 11500.




To generate the same pattern repeatedly, it is recommended to define and use a task which generates a basic pattern to be repeated.

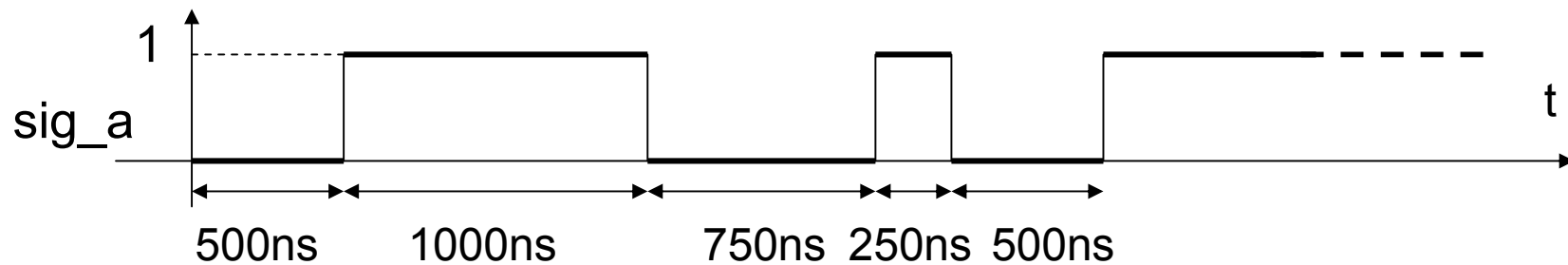First, let's think how to generate the wave form which is repeated 3 times.



The above can be generated by the initial construct shown on the right as we already studied in Ex. 2-1.
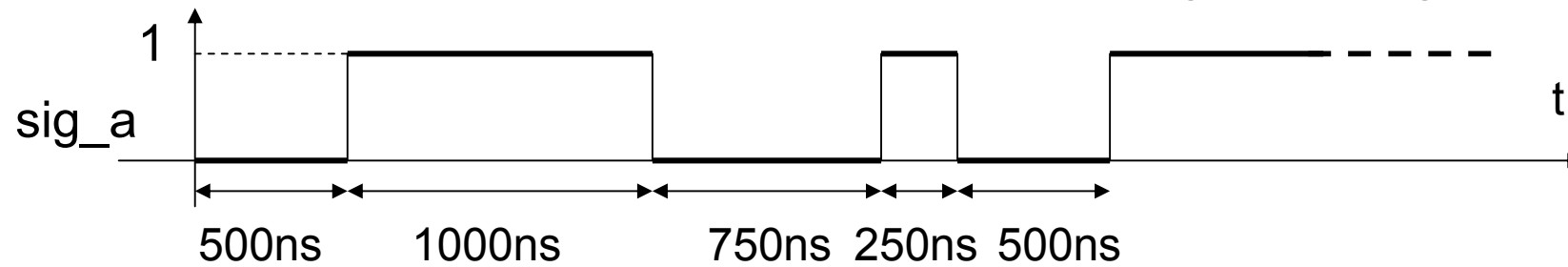
```
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
```



```

`timescale 1ns/100ps
module arbit_binary_sig ;
reg sig_a ; // non-FF, 1-bit signal
initial begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
initial begin
    $monitor("time=%d, sig_a=%b",
            $stime, sig_a ) ;
    #4000 $finish ;
end
endmodule

```

Take out the
basic wave form
creating part and
put it into a task.

```

task wave_ptrn ;
begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
endtask

```

file name: arbit_binary_sig.v

RTL programming rules

- (1) A task is executed only **when it is invoked**.
- (2) To invoke a task, write the task name in a procedure as shown below.
- (3) If LHS in a task is not declared as output argument, then assigning any value to LHS is effective at the time of the assignment.
- (4) If LHS in a task is declared as output argument, then only the last assignment is effective.

a procedure

•
•
•
•

task_name ; ← A task, *task_name*, is executed
when this sentence is executed.


•
•
•
•

end procedure

task *task_name*;

•
•
•

endtask

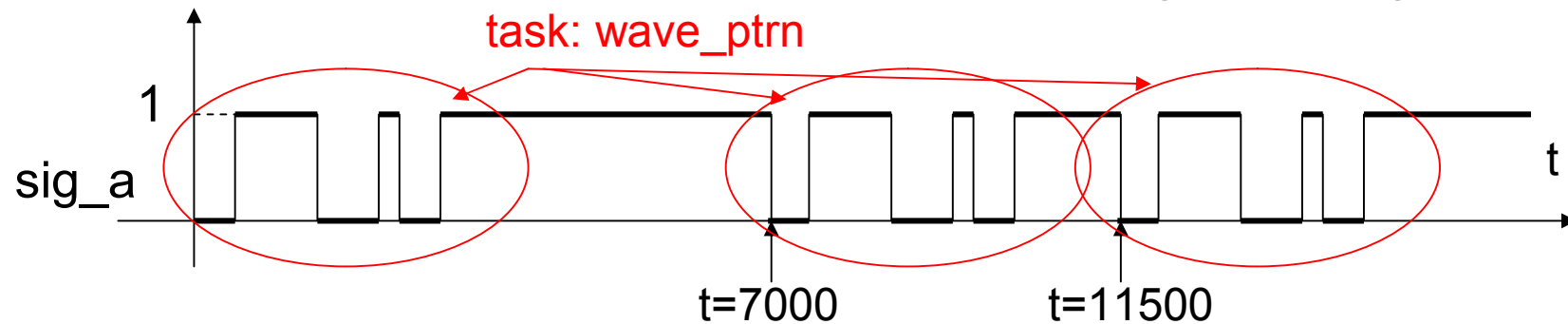

Coding example.

```
`timescale 1ns/100ps
module rept_sig ;
reg sig_a ; // non-FF, 1-bit variable
initial begin
    wave_ptrn ;
    #4000 wave_ptrn ;
    #1500 wave_ptrn ;
end
initial begin
    $monitor("time=%d, sig_a=%b",
             $stime, sig_a ) ;
    #20000 $finish ;
end
```

file name: `rept_sig.v`

To start the second basic wave pattern at time 7000, the delay here must be 4000 (= 7000 – 3000).

```
task wave_ptrn ;
begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
endtask

endmodule
```

The task has 3000 unit time delay in it.

`sig_a` becomes 1 as soon as this assignment is executed.


The result of a simulation

```
time=      0, sig_a=0
time=     500, sig_a=1
time=    1500, sig_a=0
time=    2250, sig_a=1
time=    2500, sig_a=0
time=    3000, sig_a=1
time=    7000, sig_a=0
time=    7500, sig_a=1
time=    8500, sig_a=0
time=    9250, sig_a=1
time=    9500, sig_a=0
time=   10000, sig_a=1
time=   11500, sig_a=0
time=   12000, sig_a=1
time=   13000, sig_a=0
time=   13750, sig_a=1
time=   14000, sig_a=0
time=   14500, sig_a=1
Halted at location **rept_sig.v(12) time 20000000 ps from call to $finish.
```



Ex 2-6. How to use implicit event: Write a logic block to generate and observe signals (sig_a and sig_trig) of which waveforms are shown below. sig_a's change must be triggered by the change of sig_trig.

sig_a changes every time sig_trig changes. Whenever sig_trig changes, except at time 0, sig_a starts to change as defined by the task, wave_ptrn, in the previous exercise.

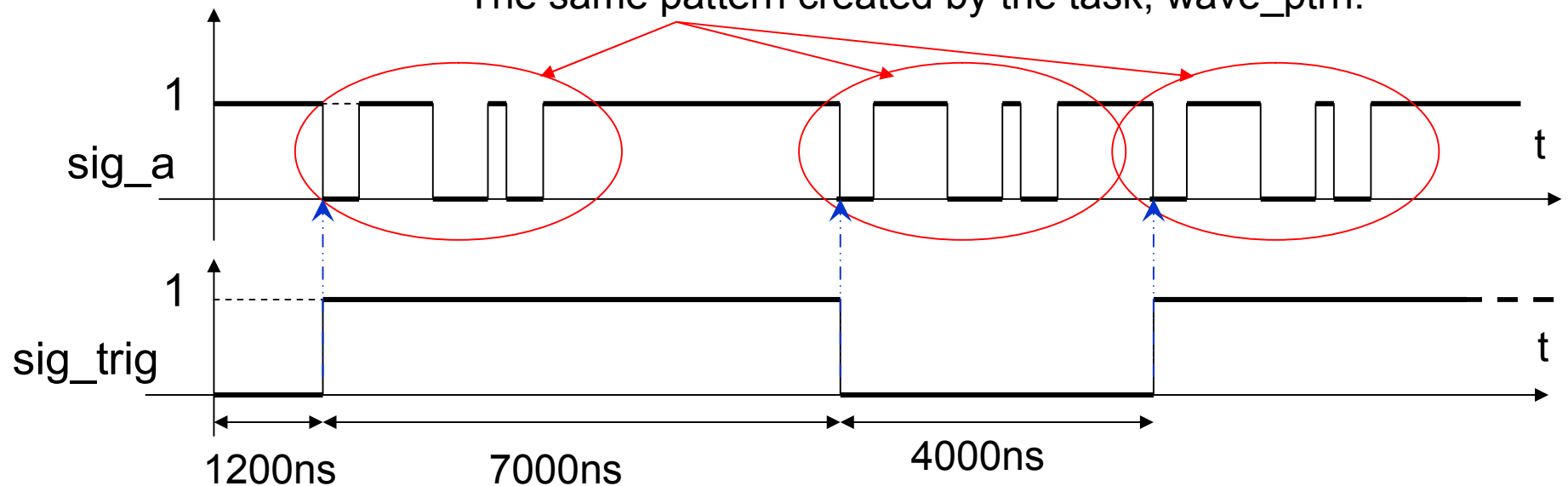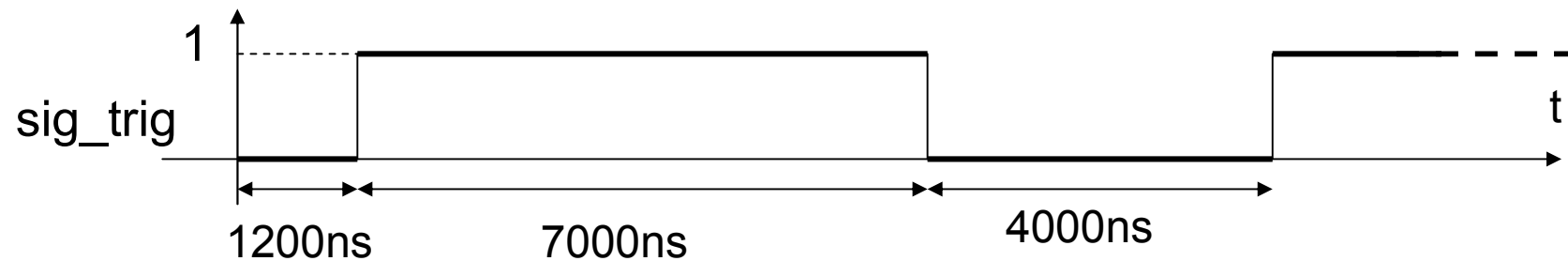The same pattern created by the task, wave_ptrn.



Signal's value change causes change value event in Verilog. It is called an implicit event, and can be used to synchronize procedures. To catch a timing such as sig_trig's change, we can use `@(sig_trig)`.



A process to generate `sig_trig`

```
initial begin
    sig_trig = 0 ;
    #1200 sig_trig = 1 ;
    #7000 sig_trig = 0 ;
    #4000 sig_trig = 1 ;
    #5000 $finish ;
end
```

A process to generate `sig_a`

```
initial begin
    sig_a = 1 ; // 1 at start time
    #1 @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
end
```

This delay is needed to avoid catching `sig_trig`'s change from unknown value `x` to 0 at time 0.

Each time `sig_trig` changes, the task, `wave_ptrn`, is invoked.

The total module can be written as shown on the next page.

Coding example.

```

`timescale 1ns/100ps
module rept_sig_evnt ;
reg sig_a, sig_trig ; // non-FF
initial begin
    $monitor("time=%d, sig_a=%b",
             $stime, sig_a ) ;
end

```

```

initial begin
    sig_a = 1 ; // 1 at start time
    #1 @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
end

```

```

initial begin
    sig_trig = 0 ;
    #1200 sig_trig = 1 ;
    #7000 sig_trig = 0 ;
    #4000 sig_trig = 1 ;
    #5000 $finish ;
end

```

```

task wave_ptrn ;
begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
endtask

```

```

endmodule

```

file name: rept_sig_evnt.v

Different coding (1)

We can use @, meaning wait, in a task. Therefore, we can modify the code as below.

Take @(sig_trin) out
of the initial construct
and put it into the task.

```
initial begin
  sig_a = 1 ; // 1 at start time
  #1 @ (sig_trig) wave_ptrn ;
  @ (sig_trig) wave_ptrn ;
  @ (sig_trig) wave_ptrn ;
end
```


```
task wave_ptrn ;
begin
  @ (sig_trig) sig_a = 0 ;
  #500 sig_a = 1 ;
  #1000 sig_a = 0 ;
  #750 sig_a = 1 ;
  #250 sig_a = 0 ;
  #500 sig_a = 1 ;
end
endtask
```

Different coding (2)

For this exercise, the wave pattern starting trigger is always the same, change of sig_trig, therefore we do not have to use a task, but can use initial construct and forever as shown on the right below.

```
initial begin
    sig_a = 1 ; // on at start time
    #1 @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
    @ (sig_trig) wave_ptrn ;
end

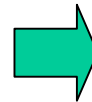task wave_ptrn ;
begin
    sig_a = 0 ;
    #500 sig_a = 1 ;
    #1000 sig_a = 0 ;
    #750 sig_a = 1 ;
    #250 sig_a = 0 ;
    #500 sig_a = 1 ;
end
endtask
```




```
initial begin
    sig_a = 1 ;
    forever begin
        #1 @(sig_trig) begin
            sig_a = 0 ;
            #500 sig_a = 1 ;
            #1000 sig_a = 0 ;
            #750 sig_a = 1 ;
            #250 sig_a = 0 ;
            #500 sig_a = 1 ;
        end
    end
end
```

This part is
repeated
forever.


This is not a recommended style.

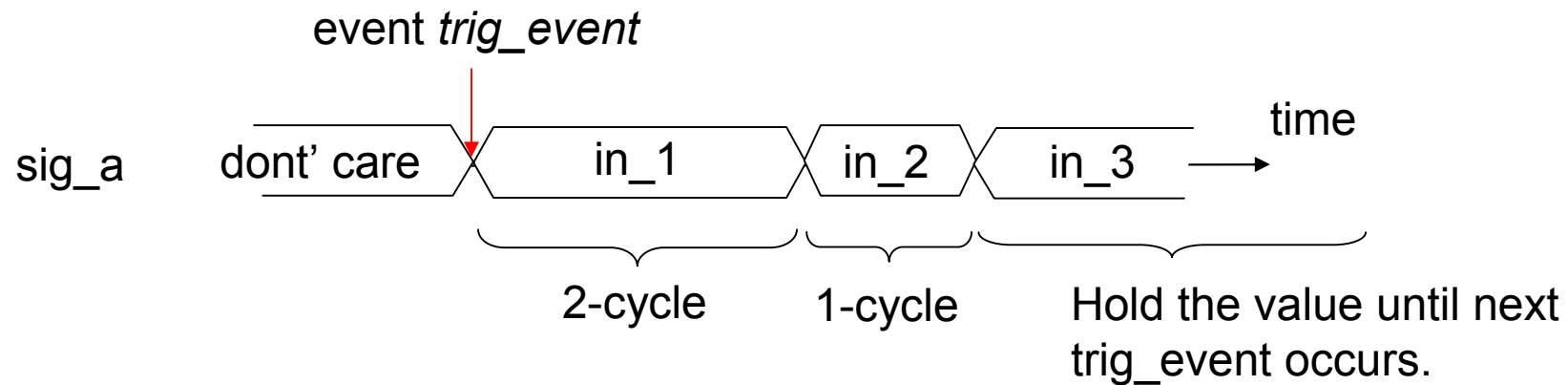Task is very suitable to describe signal change which follows the same pattern or a protocol, therefore, it is very often used to model bus, peripheral, CPU and others.


Ex 2-7. How to use named event: Design a task named `prot_1` which can create the output data pattern shown below. The task must have 3 input arguments and they are assigned to `sig_a`. For the first 2 cycles the first argument, `in_1`, must be assigned to `sig_a`, for the next 1 cycle the second argument, `in_2`, must be assigned to `sig_a`, and for the cycles after 3 cycles the third argument, `in_3`, must be assigned to `sig_a`.



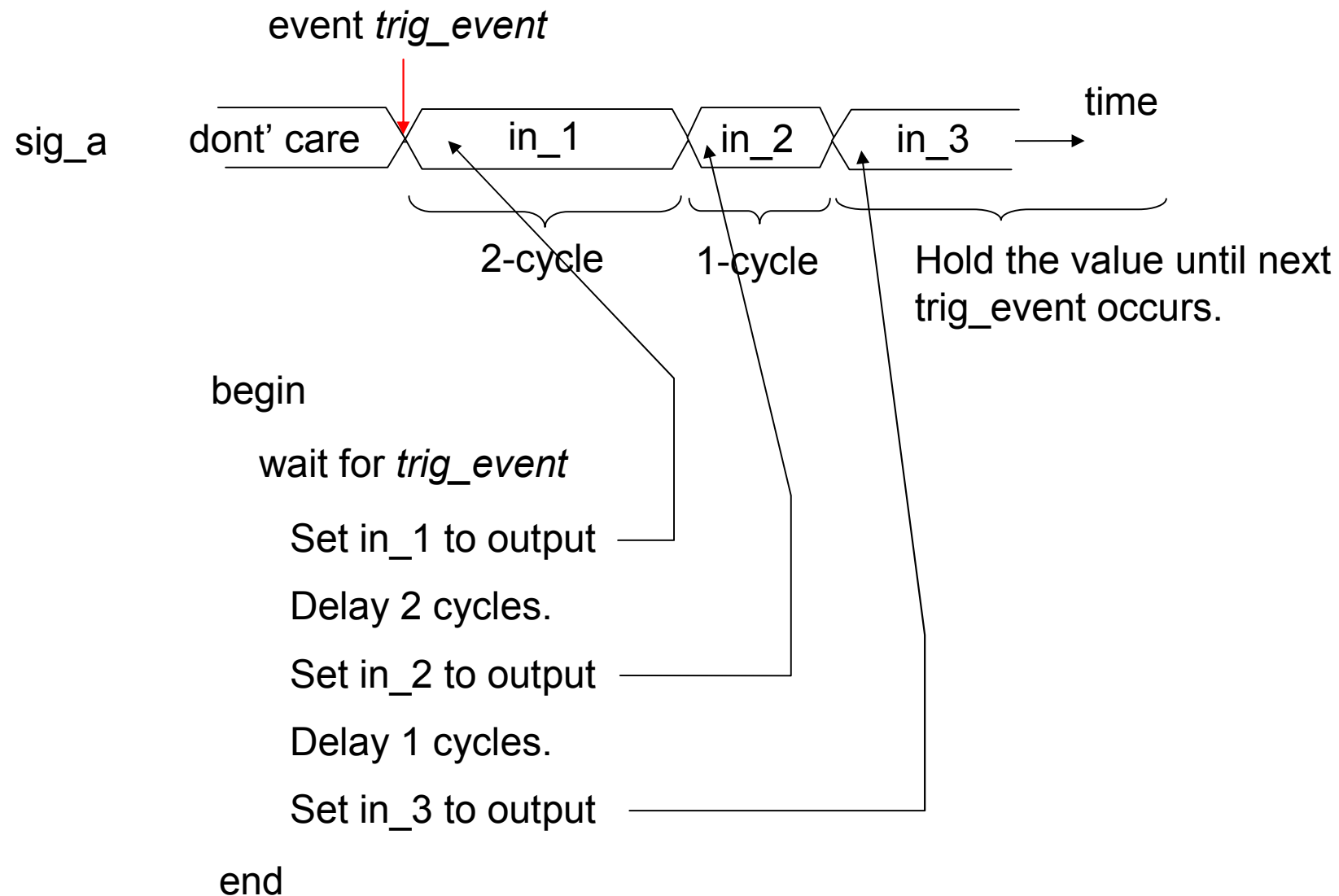We can generate named event by using Verilog operator `"->"`. To generate a named event we can use `-> event_name` and to catch it we can use `@(event_name)`.



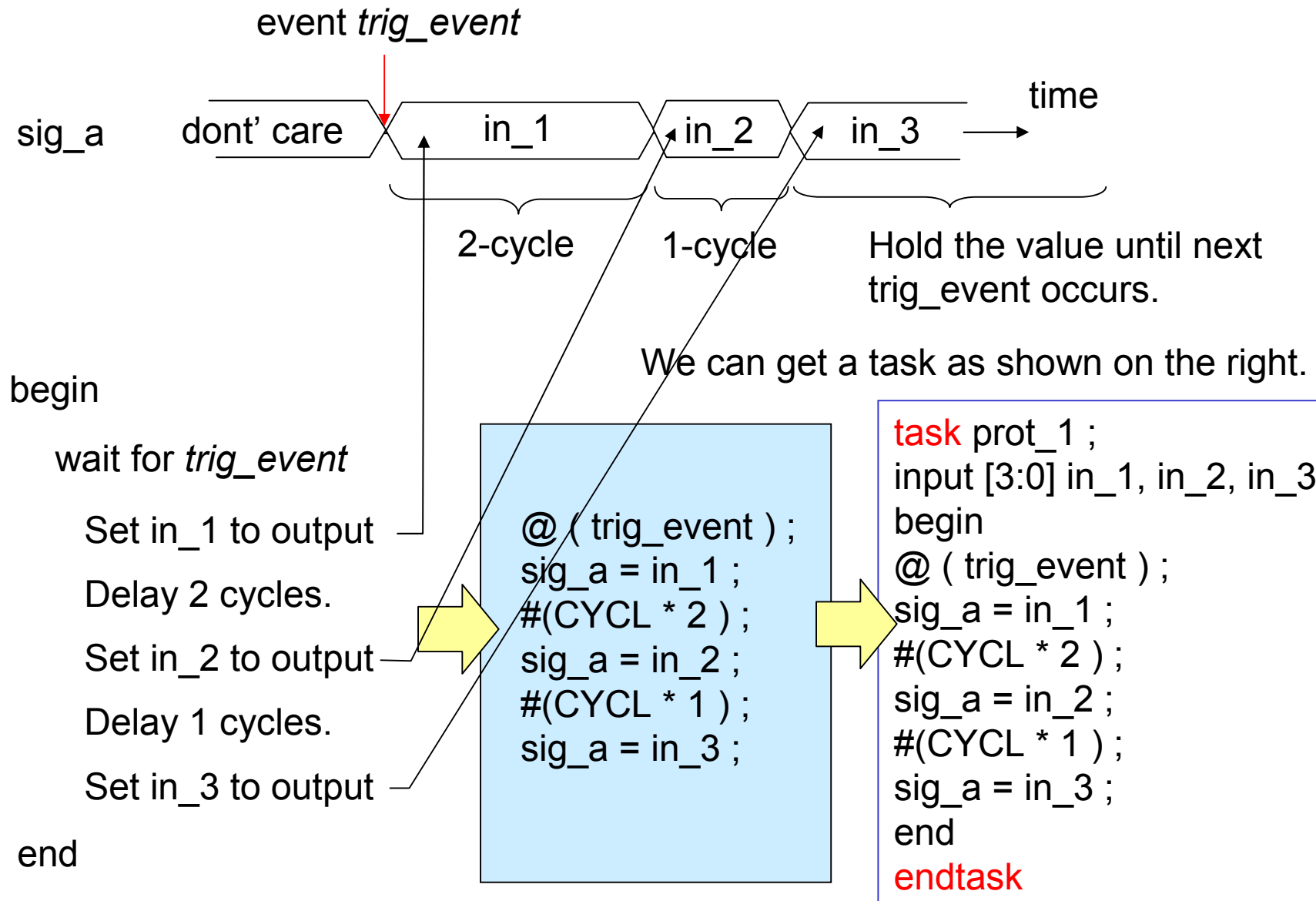This logic can be programmed as shown in the middle of the next page.




Now, write a test bench and check how task works.

```

module test_prot_1 ;
parameter CYCL = 10 ;
reg [3:0] sig_a ;
event trig_event ;
//
initial begin
    prot_1(1, 3, 2) ;
    prot_1( 7, 0, 4 ) ;
    prot_1( 5, 6, 3 ) ;
end
//
initial begin
    # CYCL -> trig_event ;
    #(CYCL*15) -> trig_event ;
    #(CYCL*20) -> trig_event ;
    #(CYCL*10) $finish ;
end
//

```

input arguments




```

initial begin
    $monitor("t=%d, sig_a=%d",
        $stime, sig_a ) ;
end
//
task prot_1 ;
    input [3:0] in_1, in_2, in_3 ;
    begin
        @ ( trig_event ) ;
        sig_a = in_1 ;
        #(CYCL * 2 ) ;
        sig_a = in_2 ;
        #(CYCL * 1 ) ;
        sig_a = in_3 ;
    end
endtask
//
endmodule

```

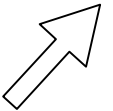“->” is a Verilog operator to generate an event.



file name: test_prot_1.v

Now, write a test bench and check how task works.

A sample result


```
t=      0, sig_a= x
t=     10, sig_a= 1
t=     30, sig_a= 3
t=     40, sig_a= 2
t=    160, sig_a= 7
t=    180, sig_a= 0
t=    190, sig_a= 4
t=    360, sig_a= 5
t=    380, sig_a= 6
t=    390, sig_a= 3
Halted at location **test_pr
```

Next, rewrite the file so that the task has output arguments.

```

module test_prot_1 ;
parameter CYCL = 10 ;
reg [3:0] sig_a ;
event trig_event ;
//
initial begin
prot_1( 1, 3, 2, sig_a ) ;
prot_1( 7, 0, 4 , sig_a ) ;
prot_1( 5, 6, 3 , sig_a ) ;
end
//
initial begin
# CYCL -> trig_event ;
#(CYCL*15) -> trig_event ;
#(CYCL*20) -> trig_event ;
#(CYCL*10) $finish ;
end
//
initial begin
$monitor("t=%d, sig_a=%d",
    $stime, sig_a ) ;
end
//

```

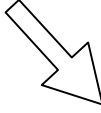

```

task prot_1 ;
input [3:0] in_1, in_2, in_3 ;
output [3:0] sig_out ;
reg [3:0] sig_out ;
begin
@ ( trig_event ) ;
sig_out = in_1 ;
#(CYCL * 2 ) ;
sig_out = in_2 ;
#(CYCL * 1 ) ;
sig_out = in_3 ;
end
endtask
//
endmodule

```

file name: test_prot_1_ng.v

Now, run this file and check the result.

former result

```

t=      0, sig_a= x
t=     10, sig_a= 1
t=     30, sig_a= 3
t=     40, sig_a= 2
t=    160, sig_a= 7
t=    180, sig_a= 0
t=    190, sig_a= 4
t=    360, sig_a= 5
t=    380, sig_a= 6
t=    390, sig_a= 3
Halted at location **test_pr

```

A sample new result

```


t=      0, sig_a= x
t=     40, sig_a= 2
t=    190, sig_a= 4
t=    390, sig_a= 3
Halted at location **test_pr

```

If a task has output argument, assigning any values to the output arguments becomes effective when endtask is executed. Therefore, only the last assignment in the task is effective. In this example, only "**sig_out** = in_3 ;" is effective because it is the last assignment in the task.

Ex 2-8. Observe signals periodically: Write a logic block to observe a 8-bit signal (sig_w) which can be generated by the logic block of Ex2-3 at every clock rise time.

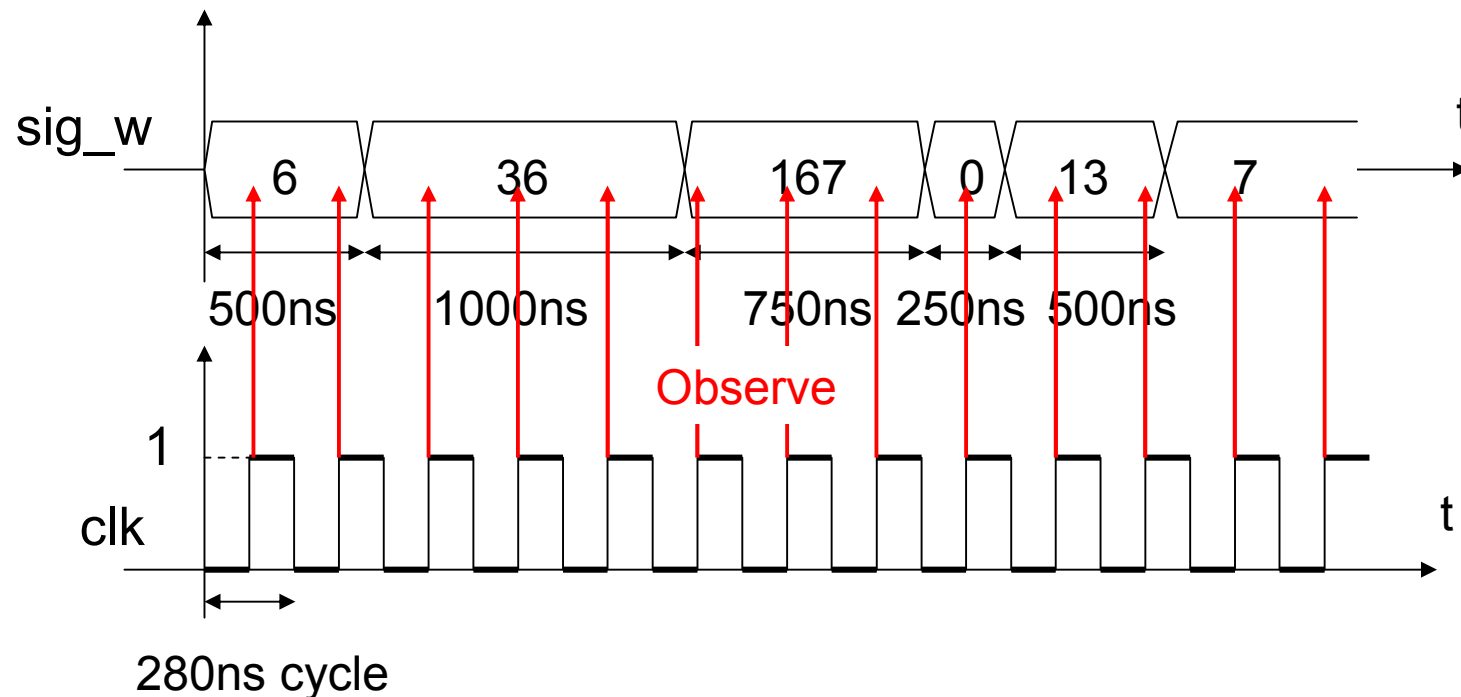Use the same logic in Ex2-3 to create sig_w.



We can use `@(posedge clk)` to catch a clock rise event. To observe signals at specific timing, we have to invoke a system task `$strobe` at such specific timing.

We can use various style as shown below to observe signals at clock rise time.

```
initial begin
  @(posedge clk )$strobe( ,,,, ) ;
  @(posedge clk )$strobe( ,,,, ) ;
  @(posedge clk )$strobe( ,,,, ) ;
  @(posedge clk )$strobe( ,,,, ) ;
  @(posedge clk )$strobe( ,,,, ) ;
  ,,,,
  ,,,
end
```

This style is applicable
only for limited times
of observation.

```
initial begin
  forever begin
    @(posedge clk )$strobe( ,,, ) ;
  end
end
```

```
always begin
  @(posedge clk) begin
    $strobe( ,,, ) ;
  end
end
```

Recommended style



```
always @ ( posedge clk ) begin
  $strobe( ,,, ) ;
end
```

The syntax of \$strobe is the same to that of \$monitor.

```
$strobe ( "format", var1, var2, var3, ,,, ) ;
```

Diagram illustrating the mapping of format specifiers to text fields:

- `format` maps to `text %b`
- `var1` maps to `text %h`
- `var2` maps to `text %d`
- `var3` maps to `text %o`

example:

```
$strobe ( "time=%d, in_a = %b, in_b = %b, out_y = %h",
          $stime, in_a,      in_b,      out_y );
```

This sentence may output the following message on the terminal when it is invoked, not when `in_a`, `in_b`, or `out_y` change.

```
t=      50, in_a =01100110, in_b =1100, out_y = 3f
```




```

`timescale 1ns/100ps
module obsrv_at_clk_rise ;
parameter HF_CYCL=140 ;
reg clk ; // non-FF, clock
reg [7:0] sig_w ; // non-FF
always @ ( posedge clk ) begin
    $strobe("t=%d, sig_w=%d",
           $stime, sig_w ) ;
end

initial begin
    sig_w = 6 ;
    #500 sig_w = 36 ;
    #1000 sig_w = 167 ;
    #750 sig_w = 0 ;
    #250 sig_w = 13 ;
    #500 sig_w = 7 ;
    #700 $finish ;
end

```

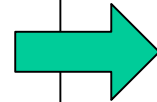

The result of
a simulation

```

t=      140, sig_w=  6
t=      420, sig_w=  6
t=      700, sig_w= 36
t=      980, sig_w= 36
t=     1260, sig_w= 36
t=     1540, sig_w=167
t=     1820, sig_w=167
t=     2100, sig_w=167
t=     2380, sig_w=  0
t=     2660, sig_w= 13
t=     2940, sig_w= 13
t=     3220, sig_w=  7
t=     3500, sig_w=  7

```

Halted at location
**obsrv_at_clk_rise.v(18) time

```

always begin
    clk = 0 ; #HF_CYCL ;
    clk = 1 ; #HF_CYCL ;
end


endmodule

```

file name: obsrv_at_clk_rise.v

Ex 2-9. Signals synchronized to clock: Write a logic block to generate a 4-bit signal (`syn_sig_a`) of which waveform is shown below. The change of the signal is triggered by fall edges of `clk`.

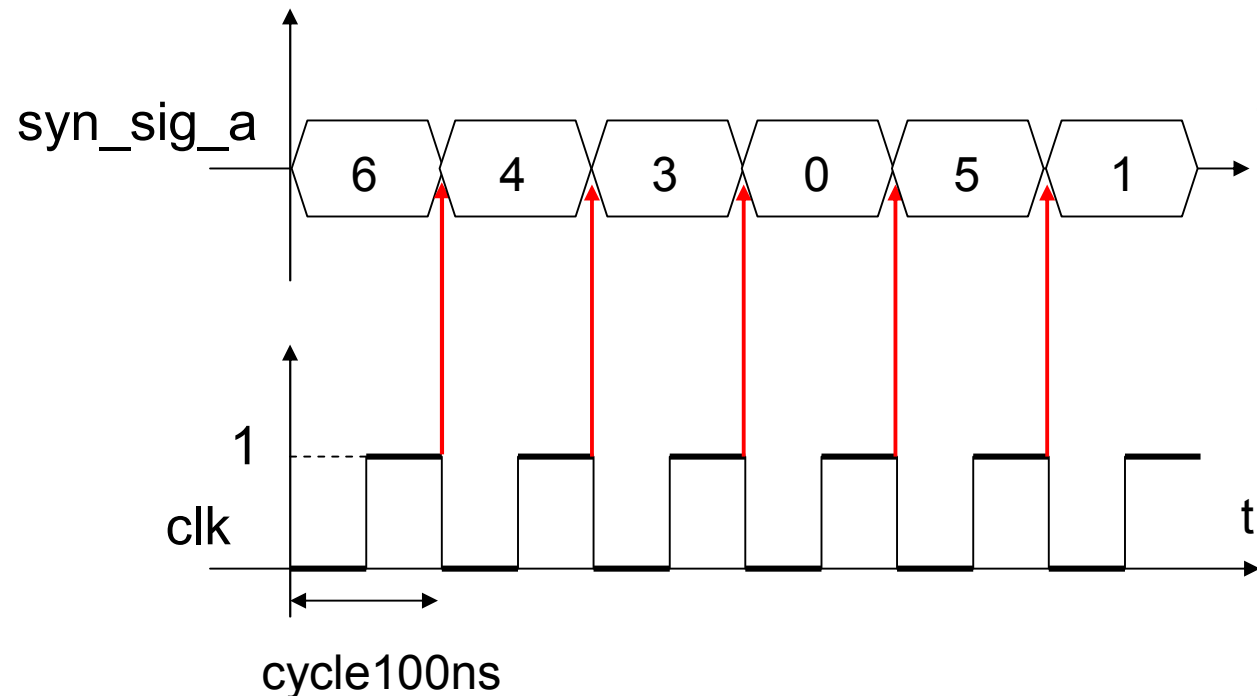In synchronous design, input signals must be stable at clock rise time. A logic block designed in this exercise can be used to generate input signals for debugging a synchronous system.



We can catch a fall edge event by using `@(negedge clk)` and use it to trigger `syn_sig_a`'s change.

```

`timescale 1ns/100ps
module gen_syn_sig ;
parameter HF_CYCL=50 ;
reg clk ; // non-FF, clock
reg [7:0] syn_sig_a ; // non-FF
initial begin
    $monitor("time=%d, clk=%b, sig_a=%d",
            $stime, clk, syn_sig_a ) ;
end
initial begin
    syn_sig_a = 6 ; #1;
    @(negedge clk) syn_sig_a = 4 ;
    @(negedge clk) syn_sig_a = 3 ;
    @(negedge clk) syn_sig_a = 0 ;
    @(negedge clk) syn_sig_a = 5 ;
    @(negedge clk) syn_sig_a = 1 ;
    #(HF_CYCL*2) $finish ;
end

```

The result of
a simulation

```

time=      0, clk=0, sig_a= 6
time=     50, clk=1, sig_a= 6
time=    100, clk=0, sig_a= 4
time=    150, clk=1, sig_a= 4
time=    200, clk=0, sig_a= 3
time=    250, clk=1, sig_a= 3
time=    300, clk=0, sig_a= 0
time=    350, clk=1, sig_a= 0
time=    400, clk=0, sig_a= 5
time=    450, clk=1, sig_a= 5
time=    500, clk=0, sig_a= 1
time=    550, clk=1, sig_a= 1
Halted at location
**gen_syn_sig.v(17) time
600000 ps from call to $finish.

```

```


always begin
    clk = 0 ; #HF_CYCL ;
    clk = 1 ; #HF_CYCL ;
end

endmodule

```

file name: gen_syn_sig.v

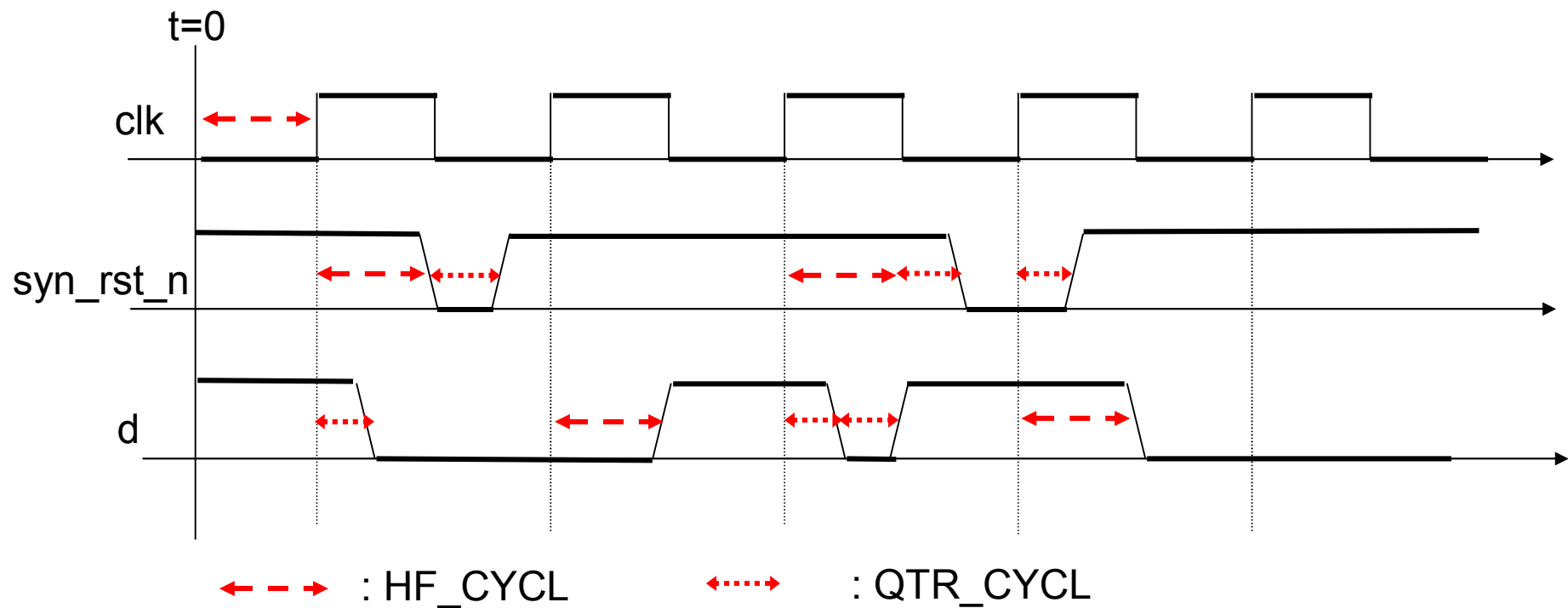Ex 2-10. Clock and signal timing: Write a logic block to generate test input signals shown below for DFF, D-type flip-flop, with synchronous active low reset.



Use the following parameters.

parameter QTR_CYCL = 20 ;

parameter HF_CYCL = QTR_CYCL * 2 ;

```

module test_dff ;
parameter QTR_CYCL = 5 ;
parameter HF_CYCL = QTR_CYCL * 2 ;

reg clk, syn_rst_n ; // non-FF
reg d ; // non-FF
wire q ;

// connect signals to shifter
dff_syn_rst dff_syn_rst_01( .clk(clk), .syn_rst_n(syn_rst_n),
                           .d(d), .q(q) ) ;
// connection end

always begin // clock generator
    clk = 1'b0 ; # HF_CYCL ;
    clk = 1'b1 ; # HF_CYCL ;
end

initial begin
    $monitor ("t= %d, clk=%b, syn_rst_n=%b, d=%b, q=%b",
             $stime, clk, syn_rst_n, d, q ) ;
end

```

```

module dff_syn_rst ( clk, syn_rst_n,
                    d, q ) ;
parameter FF_DLY = 1 ;
input clk, syn_rst_n ;
input d ;
output q ;
wire clk, syn_rst_n, d ;
reg q ; // FF
always @ ( posedge clk )
begin
    if ( syn_rst_n == 1'b0 ) begin
        q <=#FF_DLY 1'b0 ;
    end
    else begin
        q <=#FF_DLY d ;
    end
end
endmodule

```

Write this code block
right after endmodule
source line of module
test_dff.

```

initial begin // for reset signal syn_rst_n
  syn_rst_n = 1'b1 ;
  @ ( posedge clk )
    #(HF_CYCL) syn_rst_n = 1'b0 ;
    #(QTR_CYCL) syn_rst_n = 1'b1 ;
  @ ( posedge clk ) ;
  @ ( posedge clk )
    #(HF_CYCL + QTR_CYCL) syn_rst_n = 1'b0 ;
  @ ( posedge clk ) #(QTR_CYCL) syn_rst_n = 1'b1 ;
  @ ( posedge clk ) ;
  @ ( posedge clk ) $finish ;
end

```

```


initial begin // for input signal d
  d = 1'b1 ;
  @ ( posedge clk )
    #(QTR_CYCL) d = 1'b0 ;
  @ ( posedge clk )
    #(HF_CYCL) d = 1'b1 ;
  @ ( posedge clk )
    #(QTR_CYCL) d = 1'b0 ;
    #(QTR_CYCL) d = 1'b1 ;
  @ ( posedge clk )
    #(HF_CYCL) d = 1'b0 ;
end

```

```

endmodule

```

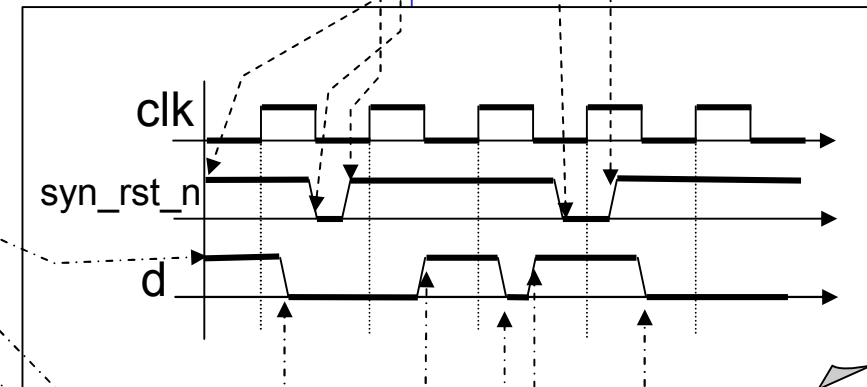


file name: test_dff.v


Insert source code lines for module dff_syn_rst here.

Chapter 3. Combinational logic and test bench

A combinational logic block does not have any memory elements in it.
It can be created by connecting simple AND, OR, NOT, EOR, etc.

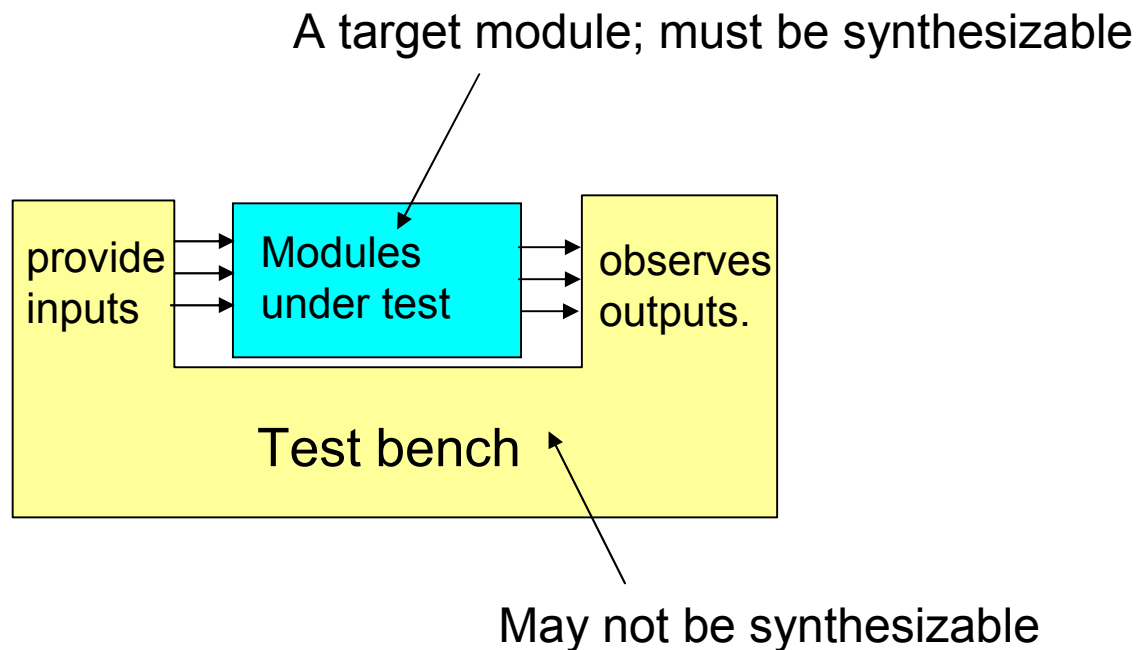

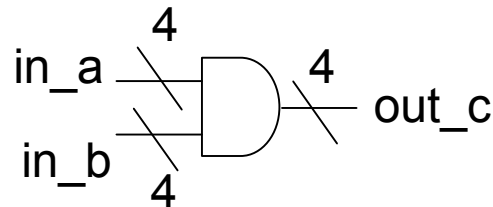Ex 3-1. All-in-one module for testing 4-bit AND: Write a module which has a 4-bit AND gate and logic blocks to generate in_a and in_b and to observe out_c to test the AND gate.



We can define out_c as an output of AND gate by using a **continuous assignment** such as "assign out_c = in_a & in_b ;". in_a and in_b can be generated by using initial construct. To observe out_c, use \$strobe system task.

RTL programming rules

- (1) An output of combinational logic gate can be given by using **continuous assign** statement.
- (2) A continuous assign must start with **assign** key word.
- (3) The data type of an **LHS of a continuous assign must be net data type**. Net data type is declared by using **wire** keyword.

out_c appears on LHS of continuous assign, therefore it must be a net.

```
wire out_c ;  
assign out_c = in_a & in_b ;
```

Unlike a procedural assignment used in a structured procedures, continuous assign is executed whenever its RHS, Right Hand Side, change the value. If in_a or in_b is changed, out_c is given the new value evaluated by the new value of in_a and in_b.

Creating the input signals and observing the output can be done by the following initial construct.

```
initial begin
```

```
    in_b[3:0] = 4'b1100 ;
```

```
    $strobe("time1=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c ) ;
```

```
#10 in_a[3:0] = 4'b0101 ;
```

```
    $strobe("time2=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c ) ;
```

```
#10 in_b[3:0] = 4'b1111 ;
```


```
    $strobe("time3=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c ) ;
```

```
#10 $finish ;
```

```
end
```

→ Set 4'b1100 to in_b at time 0.

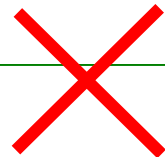→ Show the values on a terminal right after in_b is given the value 1100.



This is not a good programming style.
Use one initial construct for one LHS variable.

```

module and_gate_wo_input ;
  reg [3:0] in_a, in_b ; // non-FF
  wire [3:0] out_c ;

  // logic start
  assign out_c[3:0] = in_a[3:0] & in_b[3:0] ;

  initial begin
    in_b[3:0] = 4'b1100 ;
    $strobe("time1=%d, in_a=%b, in_b=%b,
           $stime, in_a, in_b, out_c ) ;
    #10 in_a[3:0] = 4'b0101 ;
    $strobe("time2=%d, in_a=%b, in_b=%b, out_c=%b",
           $stime, in_a, in_b, out_c ) ;
    #10 in_b[3:0] = 4'b1111 ;
    $strobe("time3=%d, in_a=%b, in_b=%b, out_c=%b",
           $stime, in_a, in_b, out_c ) ;
    #10 $finish ;
  end

endmodule

```

Note that this module has no input port nor output port. in_a and in_b are inputs to the AND gate defined in this module, but they are not the inputs to this module. out_c is the output of the AND gate, but it is not an output of this module which is going out of this module. Therefore, no input port nor output port for this module is needed.

Now create this file in your PC
and run it to see the result.

file name: and_gate_wo_input_v0.v

A sample result

time1=	0,	in_a=xxxx,	in_b=1100,	out_c=xx00	←
time2=	10,	in_a=0101,	in_b=1100,	out_c=0100	←
time3=	20,	in_a=0101,	in_b=1111,	out_c=0101	←

The diagram shows red circles around the values 20, 0101, 1100, and 1111 in the simulation table. Red arrows point from these circles to the corresponding code elements: the first arrow points from the time value '20' to the delay '#10' in the third code line; the second arrow points from the first '0101' to the value '4'b0101' in the second code line; the third arrow points from the '1100' to the value '4'b1100' in the first code line; and the fourth arrow points from the '1111' to the value '4'b1111' in the third code line.

```
initial begin
```

```
    in_b[3:0] = 4'b1100;
```

```
    $strobe("time1=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c );
```

```
    #10 in_a[3:0] = 4'b0101;
```

```
    $strobe("time2=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c );
```

```
    #10 in_b[3:0] = 4'b1111;
```

```
    $strobe("time3=%d, in_a=%b, in_b=%b, out_c=%b",  
            $stime, in_a, in_b, out_c );
```

```
    #10 $finish ;
```

```
end
```

using \$strobe

```
initial begin
    in_b[3:0] = 4'b1100 ;
    $strobe("time1=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
    #10 in_a[3:0] = 4'b0101 ;
    $strobe("time2=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
    #10 in_b[3:0] = 4'b1111 ;
    $strobe("time3=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
    #10 $finish ;
end
```

We can use \$monitor
system task to
observe signals.



```
initial begin
    in_b[3:0] = 4'b1100 ;
    #10 in_a[3:0] = 4'b0101 ;
    #10 in_b[3:0] = 4'b1111 ;
    #10 $finish ;
end
```




This is not a good
programming style.
Use one initial
construct for one
LHS variable.

using \$monitor

```
initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
end
```

RTL programming rules

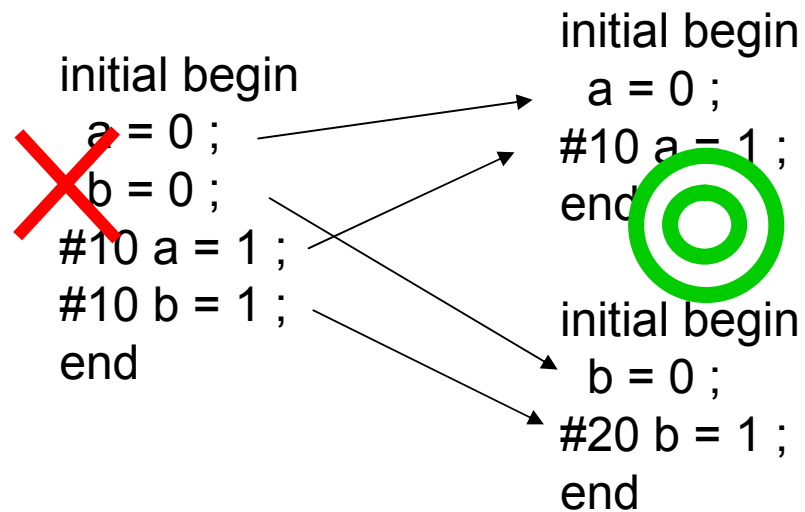(1) Use one initial construct for one LHS, Left Hand Side, variable. Do not write several variables on LHS of one initial construct.



Updating the file and_gate_wo_input.v by using \$monitor system task and using one initial construct for one LHS variable will result in the following code block.

```

module and_gate_wo_input ;
reg [3:0] in_a, in_b ;
wire [3:0] out_c ;

// logic start
assign out_c[3:0] = in_a[3:0] & in_b[3:0] ; // (1)

initial begin
#10 in_a[3:0] = 4'b0101 ;
end
initial begin
    in_b[3:0] = 4'b1100 ;
#20 in_b[3:0] = 4'b1111 ;
end

initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
#30 $finish ;
end
endmodule


```

Use one initial construct for one LHS

Run this file on your
PC and see yourself
how it works.

file name: and_gate_wo_input_v1.v

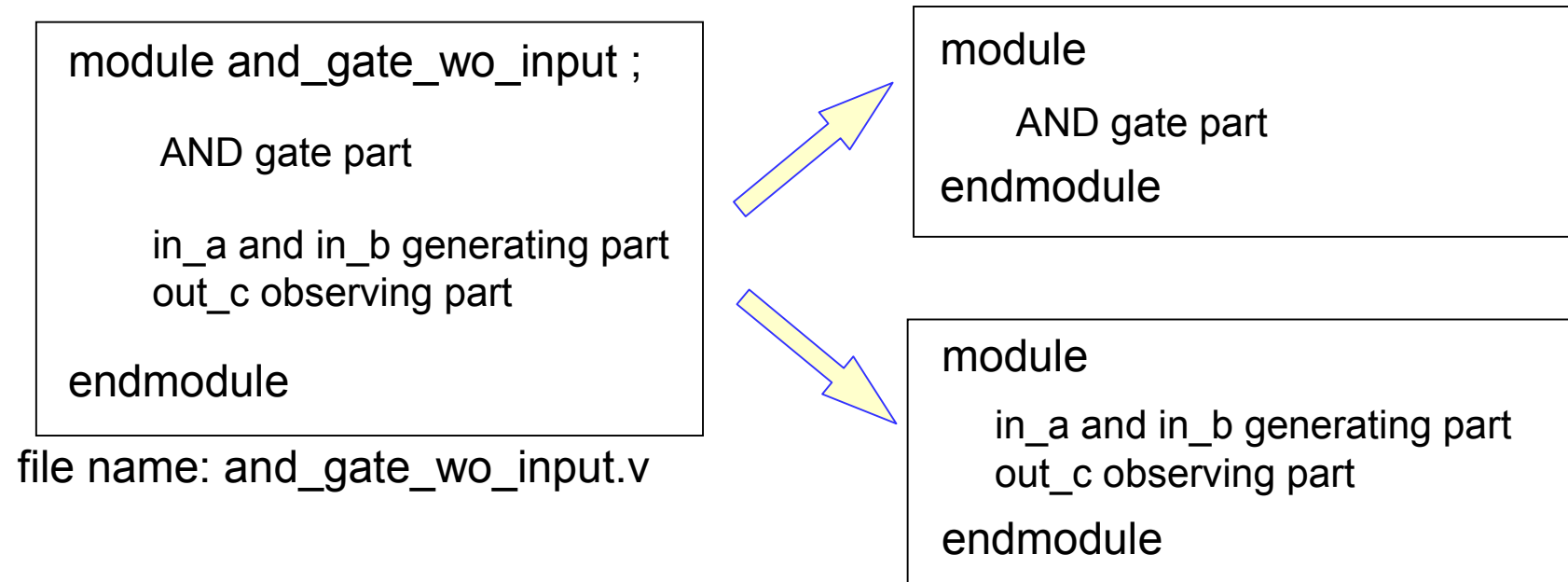Ex 3-2. Test bench and target module: Disintegrate the logic block written in Ex 3-1 into a **target module** which must be implemented into silicon and **test bench** module which does not to into silicon.



Disintegrated modules are connected together by instantiating them and connecting them together by wires. Therefore, disintegrated modules must have input port and/or output ports.

RTL programming rules

(1) The data type of an input port of a module must be net. Therefore signals appearing in the input port list must be declared by **wire** key word in data type declaration.

```
module and_gate( in_a, in_b, , , ) ;
```

```
input  [3:0] in_a, in_b ;
```

```
'''  
wire [3:0] in_a, in_b ;
```

```
endmodule
```


signals in input port
list must be declared
as wire.

Output port can be either reg or wire.

RTL programming rules

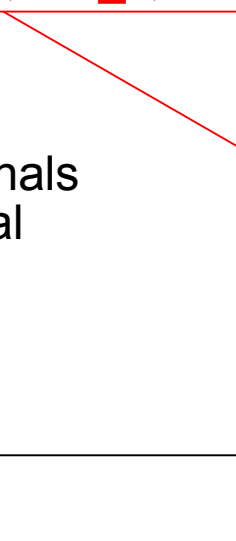(1) A module port list must be written in a **sequence of clock, reset, inputs and outputs**.

```
module abcde( clk, rst, in_a, in_b, out_c, out_d ) ;  
  
input clk ; // clock signal  
input rst ; // reset signal  
input [3:0] in_a, in_b ; // input signals  
output [3:0] out_c ; // output signal  
  
endmodule
```



List up the ports in a sequence of;
first **clock** signals, then **reset** signals,
and then **input** signals, and lastly **output** signals.

First, pull out the target module from and_gate_wo_input module.

```
module and_gate_wo_input ;
reg [3:0] in_a, in_b ;
wire [3:0] out_c ;
```

This part must be the target block.

```
// logic start
assign out_c[3:0] = in_a[3:0] & in_b[3:0];
```

```
initial begin
    in_b[3:0] = 4'b1100 ;
    #10 in_a[3:0] = 4'b0101 ;
    #10 in_b[3:0] = 4'b1111 ;
    #10 $finish ;
end
initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
        $stime, in_a, in_b, out_c);
end
endmodule
```

```
module and_gate( in_a, in_b, out_c ) ;
```

```
input  [3:0] in_a, in_b ;
output [3:0] out_c ;
```

```
wire [3:0] in_a, in_b ;
wire [3:0] out_c ;
```

```
// logic start
assign out_c[3:0] =
    in_a[3:0] & in_b[3:0] ; // (1)
```

```
endmodule
```

in_a and in_b must come from outside of this module and out_c must go out of this module. Therefore, they must be declared as input and output ports

Next, extract test input and observe block which must not go into silicon.

```
module and_gate_wor
reg [3:0] in_a, in_b ;
wire [3:0] out_c ;
```

```
// logic start
assign out_c[3:0] = in_a & in_b;
```

```
initial begin
    in_b[3:0] = 4'b1100;
    #10 in_a[3:0] = 4'b0101;
    #10 in_b[3:0] = 4'b1111;
    #10 $finish ;
end
initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c);
end
endmodule
```

```
module test_observe ( out_c, in_a, in_b ) ;
```

```
input  [3:0] out_c;
output [3:0] in_a, in_b ;
```

```
reg [3:0] in_a, in_b ;
wire [3:0] out_c ;
```

```
initial begin
    in_b[3:0] = 4'b1100 ;
    #10 in_a[3:0] = 4'b0101 ;
    #10 in_b[3:0] = 4'b1111 ;
    #10 $finish ;
end
```


```
initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
end
endmodule
```


Note that out_c is an input, and in_a and in_b are outputs in this module, whereas in_a and in_b are inputs and out_c is an output in the target module.

And also note that in_a and in_b are declared as register because procedural assignment is used to assign values to these signals.

Now the original module is disintegrated into `and_gate` module and `test_observe` module.

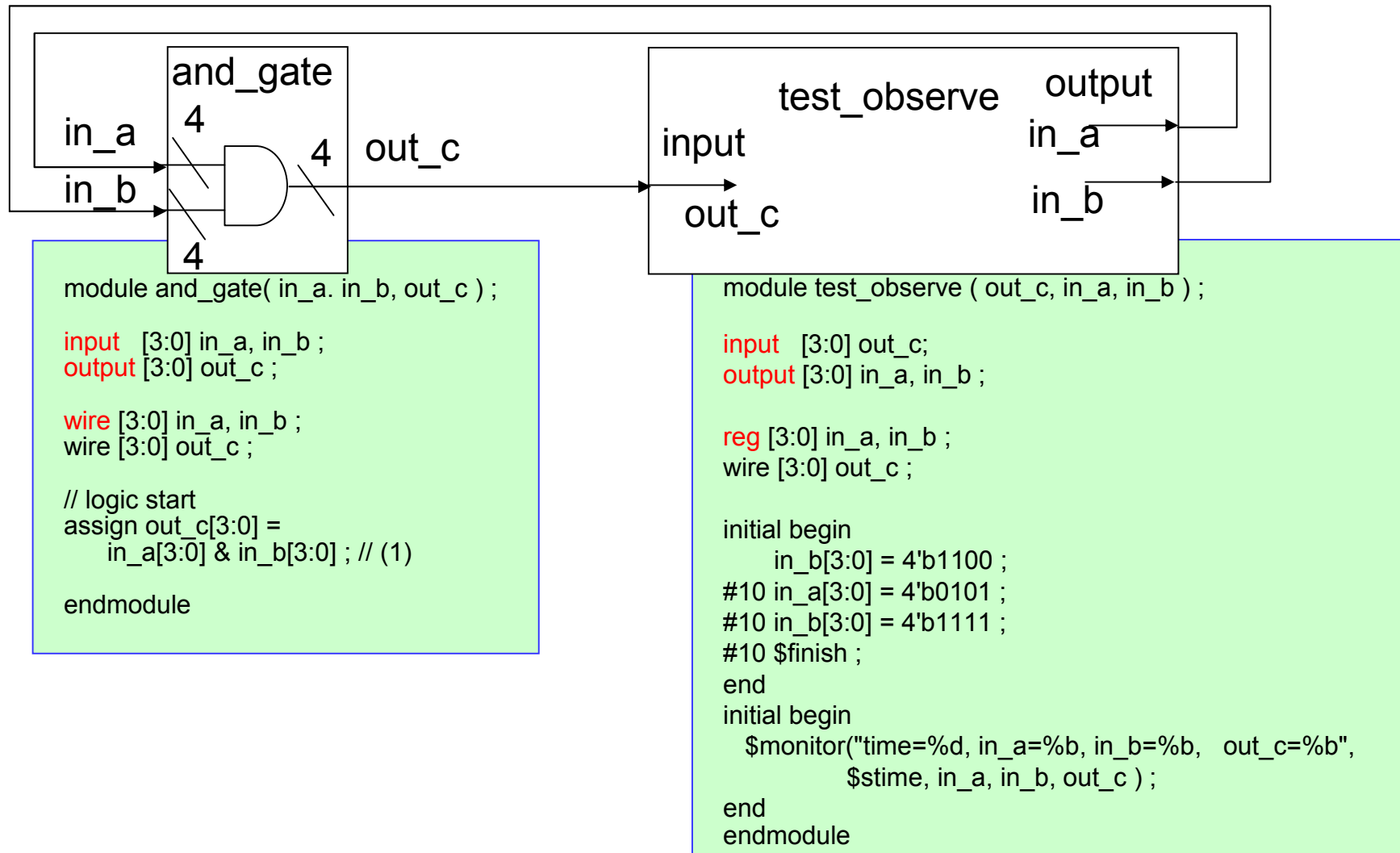We need to connect these two together as shown below by introducing a new module, `and_gate_top_lvl`.



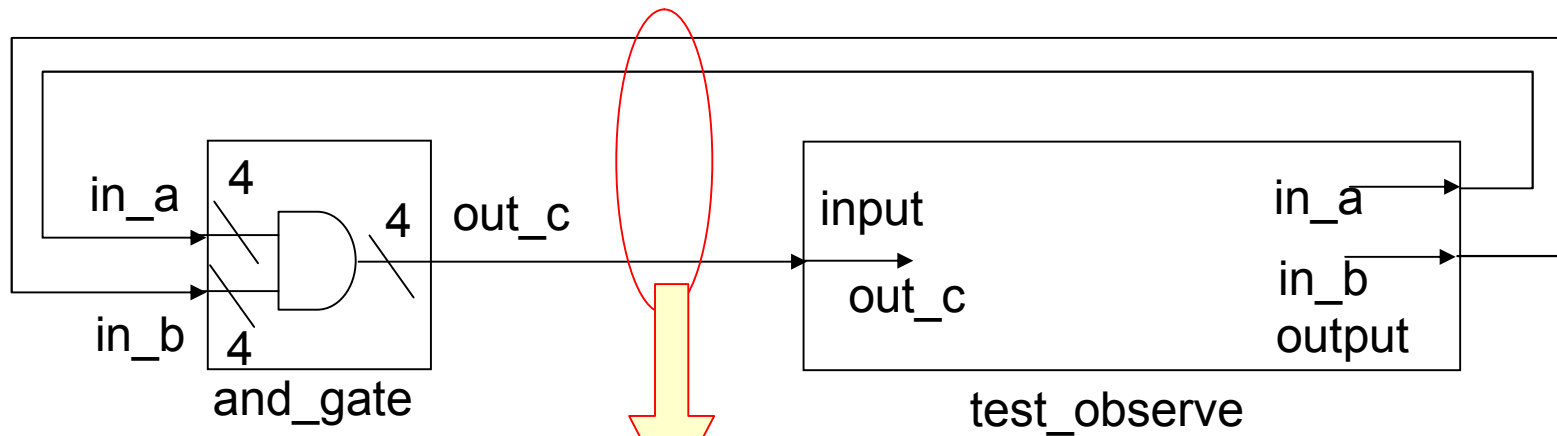

```

module and_g
input [3:0] in_
output [3:0] ou

wire [3:0] in_a
wire [3:0] out_

// logic start
assign out_c[3:0] =
in_a[3:0] &
endmodule

```

```

module and_gate_top_lvl ;

```

```

wire [3:0] in_a, in_b ;
wire [3:0] out_c ;

```

```

// module connection

```

```

and_gate and_gate_01 ( .in_a( in_a ), .in_b ( in_b ),
                        .out_c(out_c) ) ;

```

```

test_observe test_observe_01 (.out_c(out_c),
                              .in_a( in_a ), .in_b ( in_b ) ) ;

```

```

endmodule

```

and_gate_top_lvl has no input nor output port because no signal is going out of this module and coming in from outside.

In the top level module, all the connecting signal lines must be defined as nets.

```

c=%b",

```

```
// module connection
and_gate  and_gate_01 ( .in_a( in_a ). .in_b ( in_b ),
                        .out_c(out_c) );
test_observe  test_observe_01 (.out_c(out_c),
                               .in_a( in_a ). .in_b ( in_b ) );
```


“and_gate and_gate_01” means that the module and_gate is incorporated in and_gate_top_lvl module, and the instance is given the name “and_gate_01”.

It is recommended to give the name to an instance such as “modulename_01”.

Instance is an object which goes into silicon. The same module can be incorporated into a module again and again. If it is incorporated 3 times, there must be three instances, one instance for one incorporation.

The connection among the two modules are done using “port connection by name” in the example above. “.in_a” means the port name “in_a”. “.in_a(in_a)” means signal “in_a” is connected to the port “in_a”.

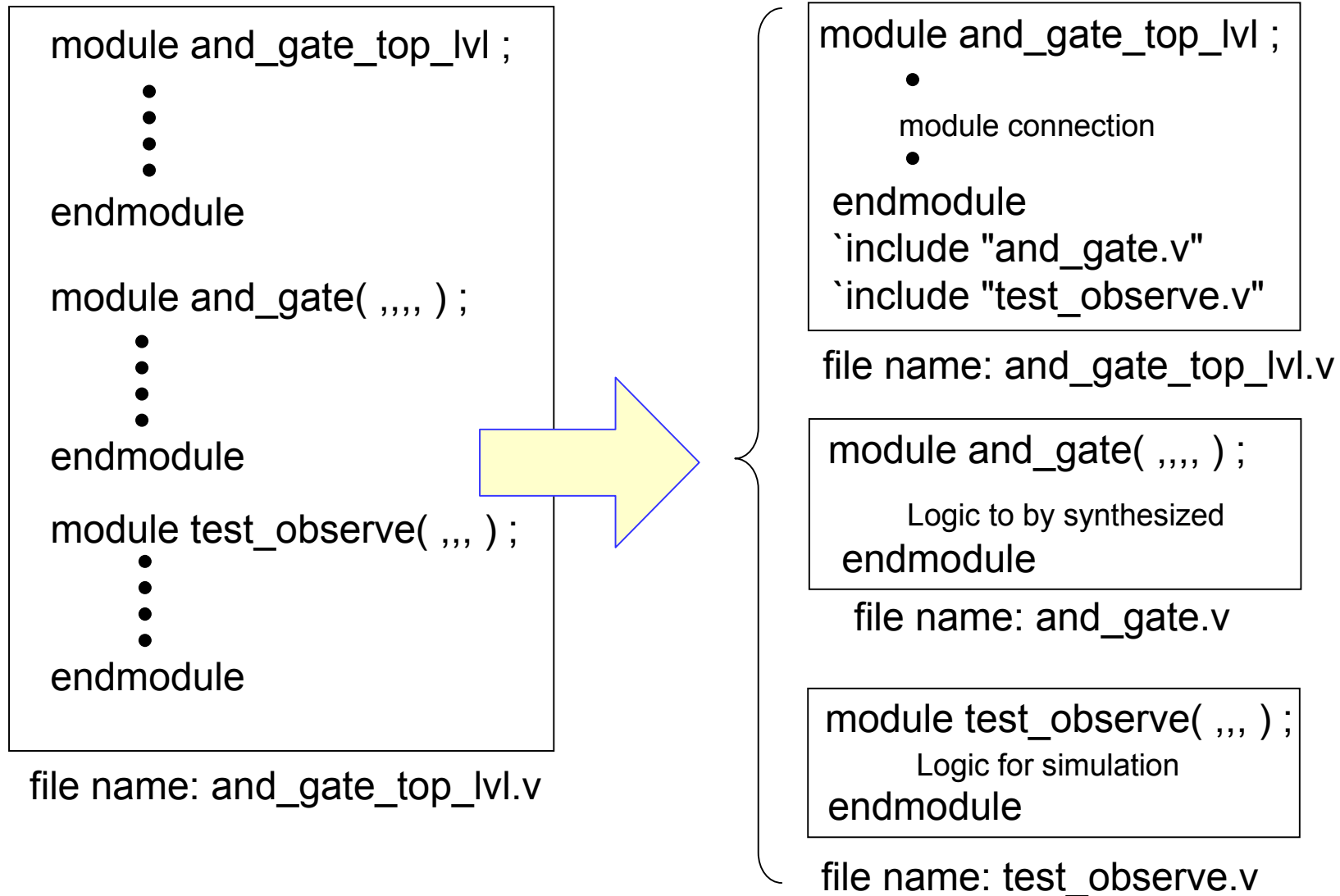Disintegrated modules can be in one file or in several files as shown in this slide or in the next slide.




```

module and_gate_top_lvl ;
    •
    module connection
    •
endmodule
`include "and_gate.v"
`include "test_observe.v"

```

file name: and_gate_top_lvl.v

```

module and_gate( ,,, ) ;
    Logic to by synthesized
endmodule

```

file name: and_gate.v

```

module test_observe( ,,, ) ;
    Logic for simulation
endmodule

```

file name: test_observe.v

```

module test_and_gate ;
    •
    •
    module connection
    •
    •
    Logic for simulation
    •
endmodule
`include "and_gate.v"

```

file name: test_and_gate.v

```

module and_gate( ,,, ) ;
    Logic to by synthesized
endmodule

```

file name: and_gate.v

Now, create files for Exercise 3-2 by using the style shown on the right.

```

module and_gate_top_lvl ;
  wire [3:0] in_a, in_b ;
  wire [3:0] out_c ;
  // module connection
  and_gate and_gate_01 ( .in_a( in_a ). .in_b ( in_b ),
                        .out_c(out_c) ) ;
  test_observe test_observe_01 (.out_c(out_c),
                               .in_a( in_a ). .in_b ( in_b ) ) ;

endmodule

```

```

module and_gate( in_a, in_b, out_c ) ;
  input [3:0] in_a, in_b ;
  output [3:0] out_c ;
  wire [3:0] in_a, in_b ;
  wire [3:0] out_c ;
  // logic start
  assign out_c[3:0] = in_a[3:0] & in_b[3:0] ; // (1)
endmodule

```

```

module test_observe ( out_c, in_a, in_b ) ;
  input [3:0] out_c;
  output [3:0] in_a, in_b ;
  reg [3:0] in_a, in_b ;
  wire [3:0] out_c ;
  initial begin
    in_b[3:0] = 4'b1100 ;
    #10 in_a[3:0] = 4'b0101 ;
    #10 in_b[3:0] = 4'b1111 ;
    #10 $finish ;
  end
  initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
  end
endmodule

```

```

module test_and_gate ;

```

```

  •
  •
  • module connection
  •
  •
  • Logic for simulation
  •

```

```

endmodule

```

```

`include "and_gate.v"

```

file name: test_and_gate.v

```

module and_gate( ,,, ) ;

```

Logic to be synthesized

```

endmodule

```

file name: and_gate.v

```

module and_gate( in_a, in_b, out_c ) ;
  input  [3:0] in_a, in_b ;
  output [3:0] out_c ;
  wire [3:0] in_a, in_b ;
  wire [3:0] out_c ;
  // logic start
  assign out_c[3:0] = in_a[3:0] & in_b[3:0] ; // (1)
endmodule

```

file name: and_gate.v

```

module test_and_gate ;
  reg [3:0] in_a, in_b ; // inputs for AND gate
  wire [3:0] out_c ; // output of AND gate

  and_gate and_gate_01 ( .in_a(in_a), .in_b(in_b),
                        .out_c(out_c) )

  initial begin
    in_b[3:0] = 4'b1100 ;
    #10 in_a[3:0] = 4'b0101 ;
    #10 in_b[3:0] = 4'b1111 ;
    #10 $finish ;
  end
  initial begin
    $monitor("time=%d, in_a=%b, in_b=%b, out_c=%b",
            $stime, in_a, in_b, out_c ) ;
  end
endmodule


`include "and_gate.v"

```

file name: test_and_gate.v


Run this file and see
the result yourself.

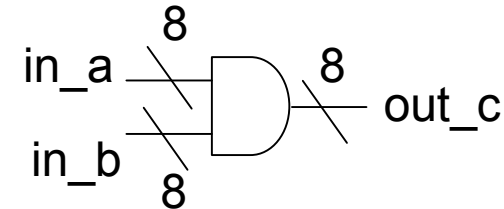Ex 3-3. Using two instances of one module: Write a module equivalent to the gate shown below by using `and_gate.v` file **without changing any single character** in the file.




In this exercise, we will learn how to use existing modules. Let's design 8-bit AND logic block by using 4-bit AND logic block, `and_gate.v` which we designed in Ex 3-2.

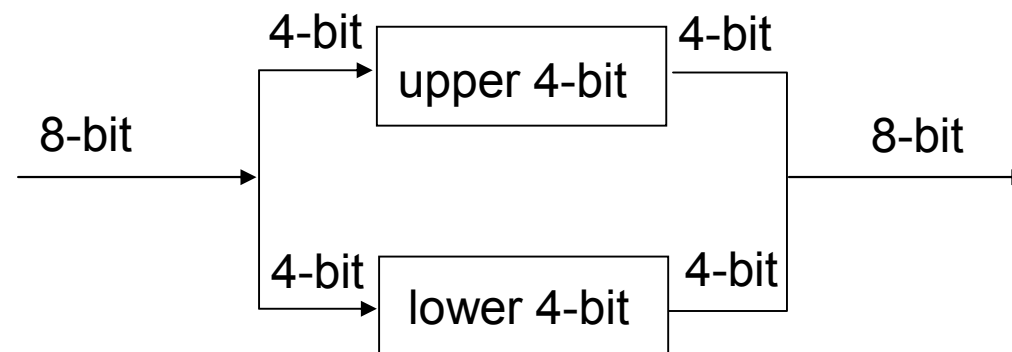Disintegrate 8-bit signals into two 4-bit signals and apply `and_gate` module to each 4-bit signals.



and_gate module can be used twice in the and_gate_byte module. Each of the and_gate module used in and_gate_byte is called “instance”.

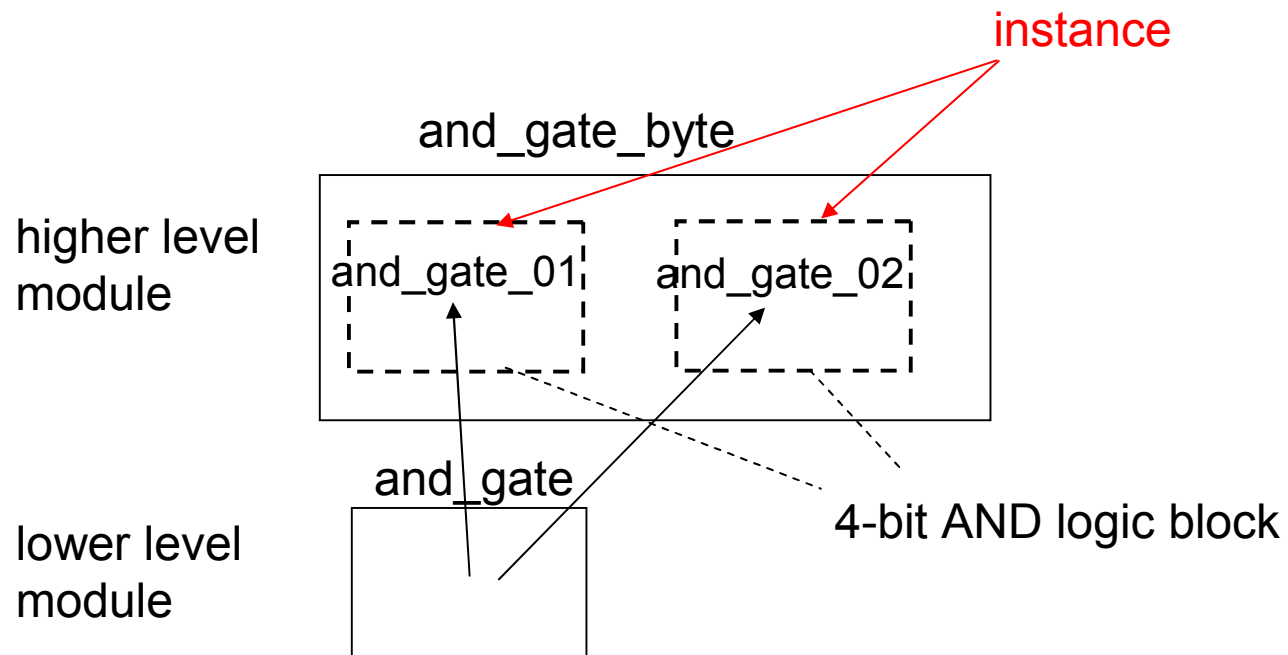
There must be two instances, and_gate_01 and and_gate_02, because two and_gate is needed to build 8-bit AND gate.



The wire connection among the two instances and the ports of and_gate_byte module are shown in this slide.


Upper 4-bit of the 8-bit input in_a must go into and_gate_01 and the output of and_gate_01 must go into upper 4-bit of the 8-bit out_c.

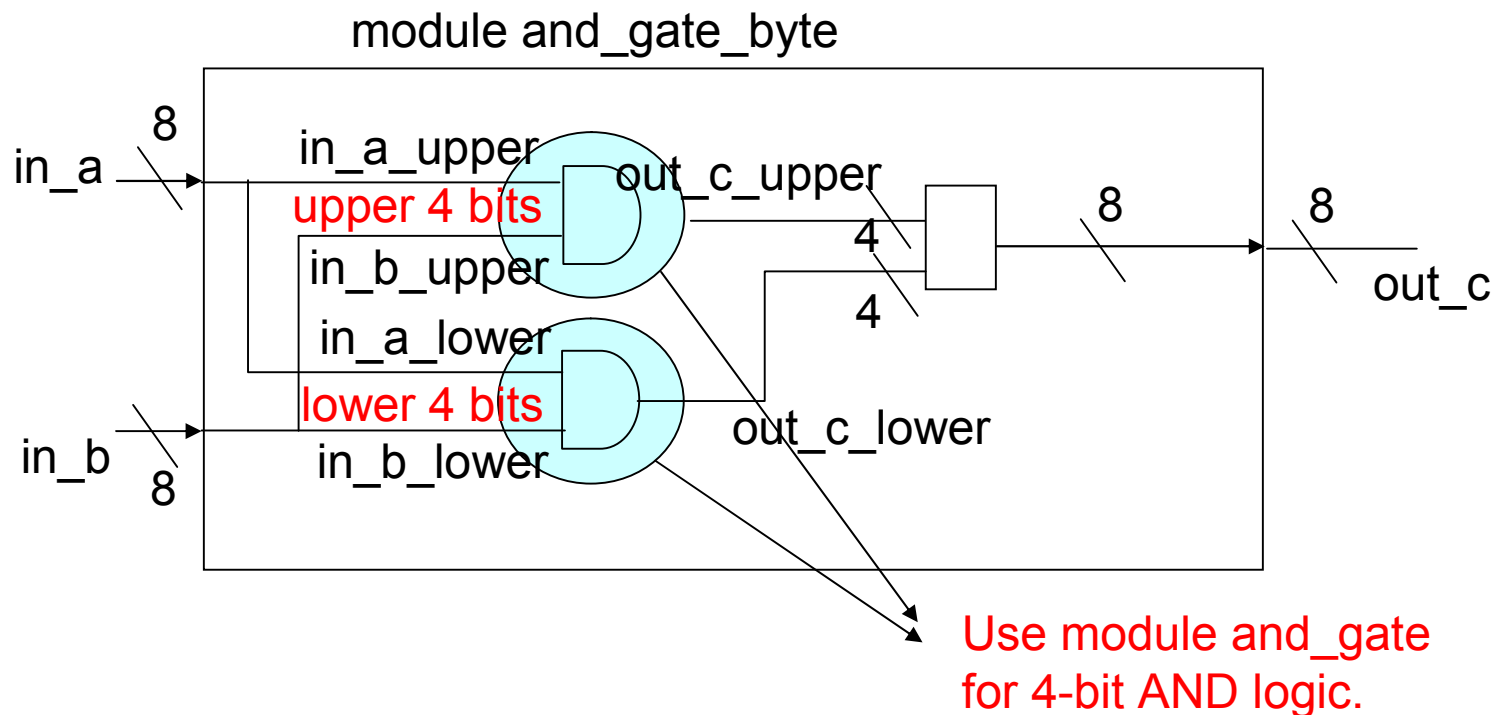Lower 4-bit of the 8-bit input in_a must go into and_gate_02 and the output of and_gate_02 must go into lower 4-bit of the 8-bit out_c.



To identify a part of n-bit vector signal, such as upper 4-bit of 8-bit signal, we can use **part selection** of a vector as shown in this slide.
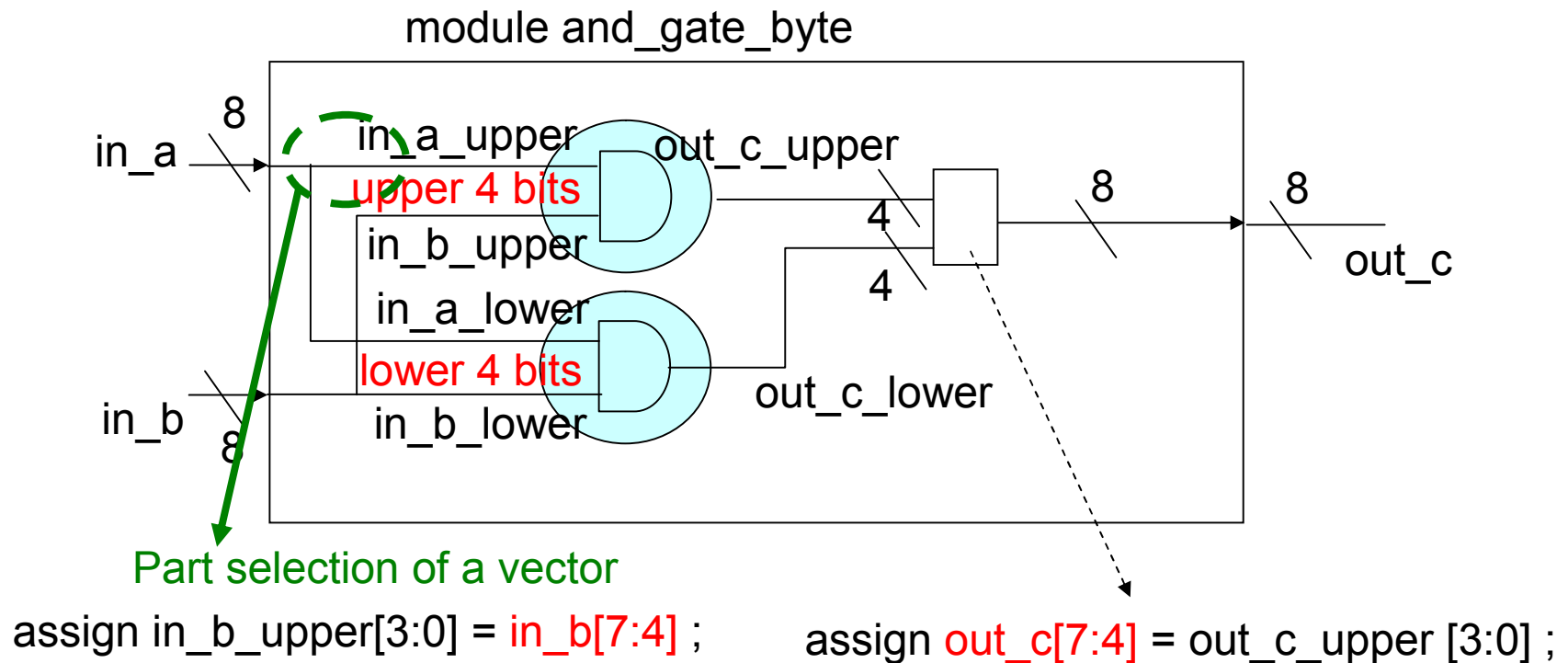
`in_b[7:4]` means 4-bit signal consists of `in_b[7]`, `in_b[6]`, `in_b[5]`, and `in_b[4]`.



Now, write the module `and_gate_byte` and name the file `and_gate_byte_v0.v`

```

module and_gate_byte ( in_a, in_b, out_c );
  input [7:0] in_a, in_b ;
  output [7:0] out_c ;

```

```

  wire [7:0] in_a, in_b ;
  wire [7:0] out_c ;
  // internal connecting wire
  wire [3:0] in_a_upper, in_a_lower ;
  wire [3:0] in_b_upper, in_b_lower ;
  wire [3:0] out_c_upper, out_c_lower ;

```

```

  // separate byte to upper and lower
  assign in_a_upper[3:0] = in_a[7:4] ;
  assign in_a_lower[3:0] = in_a[3:0] ;
  assign in_b_upper[3:0] = in_b[7:4] ;
  assign in_b_lower[3:0] = in_b[3:0] ;
  // merge upper and lower
  assign out_c[7:4] = out_c_upper [3:0] ;
  assign out_c[3:0] = out_c_lower [3:0] ;

```

```

  // module conndection
  and_gate and_gate_01 ( .in_a( in_a_upper ), .in_b ( in_b_upper ),
                        .out_c(out_c_upper) ) ;
  and_gate and_gate_02 ( .in_a( in_a_lower ), .in_b ( in_b_lower ),
                        .out_c(out_c_lower) ) ;

```

```

endmodule

```

The module and_gate_byte has 8-bit ports because the target logic is 8-bit AND logic.

“assign in_a_upper[3:0] = in_a[7:4];” means that in_a[7] is assigned to in_a_upper[3], in_a[6] to in_a_upper[2], in_a[5] to in_a_upper[1], and in_a[4] to in_a_upper[0].


Next, think of improving this code by using { } Verilog operator. { } can be used as shown in the next slide.

file name: and_gate_byte_v0.v


Byte swap;

```
wire [15:0] sig_y, sig_w ;
```
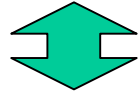
```
assign sig_y = { sig_w[7:0] , sig_w[15:8] } ;
```


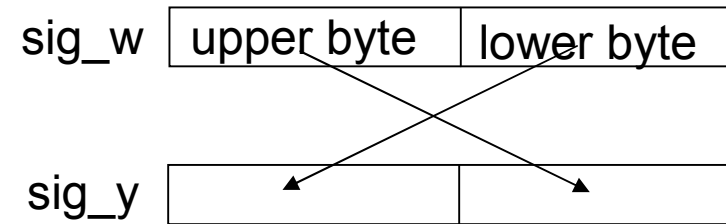
```
assign { sig_y[7:0] , sig_y[15:8] } = sig_w[15:0] ;
```



Bit rotation :

```
assign next_sig_w[15:0] = { sig_w[0] , sig_w[15:1] } ;
```

← shift rotate right

```
assign next_sig_w[15:0] = { sig_w[14:0] , sig_w[15] } ;
```

← shift rotate left

Bit size flexibility

```
parameter B_WD = 16 ;
```

```
reg [B_WD-1:0] sig_w ;
```

```
sig_w = { B_WD {1'b0} } ;
```

← set 16'b0 to sig_w

```
sig_w = { {(B_WD-1) {1'b0} } , 1'b1 } ;
```

← set 16'b1 to sig_w

```

module and_gate_byte ( in_a, in_b, out_c ) ;
  input [7:0] in_a, in_b ;
  output[7:0] out_c ;

```

```

  wire [7:0] in_a, in_b ;
  wire [7:0] out_c ;
  // internal connecting wire
  wire [3:0] in_a_upper, in_a_lower ;
  wire [3:0] in_b_upper, in_b_lower ;
  wire [3:0] out_c_upper, out_c_lower ;

```

```

  // separate byte to upper and lower
  assign { in_a_upper, in_a_lower } = in_a ;
  assign { in_b_upper, in_b_lower } = in_b ;
  // merge upper and lower
  assign out_c = { out_c_upper, out_c_lower } ;

```

```

  // module connection
  and_gate and_gate_01 ( .in_a( in_a_upper ), .in_b ( in_b_upper ),
                        .out_c(out_c_upper) ) ;
  and_gate and_gate_02 ( .in_a( in_a_lower ), .in_b ( in_b_lower ),
                        .out_c(out_c_lower) ) ;

```

```
endmodule
```

file name: and_gate_byte_v1.v

An example of improved code block using { }.

Next, write a test bench to test this module.

Name the file: test_and_gate_byte.v.

```

module test_and_gate_byte ;
reg [7:0] in_a, in_b ;
wire [7:0] out_c ;

and_gate_byte and_gate_byte_01 (
    .in_a( in_a), .in_b(in_b),
    .out_c(out_c)
) ;


initial
begin
    in_b[7:0] = 8'hC0 ;
    #10 in_a[7:0] = 8'h55 ;
    #10 in_b[7:0] = 8'hF3 ;
    #10 $finish ;
end
initial begin
    $monitor("time=%d, in_a=%h, in_b=%h, out_c=%h",
        $stime, in_a, in_b, out_c ) ;
end
endmodule
`include "and_gate.v"
`include "and_gate_byte_v1.v"

```

Now, run this file on your
PC to see the result.

file name: test_and_gate_byte.v

A sample result

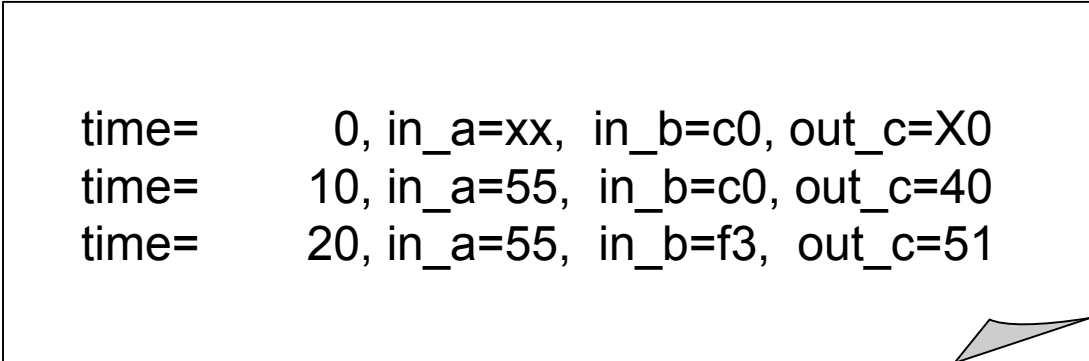

```
time=      0, in_a=xx, in_b=c0, out_c=X0  
time=     10, in_a=55, in_b=c0, out_c=40  
time=     20, in_a=55, in_b=f3, out_c=51
```

Next think further
simplification.



You may use part
selection of a
vector.

```
module and_gate_byte ( in_a, in_b, out_c );
  input [7:0] in_a, in_b ;
  output[7:0] out_c ;
```

```
  wire [7:0] in_a, in_b ;
  wire [7:0] out_c ;
```

```
  // internal connecting wire
```

```
  wire [3:0] in_a_upper, in_a_lower ;
  wire [3:0] in_b_upper, in_b_lower ;
  wire [3:0] out_c_upper, out_c_lower ;
```

```
  // separate byte to upper and lower
```

```
  assign { in_a_upper, in_a_lower } = in_a ;
```

```
  assign { in_b_upper, in_b_lower } = in_b ;
```

```
  // merge upper and lower
```


```
  assign out_c = { out_c_upper, out_c_lower } ;
```

```
  // module conndection
```

```
  and_gate  and_gate_01 ( .in_a( in_a_upper ),.in_b ( in_b_upper ),
                           .out_c(out_c_upper) ) ;
```

```
  and_gate  and_gate_02 ( .in_a( in_a_lower ), .in_b ( in_b_lower ),
                           .out_c(out_c_lower) ) ;
```

```
endmodule
```

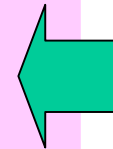

Can't we eliminate
this part?

file name: and_gate_byte_v1.v

```
module and_gate_byte ( in_a, in_b, out_c ) ;
```

```
  input [7:0] in_a, in_b ;
```

```
  output [7:0] out_c ;
```

```
  wire [7:0] in_a, in_b ;
```

```
  wire [3:0] out_c_upper, out_c_lower , // internal connecting wire
```

```
  wire [7:0] out_c = { out_c_upper, out_c_lower } ;
```

```
  // separate byte to upper and lower
```

```
  and_gate and_gate_01 ( .in_a( in_a[7:4] ), .in_b ( in_b[7:4] ),  
                        .out_c(out_c_upper) ) ;
```

```
  and_gate and_gate_02 ( .in_a( in_a[3:0] ), .in_b ( in_b[3:0] ),  
                        .out_c(out_c_lower) ) ;
```

```
endmodule
```

This is called net declaration assignment.
It is same to;

```
  wire [7:0] out_c ;  
  assign out_c = { out_c_upper, out_c_lower }  
  ;
```

Part selection is used. 4-bit out of 8-bit vector is used to connect ports.

file name: and_gate_byte_v2.v

It is not recommended to use net declaration assignment in general. However, we may use it when the assignment is very simple and obvious.

```

module and_gate_byte ( in_a, in_b, out_c ) ;
  input [7:0] in_a, in_b ;
  output [7:0] out_c ;

  wire [7:0] in_a, in_b ;

wire [3:0] out_c_upper, out_c_lower, // internal connecting wire

wire [7:0] out_c = { out_c_upper, out_c_lower } ;

  // separate byte to upper and lower
  and_gate and_gate_01 ( .in_a( in_a[7:4] ), .in_b ( in_b[7:4] ),
                        .out_c(out_c_upper) ) ;
                        out_c[7:4]
  and_gate and_gate_02 ( .in_a( in_a[3:0] ), .in_b ( in_b[3:0] ),
                        .out_c(out_c_lower) ) ;
                        out_c[3:0]

endmodule


```

We can eliminate these part by using part select of out_c.

file name: and_gate_byte_v2.v
v3

Run those files, and_gate_byte_v0.v, _v1.v, _v2.v, and _v3.v on your PC and check yourself if the results are exactly the same.

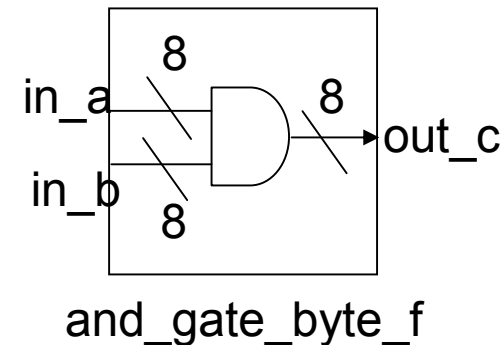Ex 3-4. How to use function: Write a function `func_and_gate` having the same functionality to module `and_gate`, and rewrite the code in `and_gate_byte_v3.v` using it.
Name the updated module `and_gate_byte_f`.



Logic in `and_gate.v` is so simple and there is no memory element in it. Therefore, it can be described by using function instead of module.

Function can be invoked as many time as you like. Each line invoking a function needs silicon area for the function. That is, if a function is called in many lines, silicon size will increase.

module

```
assign y = func_name( argy,,, ) ;
assign w = func_name( argw,,, ) ;
```

← A function can be invoked by continuous assign and by procedural assign.

```
function [n:0] func_name ;
input ,,, ;
reg ,,, ;


endfunction
```

} A function definition starts with function key word and end with endfunction key word. It must have at least one input argument.

endmodule

RTL programming rules

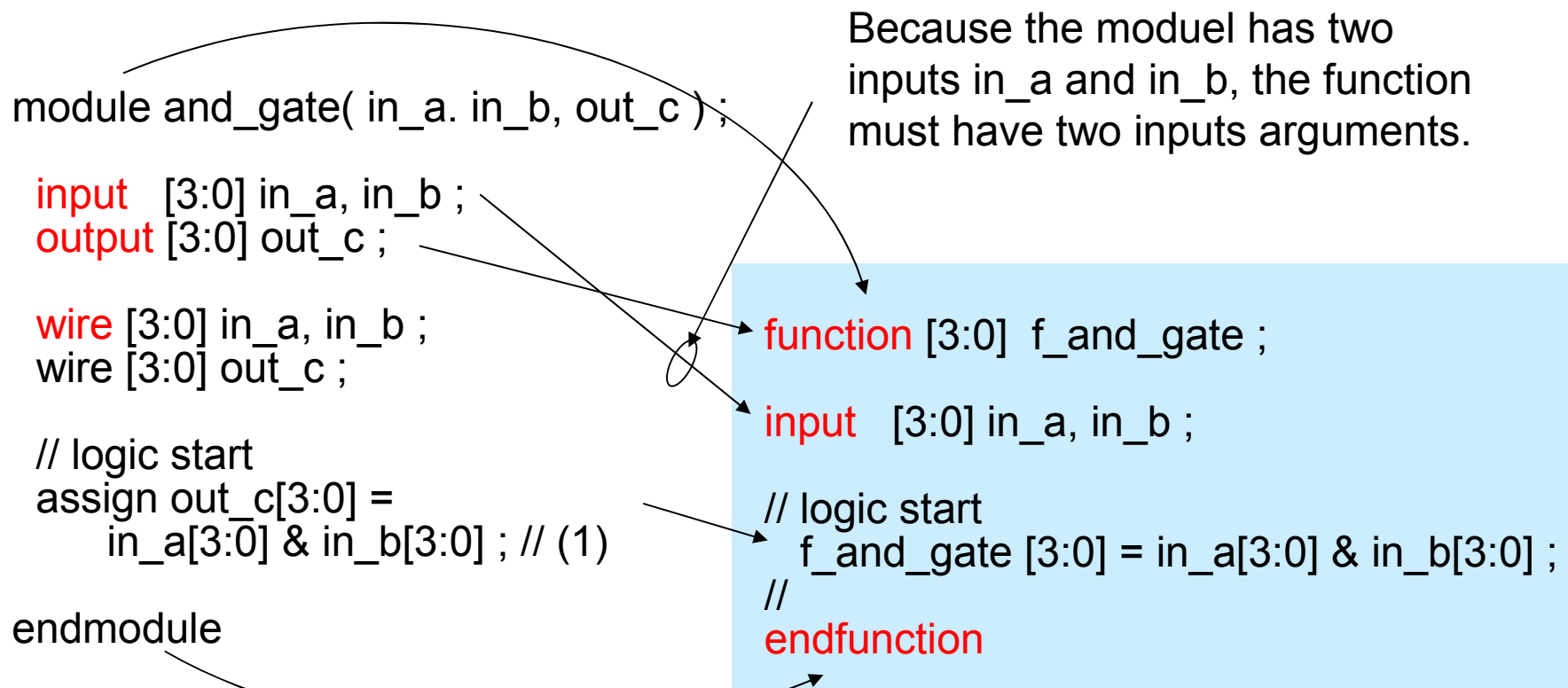- (1) function must be declared inside the module.
- (2) function can not go beyond module boundary.
- (3) In function, **LHS must be register data type**.
- (4) function can have only on output. (No output argument allowed, output is given through its name.)
- (5) function must have at least one input argument. It may have several inputs.
- (6) **No # nor @ allowed** in function.



We do not have to declare data type for the input arguments of a function. We do not have to declare data type of in_a and in_b.


The output of a function is defined by the function name. We have to assign values to f_and_gate [3:0]. If the output consists of multi bits, we need bit width declaration for the function.

```
module and_gate_byte ( in_a, in_b, out_c ) ;  
  input [7:0] in_a, in_b ;  
  output[7:0] out_c ;  
  
  wire [7:0] in_a, in_b ;  
  wire [7:0] out_c ;  
  //  
  assign out_c[7:4] = f_and_gate( in_a[7:4] , in_b[7:4] ) ;  
  assign out_c[3:0] = f_and_gate( in_a[3:0] , in_b[3:0] ) ;  
  //  
  // function  
  function [3:0] f_and_gate ;  
  input  [3:0] in_a, in_b ;  
  // logic start  
  f_and_gate [3:0] = in_a[3:0] & in_b[3:0] ;  
  //  
  endfunction  
  //  
endmodule
```

and_gate_byte.f.v

Run this file on your simulator and see yourself if it works correctly.

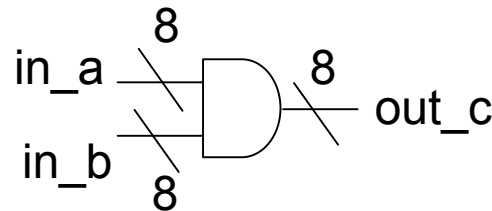Ex 3-5. Parameterize bit width: Write a module equivalent to the gate shown below by **modifying and_gate.v** file. Use parameter to extend the bit width of in_a, in_b, and out_c.



In this exercise , we will learn how to use parameter.

Usually we do not use 4-bit AND logic block to create 8-bit AND logic block. We apply AND operator directly on 8-bit signals to get 8-bit AND. In this exercise we will learn a method to make bit size flexible.

First, think of changing bit width declaration of the signals.

We can modify and_gate module by changing 3 to 7 to get 8-bit AND as below.

```
module and_gate( in_a, in_b, out_c ) ;
input  [3:0] in_a, in_b ;
output [3:0] out_c ;

wire [3:0] in_a, in_b ;
wire [3:0] out_c ;

// logic start
assign out_c[3:0] =
    in_a[3:0] & in_b[3:0] ; // (1)

endmodule
```

Rewriting the bit width

```
module and_gate( in_a, in_b, out_c ) ;
input  [7:0] in_a, in_b ;
output [7:0] out_c ;

wire [7:0] in_a, in_b ;
wire [7:0] out_c ;

// logic start
assign out_c[7:0] =
    in_a[7:0] & in_b[7:0] ; // (1)

endmodule
```

Isn't there more flexible way??

Parameterize



```

module and_gate( in_a, in_b, out_c ) ;

// parameter
parameter SIG_BW = 8 ;

// port
input  [SIG_BW-1:0] in_a, in_b ;
output [SIG_BW-1:0] out_c ;

wire [SIG_BW-1:0] in_a, in_b ;
wire [SIG_BW-1:0] out_c ;

// logic start
assign out_c = in_a & in_b ; // (2)

endmodule

```

file name: and_gate_p.v


An example shown in this slide defines a parameter named SIG_BW whose value is 8.

“input [SIG_BW-1:0] in_a, in_b ;” means that input port in_a and in_b have the bit-width SIG_BW, 8 in this example.

By using this parameter, when we are asked to create AND logic for 32 bits signal, only one line, **parameter** SIG_BW = 8 ;, has to be changed to “**parameter** SIG_BW = 32 ;”. No other lines have to be modified.

This is an answer for Ex 3-5.

Parameterize

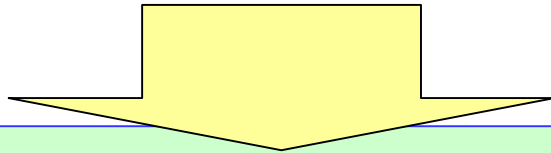

```
module and_gate( in_a, in_b, out_c ) ;

// parameter
parameter SIG_BW = 8 ;

// port
input  [SIG_BW-1:0] in_a, in_b ;
output [SIG_BW-1:0] out_c ;

wire [SIG_BW-1:0] in_a, in_b ;
wire [SIG_BW-1:0] out_c ;

// logic start
assign out_c = in_a & in_b ; // (2)

endmodule
```

file name: and_gate_p.v

When the bit width of the parameter itself has to be defined, we can use declarations shown below.

Unless the bit width is not declared, parameter has 32-bit length.

```
parameter SIG_BW = 16'h08 ;
parameter [15:0] SIG_BW = 8 ;
```

Now, type the file on the left and create a test bench file "test_and_gate_p.v" to test the module on the left.


```

module test_and_gate_p ;
// parameter
parameter SIG_BW = 16 ;
defparam and_gate_01.SIG_BW = SIG_BW ;
// signals
reg [SIG_BW-1:0] in_a, in_b ;
wire [SIG_BW-1:0] out_c ;

and_gate and_gate_01 (
    .in_a(in_a), .in_b(in_b),
    .out_c(out_c)
) ;

initial begin
    in_b = 16'hC0C0 ;
    #10 in_a = 16'h55AA ;
    #10 in_b = 16'hF310 ;
    #10 $finish ;
end

initial begin
    $monitor("time=%d, in_a=%h, in_b=%h, out_c=%h",
        $stime, in_a, in_b, out_c ) ;
end

endmodule
`include "and_gate_p.v"

```

Parameter can be overwritten by using defparam key word.

“defparam and_gate_01.SIG_BW = 32;” means the parameter SIG_BW defined in an instance and_gate_01 shall be overwritten by 32.

“defparam and_gate_01.SIG_BW = SIG_BW ;” means that the parameter defined in the instance and_gate_01 shall be overwritten by SIG_BW defined in the module test_and_gate_p, that is 16.

Now, run this file on your PC and see yourself how defparam works.

file name: test_and_gate_p.v

Ex 3-6. Assign for combinational logic: Write a module equivalent to the truth table shown below. An input port is 4-bit in_a and an output port is 3-bit out_y. Use continuous assign only to write the module. **Do not use always constructs** for the module.

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

In this exercise , we will learn how to use assign and conditional operator. A sentence may

assign yyy = (*expression*)? *expression1* : *expression2* ;

First, expression is evaluated and if it is true then the value of expression1 is assigned to yyy. If the expression is not true, then the value of expression2 is assigned to yyy.

Do not try to find a solution for all bits at one time. Think the logic for each bit. First find the logic for out_y[2] and then out_y[1] and then finally out_y[0].

Investigating the truth table, we can find out that out_y[2] is 1 only when in_a is 4'b0000.

The sentence below will assign 0 to out_y[2] if in_a is not 4'b0000, and assign 1 if in_a is 4'b0000.

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

```
assign out_y[2] = ( in_a == 4'b0000 )? 1 : 0 ;
```



Now, did you get the idea??


Think how can we write a code line for out_y[1] before going to the next slide.

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

```
assign out_y[2] = ( in_a == 4'b0000 )? 1 : 0 ;
```

```
assign out_y[1] = ( (in_a[3] == 1'b1 ) | ( in_a[3:2]==2'b01) )? 1 : 0 ;
```

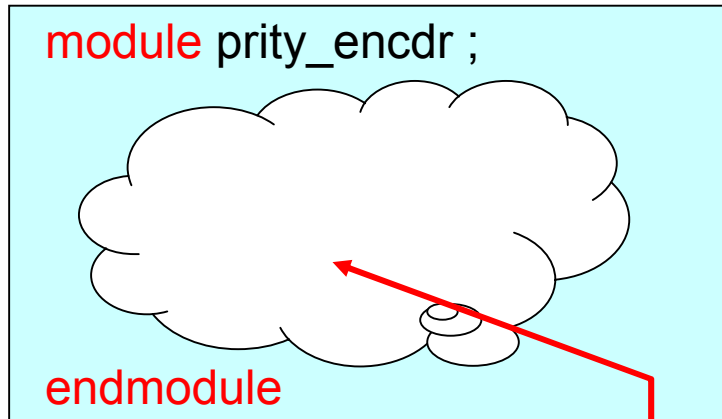Before going to the next slide,
think about out_y[0].



in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

assign out_y[2] = (in_a == 4'b0000)? 1 : 0 ;

assign out_y[1] = ((in_a[3] == 1'b1) | (in_a[3:2]==2'b01))? 1 : 0 ;

assign out_y[0] = ((in_a[3] == 1'b1) | (in_a[3:1]==3'b001))? 1 : 0 ;

Now create a file named prity_encdr.v by using the idea on this page.

```

module prity_encdr ( in_a, out_y );
input [3:0]  in_a ;
output [2:0] out_y ;
//
wire [3:0]  in_a ;
wire [2:0] out_y ;
//
assign out_y[2] = ( in_a == 4'b0000 )? 1'b1 : 1'b0 ;
assign out_y[1] = ( (in_a[3] == 1'b1 ) | ( in_a[3:2]==2'b01) )? 1'b1 : 1'b0 ;
assign out_y[0] = ( (in_a[3] == 1'b1 ) | ( in_a[3:1]==3'b001) )? 1'b1 : 1'b0 ;

endmodule

```

Parameter is not used, because this logic can not work correctly for bit sizes other than 4.

file name : prity_encdr.v

```

integer i ;
for ( i=0 ; i<=15 ; i=i+1 ) begin

end

```

Next, create a test bench to test the file above. Use “for statement” to generate all the possible patterns of in_a[3:0]. Name the file test_prity_encdr.v.

```
module test_prity_encdr ;
reg [3:0] in_a;
wire [2:0] out_y ;

prity_encdr prity_encdr_01 (
    .in_a(in_a), .out_y(out_y)
);

integer i ;
initial begin
    for ( i=0 ; i<=15 ; i=i+1 ) begin
        #10 in_a = i ;
    end
    #10 $finish ;
end

initial begin
    $monitor( "in_a=%b. out_y=%d", in_a, out_y ) ;
end
endmodule
`include "prity_encdr.v"
```

file name : test_prity_encdr.v

Without this delay, the simulation will not end successfully.
Think why??

```

module test_prity_encdr ;
reg [3:0] in_a;
wire [2:0] out_y ;

prity_encdr prity_encdr_01 (
    .in_a(in_a), .out_y(out_y)
);

integer i ;
initial begin
    for ( i=0 ; i<=15 ; i=i+1 ) begin
        #10 in_a = i ;
    end
    #10 $finish ;
end

initial begin
    $monitor( "in_a=%b. out_y=%d", in_a, out_y ) ;
end
endmodule
`include "prity_encdr.v"

```

file name : test_prity_encdr.v

The for statement is equal to the following code lines.

```

initial begin
    #10 in_a = 0 ;
    #10 in_a = 1 ;
    #10 in_a = 2 ;
    #10 in_a = 3 ;
    #10 in_a = 4 ;
    #10 in_a = 5 ;
    .
    .
    .
    #10 in_a = 12 ;
    #10 in_a = 13 ;
    #10 in_a = 14 ;
    #10 in_a = 15 ;

```

Run this file on your PC to see the result.


```

module test_prity_encdr ;
reg [3:0] in_a;
wire [2:0] out_y ;

prity_encdr prity_encdr_01 (
    .in_a(in_a), .out_y(out_y)
);

integer i ;
initial begin
    for ( i=0 ; i<=15 ; i=i+1 ) begin
        #10 in_a = i ;
    end
    #10 $finish ;
end

initial begin
    if in_a is unknown
        $monitor(
            assign out_y[2] =
                ( in_a == 4'b0000 )?
                1'b1 : 1'b0 ;
            if in_a is unkown
                ( in_a == 4'b0000 ) is 1'bx
            out_y[2] is 1'bx ;
        )
end
endmodule
`include "prity_encdr.v"

```

in_a is not given any value before t=10.

in_a=xxxx. out_y=x

in_a=0000. out_y=4

in_a=0001. out_y=0

in_a=0010. out_y=1

in_a=0011. out_y=1

in_a=0100. out_y=2

in_a=0101. out_y=2

in_a=0110. out_y=2

in_a=0111. out_y=2

in_a=1000. out_y=3

in_a=1001. out_y=3

in_a=1010. out_y=3

in_a=1011. out_y=3

in_a=1100. out_y=3

in_a=1101. out_y=3

in_a=1110. out_y=3

in_a=1111. out_y=3

file name : test_prity_encdr.v

An example of the simulation result

```

module test_prity_encdr ;
reg [3:0] in_a;
wire [2:0] out_y ;

prity_encdr prity_encdr_01 (
    .in_a(in_a), .out_y(out_y)
);

initial begin
// for ( i=0 ; i<=15 ; i=i+1 ) begin
    for ( in_a = 0 ; in_a<=15; in_a = in_a +1 ) begin
        #10 ;
    end
    #10 $finish ;
end

initial begin
    $monitor( "in_a=%b. out_y=%d", in_a, out_y ) ;
end
endmodule
`include "prity_encdr.v"

```

Modify the file as show
on the left and name it
test_prity_encdr_ng.v.

Run it to see yourself
what will happen.

file name : test_prity_encdr_ng.v

```

module test_prity_encdr ;
reg [3:0] in_a;
wire [2:0] out_y ;

prity_encdr prity_encdr_01 (
    .in_a(in_a), .out_y(out_y)
);

initial begin
// for ( i=0 ; i<=15 ; i=i+1 ) begin
    for ( in_a = 0 ; in_a<=15; in_a = in_a +1 ) begin
        #10 ;
    end
    #10 $finish ;
end


initial begin
    $monitor( "in_a=%b. out_y=%d", in_a, out_y ) ;
end
endmodule
`include "prity_encdr.v"

```

file name : test_prity_encdr_ng.v

Modify the file as show
on the left and name it
test_prity_encdr_ng.v.

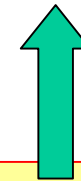Run this to see yourself
what will happen.



Your simulator will fall into
infinite loop because in_a
cannot become larger than
15. Note that in_a is a 4-bit
signal. 15 added by one is 0
for 4-bit data.

Ex 3-7. Always for combinational logic: Write a module equivalent to the truth table, the same to the previous Ex, shown below **using an always construct**. An input port is 4-bit in_a and an output port is 3-bit out_y.

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

Combinational logic used many times in a module must be written by using function. But if it is used only once, always construct can be used.

```

always @ ( a or b or c or ,,,, ) begin
    .
    .
    .
    .
    .
    out_y = ,,,, ;
end

```


sensitivity list

RTL programming rules

always construct can generate combinational logic block if

- (1) **all signals appearing in RHS**, Right Hand Side, are written in the **sensitivity list** as change value events,
- (2) all variable appearing in LHS are **given values in every path**, and
- (3) **blocking procedural assign** is used for assignment.

a = b & c ;

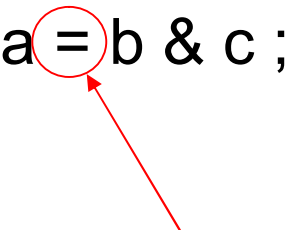

This is **blocking procedural assignment**.

RHS: Right Hand Side

LHS: Left Hand Side

In this exercise, we must use always construct, which is a procedure. We can use case statement instead of simple conditional operator.

First, think of case statement which is equivalent to the truth table.

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

For casez, ? means don't care. For example, case item 4'b01?? means that case expression and the case item will match if case expression is 4'b0100, 4'b0101, 4'b0110, or 4'b0111.

```

casez (in_a)
  4'b1??? : begin
    out_y = 3'd3 ;
  end
  4'b01?? : begin
    out_y = 3'd2 ;
  end
  4'b001? : begin
    out_y = 3'd1 ;
  end
  4'b0001 : begin
    out_y = 3'd0 ;
  end
  4'b0000 : begin
    out_y = 3'd4 ;
  end
endcase
  
```

Diagram annotations:

- Red circle around `(in_a)` with an arrow pointing to the text "case expression".
- Red circle around `4'b01??` with an arrow pointing to the text "case item".

The casez statement must go into the always construct because case statement is allowed only in procedures.

```
always @ ( in_a ) begin
```

```
  .  
  .  
  .  
  .
```

```
end
```

in_a[3]	in_a[2]	in_a[1]	in_a[0]	out_y
1	x	x	x	3'b011
0	1	x	x	3'b010
0	0	1	x	3'b001
0	0	0	1	3'b000
0	0	0	0	3'b100

```
casez ( in_a )
  4'b1??? : begin
    out_y = 3'd3 ;
  end
  4'b01?? : begin
    out_y = 3'd2 ;
  end
  4'b001? : begin
    out_y = 3'd1 ;
  end
  4'b0001 : begin
    out_y = 3'd0 ;
  end
  4'b0000 : begin
    out_y = 3'd0 ;
  end
endc
```

case expression

case item

Modify the file prity_encdr.v by using
always construct instead of using
assign and name it prity_encdr_alwly.v.

The module prity_encdr must look like an example shown in this slide.

out_y can not be net data type in this module. It must be register data type, because it appears on LHS of a procedural assignment.

```
module prity_encdr ( in_a, out_y ) ;
input [3:0] in_a ;
output [2:0] out_y ;
//
wire [3:0] in_a ;
reg [2:0] out_y ;
//
```

Parameter is not used, because this logic can not work correctly for bit sizes other than 4.

```
always @ ( in_a ) begin
  casez ( in_a )
    4'b1??? : begin
      out_y = 3'd3 ;
    end
    4'b01?? : begin
      out_y = 3'd2 ;
    end
    4'b001? : begin
      out_y = 3'd1 ;
    end
    4'b0001 : begin
      out_y = 3'd0 ;
    end
    4'b0000 : begin
      out_y = 3'd4 ;
    end
  endcase
end
endmodule
```

Run this file on your PC to see yourself if the module works correctly.


file name : prity_encdr_alwy.v

Ex 3-8. Sign bit and oncatenating operator: Write a module which shift a 4-bit input signal sig_a to the right and output the 4-bit result out_y. The sift count is given by a 2-bit input signal sft_cnt.


Use Verilog1995, do not use Verilog2001.

Although Verilog1995 can not handle signed signal, the module must extend the MSB bit in shifting to the right, for example, if sig_a's MSB is on, 1 must be filled to the bit positions where they are shifted out.

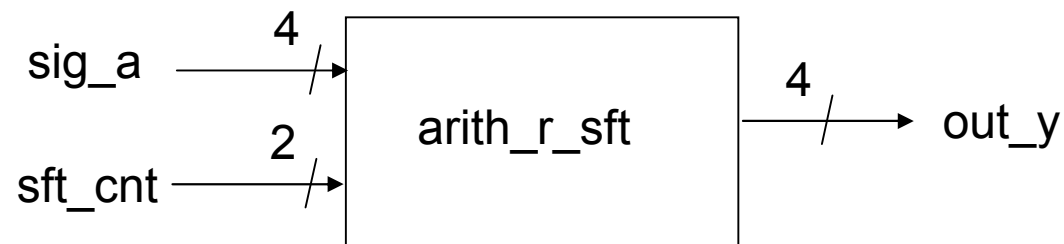Do not use Verilog shift operators, >> and >>>.



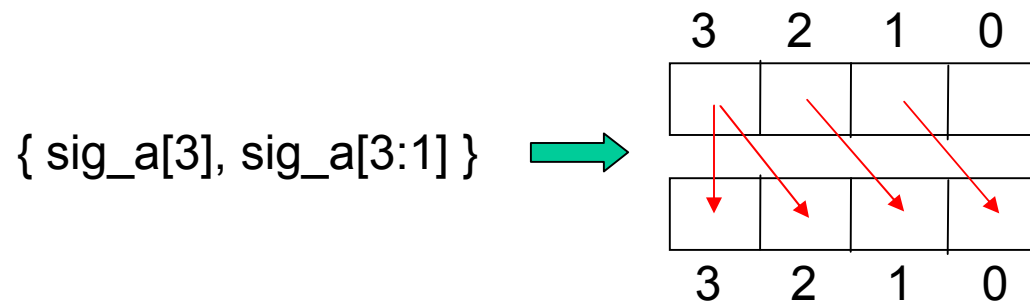A combinational logic can be described by using always construct .
The sift operation can be written by using a Verilog operator { } .



The operation may be different depending on the shift count `sft_cnt`, therefore case statement can be applied for different shift count. Such logic can be described by using case statement as shown below.

Case statement can be written only in always construct, initial construct, function, and task.

We must write the case statement in always construct so that whenever `sft_cnt` or `sig_a` changes, `out_y` is to be updated.

```
case ( sft_cnt )
  2'd0 : begin out_y = sig_a ; end
  2'd1 : begin out_y = { sig_a[3], sig_a[3:1] } ; end
  2'd2 : begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
  2'd3 : begin out_y = {4{sig_a[3]} } ; end
  default : begin out_y = 4'bxxxx ; end
endcase
```



However, code lines in case item 2'd0, 2'd1, 2'd2, and 2'd3 are different in many parts.

Consistent style, beauty of the code

```
case ( sft_cnt )
  2'd0 : begin out_y = sig_a ;           end
  2'd1 : begin out_y = { sig_a[3], sig_a[3:1] } ; end
  2'd2 : begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
  2'd3 : begin out_y = {4{sig_a[3]} } ; end
default : begin out_y = 4'bxxxx ; end
endcase
```



We can not apply systematic checking if every code line has different structures.

The following code lines have the same structure and are almost identical, except the numbers in *Italic*.

It is very easy to check them. We can say that if one line is correct, then other lines are correct just by checking *Italic* part only.

```
2'd0 : begin out_y = { {0{sig_a[3]} }, sig_a[3:0] } ; end
2'd1 : begin out_y = { {1{sig_a[3]} }, sig_a[3:1] } ; end
2'd2 : begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
2'd3 : begin out_y = { {3{sig_a[3]} }, sig_a[3:3] } ; end
```



Every code line has the same structures.

Consistent code and checking

```

case ( sft_cnt )
  2'd0 : begin out_y = sig_a ; end
  2'd1 : begin out_y = { sig_a[3], sig_a[3:1] } ; end
  2'd2 : begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
  2'd3 : begin out_y = {4{sig_a[3]} } ; end
endcase

```

Is this OK?

Is this OK?

Is this OK?

Is this OK?

Every code line has different checking viewpoints.

```

2'd0: begin out_y = { {0{sig_a[3]} }, sig_a[3:0] } ; end
2'd1: begin out_y = { {1{sig_a[3]} }, sig_a[3:1] } ; end
2'd2: begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
2'd3: begin out_y = { {3{sig_a[3]} }, sig_a[3:3] } ; end

```

Is this OK?

Coding example.

```

module arith_r_sft ( sig_a, sft_cnt, out_y ) ;
input [3:0] sig_a ;
input [1:0] sft_cnt ;
output [3:0] out_y ;
wire [3:0] sig_a ;
wire [1:0] sft_cnt ;
reg [3:0] out_y ; // non-FF

```

```

always @ ( sig_a or sft_cnt ) begin
case ( sft_cnt )

```

```

2'd0 : begin out_y = { {0{sig_a[3]} }, sig_a[3:0] } ; end
2'd1 : begin out_y = { {1{sig_a[3]} }, sig_a[3:1] } ; end
2'd2 : begin out_y = { {2{sig_a[3]} }, sig_a[3:2] } ; end
2'd3 : begin out_y = { {3{sig_a[3]} }, sig_a[3:3] } ; end

```

```

default : begin out_y = 4'bxxxx ; end
endcase
end
endmodule

```

file name: arith_r_sft.v

Parameter is not used,
because this logic can
not work correctly for
bit sizes other than 4.

This style is much easier to
check the code from the
view point of consistency.

This is for debug.

Write a test bench yourself
and check the result.

Another coding style

A combinational logic can be written by using function.

```
reg [3:0] out_y ; // non-FF
```

```
always @ ( sig_a or sft_cnt ) begin
  case ( sft_cnt )
    2'd0 : begin
      out_y = { {0{sig_a[3]} }, sig_a[3:0] } ;
    end
    2'd1 : begin
      out_y = { {1{sig_a[3]} }, sig_a[3:1] } ;
    end
    2'd2 : begin
      out_y = { {2{sig_a[3]} }, sig_a[3:2] } ;
    end
    2'd3 : begin
      out_y = { {3{sig_a[3]} }, sig_a[3:3] } ;
    end
    default : begin
      out_y = 4'bxxxx ;
    end
  endcase
end
```



```
wire [3:0] out_y ; // non-FF
```

```
assign out_y = sft_r_f(sig_a, sft_cnt) ;
```

```
function [3:0] sft_r_f ;
  input [3:0] aa ;
  input [1:0] cnt ;
  begin
    case (cnt )
      2'd0 : begin
        sft_r_f = { {0{aa[3]} }, aa[3:0] } ;
      end
      2'd1 : begin
        sft_r_f = { {1{aa[3]} }, aa[3:1] } ;
      end
      2'd2 : begin
        sft_r_f = { {2{aa[3]} }, aa[3:2] } ;
      end
      2'd3 : begin
        sft_r_f = { {3{aa[3]} }, aa[3:3] } ;
      end
      default : begin
        sft_r_f = 4'bxxxx ;
      end
    endcase
  end
endfunction
```

if else, case, and conditional statement

```
case ( a )
  b : begin
    yy = 4'b0101 ;
  end
  default : begin
    yy = 4'b1100 ;
  end
endcase
```

```
if ( a == b ) begin
  yy = 4'b0101 ;
end
else begin
  yy = 4'b1100 ;
end
```

```
yy = ( a == b ) ? 4'b0101
               : 4'b1100 ;
```

case statement, if statement, and conditional statement can work in similar way.

Those shown on this page are almost the same but in detail they are different.

If a is 2'b1x and b is 2'b1x, the result of the case statement is "yy=4'b0101", the result of if statement is "yy=4'b1100", and the result of conditional statement is "yy=4'bx10x". See online text material for details.

if else, case, and conditional statement

```
case ( a )
  b : begin
    assign yy = 4'b0101 ;
  end
  default : begin
    assign yy = 4'b1100 ;
  end
endcase
```

NG

```
if ( a == b ) begin
  assign yy = 4'b0101 ;
end
else begin
  assign yy = 4'b1100 ;
end
```

NG

```
assign yy = ( a == b ) ? 4'b0101
               : 4'b1100 ;
```

OK

case statement and if statement can be used only in procedure, therefore we can not use continuous assign in case statement nor in if statement.

Only procedural assignment is allowed in structured procedures.

However we can use continuous assign for conditional statement. It can also be used in structured procedures.

Ex 3-9. Missing case item and latching: Write a module equivalent to the truth table shown below using an always construct. An input port is 2-bit in_a and an output port is 3-bit out_y.

in_a[1]	in_a[0]	out_y
0	0	3'b001
0	1	3'b110
1	0	3'b101

Let's see what happens with 2-bit case expression which can take 4 possible values if only 3 case items are given.
In this exercise we will study about case statement and default.

Create a file case_dflt.v by using case statement on the right. Type a test bench into the same file.

```

case ( in_a )
  2'b00 : begin
    out_y = 3'b001 ;
  end
  2'b01 : begin
    out_y = 3'b110 ;
  end
  2'b10 : begin
    out_y = 3'b101 ;
  end
endcase

```

```

module case_deflt ( in_a, out_y ) ;
input [1:0] in_a ;
output [2:0] out_y ;
//

```

```


wire [1:0] in_a ;
reg [2:0] out_y ; // non-FF
//

```

```

always @ ( in_a ) begin
case ( in_a )
2'b00 : begin
out_y = 3'b001 ;
end
2'b01 : begin
out_y = 3'b110 ;
end
2'b10 : begin
out_y = 3'b101 ;
end
endcase
end
endmodule

```

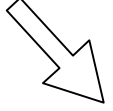

```

module test_case_deflt;
reg [1:0] in_a;
wire [2:0] out_y ;

```

```

case_deflt case_deflt_01 ( .in_a(in_a), .out_y(out_y) ) ;

```

```

initial begin
in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b10 ;
#10 in_a = 2'b11 ;
#10 $finish ;
end

```

```

initial begin
$monitor( "in_a=%b. out_y=%b", in_a, out_y ) ;
end
endmodule


```

Run this on your PC.

file name : case_deflt.v

```
initial begin
    in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b10 ;
#10 in_a = 2'b11 ;
#10 $finish ;
end
```

A sample result

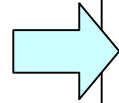


```
in_a=00. out_y=001
in_a=01. out_y=110
in_a=10. out_y=101
in_a=11. out_y=101
```

The result must looks like the one shown above.

Note that for unexpected input in_a=11, we got the result out_y=101 which is the same to the previous line, in_a=10 and out_y=101.
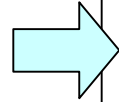
```
initial begin
    in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b10 ;
#10 in_a = 2'b11 ;
#10 $finish ;
end
```



```
in_a=00. out_y=001
in_a=01. out_y=110
in_a=10. out_y=101
in_a=11. out_y=101
```




```
initial begin
    in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b11 ;
#10 in_a = 2'b10 ;
#10 $finish ;
end
```



Now, change the initial construct as shown on the left and run the modified file.

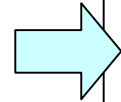
```
initial begin
    in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b10 ;
#10 in_a = 2'b11 ;
#10 $finish ;
end
```



```
in_a=00. out_y=001
in_a=01. out_y=110
in_a=10. out_y=101
in_a=11. out_y=101
```


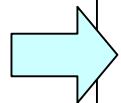
```
initial begin
    in_a = 2'b00 ;
#10 in_a = 2'b01 ;
#10 in_a = 2'b11 ;
#10 in_a = 2'b10 ;
#10 $finish ;
end
```



```
in_a=00. out_y=001
in_a=01. out_y=110
in_a=11. out_y=110
in_a=10. out_y=101
```




Note that, this time, for unexpected inout in_a=11, we got out_y=110 which is the same to the previous line, in_a=01 and out_y=110.

```

in_a=00. out_y=001
in_a=01. out_y=110
in_a=10. out_y=101
in_a=11. out_y=101

```

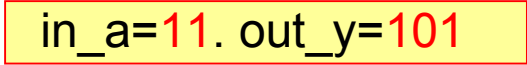

This phenomena is called latching.

The case statement dose not say anything about the case where in_a is 2'b11. A simulator tries to output some value even for such case, and output previous value of out_y. Because register type signal is expected to hold the value assigned until an new assignment is done, it is natural to output the previous value.

```

case ( in_a )
  2'b00 : begin
    out_y = 3'b001 ;
  end
  2'b01 : begin
    out_y = 3'b110 ;
  end
  2'b10 : begin
    out_y = 3'b101 ;
  end
endcase

```




simulation : latching

synthesis : creating a latch

```

in_a=00. out_y=001
in_a=01. out_y=110
in_a=10. out_y=101
in_a=11. out_y=101

```

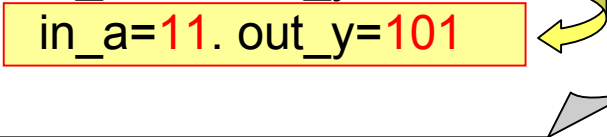

```

case ( in_a )
  2'b00 : begin
    out_y = 3'b001 ;
  end
  2'b01 : begin
    out_y = 3'b110 ;
  end
  2'b10 : begin
    out_y = 3'b101 ;
  end
endcase

```

A synthesis tool will create a memory element called latch for such cases.

However, a latch is difficult to use in large scale design. It is better to avoid using a latch.

Moreover, if a latch is created when you wrote an always construct to define combinational logic, it will cause some malfunction of your logic.

We need some countermeasure to avoid latches.



simulation : latching


synthesis : creating a latch

To avoid latches, default is used.

A sample code on the left assigns 0 to out_y when in_a is unexpected 2'b11. Another sample code on the right assigns unknown value to out_y when in_a is unexpected 2'b11.


Either code will do. The default on the right will be neglected in synthesis because it assigns unknown value. The default on the left will not be neglected.
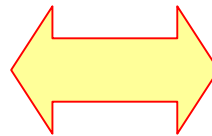
```
case ( in_a )
  2'b00 : begin
    out_y = 3'b001 ;
  end
  2'b01 : begin
    out_y = 3'b110 ;
  end
  2'b10 : begin
    out_y = 3'b101 ;
  end
  default : begin
    out_y = 3'b000 ;
  end
endcase
```



```
case ( in_a )
  2'b00 : begin
    out_y = 3'b001 ;
  end
  2'b01 : begin
    out_y = 3'b110 ;
  end
  2'b10 : begin
    out_y = 3'b101 ;
  end
  default : begin
    out_y = 3'bxxx ;
  end
endcase
```

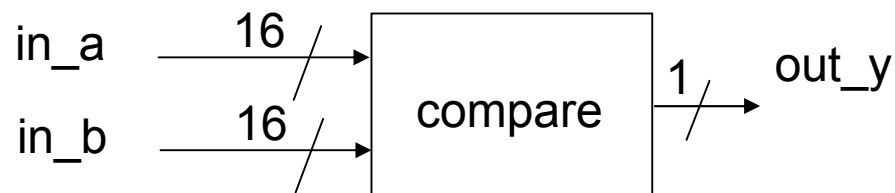
Ex 3-10. Compare signed data in Verilog1995: Write a module using combinational logic to compare two 16-bit signals, in_a and in_b, and outputs 1 if in_a is smaller than in_b, otherwise outputs 0. Both in_a and in_b can be negative, and use Verilog1995.




In this exercise we will study how to handle negative values in Verilog1995. In Verilog1995, all the signals are treated as unsigned, that is, positive. Therefore, when handling negative value, a programmer has to take care of negative values.

Because Verilog1995 can not handle negative values, take special care for the cases where sign-bit is 1.

RTL programming rules

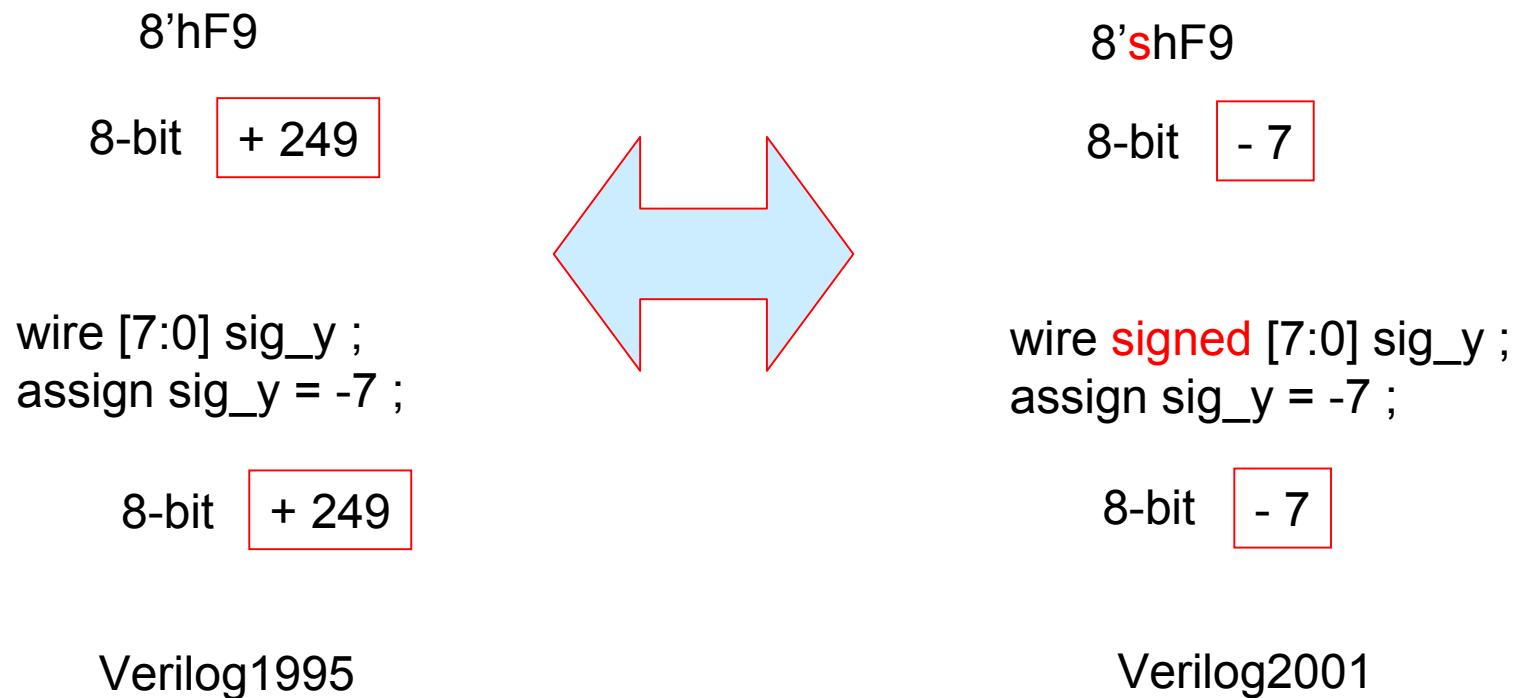- (1) Based numbers are unsigned, unless they are declared with s character in base numbers.
- (2) Use signed key word for signed variables and nets.



8'b1000_0000  128


8'sb1000_0000  -128

The MSB is set 1 and “s” declared in base number, therefore it means minus value, -128.

```
wire signed [7:0] sig_y ;
```

```
assign sig_y = 8'b1000_0000 ;
```

```
assign flg = ( sig_y < -10 )? 1 : 0 ;
```


 sig_y = -128
flg = 1

sig_y is declared as signed, and the MSB bit is given the value 1 by the assign statement. Therefore, sig_y is -128.

```
wire [7:0] sig_w ;
```

```
assign sig_w = 8'sb0000_1010 ;
```

```
assign flg = ( sig_w < -10 )? 1 : 0 ;
```


 sig_w = 10
flg = 1

sig_w is not declared as a signed variable, therefore the comparison is done assuming both operands are positive.

-10 is a large positive value if it is treated as a positive value. We have to declare sig_w signed so that the result of the comparison, 10 <= -10, results in false.

Let's think how to handle sign bit.

sign-bit

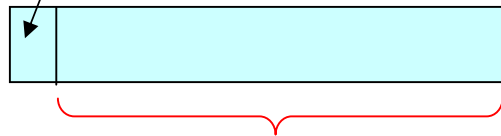

Larger the value of this part, the larger positive value when sign-bit is 0 or the larger negative value when sign-bit is 1.



1101 > 1001
-3 > -7

0101 > 0001
5 > 1

0011 > 1110
3 > -2

0111 > 1001
7 > -7

Depending on the value of the MSB, we have to apply different way of comparing.


Especially when the two operand have different MSB value such as comparing 0011(3) and 1110(-2).

```

case ( { in_a[SIG_BW-1], in_b[SIG_BW-1] } )
  2'b11, 2'b00 : begin
    out_y = ( in_a[SIG_BW-2:0] < in_b[SIG_BW-2:0] )?
              1'b1 : 1'b0 ;
  end
  2'b10 : begin // in_a negative, in_b positive
    out_y = 1'b1 ;
  end
  2'b01 : begin // in_a positive, in_b negative
    out_y = 1'b0 ;
  end
end

```

sign-bit

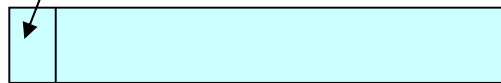

Larger the value of this part, the larger positive value when sign-bit is 0 or the larger negative value when sign-bit is 1.



1101 > 1001

-3

-7

0101 > 0001

5

1

0011 > 1110

3

-2


0111 > 1001


7

-7

Now, create compare logic and a test bench into one file named smaller_chk.v.

```
module smaller_chk ( in_a, in_b, out_y );
parameter SIG_BW = 16 ; // must be larger than 1
input [SIG_BW-1:0] in_a, in_b ;
output out_y ;
//
wire [SIG_BW-1:0] in_a, in_b ;
reg out_y ;
//
always @ ( in_a or in_b ) begin
  case ( { in_a[SIG_BW-1], in_b[SIG_BW-1] } )
    2'b11, 2'b00 : begin // both negative, or both positive
      out_y = ( in_a[SIG_BW-2:0] < in_b[SIG_BW-2:0] )? 1'b1 : 1'b0 ;
    end
    2'b10 : begin // in_a negative, in_b positive
      out_y = 1'b1 ;
    end
    2'b01 : begin // in_a positive, in_b negative
      out_y = 1'b0 ;
    end
    default : begin // for debug. This will not be reached in normal case
      out_y = 1'bx ;
    end
  endcase
end
endmodule
```



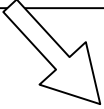

```
module test_smaller_chk ;
parameter SIG_BW = 16 ;
reg [SIG_BW-1:0] in_a, in_b ;
wire out_y ;
//
smaller_chk    smaller_chk_01 ( .in_a(in_a), .in_b(in_b), .out_y(out_y) ) ;
//
initial begin
    in_a = 16'h5101 ;
#10 in_a = 16'h8F45 ;
#10 in_a = 16'h6310 ;
#10 in_a = 16'h7682 ;
#10 in_a = 16'hE503 ;
#10 $finish ;
end
initial begin
    in_b = 16'h5131 ;
#10 in_b = 16'h7023 ;
#10 in_b = 16'hE237 ;
#10 in_b = 16'h7335 ;
#10 in_b = 16'hE99F ;
end
initial begin
    $monitor( " in_a=%b. \n in_b=%b, out_y=%b", in_a, in_b, out_y ) ;
end
endmodule
```

Run this file on your
PC to see the result.

file name: smaller_chk.v

The result shall look like the one shown below.

```
in_a=0101000100000001.  
in_b=0101000100110001, out_y=1  
in_a=1000111101000101.  
in_b=0111000000100011, out_y=1  
in_a=0110001100010000.  
in_b=1110001000110111, out_y=0  
in_a=0111011010000010.  
in_b=0111001100110101, out_y=0  
in_a=1110010100000011.  
in_b=1110100110011111, out_y=1
```

Now, let's update the module by using Verilog2001.

In Verilog2001, we can handle negative values by using signed key word.

relational operators: >, >=, <, <=

Logical equality operator: ==

Arithmetic shift operator: >>>, <<<

} These are applicable
for negative values.

The code becomes as simple as shown in the next page, because we do not have to take care of the sign bits. Verilog2001 can take care of them.

The code must be very simple as shown on this slide.

```
module smaller_chk ( in_a, in_b, out_y ) ;  
parameter SIG_BW = 16 ;  
input signed[SIG_BW-1:0] in_a, in_b ;  
output out_y ;  
//  
wire signed[SIG_BW-1:0] in_a, in_b ;  
reg out_y ; // non-FF  
//  
always @ ( in_a or in_b ) begin  
    out_y = ( in_a < in_b )? 1'b1 : 1'b0 ;  
end  
endmodule
```

test bench part not shown here

file name : smaller_chk_sign.v



```
wire out_y ;  
assign out_y = ( in_a < in_b )? 1'b1 : 1'b0 ;
```

It is so simple that we do not have to use always construct.
The module can be modified by using continuous assign.

```
module smaller_chk ( in_a, in_b, out_y ) ;  
parameter SIG_BW = 16 ;  
input signed[SIG_BW-1:0] in_a, in_b ;  
output out_y ;  
//  
wire signed[SIG_BW-1:0] in_a, in_b ;  
reg out_y ;  
//  
always @ ( in_a or in_b ) begin  
    out_y = ( in_a < in_b )? 1'b1 : 1'b0 ;  
end  
endmodule
```

test bench part not shown here

file name : smaller_chk_sign_sign.v

Run this file on your
PC to see the result.

RTL programming rules

(1) Part select of vector is always unsigned even if the vector is declared signed and part select specifies entire bits.

Now, modify the code as shown below to see how part selection of vector works. Run the code below on your PC and check the result yourself.


```
module smaller_chk ( in_a, in_b, out_y ) ;
parameter SIG_BW = 16 ;
input signed[SIG_BW-1:0] in_a, in_b ;
output out_y ;
//
wire signed[SIG_BW-1:0] in_a, in_b ;
reg out_y ;
//
always @ ( in_a or in_b ) begin
  out_y = ( in_a [SIG_BW-1:0] < in_b [SIG_BW-1:0] )? 1'b1 : 1'b0 ;
end
endmodule
```

test bench part not shown here

file name : smaller_chk_sign_bgy.v

This code will not get a correct result because part select is used.

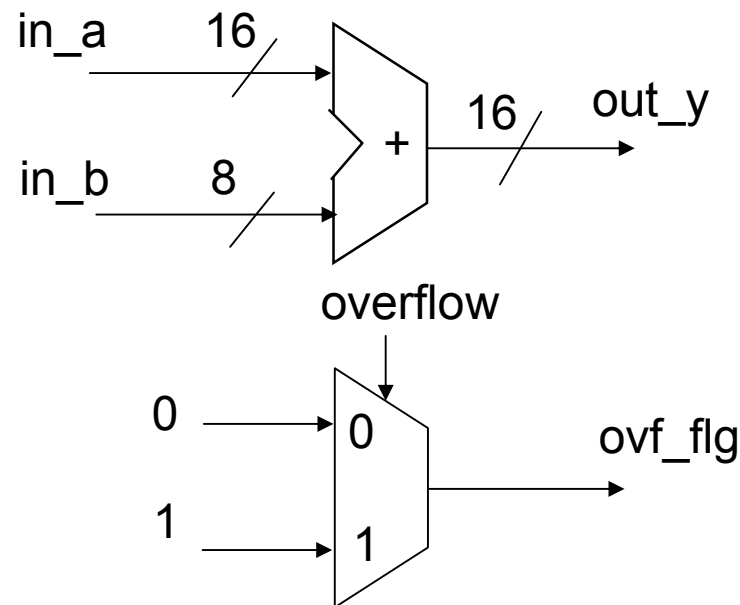Ex 3-11. Arithmetic operation in Verilog1995: Write a module which adds 16-bit input `in_a` and 8-bit input `in_b` and places 16-bit result on `out_y`. `in_a` and `in_b` may be negative. The logic must output `ovf_flg` to indicate overflow. Use Verilog1995.




Because today's synthesis tools are good in efficiency, use Verilog arithmetic operator instead of hand-craft arithmetic logic block.

If we can use Verilog2001, it shall be as simple as below left.

Verilog2001

```
wire signed [15:0] in_a ;  
wire signed [7:0] in_b ;  
wire signed [15:0] out_y ;  
//  
assign out_y = in_a + in_b ;
```


sign bit of in_b is extended
automatically

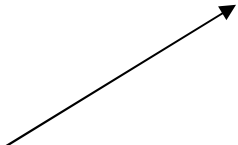

Verilog1995

```
wire [15:0] in_a ;  
wire [7:0] in_b ;  
wire [15:0] out_y ;  
//  
assign out_y = in_a + in_b ;
```

**sign bit not
extended.**




How to extend the sign bit??

Verilog1995

```
wire [15:0] in_a ;
wire [7:0] in_b ;
wire [15:0] out_y ;
//
assign out_y = in_a + in_b ;
```

sign bit not extended.

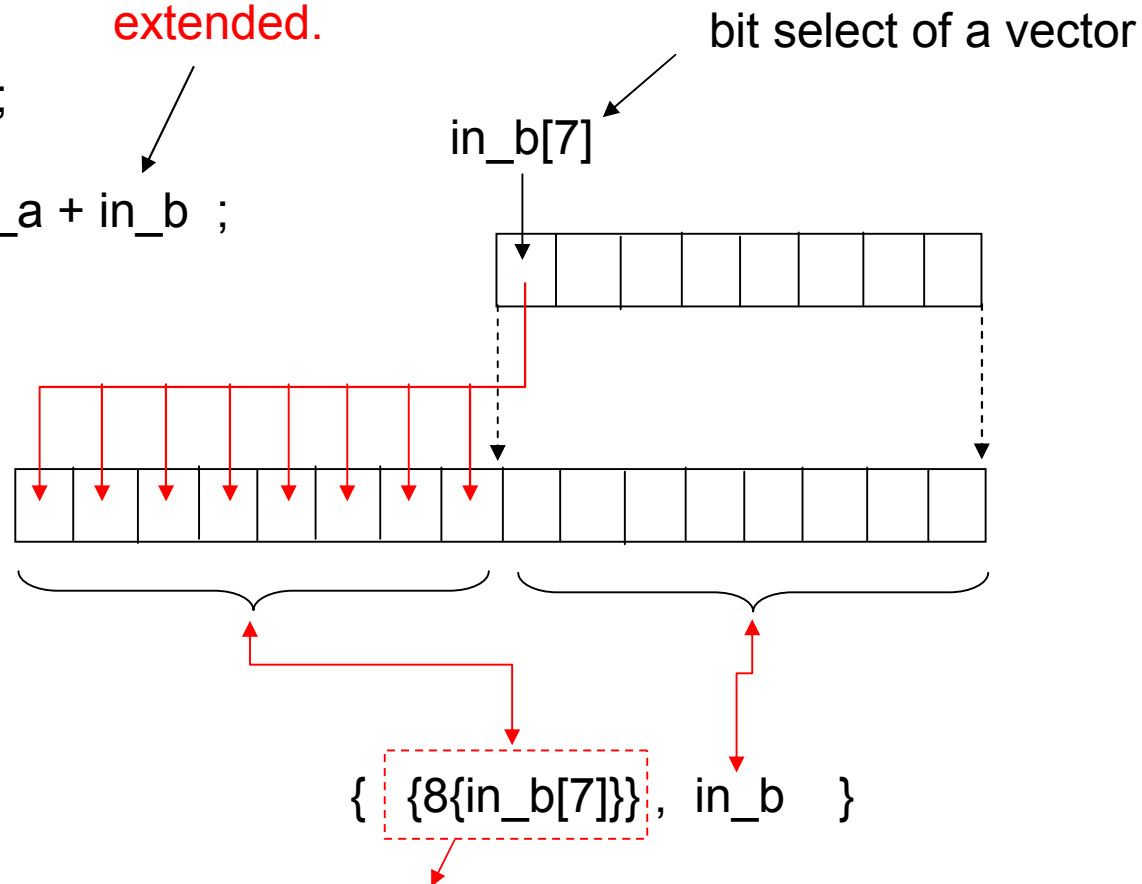


`{ 8 { yyy } }` means `{yyy}` repeated 8 times.

in_a	in_b	out_y	ovf_flg
positive	positive	positive	0
positive	positive	negative	1
positive	negative	positive	0
positive	negative	negative	0
negative	positive	positive	0
negative	positive	negative	0
negative	negative	positive	1
negative	negative	negative	0

ovr_flg must be set base on the truth table shown in this slide.

If you agree to this table, go to the next page.

in_a	in_b	out_y	ovf_flg
positive	positive	positive	0
positive	positive	negative	1
positive	negative	positive	0
positive	negative	negative	0
negative	positive	positive	0
negative	positive	negative	0
negative	negative	positive	1
negative	negative	negative	0

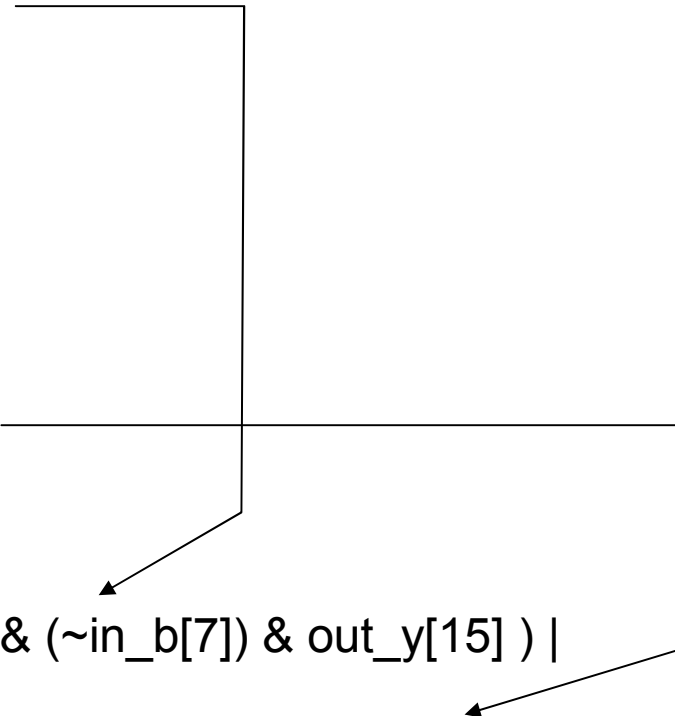

```

assign ovf_flg = ( (~in_a[15]) & (~in_b[7]) & out_y[15] ) |
( in_a[15] & in_b[7] & (~out_y[15]) )? 1 : 0 ;

```


Now, create a file named `arith_add_95.v` which can add 16-bit input `in_a` and 8-bit input `in_b` and check overflow. Type a test bench in the same file. Introduce parameter to make bit width adjustable.

revised in V2r04

```
module arith_add ( in_a, in_b, out_y, ovf_flg ) ;  
parameter LNG_BW = 16 ;  
parameter SHRT_BW = 8 ; // must be smaller or equal to LNG_BW  
input [LNG_BW-1:0] in_a ;  
input [SHRT_BW-1:0] in_b ;  
output [LNG_BW-1:0] out_y ;  
output ovf_flg ; // over flow indicator  
//  
wire [LNG_BW-1:0] in_a ;  
wire [SHRT_BW-1:0] in_b ;  
wire [LNG_BW-1:0] out_y ;  
wire ovf_flg ;  
//  
assign out_y = in_a + { {(LNG_BW-SHRT_BW){in_b[SHRT_BW-1]}}, in_b } ;  
assign ovf_flg = ( (~in_a[LNG_BW-1]) & (~in_b[SHRT_BW-1]) &  
                   out_y[LNG_BW-1] ) | ( in_a[LNG_BW-1] &  
                   in_b[SHRT_BW-1] & (~out_y[LNG_BW-1]) )? 1'b1 : 1'b0 ;  
//  
endmodule
```
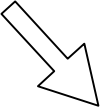
```
module test_arith_add ;  
parameter LNG_BW = 16 ;  
parameter SHRT_BW = 8 ;  
reg [LNG_BW-1:0] in_a ;  
reg [SHRT_BW-1:0] in_b ;  
wire [LNG_BW-1:0] out_y ;
```





```

wire ovf_flg ;
//
arith_add  arith_add_01 ( .in_a(in_a), .in_b(in_b),
                           .out_y(out_y), .ovf_flg(ovf_flg) ) ;

initial begin
    in_a = 1096 ;
    #10 in_a = 32765 ;
    #10 in_a = -32760 ;
    #10 in_a = -32760 ;
    #10 in_a = -2970 ;
    #10 in_a = -32700 ;
    #10 $finish ;
end
initial begin
    in_b = 20 ;
    #10 in_b = 7 ;
    #10 in_b = -2 ;
    #10 in_b = -200 ;
    #10 in_b = -180 ;
    #10 in_b = -120 ;
end
initial begin
    $monitor( "in_a=  %b,\n in_b=      %b,\n out_y= %b,   ovf=%b\n",
              in_a, in_b, out_y, ovf_flg ) ;
end
endmodule

```

Run this file on your PC
and check the result.

file name : arith_add_95.v

A sample result

```
in_a= 0000010001001000,  
in_b=          00010100,  
out_y= 0000010001011100,  ovf=0
```

```
in_a= 0111111111111101,  
in_b=          00000111,  
out_y= 1000000000000100,  ovf=1
```

```
in_a= 10000000000001000,  
in_b=          11111110,  
out_y= 1000000000000110,  ovf=0
```

```
in_a= 10000000000001000,  
in_b=          00111000,  
out_y= 1000000001000000,  ovf=0
```

```
in_a= 1111010001100110,  
in_b=          01001100,  
out_y= 1111010010110010,  ovf=0
```

```
in_a= 1000000001000100,  
in_b=          10001000,  
out_y= 0111111111001100,  ovf=1
```

Halted at location **arith_add_95.v(39)

Ex 3-12. Test bench and coverage: **Copy and paste** the following modules and run them to check the 8-bit unary EOR logic module can place its 1-bit output out_y correctly depending on the number of on-bits in its 8-bit input in_a.

```
module u_eor( in_a, out_y );
input [7:0] in_a ;
output out_y ;
wire [7:0] in_a ;
reg out_y ;
//
integer k, cnt ;
always @( in_a ) begin
    cnt=0;
    for (k=0; k<=3; k=k+1) begin
        cnt=cnt+in_a[k]+in_a[k+3] ;
    end
    out_y=( cnt[0] )? 1 : 0 ;
end
endmodule
```

file name: u_eor.v

**Run test_u_eor.v on you PC
to see the result.**

```
module test_u_eor ;
reg [7:0] aa ;
wire yy ;
u_eor u_eor_01(.in_a(aa), .out_y(yy));
initial begin
    aa=8'b0000_0000 ; // bit count=0
    #5 aa=8'b0000_0001 ; // bit count=1
    #5 aa=8'b1000_1000 ; // bit count=2
    #5 aa=8'b0101_0100 ; // bit count=3
    #5 aa=8'b1100_1001 ; // bit count=4
    #5 aa=8'b0101_0111 ; // bit count=5
    #5 aa=8'b1110_1011 ; // bit count=6
    #5 aa=8'b1111_1101 ; // bit count=7
    #5 aa=8'b1111_1111 ; // bit count=8
    #5 $finish ;
end
initial begin
    $monitor("in_a=%b, out_y=%b", aa, yy );
end
endmodule
`include "u_eor.v"
```

file name: test_u_eor.v

A simulation result

bit count

in_a=00000000, out_y=0	←	0 bit
in_a=00000001, out_y=1	←	1 bit
in_a=10001000, out_y=0	←	2 bits
in_a=01010100, out_y=1	←	3 bits
in_a=11001001, out_y=0	←	4 bits
in_a=01010111, out_y=1	←	5 bits
in_a=11101011, out_y=0	←	6 bits
in_a=11111101, out_y=1	←	7 bits
in_a=11111111, out_y=0	←	8 bits

Halted at location **test_u_eor

For all possible bit count, 0 to 8, the result is OK.
And the test data cover all the paths in RTL code lines.



The target module, u_eor, is correct, because
the above simulation result is correct.



Do you agree with this conclusion??

If you agree, then try the test data `aa=8'b0000_1001` to find a bug.

Do not think
“my code is correct, because
the simulation result is OK.”

In many cases, "simulation result OK"
just means your test data or test bench
is poorly designed.

Chapter 4. Flip-flops and sequential logic

Flip-flop is a most important logic element in RTL design.

It can be defined by using an always construct.

Registers (variables) in Verilog RTL can hold values in simulator, but they **can not hold any value in actual silicon** unless they are mapped into flip-flops by a synthesis tool.

```
reg sig_a ;
```

```
begin
```


```
...
```

```
sig_a = ----- ;
```

```
...
```

```
end
```

mapping
to circuit

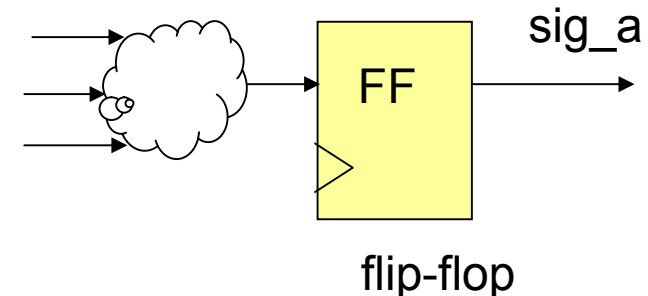

RTL programming rules


always construct can generate a flip-flop if
 (1) “posedge clk” is written in a sensitivity list. No change value event must appear in the sensitivity list. (posedge rst or negedge rst_n is allowed.)

```
always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    sig_a <= 0 ;
  end
  else begin
    sig_a <= next_sig_a ;
  end
end
```

nonblocking
procedural
assignment

assign next_sig_a = ,,,,,, ;

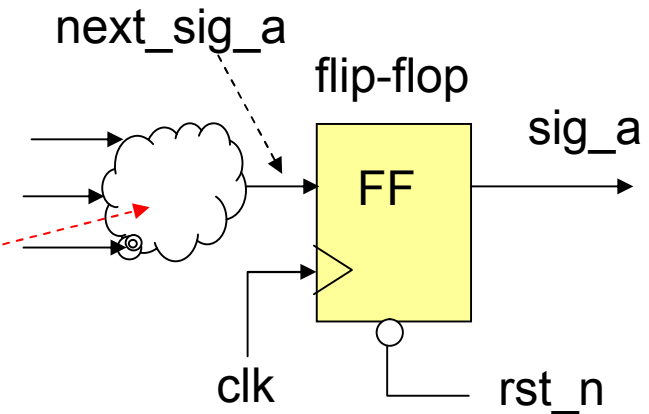Do not use **other** styles until you fully understand what each line means.



You must write “posedge clk or negedge rst_n” exactly the same order for “posedge clk” and “negedge rst_n”. If your write “negedge rst_n or posedge clk”, a synthesis tool can not create a correct flip-flop.

The tool thinks that the first argument is a clock signal.

Ex 4-1. Sequential lamps: Write a module `lp_seq` of which specification is given below.

There are 3 lamps, #0, #1, and #2 lamps.

#0 lamp illuminates **one** clock cycle,

#1 lamp illuminates **two** clock cycles, and

#2 lamp illuminates **three** clock cycles.

They illuminate in turn, that is, first #0 lamp and next #1 lamp and lastly #2 lamp.


While one lamp is on, other lamps are off.

After #2 lamp illuminate 3 cycles, #0 lamp illuminates again and keeps the same on off operation forever unless reset asserted.

When reset (asynchronous active high) asserted, all lamps become off.


At the first rise edge of the clock after reset negated, #0 lamp must turn on.

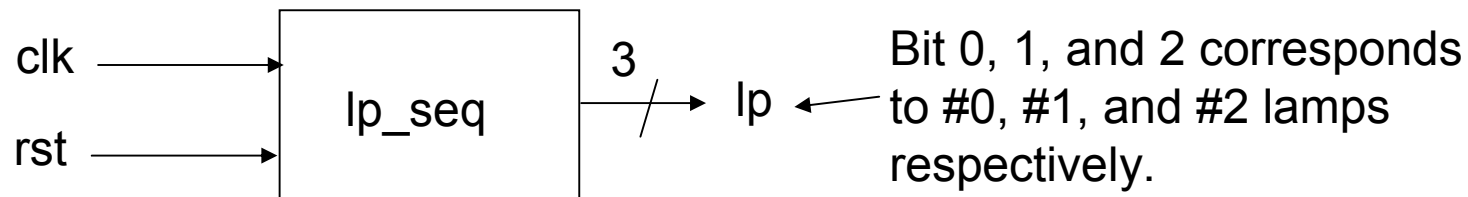Each lamp's turn on and off occur at clock rise time.



This is a typical sequential logic, we need memory elements to implement this features into silicon. The first thing we have to do is to determine how many and what kind of memory elements are needed.


The system must behave as shown below.

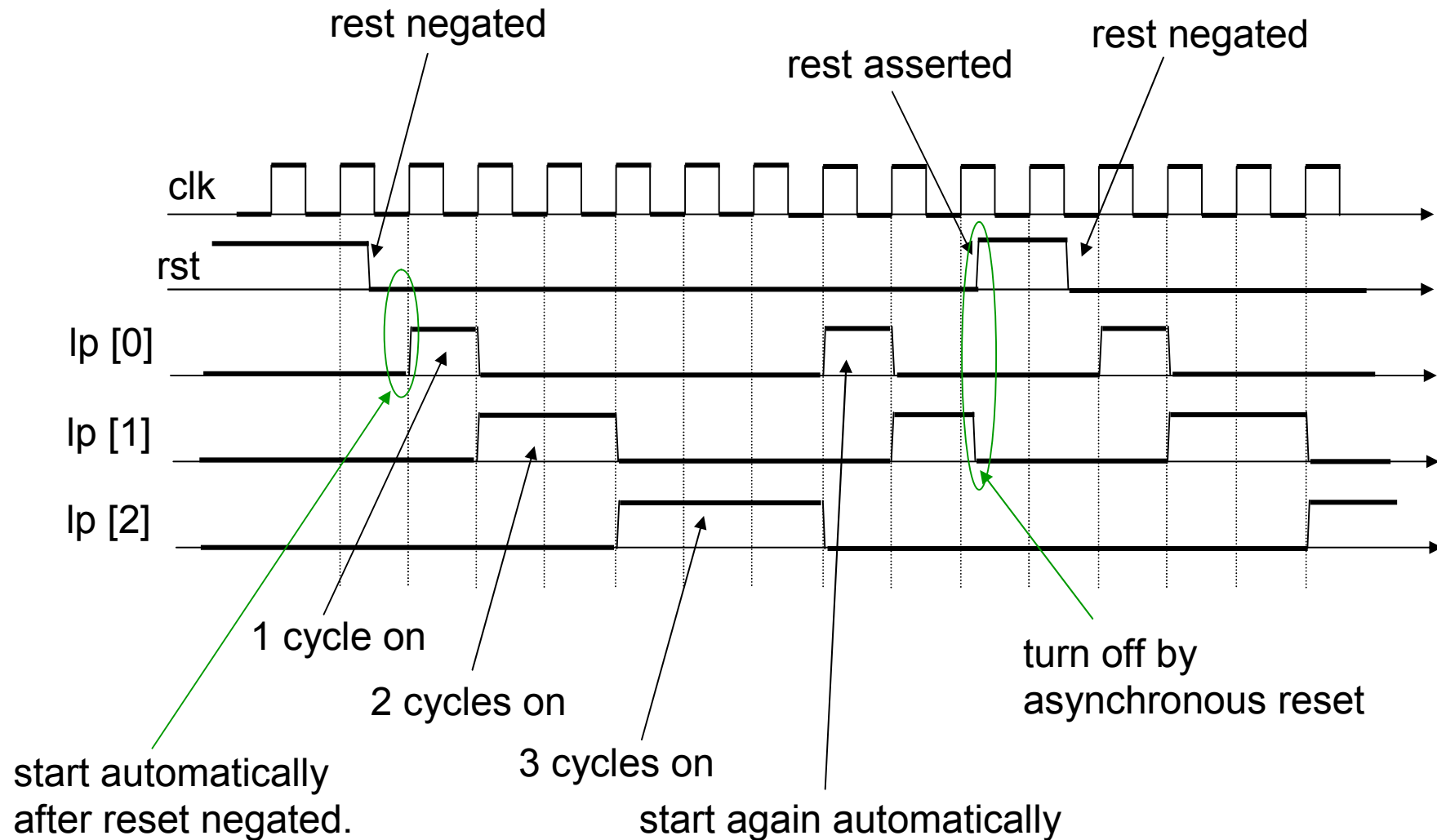

lamp itself : Assign one flip-flop for one lamp.

→ This idea can be extended to implement the specified logic as below.

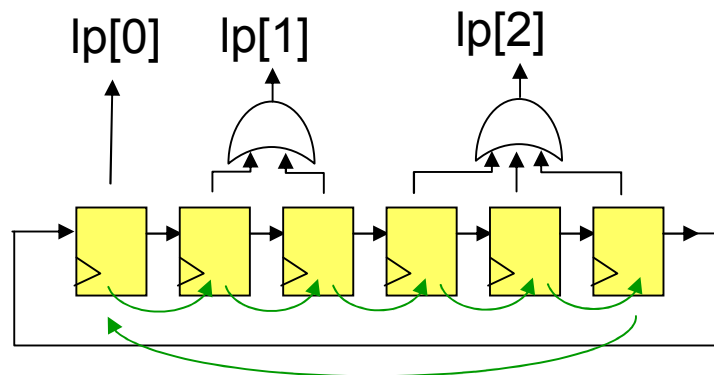Assign one flip-flop to lp [0], two flip-flops to lp [1], and three flip-flops to lp[2] as shown below. Then shifting 1 bit through this shift register can realize the logic needed.




This shift registers can be modeled by the code on the right.

This idea is same to assigning memory element for state variable. "On" position of flip-flops represents the state.

```
always @ ( posedge clk ) begin
    lp_reg[5:0] <=
        { lp_reg[4:0] , lp_reg[5] } ;
end
```

1 bit shift rotate operation

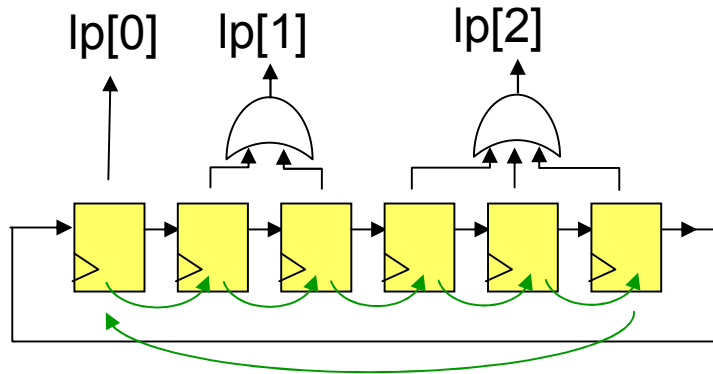

```
always @ ( posedge clk ) begin
    lp_reg[5:0] <=
        { lp_reg[4:0] , lp_reg[5] } ;
end
```

Next think about reset ;

On reset, these flip-flop must be turned off.

When reset negated, we must turn on lp_reg[0].

This can be done as below.

```
always @ ( posedge clk or posedge rst ) begin
    if ( rst_n ) begin
        lp_reg[5:0] <= 6'b00_0000 ;
    end
    else begin
        lp_reg[5:0] <= 6'b00_0001 ;
    end
end
```

```

always @ ( posedge clk ) begin
  lp_reg[5:0] <=
    { lp_reg[4:0] , lp_reg[5] } ;
end

```

```

always @ ( posedge clk or posedge rst ) begin
  if ( rst_n ) begin
    lp_reg[5:0] <= 6'b00_0000 ;
  end
  else begin
    lp_reg[5:0] <= 6'b00_0001 ;
  end
end
end

```

```

always @ ( posedge clk or posedge rst ) begin
  if ( rst_n ) begin
    lp_reg[5:0] <= 6'b00_0000 ;
  end
  else begin
    lp_reg[5:0] <= next_lp_reg[5:0] ;
  end
end
assign next_lp_reg[5:0] =
  ( lp_reg ) ? { lp_reg[4:0] , lp_reg[5] } : 6'b00_0001 ;

```

```

module lp_seq ( clk, rst, lp ) ;
input clk, rst ;
output [2:0] lp ;
wire clk, rst ;
wire [2:0] lp ;

```

This is a module we wanted. It is synthesizable, timing accurate and hardware resource accurate.

```

reg [5:0] lp_reg ; // FF for state
wire [5:0] next_lp_reg ; // combinational logic

assign lp[0] = lp_reg[0] ;
assign lp[1] = lp_reg[1] | lp_reg[2] ;
assign lp[2] = lp_reg[3] | lp_reg[4] | lp_reg[5] ;

always @ ( posedge clk or posedge rst ) begin
  if ( rst ) begin
    lp_reg <= 6'b00_0000 ;
  end
  else begin
    lp_reg <= next_lp_reg ;
  end
end

assign next_lp_reg =
  ( lp_reg ) ? { lp_reg[4:0] , lp_reg[5] } : 6'b00_0001 ;

endmodule

```

Parameter is not used because this logic works correctly only when number of lamps are 3.

Run this code by using the test bench on the next page.

file name: lp_seq.v


```

module test_lp_seq ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL * 2 ;
//
reg clk, rst ;
wire [2:0] lp ;
//
lp_seq lp_seq_01( .clk(clk), .rst_n(rst), .lp(lp) ) ;
//
initial begin
    $monitor("t=%d, rst=%b, lp=%b",
              $stime, rst, lp ) ;
    rst = 1'b1 ;
    # CYCL rst = 1'b0 ;
    #(CYCL * 20 ) $finish ;
end
//
always begin
    clk = 1'b0 ; #HF_CYCL ;
    clk = 1'b1 ; #HF_CYCL ;
end
endmodule
`include "lp_seq.v"

```

file name: test_lp_seq.v

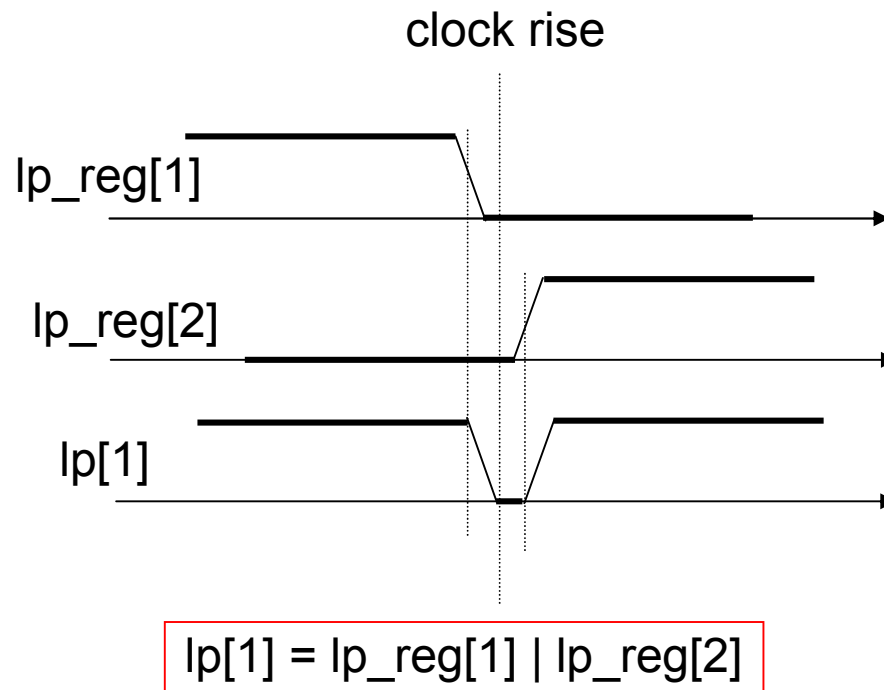Our module `lp_seq` does not output `lp[2:0]` directly from FF. The output is given through combinational logic.



Therefore, if there is some skew on FF output signals then `lp` signal may experience some flicker as shown on the left.

```

module lp_seq_cnt ( clk, rst, lp ) ;
input clk, rst ;
output [2:0] lp ;
wire clk, rst ;
wire [2:0] lp ;

reg [2:0] st_reg ; // FF for state
reg [2:0] next_st_reg ; // combinational logic

assign lp[0] = ( st_reg == 1 ) ;
assign lp[1] = ( (st_reg == 2) | (st_reg == 3) ) ;
assign lp[2] = ( (st_reg == 4) | (st_reg == 5) | (st_reg == 6) ) ;

always @ ( posedge clk or posedge rst ) begin
    if ( rst ) begin
        st_reg <= 3'b000 ;
    end
    else begin
        st_reg <= next_st_reg ;
    end
end

always @ ( st_reg ) begin
    if ( st_reg >= 3'h6 ) begin
        next_st_reg = 3'b001 ;
    end
    else begin
        next_st_reg = st_reg + 3'b001 ;
    end
end
endmodule

```

This code is almost same to the previous code. It uses counter instead of shifter and uses the counter as state variable.

Parameter is not used because this logic works correctly only when number of lamps are 3.

Number of FF is reduced from previous 6 to 3. However adder and 7 3-bit comparators are newly needed.

file name: lp_seq_cnt.v

You may come to an idea shown below. It can work almost same to the module we wrote. But it is not synthesizable. Do not try to write a target module code in this way. The target module must go into silicon.

At each clock rise time do something, and it must be repeated forever.
The basic behavior of the lamps must look like the code below.

always begin

@ (posedge clk) lp[2:0] = 3'b001 ;

@ (posedge clk) lp[2:0] = 3'b010 ;

@ (posedge clk) ;

@ (posedge clk) lp[2:0] = 3'b100 ;

@ (posedge clk) ;


@ (posedge clk) ;

end

This does not care
about reset signal.



Next think how to
handle reset.

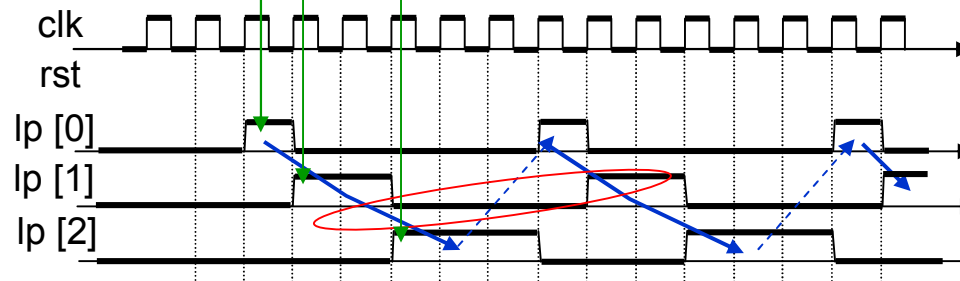

A code block below written on the idea in the previous page is **not synthesizable**. It can be used only as a model of the target module, if you want.

- {

 Discontinue loop of updating lamp signal.

 Use “disable” to discontinue the loop.
- Turn off lamps triggered by reset signal.

 Use another always construct and reset lp when rst asserted.

always begin : **main_loop**

```

  @ ( posedge clk ) lp[2:0] = 3'b001 ;
  @ ( posedge clk ) lp[2:0] = 3'b010 ;
  @ ( posedge clk ) ;
  @ ( posedge clk ) lp[2:0] = 3'b100 ;
  @ ( posedge clk ) ;
  @ ( posedge clk ) ; } Just wait for another
                        two cycles.
end


```

```

always
  @ ( posedge clk or posedge rst )
begin
  if ( rst == 1'b1 ) begin
    lp[2:0] = 3'b000 ;
    disable main_loop ;
  end
end
end


```

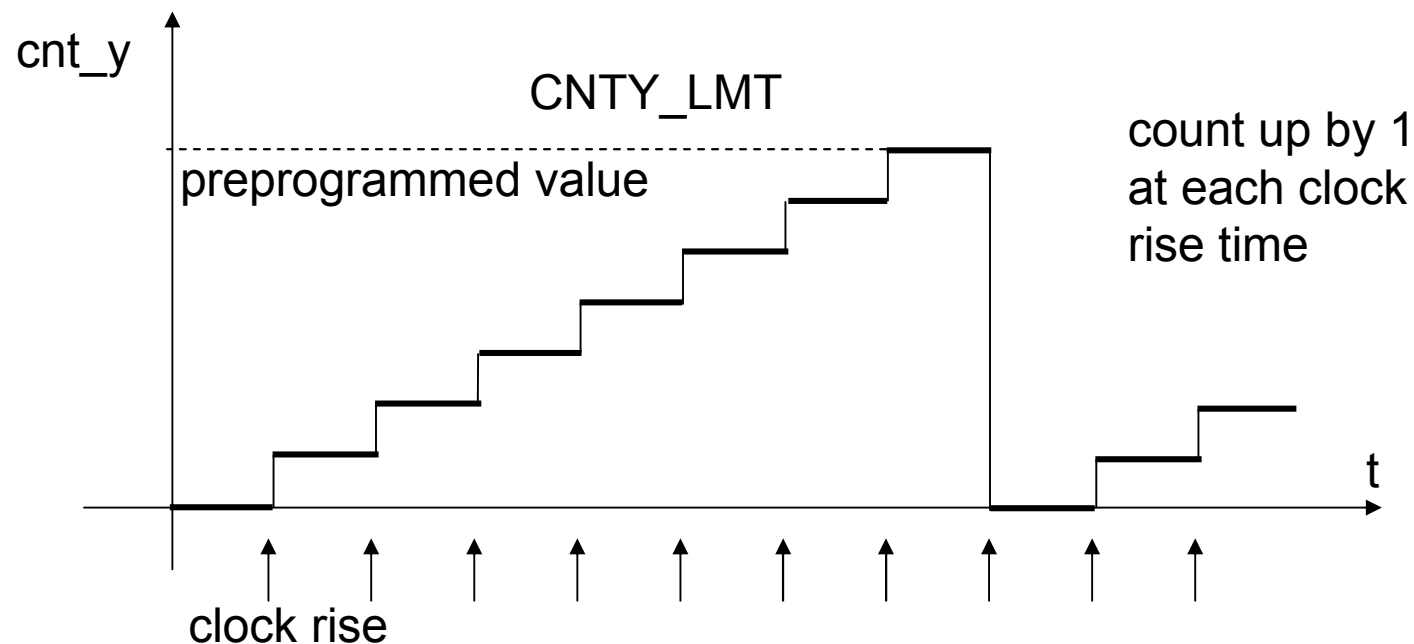Ex 4-2. Counter with limiter: Write a 8-bit counter module which add 1 to its 8-bit output `cnt_y` at each clock rise time. The counter value must become 0 on reset and each time it is going to become larger than a constant value (`CNTY_LMT`).




The value of the counter must be memorized so that it can be incremented by 1 at each clock rise time. Therefore, it must be implemented as a 8-bit flip-flop.

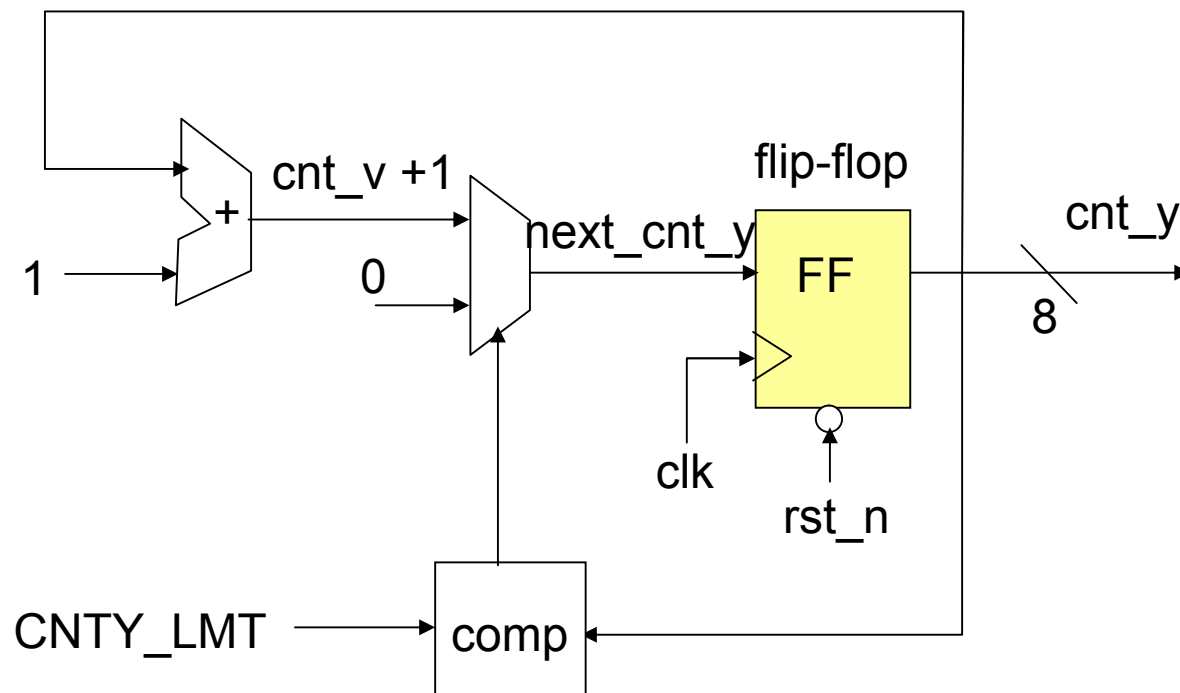cnt_y must be defined as an output of a flip-flop whose bit width is 8.
And the input for this flip-flop, next_cnt_y, can be defined as an output of the combinational logic shown in this slide.



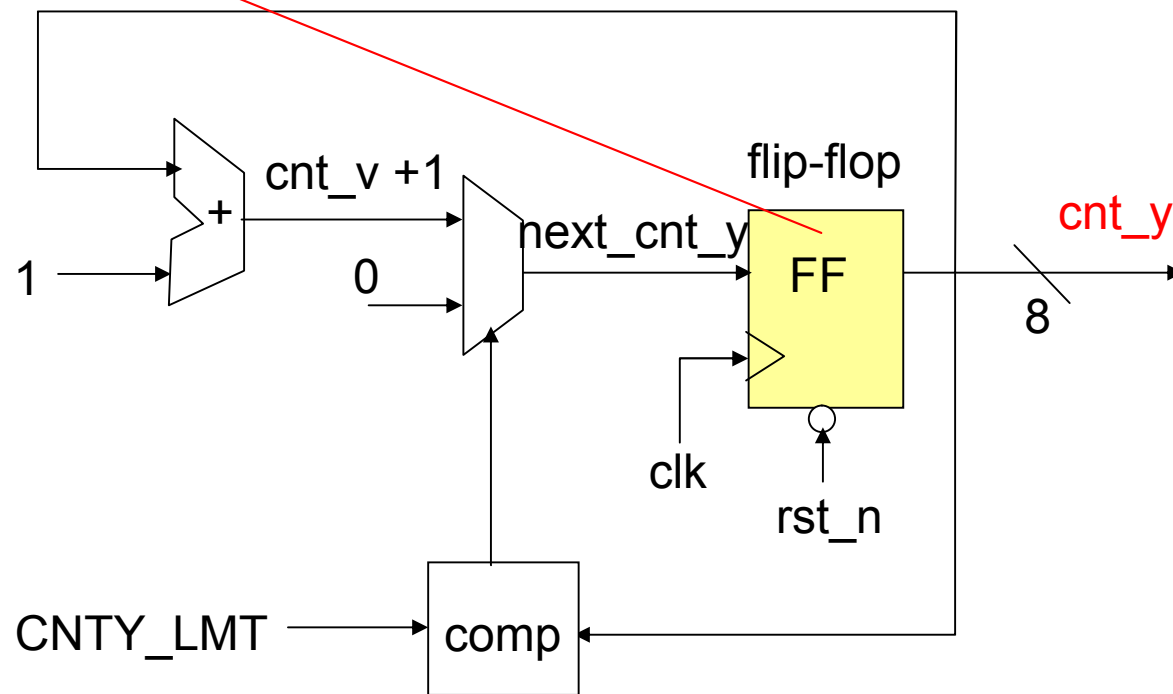
```
always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    cnt_y <= 0 ;
  end
  else begin
    cnt_y <= next_cnt_y ;
  end
end
```



next_cnt_y, the output of the combinational logic shaded by the blue oval, can be coded as shown in this slide.

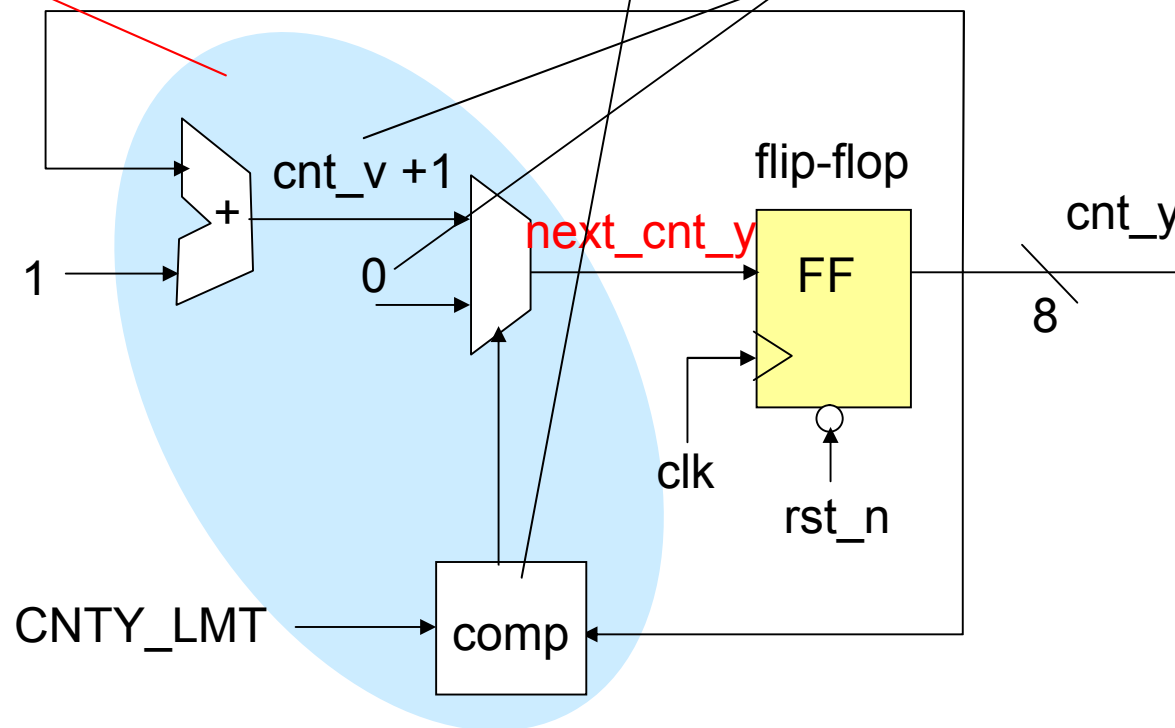
```
assign next_cnt_y = ( cnt_y == CNTY_LMT )? 0 : cnt_y + 1 ;
```




Now, create a file named `cntr_w_lmt.v` for Ex 4-2. Write a test bench in the same file.


```
module cntr_w_lmt ( clk, rst_n, cnt_y );
parameter CNTY_BW = 8 ;
parameter CNTY_LMT = 200 ; // limiter for counter max
//
input clk, rst_n ;
output [CNTY_BW-1:0] cnt_y ;
//
wire clk, rst_n ;
reg [CNTY_BW-1:0] cnt_y ; // FF for counter
//
wire [CNTY_BW-1:0] next_cnt_y ; // input for counter FF
//
always @ (posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        cnt_y <= { CNTY_BW {1'b0} } ;
    end
    else begin
        cnt_y <= next_cnt_y ;
    end
end
assign next_cnt_y = ( cnt_y == CNTY_LMT )?
                    { CNTY_BW {1'b0} } : cnt_y + 1 ;

endmodule
```

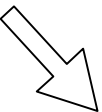



```
module test_cntr_w_lmt ;
parameter HF_CYCL = 50 ;
parameter CYCL = HF_CYCL * 2 ;
parameter CNTY_BW = 8 ;
defparam cntr_w_lmt_01.CNTY_LMT = 7 ;
//
reg clk, rst_n ;
wire [CNTY_BW-1:0] cnt_y ;
//
cntr_w_lmt  cntr_w_lmt_01 ( .clk(clk), .rst_n(rst_n), .cnt_y(cnt_y) ) ;
//
initial begin
rst_n = 1'b0 ;
#(CYCL*2) rst_n = 1'b1 ;
#(CYCL*20) $finish ;
end
always begin
clk = 0 ; #HF_CYCL ;
clk = 1 ; #HF_CYCL ;
end
always @ ( posedge clk ) begin
    $strobe( "time=%d, rst_n=%b, cnt_y=%d",
            $stime, rst_n, cnt_y ) ;
end
endmodule
```


Run this file and
check the result.

file name: cntr_w_lmt.v

A sample result

```
time=      50, rst_n=0, cnt_y= 0
time=     150, rst_n=0, cnt_y= 0
time=     250, rst_n=1, cnt_y= 1
time=     350, rst_n=1, cnt_y= 2
time=     450, rst_n=1, cnt_y= 3
time=     550, rst_n=1, cnt_y= 4
time=     650, rst_n=1, cnt_y= 5
time=     750, rst_n=1, cnt_y= 6
time=     850, rst_n=1, cnt_y= 7
time=     950, rst_n=1, cnt_y= 0
time=    1050, rst_n=1, cnt_y= 1
time=    1150, rst_n=1, cnt_y= 2
time=    1250, rst_n=1, cnt_y= 3
time=    1350, rst_n=1, cnt_y= 4
time=    1450, rst_n=1, cnt_y= 5
time=    1550, rst_n=1, cnt_y= 6
time=    1650, rst_n=1, cnt_y= 7
time=    1750, rst_n=1, cnt_y= 0
time=    1850, rst_n=1, cnt_y= 1
time=    1950, rst_n=1, cnt_y= 2
time=    2050, rst_n=1, cnt_y= 3
time=    2150, rst_n=1, cnt_y= 4
Halted at location **cntr_w_lmt.v(
```


Ex 4-3. Up down counter and STT: Write an up/down counter which count up to CNT_MX by 1 and then count down to CNT_MIN by 2. When it reaches CNT_MIN or going to become smaller than CNT_MIN, start counting up again to CNT_MX and after it reaches CNT_MX, count down to CNT_MIN. Repeat this up and down operation until asynchronous active low reset signal applied. Use Verilog2001. Write a state transition table, STT, before writing the code.

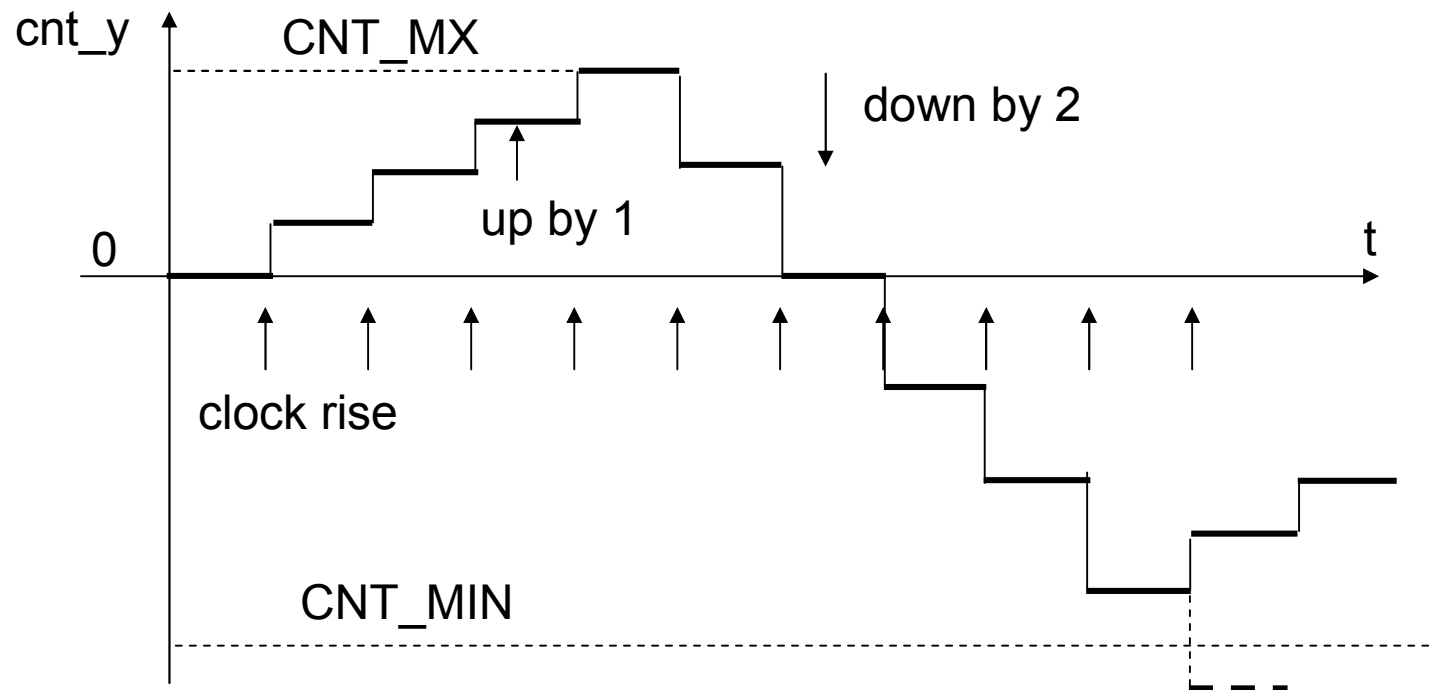

Because this system must behave differently while counting up and counting down. There must be some kind of state variable needed. cnt_y and state must be defined as flip-flop to memorize their values.


How many signals do we need
which must be memorized???

Do we need state??

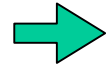


Yes, we need.

State must be memorized.

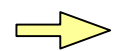


State variable must
be a flip-flop.

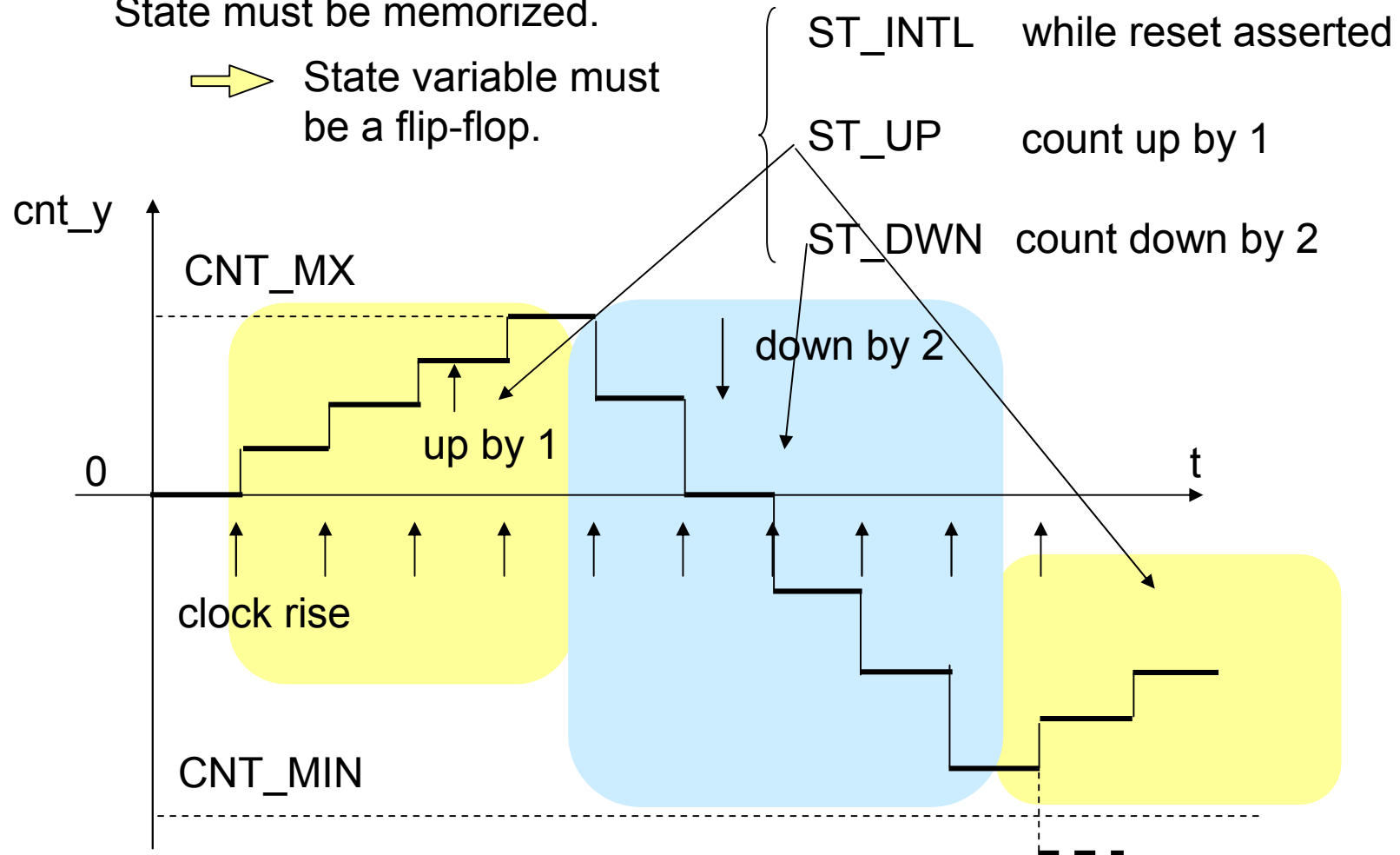

How many signals do we need
which must be memorized???


Do we have to memorize counter value??

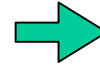


Yes, we have to because it
must keep its value for one
cycle.

cnt_y must be memorized.

→ cnt_y must be a flip-flop.

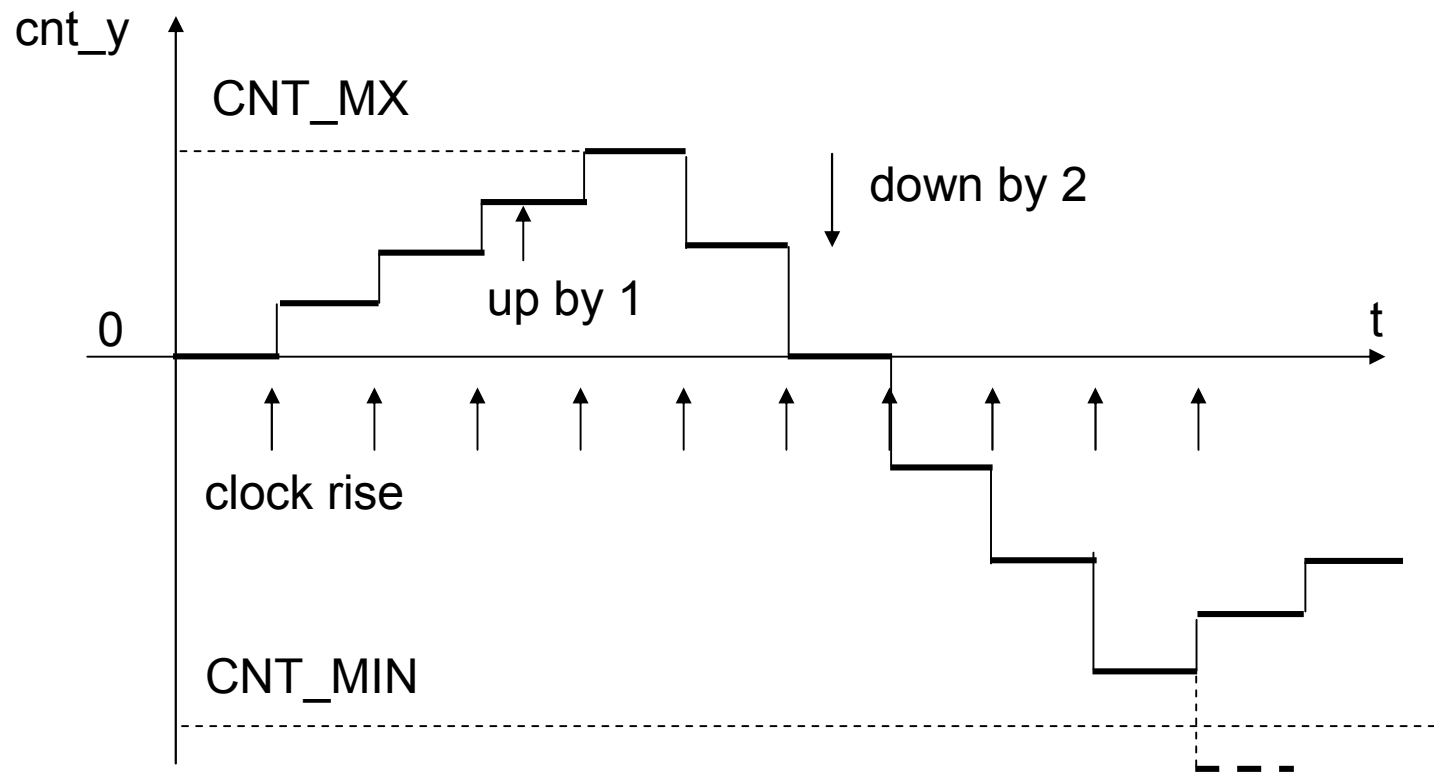

Now, draw a state transition table for state variable and cnt_y.

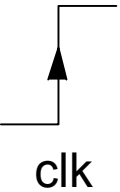event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		⇒ ST_INTL		
rst_n=1	 clk	cnt_y = 0 ⇒ ST_UP	if cnt_y ≥ CNT_MX cnt_y = cnt_y - 2 ⇒ ST_DWN else cnt_y = cnt_y + 1	if cnt_y ≤ CNT_MIN + 1 cnt_y = cnt_y + 1 ⇒ ST_UP else cnt_y = cnt_y - 2
	other than above	no-operation		

Now, define flip-flops for state and cnt_y.

```
always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    state <= ST_INTL ;
  end
  else begin
    state <= next_state ;
  end
end
```


```
always @ ( posedge clk ) begin
  cnt_y <= next_cnt_y ;
end
```

The code must look like the one shown on this slide.

You must follow the template of a flip-flop.

You may use reset signal to initialize cnt_y, but we do not have to apply reset signal to cnt_y. The code shown in this slide does not apply reset on cnt_y.


Next, create logic for
next_state.

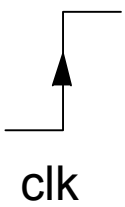event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		⇒ ST_INTL		
rst_n=1		<div style="border: 1px dashed green; padding: 5px; display: inline-block;"> ⇒ ST_UP </div>	if cnt_y ≥ CNT_MX ⇒ ST_DWN else no change	if cnt_y ≤ CNT_MIN+1 ⇒ ST_UP else no change

next_state = ST_UP ;


For the state ST_INTL, state always changes to ST_UP.

Therefore the code corresponding this box, is "next_state = ST_UP ;".

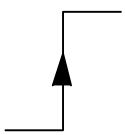event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		⇒ ST_INTL		
rst_n=1		⇒ ST_UP	if cnt_y ≥ CNT_MX ⇒ ST_DWN	if cnt_y ≤ CNT_MIN+1 ⇒ ST_UP
	clk		else no change	else no change

next_state = ST_UP ;

next_state = (cnt_y ≥ CNT_MX)? ST_DWN : state ;

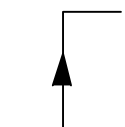
event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		⇒ ST_INTL		
rst_n=1		⇒ ST_UP	if cnt_y ≥ CNT_MX ⇒ ST_DWN else no change	if cnt_y ≤ CNT_MIN+1 ⇒ ST_UP else no change
	clk			

next_state = ST_UP ;

next_state = (cnt_y ≥ CNT_MX)? ST_DWN : state ;

next_state = (cnt_y ≤ CNT_MIN+1)? ST_UP : state ;

Integrate these three sentences into one by using case statement.

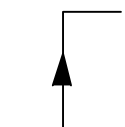state \ event		ST_INTL	ST_UP	ST_DWN
rst_n=0		⇒ ST_INTL		
rst_n=1		⇒ ST_UP	if cnt_y ≥ CNT_MX ⇒ ST_DWN else no change	if cnt_y ≤ CNT_MIN+1 ⇒ ST_UP else no change
	clk			

case (state)

ST_INTL :

next_state = ST_UP ;

ST_UP :

next_state = (cnt_y ≥ CNT_MX)? ST_DWN : state ;


ST_DWN :

next_state = (cnt_y ≤ CNT_MIN+1)? ST_UP : state ;


endcase

Next, let's think next_cnt_y logic.

We can get this table for cnt_y.

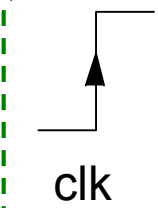event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		no-operation		
rst_n=1		cnt_y = 0	if cnt_y >= CNT_MX cnt_y = cnt_y - 2 else cnt_y = cnt_y + 1	if cnt_y <= CNT_MIN + 1 cnt_y = cnt_y + 1 else cnt_y = cnt_y - 2
	clk			

Applying the same procedure, we can get a logic block for cnt_y.

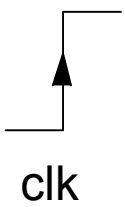event \ state		ST_INTL	ST_UP	ST_DWN
rst_n=0		no-operation		
rst_n=1		cnt_y = 0	if cnt_y >= CNT_MX cnt_y = cnt_y - 2 else cnt_y = cnt_y + 1	if cnt_y <= CNT_MIN + 1 cnt_y = cnt_y + 1 else cnt_y = cnt_y - 2
	clk			

```

case ( state )
  ST_INTL : begin
    next_cnt_y = 0 ;
  end
  ST_UP   : begin
    next_cnt_y = (cnt_y >= CNT_MX)? cnt_y-2 : cnt_y+1 ;
  end
  ST_DWN  : begin
    next_cnt_y = (cnt_y <= CNT_MIN+1)? cnt_y+1 : cnt_y-2 ;
  end
endcase

```

Now, combine these pieces of code into one file named updown_cntr_w_lmt.v.


```


module updown_cntr_w_lmt ( clk, rst_n, cnt_y );
parameter CNTY_BW = 8 ;
parameter CNT_MX = 100 ; // must not be smaller than 2,
                        // nor larger than 2**CNTY_BW -1
parameter CNT_MIN = -30 ; // must smaller than CNT_MX-1, but
                        // must not be smaller than -2**(CNTY_BW-1)

//
parameter ST_INTL = 2'b00 ;
parameter ST_UP = 2'b01 ;
parameter ST_DWN = 2'b10 ;
//
input clk, rst_n ;
output signed [CNTY_BW-1:0] cnt_y ;
//
wire clk, rst_n ;
reg signed [CNTY_BW-1:0] cnt_y ; // FF for counter
//
reg [1:0] state ; // FF for state variable
reg [1:0] next_state ; // non-FF, input for state FF
reg signed [CNTY_BW-1:0] next_cnt_y ; // non-FF, input for counter FF
//

```

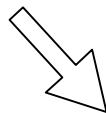cnt_y must be declared as signed because it must be able to handle negative value.






```
// FF definitions
always @ (posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        state <= ST_INTL ;
    end
    else begin
        state <= next_state ;
    end
end

// inputs for FF data creattion
always @ ( state or cnt_y ) begin
    case ( state )
        ST_INTL : begin
            next_state = ST_UP ;
        end
        ST_UP : begin
            next_state = (cnt_y >= CNT_MX)? ST_DWN : state ;
        end
        ST_DWN : begin
            next_state = (cnt_y <= CNT_MIN+1)? ST_UP : state ;
        end
        default : begin
            next_state = 2'bxx ;
        end
    endcase
end
```

default is added to avoid
creating a latch for next_state.






```
always @ ( posedge clk ) begin
    cnt_y <= next_cnt_y ;
end
```

```
always @ ( state or cnt_y ) begin
    case ( state )
        ST_INTL : begin // initialize counter in INTL state
            next_cnt_y = { CNTY_BW {1'b0} } ;
        end
        ST_UP : begin // next_cnt_y must not exceed CNT_MX
            next_cnt_y = (cnt_y >= CNT_MX)? cnt_y-2 : cnt_y+1 ;
        end
        ST_DWN : begin // next_cnt_y must not be smaller than CNT_MIN
            next_cnt_y = (cnt_y <= CNT_MIN+1)? cnt_y+1 : cnt_y-2 ;
        end
        default : begin
            next_cnt_y = { CNTY_BW {1'bx} } ;
        end
    endcase
end
//
endmodule
```


default is added to avoid a latch for next_cnt_y.


file name: updown_cntr_w_lmt.v

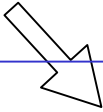

```
module test_updown_cntr_w_lmt ;
parameter HF_CYCL = 50 ;
parameter CYCL = HF_CYCL * 2 ;
parameter CNTY_BW = 8 ;
defparam updown_cntr_w_lmt_01.CNT_MX = 4 ;
defparam updown_cntr_w_lmt_01.CNT_MIN = -5 ;
//
reg clk, rst_n ;
wire signed[CNTY_BW-1:0] cnt_y ;
//
updown_cntr_w_lmt updown_cntr_w_lmt_01 (
                                .clk(clk), .rst_n(rst_n), .cnt_y(cnt_y)
                                ) ;

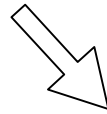//
initial begin
rst_n = 1'b0 ;
#(CYCL*2) rst_n = 1'b1 ;
#(CYCL*20) $finish ;
end
```





```
always begin
clk = 0 ; #HF_CYCL ;
clk = 1 ; #HF_CYCL ;
end

always @ ( posedge clk ) begin
    $strobe( "time=%d, rst_n=%b, cnt_y=%d",
            $stime, rst_n, cnt_y ) ;
end
endmodule
//
`include "test_updown_cntr_w_lmt.v"
```

file name: test_updown_cntr_w_lmt.v


Run test_updown_cntr_w_lmt.von your PC
and check the result.
Try changing parameters.

A sample result


```
defparam updown_cntr_w_lmt_01.CNT_MX = 4 ;
defparam updown_cntr_w_lmt_01.CNT_MIN = -5 ;
```

```
time=      50, rst_n=0, cnt_y=  0
time=     150, rst_n=0, cnt_y=  0
time=     250, rst_n=1, cnt_y=  0
time=     350, rst_n=1, cnt_y=  1
time=     450, rst_n=1, cnt_y=  2
time=     550, rst_n=1, cnt_y=  3
time=     650, rst_n=1, cnt_y=  4
time=     750, rst_n=1, cnt_y=  2
time=     850, rst_n=1, cnt_y=  0
time=     950, rst_n=1, cnt_y= -2
time=    1050, rst_n=1, cnt_y= -4
time=    1150, rst_n=1, cnt_y= -3
time=    1250, rst_n=1, cnt_y= -2
time=    1350, rst_n=1, cnt_y= -1
time=    1450, rst_n=1, cnt_y=  0
time=    1550, rst_n=1, cnt_y=  1
time=    1650, rst_n=1, cnt_y=  2
time=    1750, rst_n=1, cnt_y=  3
time=    1850, rst_n=1, cnt_y=  4
time=    1950, rst_n=1, cnt_y=  2
time=    2050, rst_n=1, cnt_y=  0
time=    2150, rst_n=1, cnt_y= -2
Halted at location **updown_cntr_w_
```

Ex. 4-4. Sequential accumulator with overflow checker: Write a module which accumulates 4-bit input `in_a` at each clock rise time. The accumulation must be done only when `in_a` is valid. If it is not valid, discard it. `in_a` is invalid when $\text{ABS}(\text{in_a})$ is larger than a predefined value `MX_IN` or accumulation will cause overflow. The first `in_a`, right after reset negated, must be neglected. The accumulated value must be placed on 8-bit output, `sig_acc`. The module must place 1 to output `ovf_flg` when `in_a` will cause overflow. Also it must place 1 to output `ovr_mx` when $\text{ABS}(\text{in_a})$ is larger than `MX_IN`. Use Verilgo2001. The initial value of `sig_acc` must be 0.

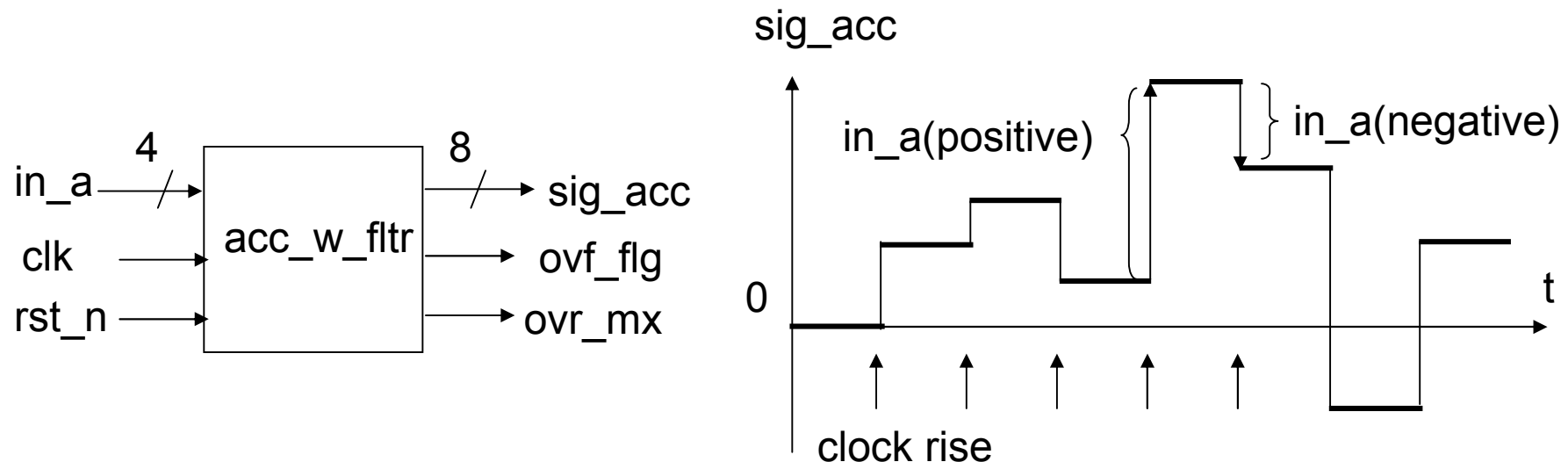

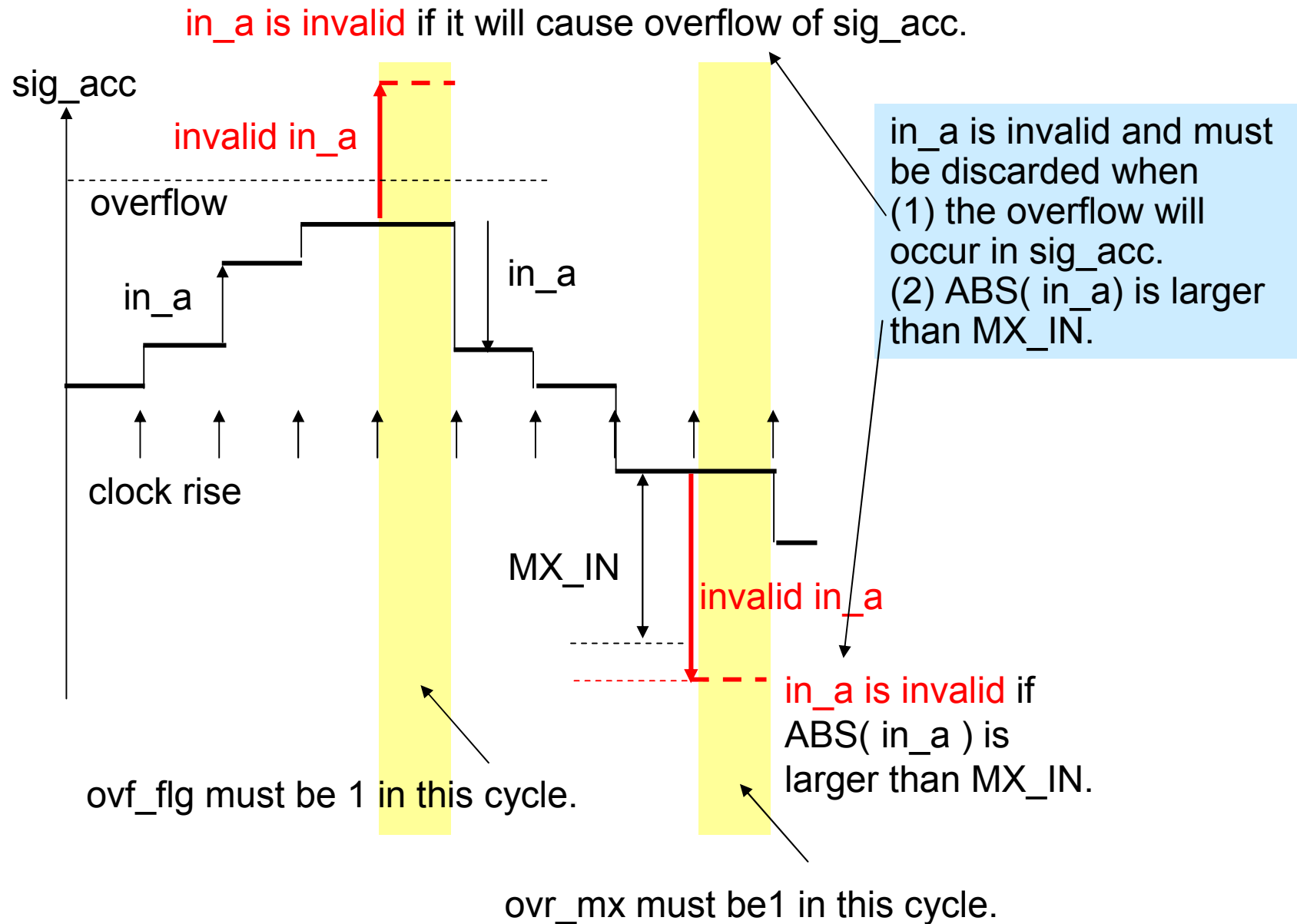Use FF for outputs, `sig_acc`, `ovf_flg`, and `ovr_mx`. Use `$random` to generate random number for test inputs.




Do we need state to realize the system???

Yes, we do.

Because, there are two cases,

(1) reset is asserted and no accumulation done, and

(2) reset is negated and accumulation must be done.



ST_INTL
no accumulation

ST_RUN
accumulate in_a

How many signals do we need which must be memorized???

(1) sig_acc must be memorized to hold the accumulated value.

(2) ovf_flg must be memorized so it keeps the same value for one cycle.

(3) ovr_mx must be memorized so it keeps the same value for one cycle.

About FF output of ovr_mx and ovf_flg

You may have a question like “ovr_mx and ovf_flg can be implemented as outputs of combinational logic, they may not be implemented as FFs.”

Combinational logic idea must look like the following;

```
reg [7:0] sum ;
```

```
always @ ( in_a or sig_acc ) begin
```


```
sum = in_a + sig_acc ;
```

```
ovf_flg = ((in_a[3] & sig_acc[7] ) & (~sum[7]) ) |  
          (((~in_a[3]) & (~sig_acc[7]) ) & sum[7] )
```


```
end
```

Flag is an output
of combinational
logic.

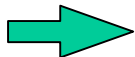The logic means that whenever `in_a + sig_acc` causes overflow, `ovf_flg` becomes 1. Therefore `ovf_flg` can change its value whenever `in_a` or `sig_acc` changes.



This will cause the problem shown on the next page.

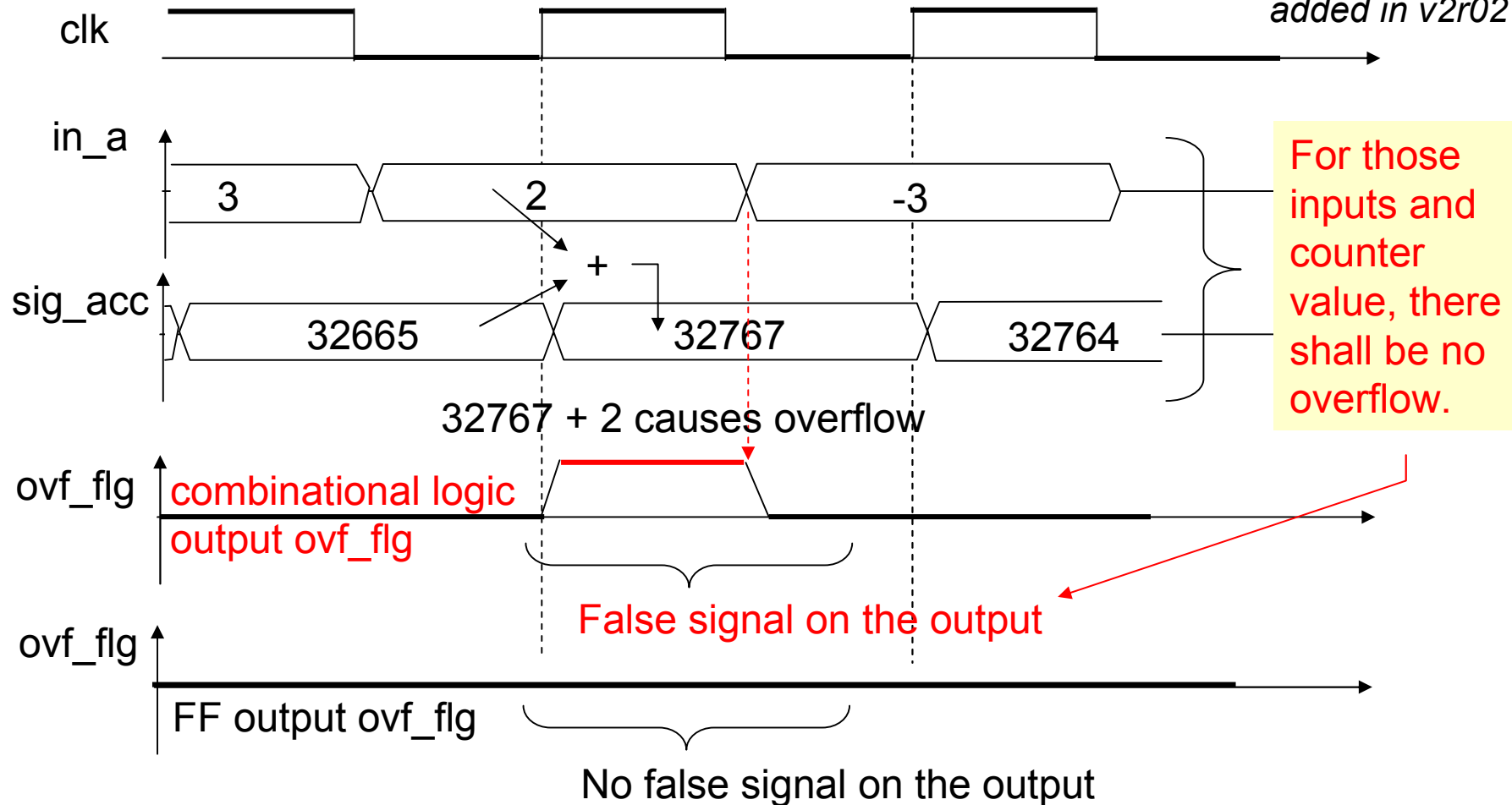
added in v2r02

The logic on the previous slide shows that `ovf_flg` becomes 1, while `in_a` is 2 and `sig_acc` is 32767 because signed 16-bit data can not hold 32769.

Therefore, false signal will appear on `ovf_flg`.


If we use FF for `ovf_flg`, such false data will not come out. Please look carefully into the sample code and see yourself such false data will not come out.

Now we can get the state transition table as below.

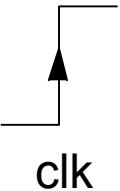event \ state		ST_INTL	ST_RUN
rst_n=0		sig_acc = 0	ovf_flg = 0 ovr_mx = 0 ➡ ST_INTL
rst_n=1	 clk	no-operation	(1) if ABS(in_a) > MX_IN , ovr_mx=1 else ovr_mx=0 (2) if <i>overflow</i> , ovf_flg =1 else ovf_flg = 0 (3) if ~ovr_mx & ~ovr_flg , sig_acc = sig_acc + in_a else sig_acc = sig_acc
	other than above	➡ ST_RUN	no-operation

First, think state control logic.

This is a state transition table focusing on just a state variable only.

event		ST_INTL	ST_RUN
rst_n=0		⇒ ST_INTL	
rst_n=1		⇒ ST_RUN	no-change
	other than above	no-change	

```

always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    state <= ST_INTL ;
  end
  else begin
    state <= next_state ;
  end
end
//
assign next_state = ST_RUN ;

```


We can get this code.

From ST_INTL, state changes to ST_RUN if reset negated.

So far as reset asserted, state will never change to ST_RUN even if next_state is assigned the value ST_RUN always.

Next, think ovr_mx.

This is a state transition table focusing on just ovr_mx only. *revised in v2r02*

event		ST_INTL	ST_RUN
rst_n=0		ovr_mx=0	
rst_n=1		no-operation	(1) if ABS(in_a) <= MX_IN, ovr_mx=0 else ovr_mx=1
	other than above	no-operation	

```
always @ ( posedge clk or negedge rst_n ) begin
```

```
  if ( rst_n == 1'b0 ) begin
```

```
    ovr_mx <= 0 ;
```

```
  end
```

```
  else begin
```

```
    ovr_mx <= next_ovr_mx ;
```

```
  end
```

```
end
```

```
//
```

```
wire [3:0] abs_in_a;
```

```
assign abs_in_a =
```

```
  ( in_a[3] )? -in_a : in_a ;
```

```
always @ ( state or abs_in_a ) begin
```

```
  case ( state )
```

```
    ST_INTL : begin
```

```
      next_ovr_mx = ovr_mx ;
```

```
    end
```

```
    ST_RUN : begin
```

```
      next_ovr_mx_flg =
```

```
        ( abs_in_a <= MX_IN ) ? 0 : 1 ;
```


```
    end
```

```
  endcase
```

```
end
```

Next, think ovf_flg.

This is a state transition table focusing on just ovf_flg only.

event		ST_INTL	ST_RUN
rst_n=0		ovf_flg =0	
rst_n=1		no-operation	(2) if <i>overflow</i> , ovf_flg =1 else ovf_flg = 0
	other than above	no-operation	

```

always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    ovf_flg <= 0 ;
  end
  else begin
    ovf_flg <= next_ovf_flg ;
  end
end
//

```

```

always @ ( state or in_a ) begin
  case ( state )
    ST_INTL : begin
      next_ovf_flg = ovf_flg ;
    end
    ST_RUN : begin
      next_ovf_flg = See next page
    end
  endcase
end

```

Overflow can be detected by checking sign bits of the result and operands as in the expression below. It checks sign bits of next_sig_acc, that is a result of sig_acc+in_a, and in_a.

positive + positive becomes negative


↑

```
next_ovf_flg = ((~sig_acc[7]) & (~in_a[3]) & next_sig_acc[7]) |  
               (sig_acc[7] & in_a[3] & (~next_sig_acc[7]))? 1 : 0 ;
```

↓

negative + negative becomes positive

This is a state transition table focusing on sig_acc

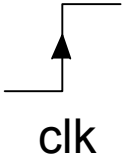event		ST_INTL	ST_RUN
rst_n=0		sig_acc = 0	
rst_n=1		no-operation	<div style="border: 1px dashed green; padding: 5px;"> (3) if $\sim\text{ovr_mx} \ \& \ \sim\text{ovr_flg}$, $\text{sig_acc} = \text{sig_acc} + \text{in_a}$ else $\text{sig_acc} = \text{sig_acc}$ </div>

In this procedure, sig_acc is given a new value in a path but not given any value in the other path. There are two ways to implement this as shown below. A style on the left is used for ovr_mx and ovr_flg.

```

always @ ( posedge ,,,) begin
  sig_acc = next_sig_acc ;
end
always @ ( ,,,, ) begin
  if ( condition ) begin
    next_sig_acc =
    sig_acc+in_a;
  end
  else begin
    next_sig_acc = sig_acc ;
  end
end

```

end

FF without enable input

```

always @ ( posedge ,,,) begin
  if ( condition ) begin
    sig_acc = next_sig_acc ;
  end
end

```

```

always @ ( ,,,, ) begin
  next_sig_acc = sig_acc+in_a;
end

```

FF with enable input

FF without enable input

```

always @ ( posedge ,,,) begin
  sig_acc = next_sig_acc ;
end
always @ ( ,,,, ) begin
  if ( condition ) begin
    next_sig_acc = sig_acc+in_a;
  end
  else begin
    next_sig_acc = sig_acc ;
  end
end
end

```

FF with enable input

```

always @ ( posedge ,,,) begin
  if ( condition ) begin
    sig_acc = next_sig_acc ;
  end
end
always @ ( ,,,, ) begin
  next_sig_acc = sig_acc+in_a;
end
end

```

Logically
the same

different

next_sig_acc is **not** sig_acc+in_a
depending on condition.

next_sig_acc is always sig_acc+in_a
regardless of *condition*.

next_ovf_flg **can not be calculated correctly** by the expression below
because depending on *condition*, **next_sig_acc is not sig_acc+in_a.**

```


next_ovf_flg = ( (~sig_acc[7]) & (~in_a[3]) & next_sig_acc[7] ) |
               ( sig_acc[7] & in_a[3] & (~next_sig_acc[7]) )? 1 : 0 ;

```

next_ovf_flg is correct only when next_sig_acc is sig_acc+in_a.

We have to use "FF with enable input" style for sig_acc so that next_ovf_flg has correct value always.

This is a state transition table focusing on sig_acc

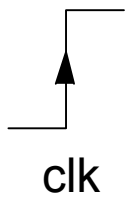event		ST_INTL	ST_RUN
rst_n=0		sig_acc = 0	
rst_n=1		no-operation	<div style="border: 1px dashed green; padding: 5px;"> (3) if $\sim\text{ovr_mx} \ \& \ \sim\text{ovr_flg}$, $\text{sig_acc} = \text{sig_acc} + \text{in_a}$ else $\text{sig_acc} = \text{sig_acc}$ </div>
	clk		

always @ (posedge clk or negedge rst_n) begin

if (rst_n == 0) begin

sig_acc = 0 ;

end

else begin

if (in_a_valid) begin

sig_acc = next_sig_acc ;

end

end

end

//

assign next_sig_acc =

sig_acc + in_a ;

reg in_a_valid ;

always @ (state or ovr_mx
or ovf_flg) begin

case (state)

ST_INTL : begin

in_a_valid = 0 ;

end

ST_RUN : begin

in_a_valid = (($\sim\text{ovr_mx}$)& ($\sim\text{ovf_flg}$))? 1 : 0 ;

end

endcase


end

This is to discard the first
input. If you want to
accept it, change this to 1.

```
module acc_w_filtr ( clk, rst_n, in_a, sig_acc, ovr_mx, ovf_flg ) ;  
parameter IN_BW = 4 ;  
parameter OUT_BW = 8 ;  
parameter MX_IN = 5 ;  
//  
parameter ST_INTL = 1'b0 ;  
parameter ST_RUN = 1'b1 ;  
//  
input clk, rst_n ;  
input signed [IN_BW-1:0] in_a ;  
output signed [OUT_BW-1:0] sig_acc ;  
output ovr_mx, ovf_flg ; // overflow indicator and over MX_IN indicator  
//  
wire clk, rst_n ;  
wire signed [IN_BW-1:0] in_a ;  
reg signed [OUT_BW-1:0] sig_acc ; // FF for accumulation  
reg ovr_mx, ovf_flg ; // FF for overflow indicator and over MX_IN indicator  
//
```

Parameters are introduced
to make the code flexible.







```
reg state ; // FF, state
wire next_state ; // input for state FF
wire signed [OUT_BW-1:0] next_sig_acc ; // input for FF sig_acc
reg next_ovf_flg, next_ovr_mx ; // non-FF, input for ovf_flg FF and ovr_mx FF
reg in_a_valid ; // non-FF, enable flag to set sig_acc FF
wire [IN_BW-1:0] abs_in_a ; // absolute value of in_a
//

// logic start

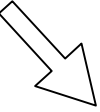
// state FF and state control logic
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        state <= ST_INTL ;
    end
    else begin
        state <= next_state ;
    end
end
//
assign next_state = ST_RUN ;
```







```
// over max flag
assign abs_in_a = ( in_a[IN_BW-1] )? -in_a : in_a ; // absolute value of in_a
always @ ( state or abs_in_a ) begin
  case ( state )
    ST_INTL : begin
      next_ovr_mx = ovr_mx ;
    end
    ST_RUN : begin
      next_ovr_mx = ( abs_in_a <= MX_IN ) ? 1'b0 : 1'b1 ;
    end
    default : begin next_ovr_mx = 1'bx ; end
  endcase
end

always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    ovr_mx <= 0 ;
  end
  else begin
    ovr_mx <= next_ovr_mx ;
  end
end
//
```




default is added for debug

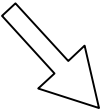





```
// overflow flag
wire ovf_tmp ; // temporarily work for next_ovf_flg
assign ovf_tmp =
    ( (~sig_acc[OUT_BW-1]) & (~in_a[IN_BW-1]) & next_sig_acc[OUT_BW-1] ) |
    ( sig_acc[OUT_BW-1] & in_a[IN_BW-1] & (~next_sig_acc[OUT_BW-1]) )?
    1'b1 : 1'b0 ;
always @ ( state or in_a ) begin
    case ( state )
        ST_INTL : begin
            next_ovf_flg = ovf_flg ;
        end
        ST_RUN : begin
            next_ovf_flg = ovf_tmp ;
        end
        default : begin next_ovf_flg = 1'bx ; end
    endcase
end
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        ovf_flg <= 0 ;
    end
    else begin
        ovf_flg <= next_ovf_flg ;
    end
end
```




default is added for debug






```
//  
// enable flag, in_a_valid, control logic  
always @ ( state or next_ovr_mx or next_ovf_flg ) begin  
  case ( state )  
    ST_INTL : begin  
      in_a_valid = 1'b1 ;  
    end  
    ST_RUN : begin  
      in_a_valid = ((~next_ovr_mx) & (~next_ovf_flg))? 1'b1 : 1'b0 ;  
    end  
    default : begin  
      in_a_valid = 1'bx ;  
    end  
  endcase  
end
```

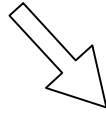next_ovf_flg is used instead of ovf_flg.
next_ovr_mx is used instead of ovr_mx.
default is added for debug







```
//  
// sig_acc FF and sig_acc control logic  
always @ ( posedge clk or negedge rst_n ) begin  
    if ( rst_n == 1'b0 ) begin  
        sig_acc = {OUT_BW{1'b0}} ;  
    end  
    else begin  
        if ( in_a_valid ) begin  
            sig_acc = next_sig_acc ;  
        end  
    end  
end  
// next_sig_acc must always be set to calculate ovf_ind  
assign next_sig_acc = sig_acc + in_a ; // Verilog2001  
//  
  
endmodule
```

file name: acc_w_fltr.v


```
module test_acc_w_fltr ;  
parameter IN_BW = 4 ;  
defparam acc_w_fltr_01.IN_BW = IN_BW ;  
parameter OUT_BW = 8 ;  
defparam acc_w_fltr_01.OUT_BW = OUT_BW ;  
defparam acc_w_fltr_01.MX_IN = 5 ;  
//  
parameter HF_CYCL = 5 ;  
parameter CYCL = HF_CYCL * 2 ;  
parameter TST_CYCL = 300 ;  
//  
reg clk, rst_n ;  
reg signed [IN_BW-1:0] in_a ;  
wire signed [OUT_BW-1:0] sig_acc ;  
wire ovf_flg, ovr_mx ;  
integer k ;  
//
```

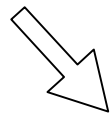

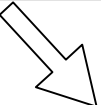


```
// module connection
acc_w_fltr  acc_w_fltr_01 ( .clk(clk), .rst_n(rst_n),
                           .in_a(in_a), .sig_acc(sig_acc),
                           .ovr_mx(ovr_mx), .ovf_flg(ovf_flg) );

//
always begin
  clk=0 ; #HF_CYCL ;
  clk=1 ; #HF_CYCL ;
end
//
initial begin
  rst_n = 1'b0 ;
  #CYCL rst_n = 1'b1 ;
  #(CYCL*29) rst_n = 1'b0 ;
  #CYCL rst_n = 1'b1 ;
  #(CYCL * TST_CYCL ) $finish ;
end
//
```





```
// give random numbers for in_a
initial begin
    #CYCL ;
    for ( k=0 ; k <= TST_CYCL+30 ; k = k+1 ) begin
        in_a = $random ;
        #CYCL ;
    end
end
//
// observe signals at clock rise time
always @ ( posedge clk ) begin
    $strobe
    ("t=%d, r=%b, in_a=%d, acc=%d, ovr_mx=%b, ovf=%b",
    $time, rst_n, in_a, sig_acc, ovr_mx, ovf_flg ) ;
end

endmodule
`include "acc_w_filtr.v"
```

32-bit random number is created.


file name: test_acc_w_filtr.v

Now, run this file on your
PC and see the result.

parameter OUT_BW = 8 ;

A part of a sample result


```
t= 515, r=1, in_a= 2, acc= -1, ovr_mx=0, ovf=0
t= 525, r=1, in_a= -6, acc= -1, ovr_mx=1, ovf=0
t= 535, r=1, in_a= 1, acc= 0, ovr_mx=0, ovf=0
t= 545, r=1, in_a= -8, acc= 0, ovr_mx=1, ovf=0
t= 555, r=1, in_a= -8, acc= 0, ovr_mx=1, ovf=0
t= 565, r=1, in_a= -7, acc= 0, ovr_mx=1, ovf=0
t= 575, r=1, in_a= -5, acc= -5, ovr_mx=0, ovf=0
t= 585, r=1, in_a= 6, acc= -5, ovr_mx=1, ovf=0
t= 595, r=1, in_a= 6, acc= -5, ovr_mx=1, ovf=0
t= 605, r=1, in_a= -2, acc= -7, ovr_mx=0, ovf=0
t= 615, r=1, in_a= -4, acc= -11, ovr_mx=0, ovf=0
t= 625, r=1, in_a= -6, acc= -11, ovr_mx=1, ovf=1
t= 635, r=1, in_a= -5, acc= -16, ovr_mx=0, ovf=0
```

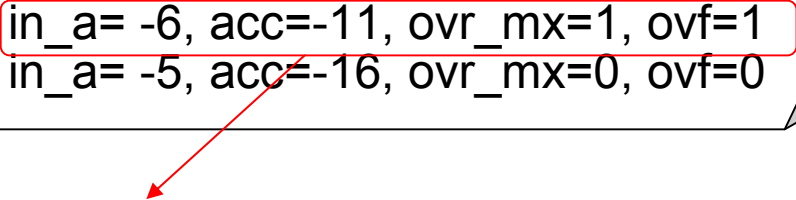

-11 + (-6) = -17, it can not be held in 5-bit variable,
therefore overflow detected.


To make overflow easily occur, OUT_BW is changed to 5 instead of 8.

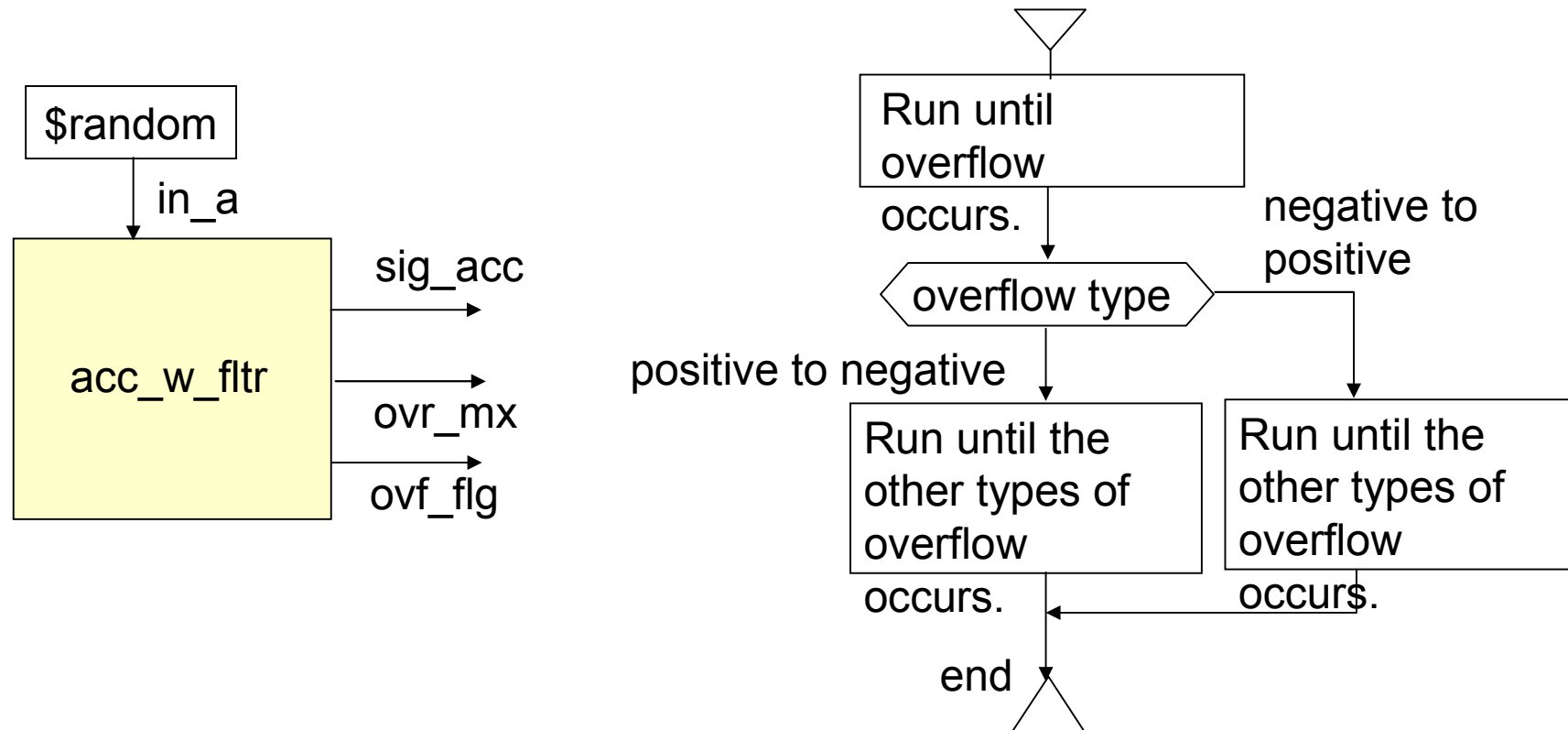
Ex. 4-5. Automatic test bench: Write a test bench which can automatically test the module `acc_w_fltr` written in Ex. 4-4. The test bench must check, at each clock rise time, `sig_acc`, `ovr_mx`, and `ovf_flg` are calculated correctly.




`ovr_mx` can easily become 1, therefore the test bench focuses on overflow. There are two types of overflow, large positive number becomes negative and small negative number becomes positive. The test bench runs until both types of overflow occur.

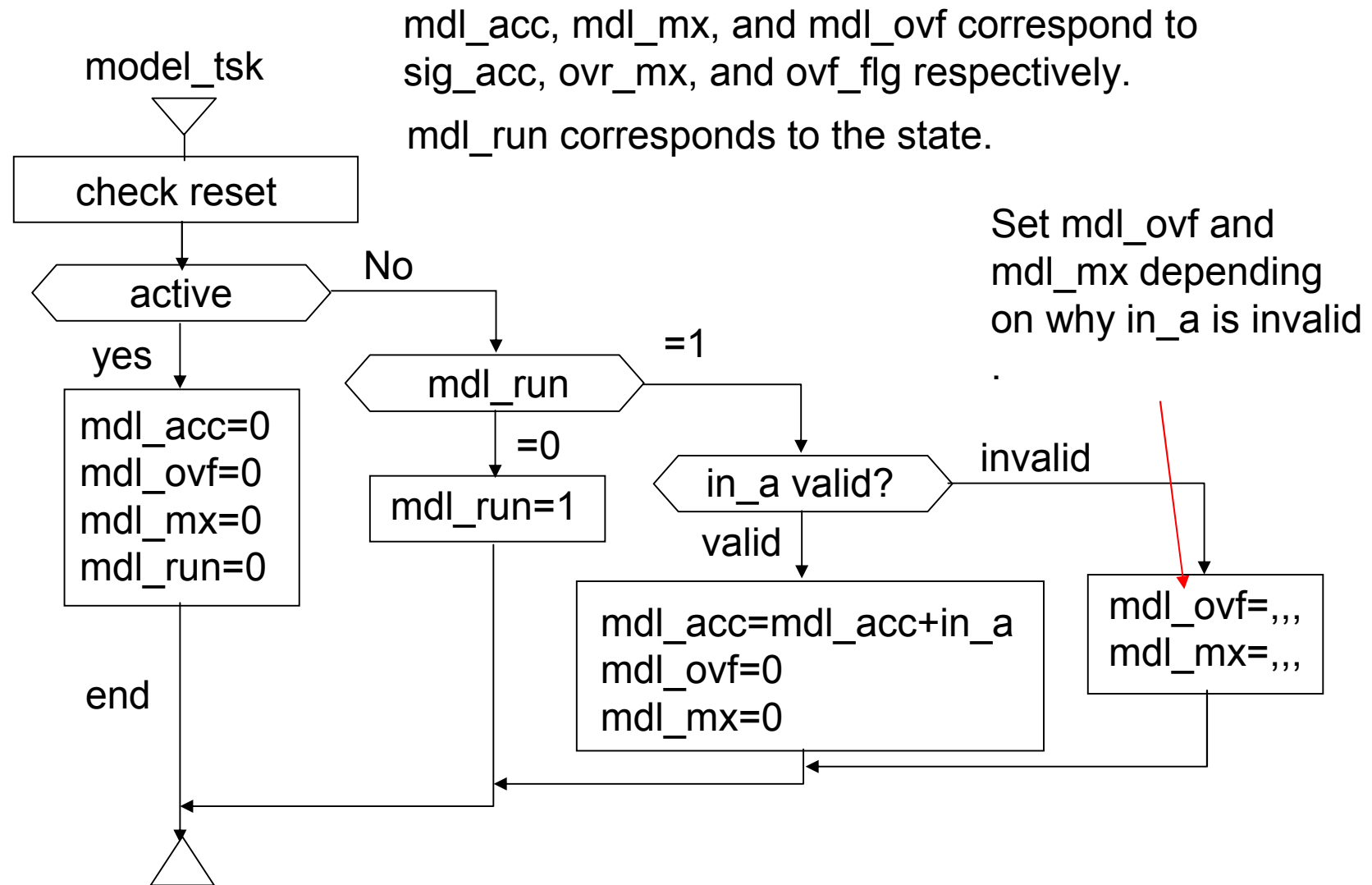First, let's write a task as a golden model of acc_w_filtr which is invoked at each clock rise time and behaves same to the target module.



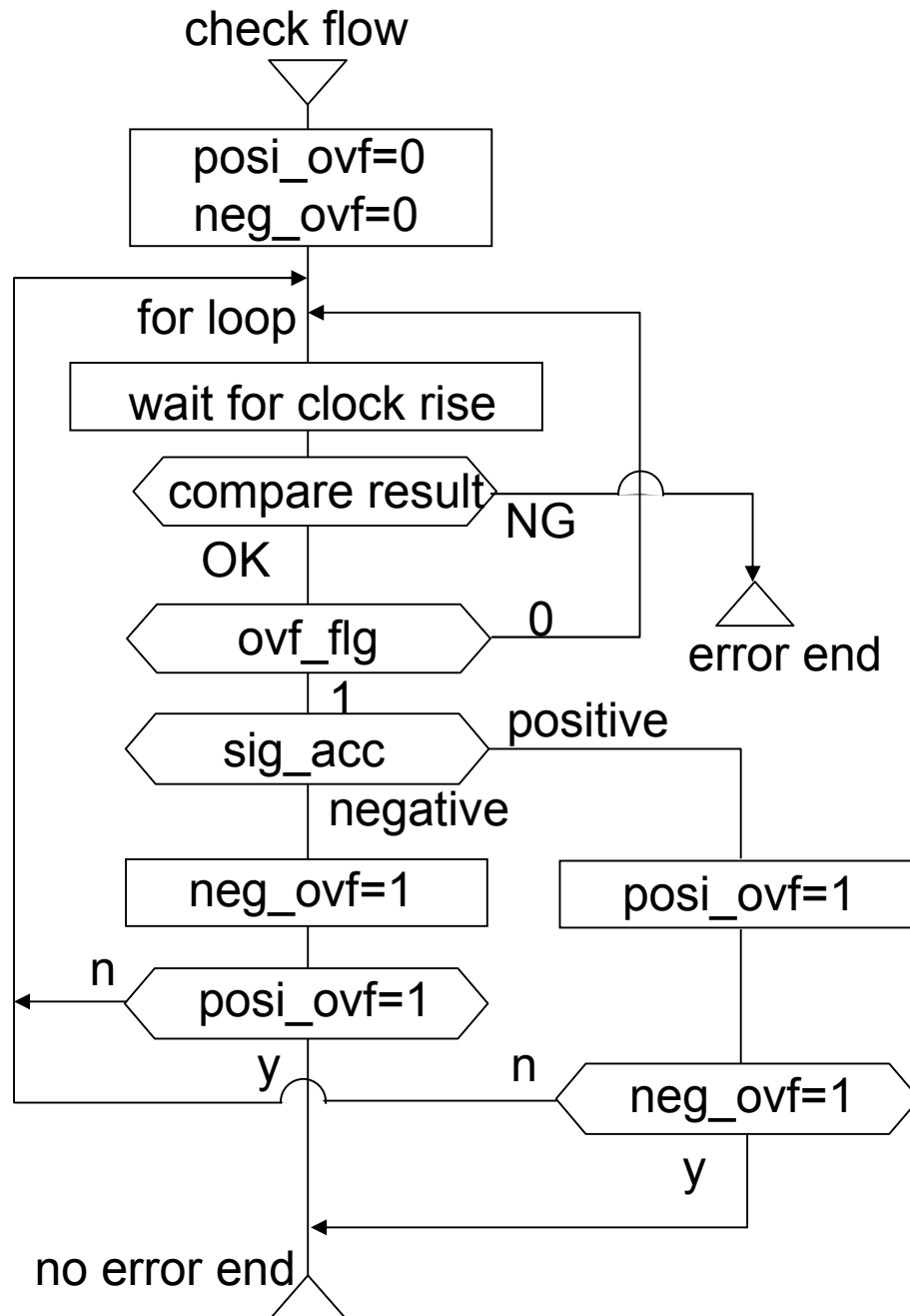

input signal generation

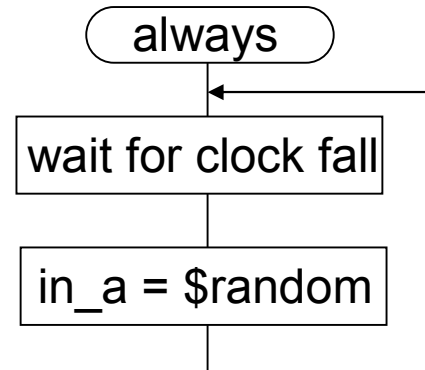


This is a procedure to check the module `acc_w_ftr`. First, input is accumulated until overflow occurs. and input is accumulated again until another type of overflow occurs.

golden model

```

task model_tsk;
reg signed [OUT_BW-1:0] next_acc ;
begin
if( rst_n == 1'b0 ) begin
    mdl_acc = 0 ;
    mdl_ovf = 0 ;
    mdl_mx = 0 ;
    mdl_run = 0 ;
end
else begin
    if ( mdl_run ) begin
        next_acc = mdl_acc + in_a ;
        mdl_ovf =
            ( (in_a >= 0) & ( mdl_acc >= 0 ) & ( next_acc < 0 ) ) |
            ( ( in_a < 0 ) & ( mdl_acc < 0 ) & (next_acc >= 0 ) ) ;
        if ( mdl_run ) begin
            mdl_mx = ( ( in_a > MX_IN ) | ( in_a < -MX_IN ) ) ?
                1 : 0;
            mdl_acc = (mdl_ovf | mdl_mx ) ?
                mdl_acc : mdl_acc + in_a ;
        end
    end
    else begin mdl_run = 1 ; end
end
endtask

```

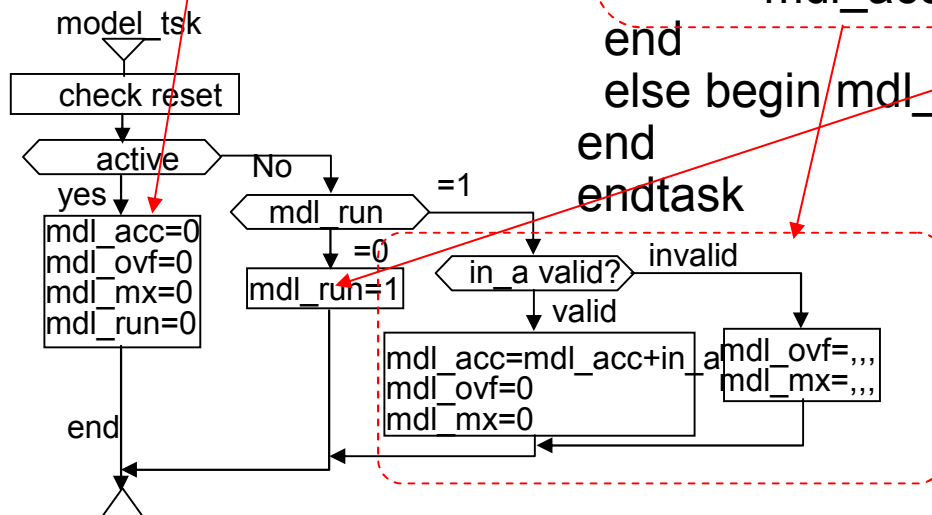

You can see golden model is much simpler than the target module. In the model, we don't have to care about hardware resources such as flip-flops.

RTL programming rules

(1) For $y = a \text{ op } b$; , where op is a verilog operator, bit size of a and b are extended to the bit size of y .

This is true for the case of $a \geq b$. a and b are sized to $\text{Max}(\text{bit size of } a, \text{bit size of } b)$. See an example below for detail.

```
wire signed [7:0] a, b ;
wire signed [7:0] c ;
reg flg1, flg2 ;
```

```
assign c = a + b ;
```

```
flg1 = ( [c > 0] )? 1: 0 ;
```


```
flg2 = ( [a + b > 0] )? 1: 0 ;
```

By this assignment, c will be **36** of which bit pattern is 0010_0100, if a is **-106** of which bit pattern is 1001_0110, b is **-114** of which bit pattern is 1000_1110. This means **overflow occurred in calculating c** .

Therefore, this may become true if **a and b are negative** and overflow occurs.

However, this will **never becomes true, even if overflow occurs** for 8-bit negative a and b . Because 0 means 32-bit value, $a + b$ is calculated after a and b are size-extended to 32-bit.

test input generation

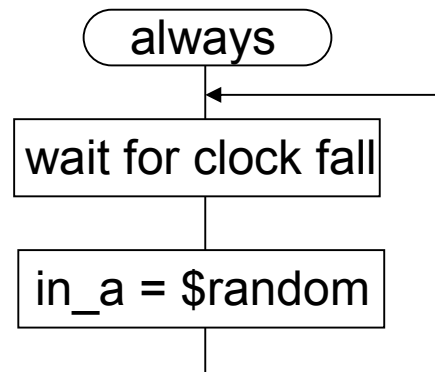


To make in_a stable at clock rise time, negedge of the clock is used.

```
always begin @ ( negedge clk );  
    in_a = ($random % 8) ; // in_a is from -7 to 7  
end
```

modulus operator


For testing 8-bit sig_acc and 4-bit in_a, random number may not be a good idea to apply. Because it will need many simulation cycles to make overflow of sig_acc.

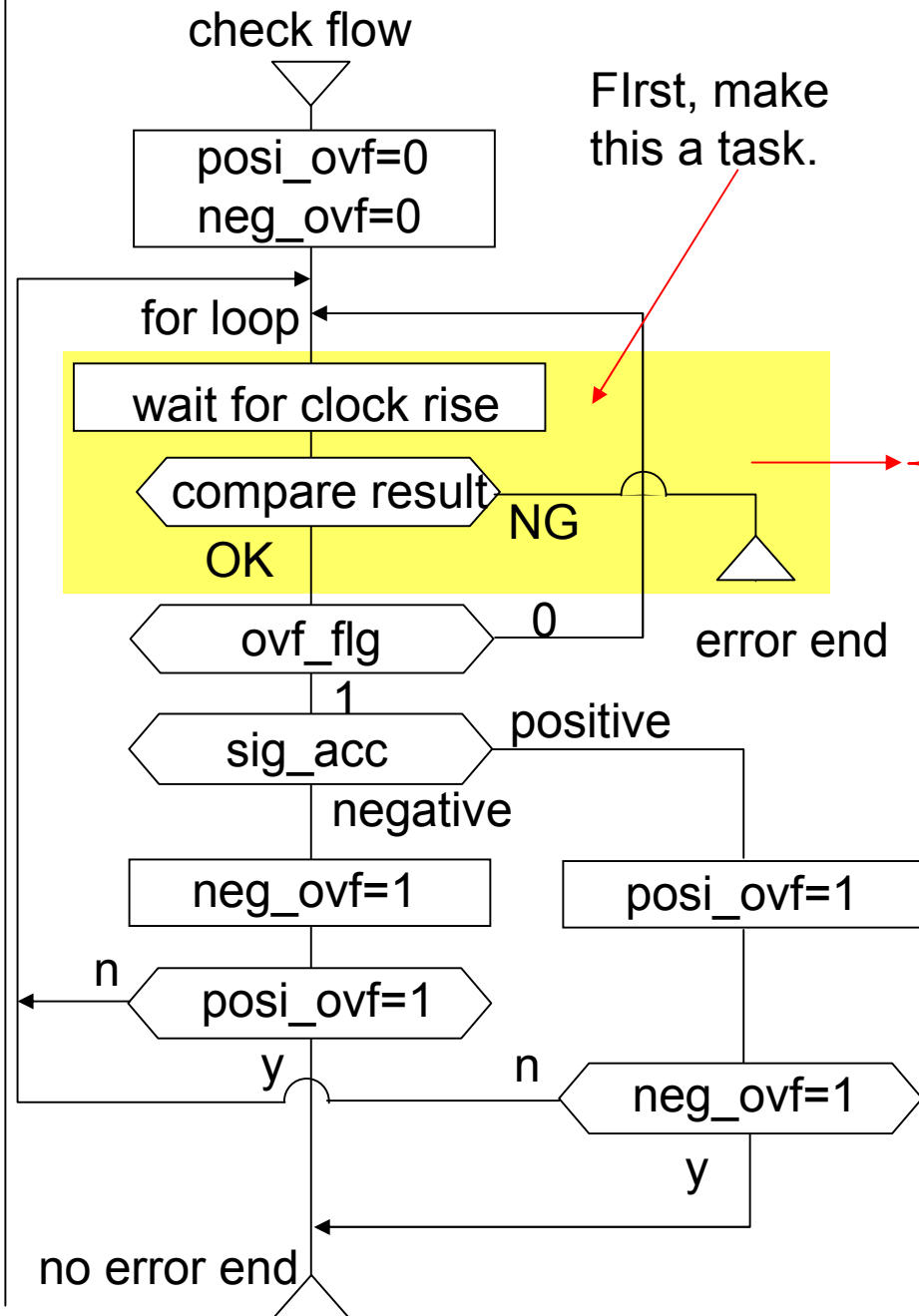To make overflow of 8-bit sig_acc by adding 4-bit in_a, apply the same sign values until overflow occurs.



```

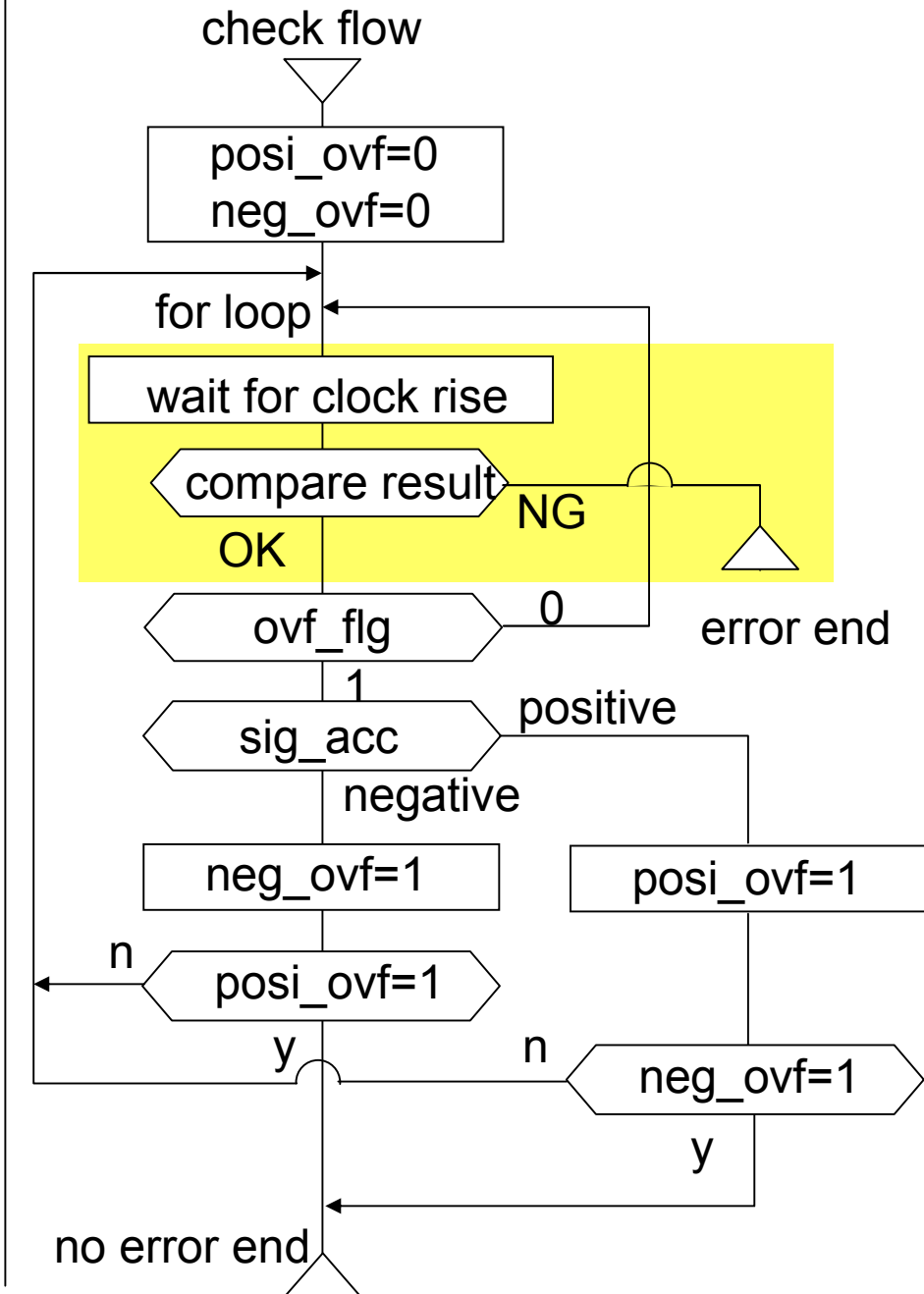task checker ;
begin
  @(posedge clk ) begin
    if ( (sig_acc != mdl_acc ) begin
      $display
        ("error in acc, model=%d, tgt=%d",
          mdl_acc, sig_acc ) ;
      #5 $finish ;
    end
    if ( (ovf_flg != mdl_ovf ) begin
      $display
        ("error in ovf_flg, model=%b, tgt=%b",
          mdl_ovf, ovf_flg ) ;
      #5 $finish ;
    end
    if ( (ovr_mx != mdl_mx ) begin
      $display
        ("error ovr_mx, model=%b, tgt=%b",
          mdl_mx, ovr_mx ) ;
      #5 $finish ;
    end
  end
endtask
  
```



```


initial begin
reg posi_ovf, neg_ovf ;
integer k;
posi_ovf = 0 ;
neg_ovf = 0 ;
for ( k = 0; k <= MX_T; k=k+1 ) begin
  checker ; //compare target and golden
  if ( ovf_flg ) begin
    if ( sig_acc > 0 ) begin
      posi_ovf = 1 ;
    end
    else begin
      neg_ovf = 1 ;
    end
  end
  if ( posi_ovf & neg_ovf ) begin
    $display ( "test OK" ) ;
    #5 $finish ;
  end
end
$display("test not complete in %d cycle",
        MX_T );
end
  
```


```

module test_auto_acc_w_fltr ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL * 2 ;
parameter MX_T = 500 ; // max test cycle time
//
parameter IN_BW = 4 ;
defparam acc_w_fltr_01.IN_BW = IN_BW ;
parameter OUT_BW = 5 ;
defparam acc_w_fltr_01.OUT_BW = OUT_BW ;
parameter MX_IN = 5 ;
defparam acc_w_fltr_01.MX_IN = MX_IN ;
//
reg clk, rst_n ;
reg signed [IN_BW-1:0] in_a ;
wire signed [OUT_BW-1:0] sig_acc ;
wire ovr_mx, ovf_flg ;
//
reg signed [OUT_BW-1:0] mdl_acc ; // output of model
reg mdl_ovf, mdl_mx, mdl_run ; // output of model
//
reg posi_ovf, neg_ovf ; // indicator to show what kind of overflow occurred
integer k ; // loop counter
//


```

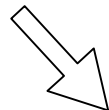
Using smaller bit width 5
for sig_acc than the
specification of Ex. 4-4.






```
initial begin // main root to check result
posi_ovf = 0 ; // first no overflow
neg_ovf = 0 ; // first no overflow
for ( k = 0; k <= MX_T; k=k+1 ) begin // loop to test
    @(posedge clk ) begin
        model_tsk ; // invoke the golden model
        #1 checker ; //compare target and golden
        if ( ovf_flg ) begin
            if ( sig_acc > 0 ) begin
                posi_ovf = 1 ; // set positive to negative overflow
            end
            else begin
                neg_ovf = 1 ; // set negative to positive overflow
            end
        end
    end
    if ( posi_ovf & neg_ovf ) begin // two types of overflow occurred
        $display ( "test OK" ) ;
        #5 $finish ;
    end
end
end
$display("test not complete in %d cycle", // only one or no overflow occurred
        MX_T );
end
```

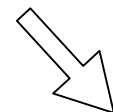



```
task checker ; // compare simulation result with golden model
begin
  if ( sig_acc != mdl_acc ) begin
    $display
      ("error in acc, model=%d, tgt=%d",
        mdl_acc, sig_acc ) ;
    #5 $finish ;
  end
  if ( ovf_flg != mdl_ovf ) begin
    $display
      ("error in ovf_flg, model=%b, tgt=%b",
        mdl_ovf, ovf_flg ) ;
    #5 $finish ;
  end
  if ( ovr_mx != mdl_mx ) begin
    $display
      ("error ovr_mx, model=%b, tgt=%b",
        mdl_mx, ovr_mx ) ;
    #5 $finish ;
  end
end
end
endtask
```



```

task model_tsk; // golden model of the target module
reg signed [OUT_BW-1:0] next_acc ;
begin
  if( rst_n == 1'b0 ) begin
    mdl_acc = 0 ;
    mdl_ovf = 0 ;
    mdl_mx = 0 ;
    mdl_run = 0 ;
  end
  else begin
    next_acc = mdl_acc + in_a ;
    mdl_ovf = ( (in_a >= 0) & ( mdl_acc >= 0 ) & ( next_acc < 0 ) ) |
              ( ( in_a < 0 ) & ( mdl_acc < 0 ) & ( next_acc >= 0 ) ) ;
    if ( mdl_run ) begin
      mdl_mx = ( ( in_a > MX_IN ) | ( in_a < -MX_IN ) ) ?
                1 : 0;
      mdl_acc = (mdl_ovf | mdl_mx )? mdl_acc : mdl_acc + in_a ;
    end
    else begin mdl_run = 1 ; end
  end
  // $strobe("t=%d, run=%b, in_a=%d, acc=%d, mx=%b, ovf=%b",
  //         $stime, mdl_run, in_a, mdl_acc, mdl_mx, mdl_ovf ); // for debug
end
endtask

```

Important

If we use $(mdl_acc + in_a) < 0$ instead of $next_acc < 0$, overflow is not detected correctly. Because 0 is 32-bit, therefore $mdl_acc + in_a$ is calculated after both operand are extended to 32-bit. Overflow will not occur for such large bit size. We are adding at most 8-bit values.

```

always begin @ ( negedge clk ) ;
    in_a = ($random % 8) ; // in_a is from -7 to 7
end
always begin
    clk = 0; #HF_CYCL;
    clk = 1; #HF_CYCL;
end
initial begin
    rst_n = 0 ;
    #(CYCL*5) rst_n = 1 ;
end
// connection to target module
acc_w_fltr  acc_w_fltr_01 ( .clk(clk), .rst_n(rst_n),
                           .in_a(in_a), .sig_acc(sig_acc),
                           .ovr_mx(ovr_mx), .ovf_flg(ovf_flg) ) ;
//always @( posedge clk ) begin // for debug
//$strobe("t=%d, rst=%b, in_a=%d, acc=%d, mx=%b, ovf=%b",
//      $stime, rst_n, in_a, sig_acc, ovr_mx, ovf_flg );
//end
endmodule
`include "acc_w_fltr.v"

```

file name: test_auto_acc_w_fltr.v

A part of a sample result:

This simulation is done with \$strobe
system task active in model_tsk.

The golden
model's
output

```

t=      185, run=1, in_a= 5, acc= 14, mx=0, ovf=0
t=      185, rst=1, in_a= 5, acc= 14, mx=0, ovf=0
t=      195, run=1, in_a= -1, acc= 13, mx=0, ovf=0
t=      195, rst=1, in_a= -1, acc= 13, mx=0, ovf=0
t=      205, run=1, in_a= -6, acc= 13, mx=1, ovf=0
t=      205, rst=1, in_a= -6, acc= 13, mx=1, ovf=0
t=      215, run=1, in_a= 7, acc= 13, mx=1, ovf=1
t=      215, rst=1, in_a= 7, acc= 13, mx=1, ovf=1
t=      225, run=1, in_a= 2, acc= 15, mx=0, ovf=0
t=      225, rst=1, in_a= 2, acc= 15, mx=0, ovf=0
t=      235, run=1, in_a= -2, acc= 13, mx=0, ovf=0

```

The target
model's
output

```


      ⋮
t=      395, rst=1, in_a= -5, acc=-14, mx=0, ovf=0
t=      405, run=1, in_a= 3, acc=-11, mx=0, ovf=0
t=      405, rst=1, in_a= 3, acc=-11, mx=0, ovf=0
t=      415, run=1, in_a= -3, acc=-14, mx=0, ovf=0
t=      415, rst=1, in_a= -3, acc=-14, mx=0, ovf=0
t=      425, run=1, in_a= -6, acc=-14, mx=1, ovf=1
t=      425, rst=1, in_a= -6, acc=-14, mx=1, ovf=1

```

test OK


Halted at location **test_auto_acc_w_filtr.v(48) time

Ex 4-6. Serial bit pattern detector: Write a module which receives 1-bit data `sirl_in` at every clock rise time and check if the received bit pattern becomes `8'b1111_1010` or `8'b1100_0011`, MSB correspond to older bit and LSB corresponds to the newest bit received. If `8'b1111_1010` received then place 1 to an 1-bit output signal `vld_flg` until `8'b1100_0011` received. If `8'b1100_0011` received then place 0 to `vld_flg`. Apply a synchronous reset signal `rst` to the module and reset `vld_flg` to 0 when `rst` asserted.


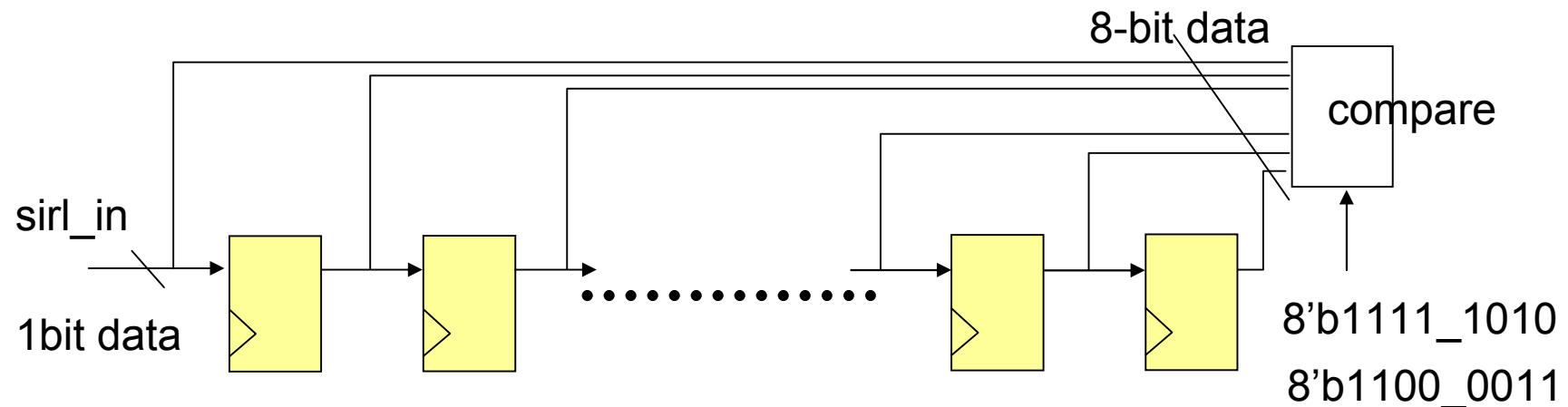



The module have to memorize 8 bits serial input bit string and compare it to `8'b1111_1010` and `8'b1100_0011`. Use shift register to memorize serially given 8-bit data.

The whole module must look like below.

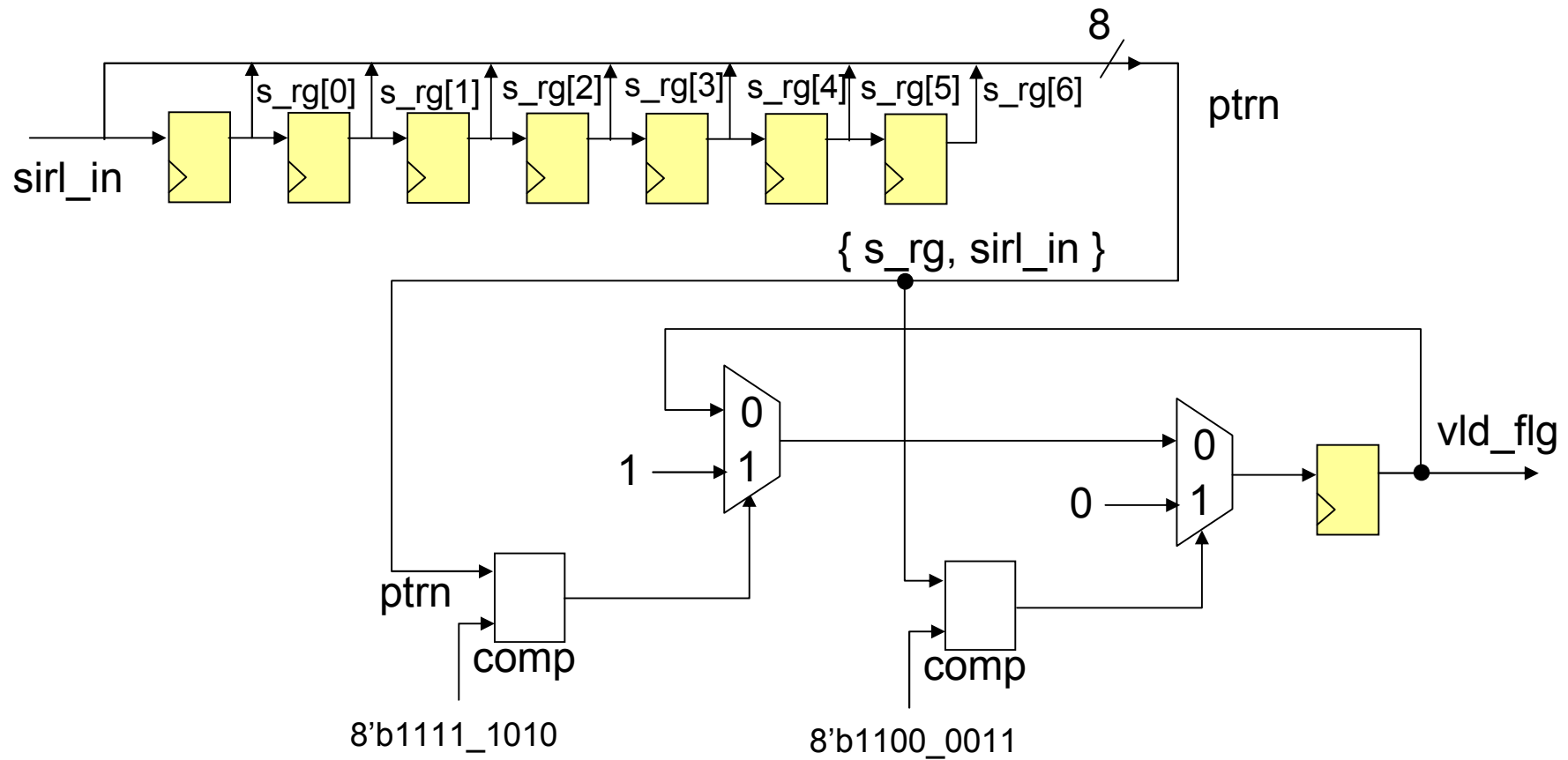


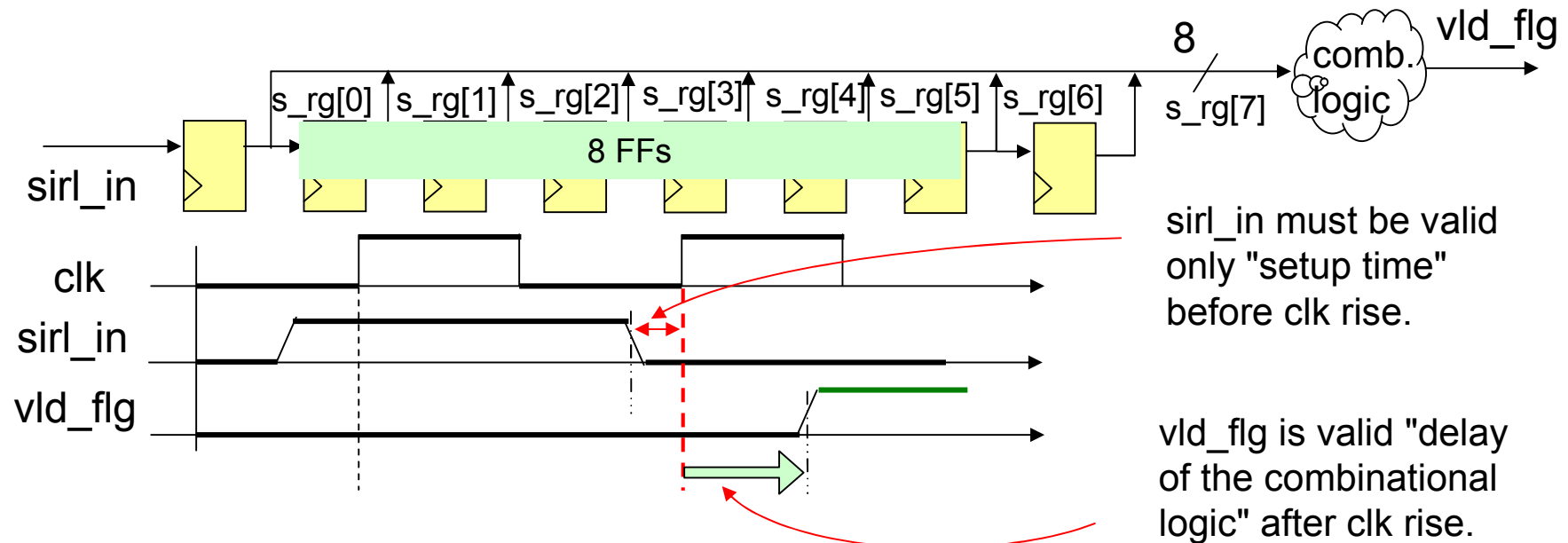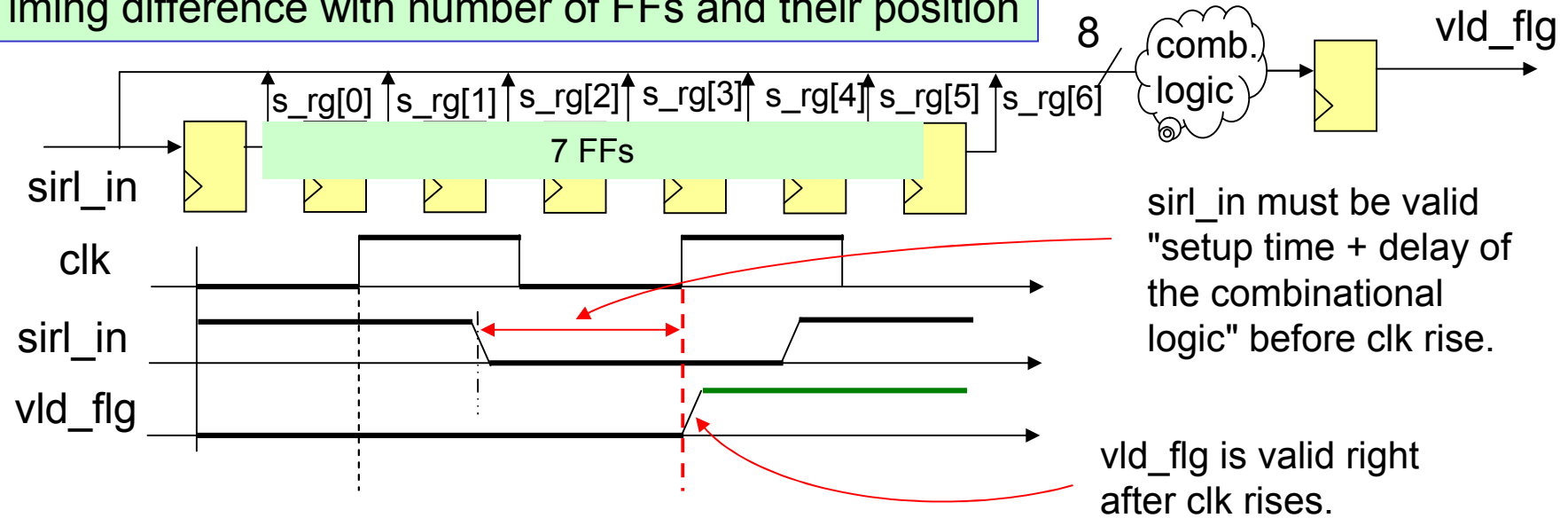Timing difference with number of FFs and their position



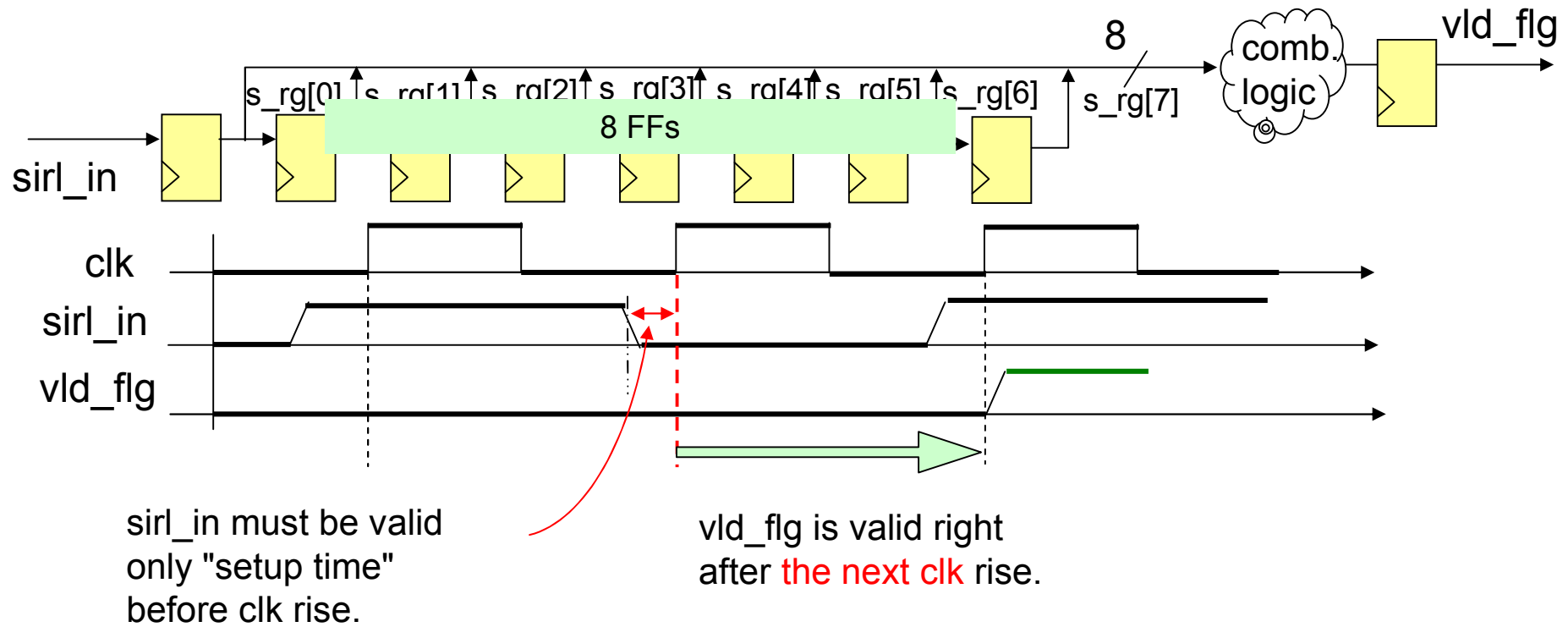

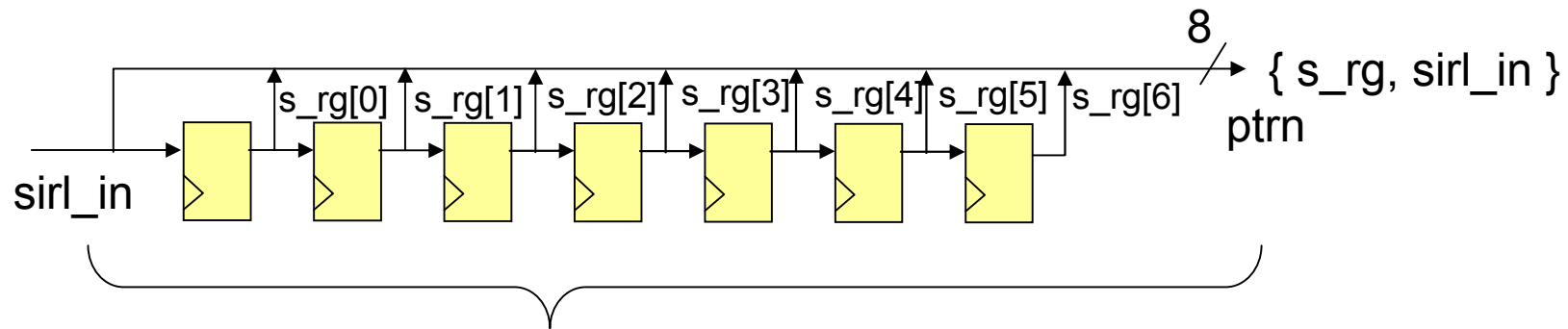
Shift register part can be written as below.



```
assign ptrn = { s_rg, sirl_in } ;
```

```
always @ ( posedge clk ) begin
  if ( rst == 1'b1 ) begin
    s_rg[6:0] <= 0 ;
  end
  else begin
    s_rg[0] <= sirl_in ;
    s_rg[1] <= s_rg[0] ;
    s_rg[2] <= s_rg[1] ;
    s_rg[3] <= s_rg[2] ;
    s_rg[4] <= s_rg[3] ;
    s_rg[5] <= s_rg[4] ;
    s_rg[6] <= s_rg[5] ;
  end
end
```

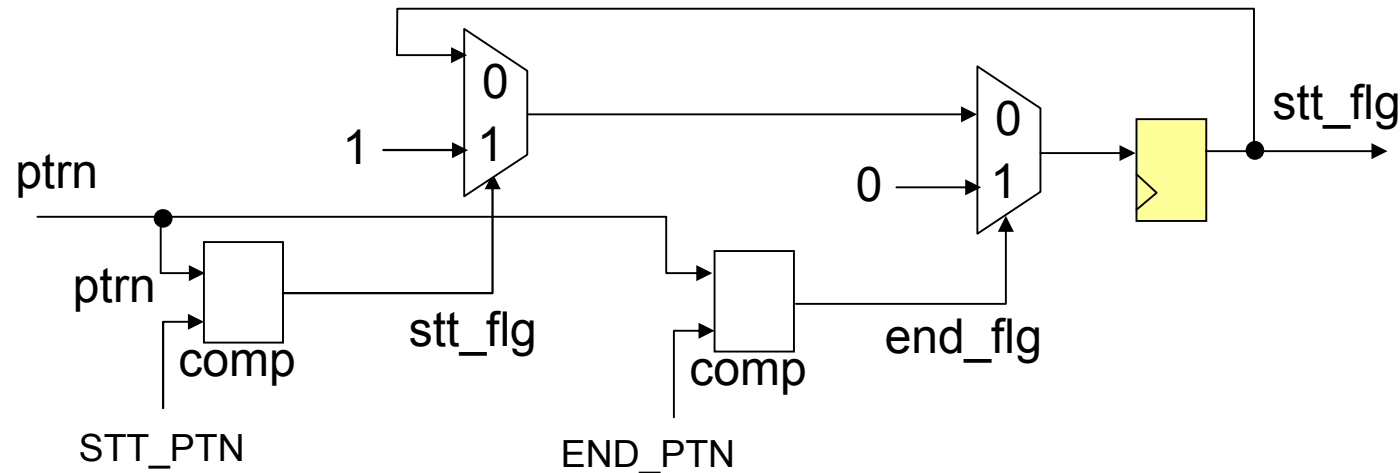Pattern checking and flag setting part can be written as below.



```
assign stt_flg = (ptrn == STT_PTN);
assign end_flg = (ptrn == END_PTN);
```

```
always @ ( ptrn or stt_flg ) begin
    if ( stt_flg ) begin
        next_vld_flg = 1 ;
    end
    else begin
        if ( end_flg ) begin
            next_vld_flg = 0 ;
        end
        else begin
            next_vld_flg = stt_flg ;
        end
    end
end
end
```

```
always @ ( posedge clk ) begin
    if ( rst == 1'b1 ) begin
        vld_flg <= 0 ;
    end
    else begin
        vld_flg <= next_vld_flg ;
    end
end
```


Coding example.

```

module bit_ptrn_chk ( clk, rst, sirl_in, vld_flg ) ;
parameter STT_PTN = 8'b1111_1010 ; // hex fa
parameter END_PTN = 8'b1100_0011 ; // hex c3
input clk ;
input rst ;
input sirl_in ;
output vld_flg ;
wire clk ;
wire rst ;
wire sirl_in ;
reg vld_flg ; // FF
reg next_vld_flg ; // non-FF
wire [7:0] ptrn ;
reg [6:0] s_rg ; // FF, shift register
reg [6:0] next_s_rg ; // non-FF
wire stt_flg ;
wire end_flg ;

assign ptrn = { s_rg, sirl_in } ;
assign stt_flg = (ptrn == STT_PTN);
assign end_flg = (ptrn == END_PTN);


```

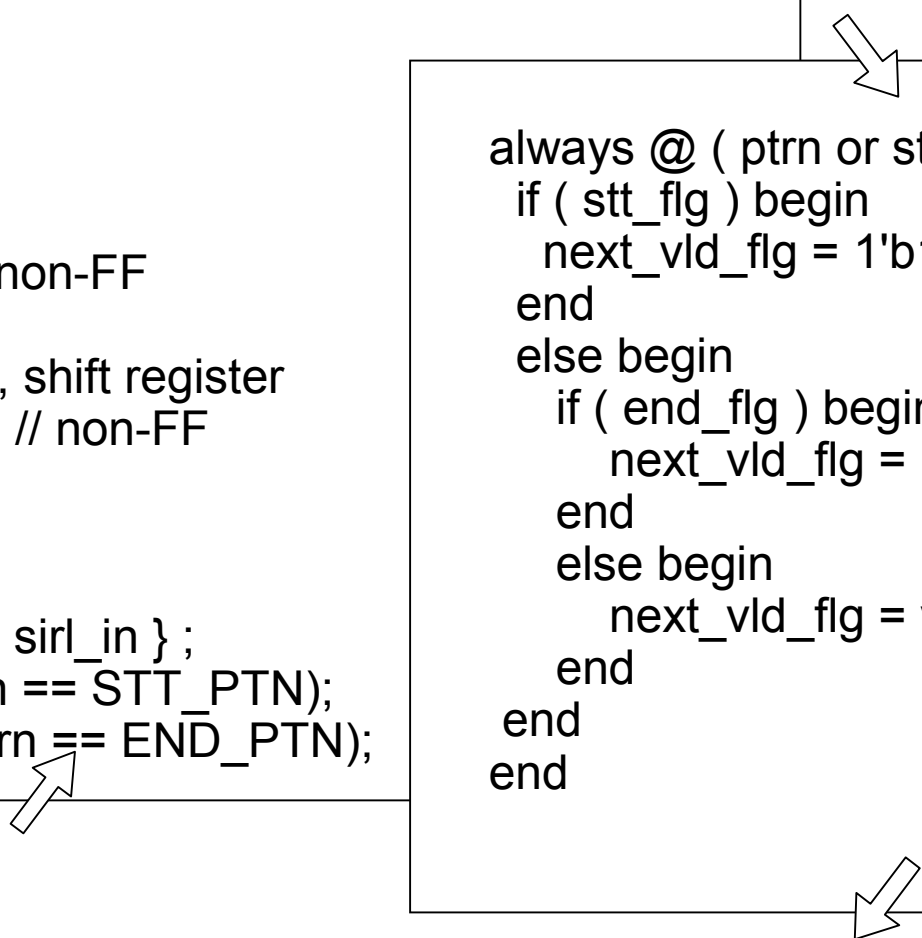

```

always @ ( ptrn or stt_flg ) begin
  if ( stt_flg ) begin
    next_vld_flg = 1'b1 ;
  end
  else begin
    if ( end_flg ) begin
      next_vld_flg = 1'b0 ;
    end
    else begin
      next_vld_flg = vld_flg ;
    end
  end
end
end

```

```
always @ ( posedge clk ) begin
  if ( rst == 1'b1 ) begin
    s_rg[6:0] <= 7'b0000_000 ;
  end
  else begin
    s_rg[0] <= sirl_in ;
    s_rg[1] <= s_rg[0] ;
    s_rg[2] <= s_rg[1] ;
    s_rg[3] <= s_rg[2] ;
    s_rg[4] <= s_rg[3] ;
    s_rg[5] <= s_rg[4] ;
    s_rg[6] <= s_rg[5] ;
  end
end
always @ ( posedge clk ) begin
  if ( rst == 1'b1 ) begin
    vld_flg <= 1'b0 ;
  end
  else begin
    vld_flg <= next_vld_flg ;
  end
end
endmodule
```

Coding example.

file name: bit_ptrn_chk.v

It is tedious to assign serial bit date by using initial construct shown below left. Therefore prepare parallel to serial conversion task and use it to generate 32-bit length serial data from 32-bit parallel data.

```
initial begin
```

```
    sirl_in = 1 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 0 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 0 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 0 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 0 ;
```

```
    # CYCL sirl_in = 1 ;
```

```
    # CYCL sirl_in = 0 ;
```

```
    ,,, ,,,
```

```
    ,,,
```

```
end
```

```
initial
```

```
    para_sirl( 32'b1101011011010,,, ) ;
```

```
    para_sirl( 32'b011100,,, ) ;
```

```
    ,,,
```

```
end
```

```
task para_sirl ;
```

```
input [31:0] para_in ;
```

```
integer k ;
```

```
begin
```

```
for ( k=0 ; k<32 ; k = k + 1 ) begin
```


```
    sirl_in = para_in[31-k] ;
```

```
    @ (negedge clk ) ;
```

```
end
```

```
end
```

```
endtask
```

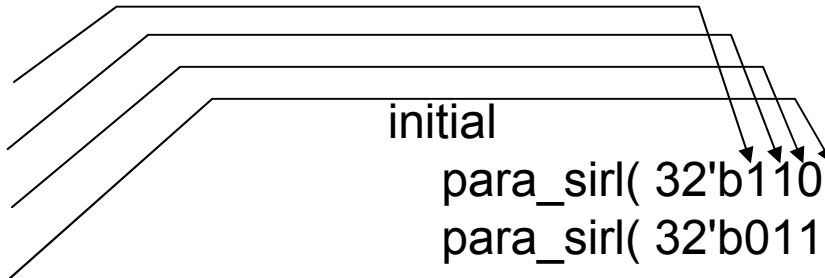


Coding example of a test bench.

```

`timescale 1ns/100ps
module test_bit_ptrn_chk ;
parameter HF_CYCL = 50 ;
parameter CYCL = HF_CYCL * 2 ;
reg clk, rst ; // non-FF
reg sirl_in ; // non-FF
wire flg ;
bit_ptrn_chk bit_ptrn_chk_01(
    .clk(clk), .rst(rst),
    .sirl_in(sirl_in), .vld_flg(flq) ) ;
initial begin
    rst = 1'b1 ;
    #(CYCL*2) rst = 1'b0 ;
    #(CYCL*12) rst = 1'b1 ;
    #CYCL rst = 1'b0 ;
    #(CYCL*60) rst = 1'b1 ;
    #CYCL rst = 1'b0 ;
    #(CYCL*10) $finish ;
end
always begin
    clk = 0 ; #HF_CYCL ;
    clk = 1 ; #HF_CYCL ;
end

```



```

initial begin
    para_sirl (32'hffaf_fa0c ) ;
    para_sirl (32'h3faf_ac3f ) ;
    para_sirl (32'hc3af_ac33 ) ;
end

task para_sirl ;
input [31:0] para_in ;
integer k ;
begin
    for ( k=0 ; k<32 ; k = k + 1 ) begin
        sirl_in = para_in[31-k] ;
        @ (negedge clk ) ;
    end
end
endtask

always @ ( posedge clk ) begin
    $strobe(
        "t=%d,rst=%b, sirl_in=%d, flg=%b",
        $stime, rst, sirl_in, flg ) ;
end
endmodule


```

file name: test_bit_ptrn_chk.v

Ex 4-7. Data change range checker: Write a module which receives 8-bit input `in_a` at every clock rise time and if a received data is different from the previously received data more than 50, then output 1 on a 1-bit output signal `dif_flg`, else output 0. When only one data is received after reset asserted, then assume 0 was received previously.

Assume `in_a` is signed and use Verilog2001 specification.

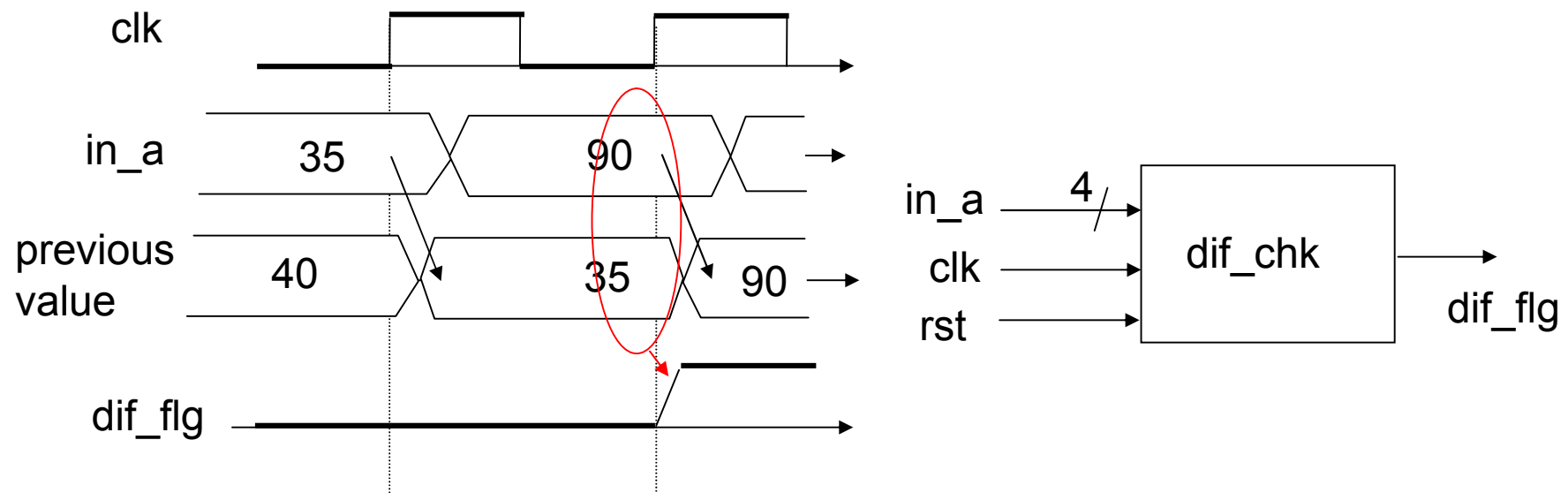
Apply an asynchronous reset `rst_n`, active low, to initialize the module. `dif_flg` must be set 0 on reset. The output `dif_flg` must come out directly from a flip-flop.




To compare current input with the previous input, we must memorize it in an 8-bit flip-flop. To handle signed signal, we have to use “signed” keyword introduced in Verilog2001.


The target logic can be structured in a several ways as shown below if there is no specification about how to use FFs. This exercise says that we have to use the diagram shown on the middle right.

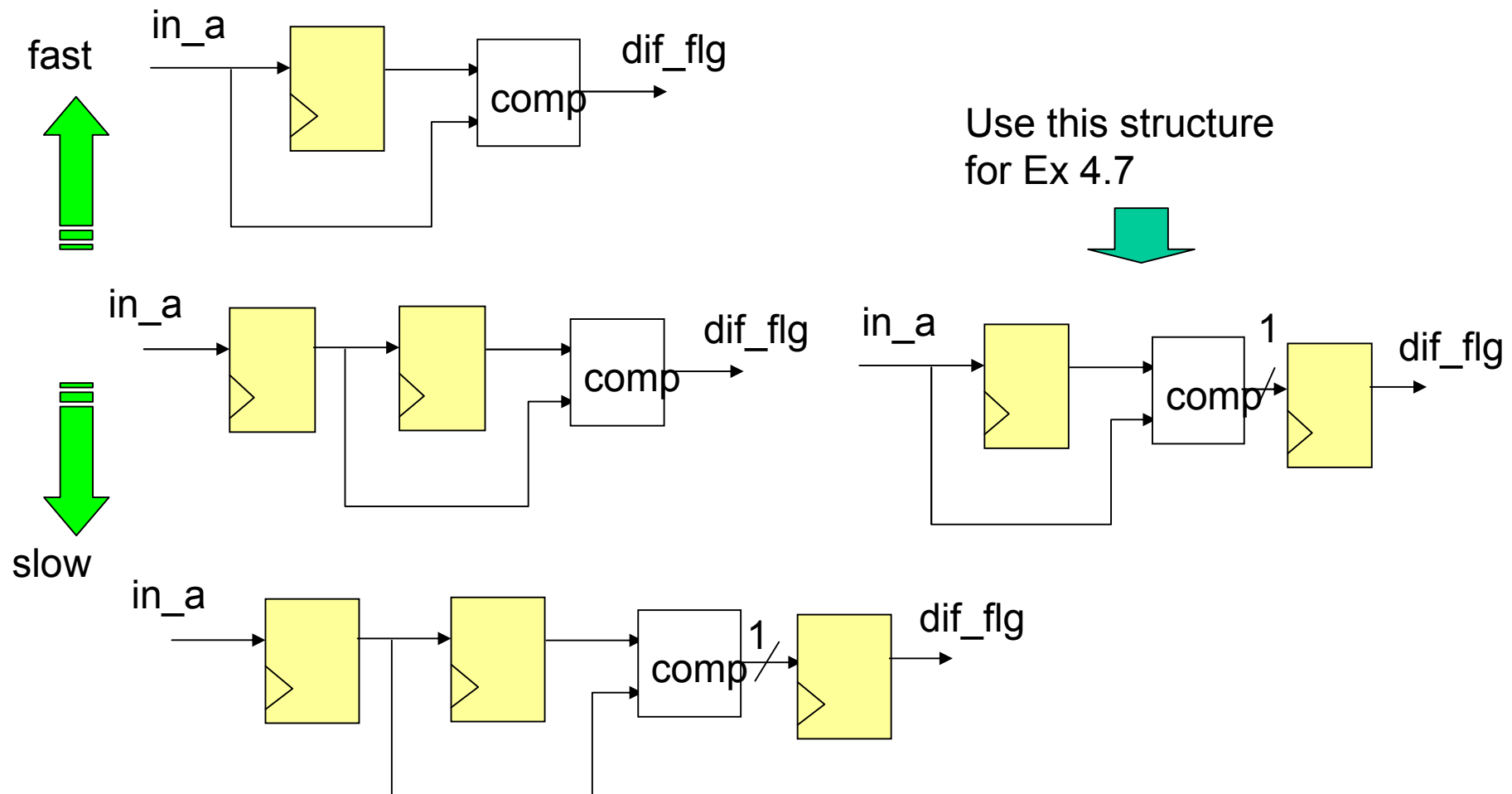
The configurations below have basically similar functionalities, but each of them has different timing issues. In general adding one FF result in one cycle delay.



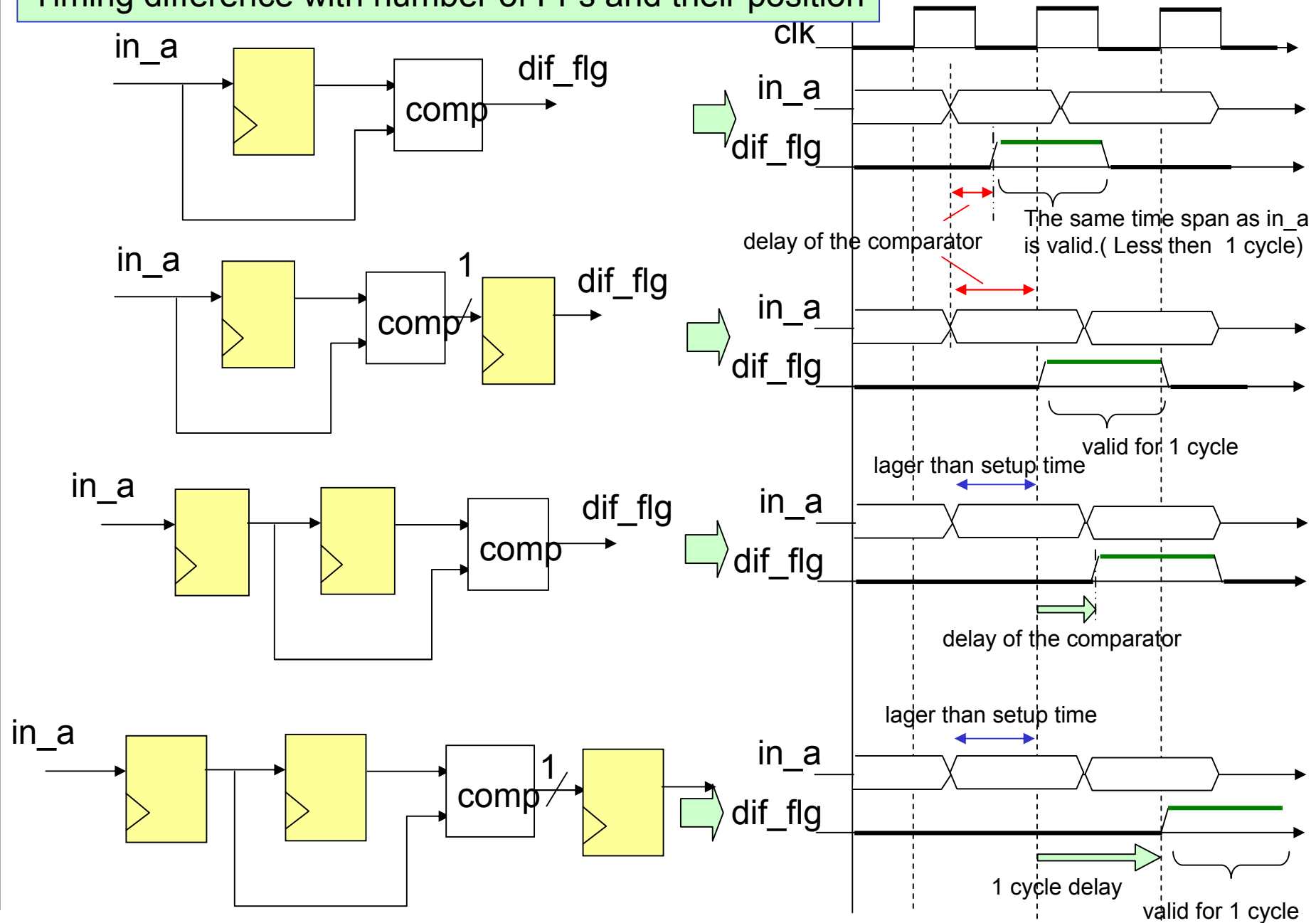Timing difference with number of FFs and their position



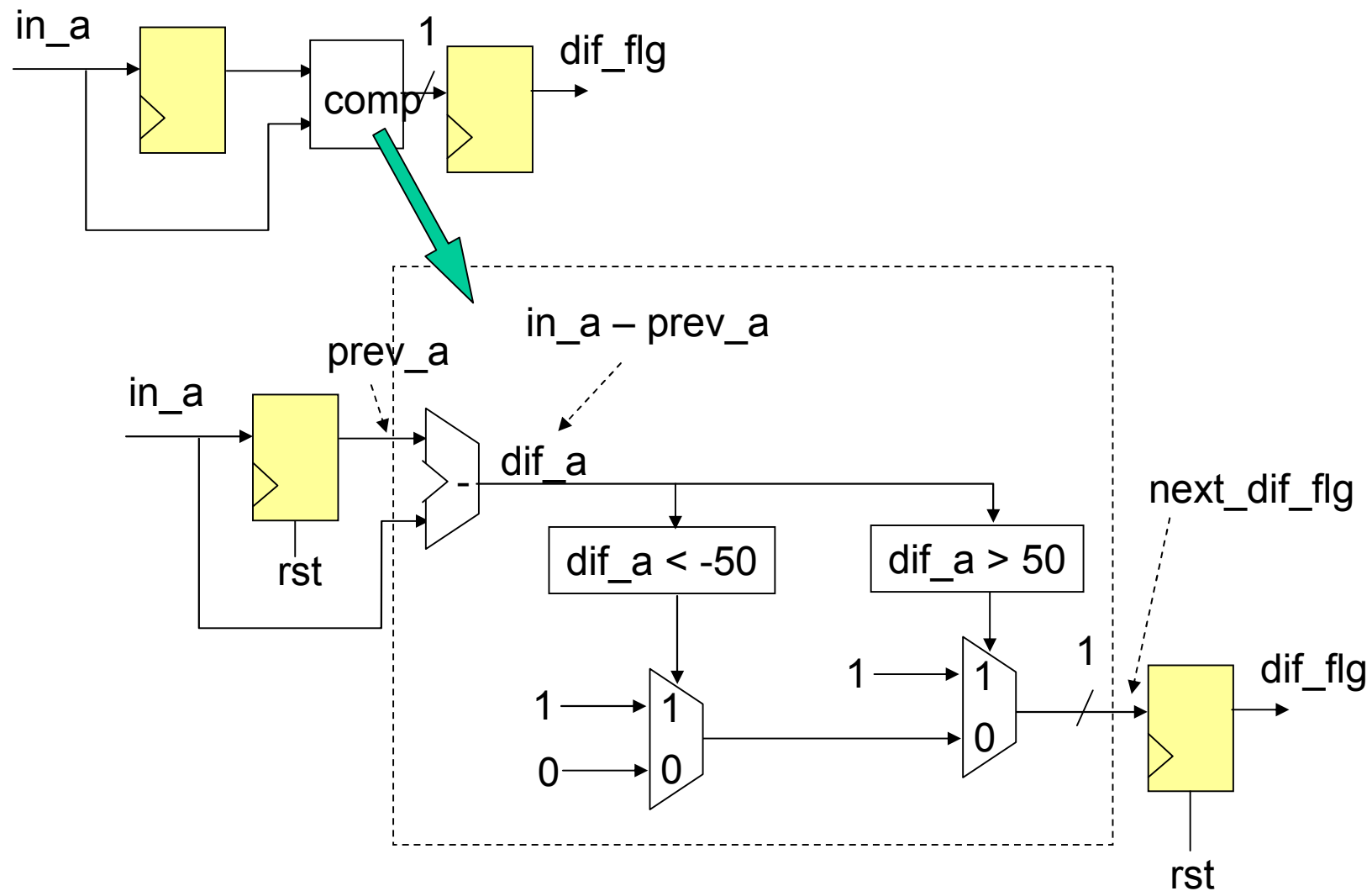

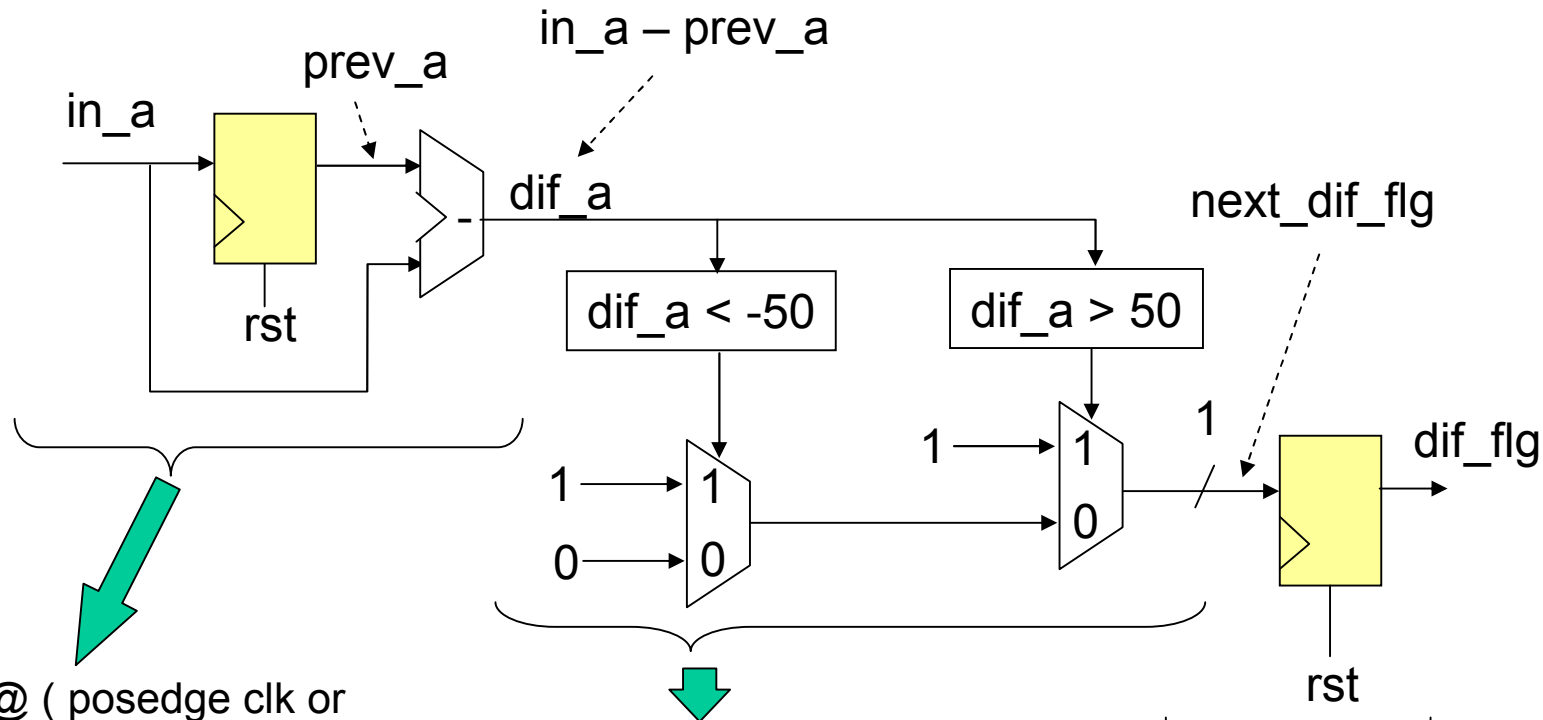

```

always @ ( posedge clk or
           posedge rst) begin
  if ( rst == 1'b1 ) begin
    prev_a <= 0 ;
  end
  else begin
    prev_a <= next_prev_a ;
  end
end
assign next_prev_a = in_a ;
assign dif_a = in_a - prev_a ;

```

```

always @ ( dif_a ) begin
  if ( dif_a > LIMIT ) begin
    next_dif_flg = 1'b1 ;
  end
  else begin
    if ( dif_a < -LIMIT ) begin
      next_dif_flg = 1'b1 ;
    end
    else begin
      next_dif_flg = 1'b0 ;
    end
  end
end
end

```

```

always @ ( posedge clk
           or posedge rst) begin
  if ( rst == 1'b1 ) begin
    dif_flg <= 0 ;
  end
  else begin
    dif_flg <= next_dif_flg ;
  end
end

```


Coding example.


```

module dif_chk( clk, rst, in_a, dif_flg ) ;
parameter A_BW=8 ;
parameter DIF_LMT = 50 ;
input clk ;
input rst ;
input signed [A_BW-1:0] in_a ;
output dif_flg ;
wire clk ;
wire rst ;
wire signed [A_BW-1:0] in_a ;
reg dif_flg ; //FF

reg next_dif_flg ; // non-FF
reg signed [A_BW-1:0] prev_a ; // FF
wire signed [A_BW-1:0] next_prev_a ;
wire signed [A_BW-1:0] dif_a ;

always @ ( posedge clk or
            posedge rst) begin
    if ( rst == 1'b1 ) begin
        prev_a <= {A_BW{1'b0}} ;
    end
    else begin
        prev_a <= next_prev_a ;
    end
end
end

```



```

assign next_prev_a = in_a ;
assign dif_a = in_a - prev_a ;

```

```

always @ ( posedge clk or
            posedge rst) begin
    if ( rst == 1'b1 ) begin
        dif_flg <= 1'b0 ;
    end
    else begin
        dif_flg <= next_dif_flg ;
    end
end

always @ ( dif_a ) begin
    if ( dif_a > DIF_LMT ) begin
        next_dif_flg = 1'b1 ;
    end
    else begin
        next_dif_flg = ( dif_a < -DIF_LMT)?
                        1'b1 : 1'b0 ;
    end
end
end
endmodule

```



file name: dif_chk.v


Coding example of a test bench.

```

module test_dif_chk ;
parameter A_BW=8 ;
parameter HF_CYCL = 50 ;
parameter CYCL= HF_CYCL * 2 ;
reg clk, rst ; // non-FF
reg signed [A_BW-1:0] in_a ; // non-FF
wire dif_flg ;

dif_chk dif_chk_01( .clk(clk), .rst(rst),
                    .in_a(in_a), .dif_flg(dif_flg) ) ;
initial begin
  rst = 1'b1 ;
  #(CYCL*2) rst = 1'b0 ;
  #(CYCL*2) rst = 1'b1 ;
  #CYCL rst = 1'b0 ;
end
always begin
  clk = 0 ; #HF_CYCL ;
  clk = 1 ; #HF_CYCL ;
end

```



```


initial begin
  in_a = 20 ;
  #CYCL in_a = 100 ;
  #CYCL in_a = 30 ;
  #CYCL in_a = 80 ;
  #CYCL in_a = 29 ;
  #CYCL in_a = -21 ;
  #CYCL in_a = -72 ;
  #CYCL in_a = 0 ;
  #CYCL in_a = 44 ;
  #CYCL in_a = 80 ;
  #CYCL in_a = 119 ;
  #CYCL $finish ;
end
always @ ( posedge clk ) begin
  $strobe(
    "t=%d,rst=%b, in_a=%d, dif_flg=%b",
    $stime, rst, in_a, dif_flg ) ;
end
endmodule

```




file name: test_dif_chk.v

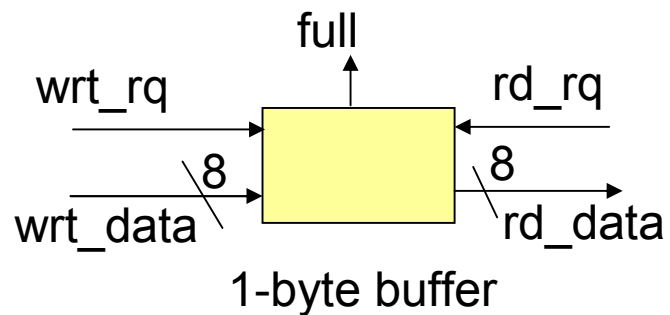Ex 4-8. One byte data buffer: Write a module of 1-byte buffer of which behavior is shown in the wave form below. Read and write operations are synchronized with one clock signal named clk. Use active low asynchronous reset.




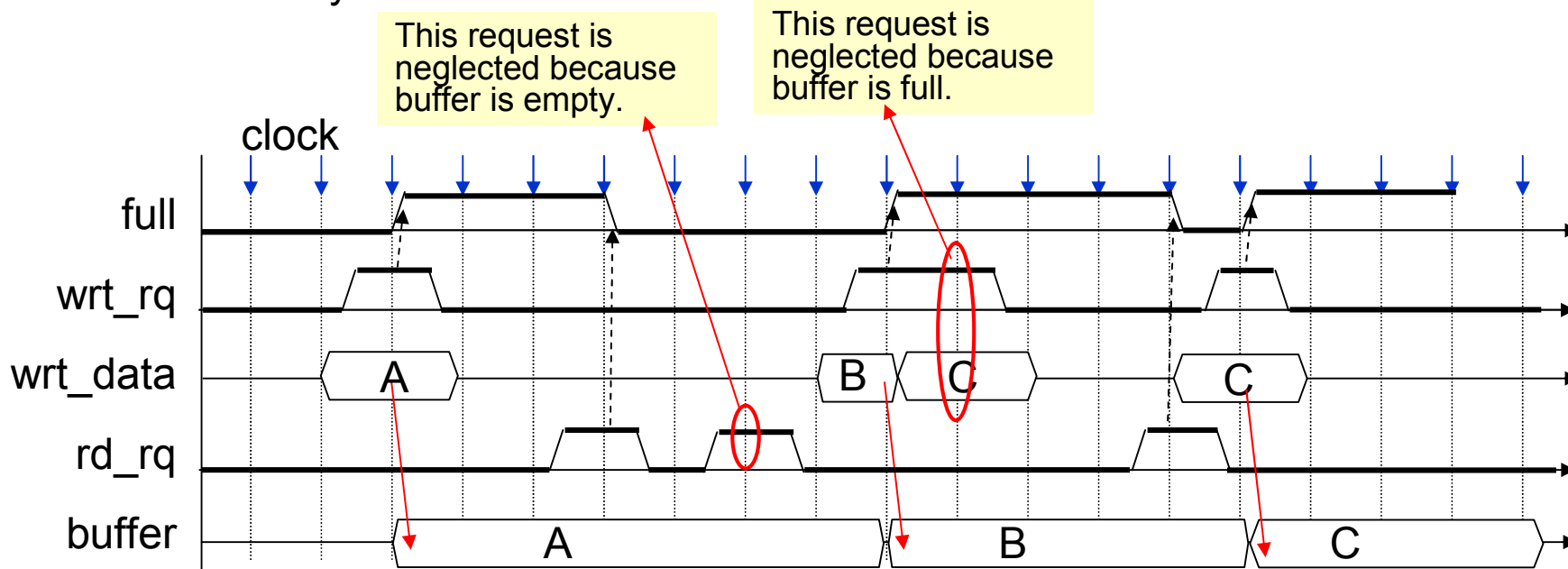If both `rd_rq` and `wrt_rq` are asserted while buffer is empty, neglect `rd_rq` and accept `wrt_rq`. If both `rd_rq` and `wrt_rq` are asserted while buffer is full, neglect `wrt_rq` and accept `rd_rq`.



There is only one buffer for simplicity.

Explanation about the specification.

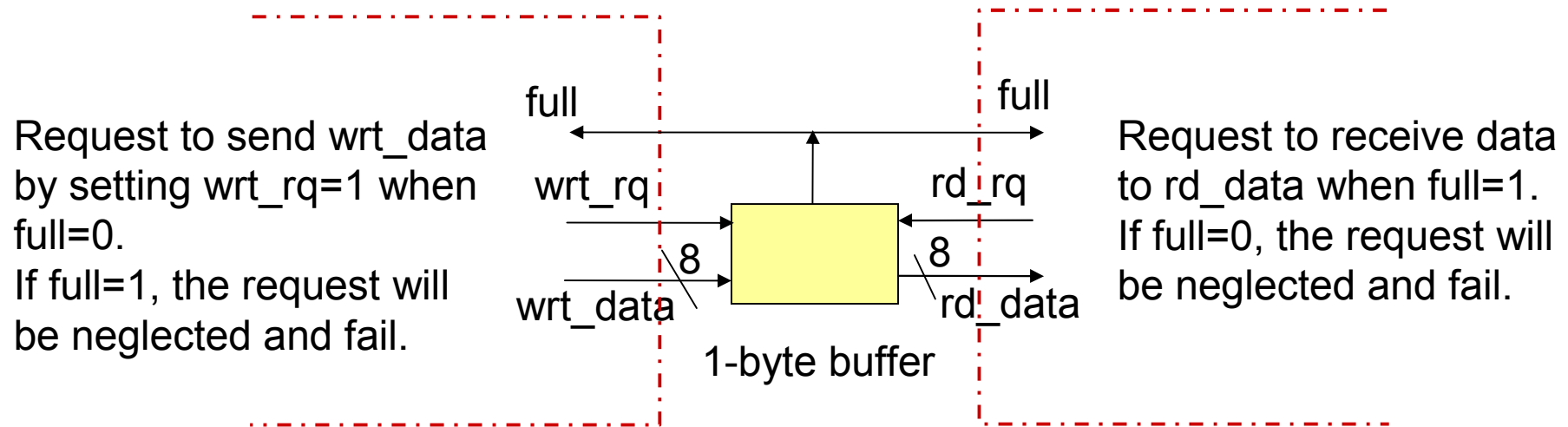


For simplicity, connect rd_data to buffer itself. This means that there is always some data on rd_data signal, but it is meaningful only when full=1.

A state transition table


rst_n	wrt_rq	rd_rq	B_EMPT	B_FUL
0	—	—	⇒ B_EMPT	⇒ B_EMPT
1	0	0	no operation	no operation
	1	0	wrt_data → d_buffr ⇒ B_FUL	no operation
	0	1	no operation	⇒ B_EMPT
	1	1	wrt_data → d_buffr ⇒ B_FUL	⇒ B_EMPT

There is no operation, d_buffr → rd_data, because it is done always as on the right figure.

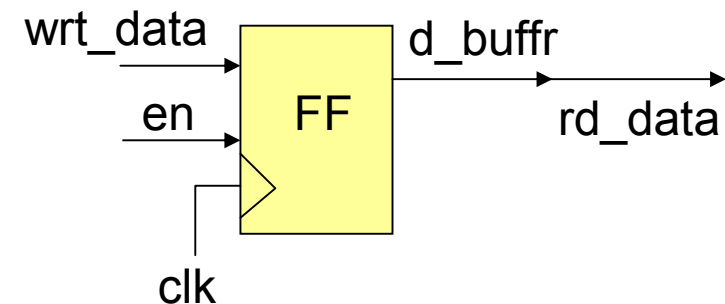Write operation to d_buffr is activated by setting enable signal of FF to 1.



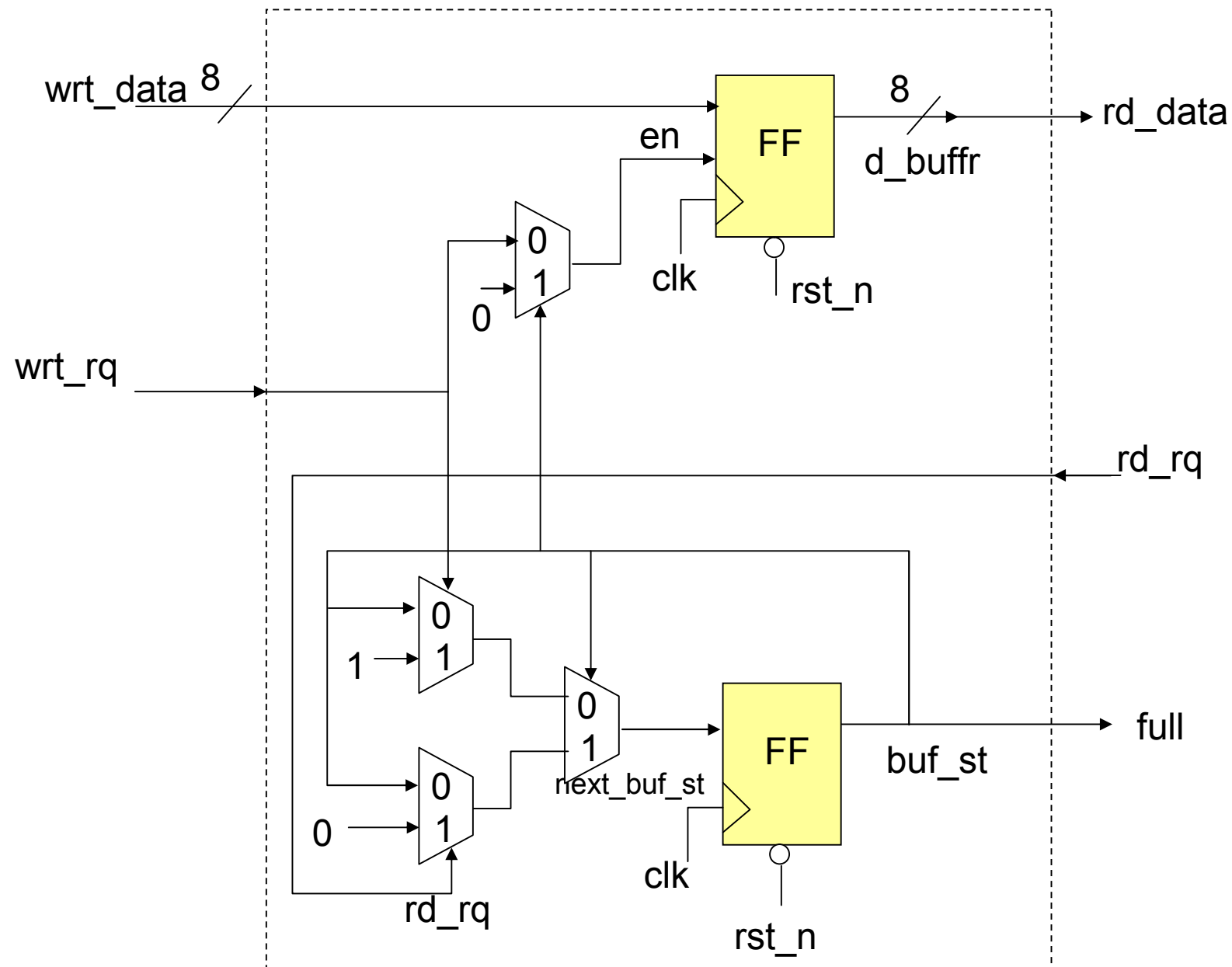
⇒ By introducing en, the table can be updated.



Final state transition table

rst_n	wrt_rq	rd_rq	B_EMPT	B_FUL
0	—	—	en=0 ⇒ B_EMPT	en=0 ⇒ B_EMPT
1	0	0	en=0	en=0
	1	0	en=1 ⇒ B_FUL	en=0
	0	1	en=0	en=0 ⇒ B_EMPT
	1	1	en=1 ⇒ B_FUL	en=0 ⇒ B_EMPT

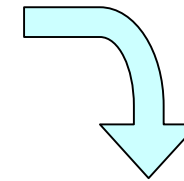The total module is shown on the next page.



This table can be mapped into RTL code as below.

```

case ( buf_st )
  B_EMPT : begin
    en = ( wrt_rq )? 1 : 0 ;
  end
  B_FUL : begin
    en = 0 ;
  end
endcase

case ( buf_st )
  B_EMPT : begin
    next_buf_st = ( wrt_rq )?
                  B_FUL : buf_st ;
  end
  B_FUL : begin
    next_buf_st = ( rd_rq )?
                  B_EMPT : buf_st ;
  end
endcase

```

```
module one_byte_buffr ( clk, rst_n, wrt_rq, wrt_data,
                      rd_rq, full, rd_data ) ;
```

```
parameter N_BW = 8 ;
parameter B_EMPT = 1'b0 ;
parameter B_FUL = 1'b1 ;
```

```
input clk, rst_n ;
input wrt_rq ;
input [N_BW-1:0] wrt_data ;
input rd_rq ;
```

```
output full ;
output [N_BW-1:0] rd_data ;
```


```
wire clk, rst_n ;
wire wrt_rq ;
wire [N_BW-1:0] wrt_data ;
wire rd_rq ;
```

```
reg buf_st ; // state FF
reg next_buf_st ; // non-FF
reg [N_BW-1:0] d_buffr ; // buffer FF
reg en ; // non-FF, enable for buffer FF
```

```
wire full = ( buf_st == B_FUL ) ;
wire [N_BW-1:0] rd_data = d_buffr ;
```

```
always @ ( posedge clk or
           negedge rst_n ) begin
    if ( rst_n==1'b0 ) begin
        buf_st <= B_EMPT ;
    end

    else begin
        buf_st <= next_buf_st ;
        if ( en ) begin
            d_buffr <= wrt_data ;
        end
    end
end
```

```

always @ ( buf_st or wrt_rq or rd_rq ) begin
    case ( buf_st )
        B_EMPT : begin
            en = ( wrt_rq )? 1'b1 : 1'b0 ;
        end
        B_FUL : begin
            en = 1'b0 ;
        end
        default : begin
            en = 1'bx ;
        end
    endcase
end
always @ ( buf_st or wrt_rq or rd_rq ) begin
    case ( buf_st )
        B_EMPT : begin
            next_buf_st = ( wrt_rq )? B_FUL : buf_st ;
        end
        B_FUL : begin
            next_buf_st = ( rd_rq )? B_EMPT : buf_st ;
        end
        default : begin
            next_buf_st = 1'bx ;
        end
    endcase
end
endmodule

```


default is added for debug


default is added for debug

file name: one_byte_buffr.v

Now run the code on the previous page with a test bench below.

```
module test_one_byte_buffr ;
parameter H_CYC = 50 ;
parameter N_BW = 8 ;
reg rst_n, clk ; // non-FF
reg rd_rq, wrt_rq ; // non-FF
reg [N_BW-1:0] wrt_data ; // non-FF
wire [N_BW-1:0] rd_data ;
wire full ;
always begin
    clk = 0 ; #H_CYC ;
    clk = 1 ; #H_CYC ;
end
one_byte_buffr one_byte_buffr_01 ( .clk(clk), .rst_n(rst_n),
    .rd_rq(rd_rq), .wrt_rq(wrt_rq), .wrt_data(wrt_data),
    .full(full), .rd_data(rd_data) ) ;
initial begin
    $monitor(
        "t=%d, rst_n=%b, r_q=%b, w_q=%b, w_d=%h, r_d=%h, full=%b",
        $stime, rst_n, rd_rq, wrt_rq, wrt_data, rd_data, full ) ;
end
```

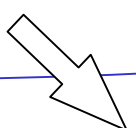

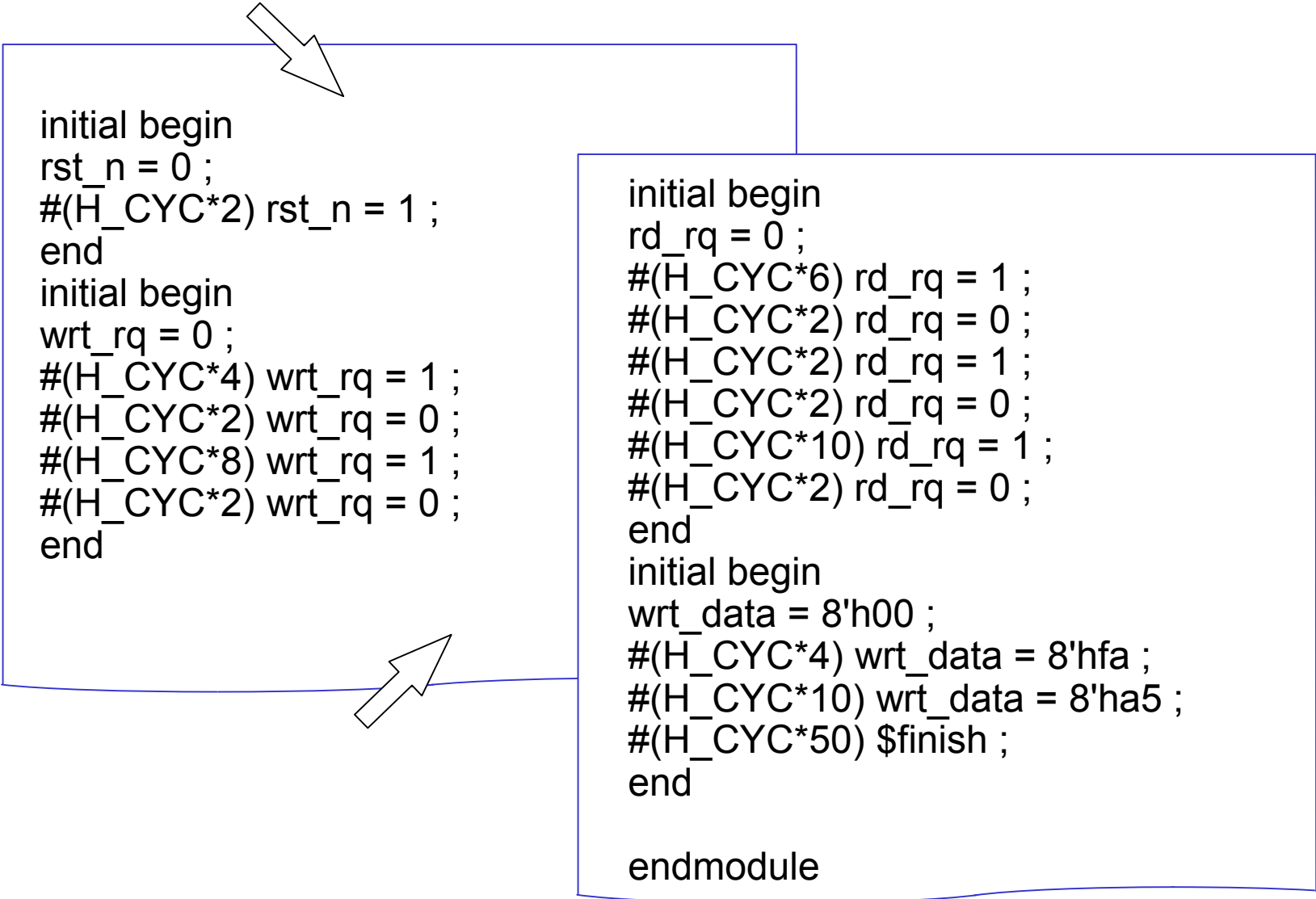

```
initial begin
rst_n = 0 ;
#(H_CYC*2) rst_n = 1 ;
end
initial begin
wrt_rq = 0 ;
#(H_CYC*4) wrt_rq = 1 ;
#(H_CYC*2) wrt_rq = 0 ;
#(H_CYC*8) wrt_rq = 1 ;
#(H_CYC*2) wrt_rq = 0 ;
end
```

```
initial begin
rd_rq = 0 ;
#(H_CYC*6) rd_rq = 1 ;
#(H_CYC*2) rd_rq = 0 ;
#(H_CYC*2) rd_rq = 1 ;
#(H_CYC*2) rd_rq = 0 ;
#(H_CYC*10) rd_rq = 1 ;
#(H_CYC*2) rd_rq = 0 ;
end
initial begin
wrt_data = 8'h00 ;
#(H_CYC*4) wrt_data = 8'hfa ;
#(H_CYC*10) wrt_data = 8'ha5 ;
#(H_CYC*50) $finish ;
end

endmodule
```

file name: test_one_byte_buffr.v

There is different idea for the buffer. The idea explained below is not a recommended way of design. It uses a technique called **asynchronous design**. The following pages are just for explanation. **Never apply the method in actual jog.**


A variable needed to manage empty/full of buffer:

→ full

A variable needed to hold written data:

→ d_bffr

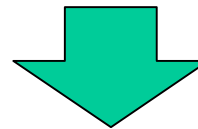Find program logic which can set values on these variables as defined in the specification.



The change of state is invoked by the change of rd_rq or wrt_rq.

Try to write code to realize the given behavior by only using variables such as rd_rq, wrt_rq, full, d_bffr, wrt_data, and rd_data.

```
always @ ( rd_rq or wrt_rq ) begin  
  
end
```

With the above structure, the buffer can be implemented.

```

always @ ( rd_rq or wrt_rq ) begin
  case ( { rd_rq, wrt_rq } )
    2'b00 : begin end // no-operation
    2'b01 : if ( ~full ) begin
              d_bffr = wrt_data ;
              full = 1 ;
            end
    2'b10 : if ( full ) begin
              rd_data = d_bffr ;
              full = 0 ;
            end
    2'b11 : if ( full ) begin
              rd_data = d_bffr ;
              full = 0 ;
            end
            else begin
              d_bffr = wrt_data ;
              full = 1 ;
            end
          endcase
end

```

← rd_req or wrt_rq activate actions.
 ← No change if no request.
 ← If wrt_rq asserted while buffer is empty, update buffer and make state=full.
 ← If rd_rq asserted while buffer is full, set rd_data and make state=empty.
 ← If rd_rq and wrt_rq asserted while buffer is full, neglect wrt_rq and set rd_data and make state=empty.
 ← If rd_rq and wrt_rq asserted while buffer is empty, neglect rd_rq and update buffer and make state=full.

The code on the previous page does not use reset signal.
Reset signal must be implemented as below.

```

always @ ( rd_rq or wrt_rq or rst_n ) begin
    if ( rst_n==1'b0 ) begin
        full = 0 ;
    end
else begin
    case ( { rd_rq, wrt_rq } )
        2'b00 : begin end // no-operation
        2'b01 : if ( ~full ) begin
                    d_bffr = wrt_data ;
                    full = 1 ;
                end
        2'b10 : if ( full ) begin
                    rd_data = d_bffr ;
                    full = 0 ;
                end
        .
        .
        .
    endcase
end

```

Add rst_n.

Add reset processing.

This will result in the following module.


```

module wrong_onebyte_buffr
    ( rst_n, rd_rq, wrt_rq, wrt_data, full, rd_data ) ;
input rst_n, rd_rq, wrt_rq ;
input [7:0] wrt_data ;
output full ;
output [7:0] rd_data ;
wire rst_n, rd_rq, wrt_rq ;
wire [7:0] wrt_data ;
reg full ;
reg [7:0] rd_data ;

reg [7:0] d_bffr ;

always @ ( rd_rq or wrt_rq
            or rst_n ) begin
    if ( rst_n==1'b0 ) full = 0 ;
    else begin

```

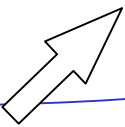


This is a target code which does not use synchronous design.

```

        case ( { rd_rq, wrt_rq } )
            2'b00 : begin end // no-operation
            2'b01 : if ( ~full ) begin
                        d_bffr = wrt_data ;
                        full = 1 ;
                    end
            2'b10 : if ( full ) begin
                        rd_data = d_bffr ;
                        full = 0 ;
                    end
            2'b11 : if ( full ) begin
                        rd_data = d_bffr ;
                        full = 0 ;
                    end
                else begin
                        d_bffr = wrt_data ;
                        full = 1 ;
                    end
        end
    endcase
end
end

endmodule

```

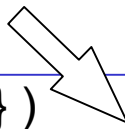

```

module test_wrong_onebyte_buffr ;
reg rst_n ;
reg rd_rq, wrt_rq ;
reg [7:0] wrt_data ;
wire full ;
wire [7:0] rd_data ;
wrong_onebyte_buffr wrong_onebyte_buffr_01 ( .rst_n(rst_n),
    .rd_rq(rd_rq), .wrt_rq(wrt_rq), .wrt_data(wrt_data), .rd_data(rd_data) ) ;
initial $monitor(
    "rst_n=%b, rd_rq=%b, wrt_rq=%b, wrt_data=%h, rd_data=%h, ful=%b",
    rst_n, rd_rq, wrt_rq, wrt_data, rd_data, full ) ;
initial begin
rst_n = 0 ;
rd_rq = 0 ; wrt_rq = 0 ;
#10 rst_n = 1 ;
#10 wrt_rq = 1 ; wrt_data = 8'h5a ;
#10 wrt_rq = 0 ; rd_rq = 1 ;
#10 wrt_rq = 1 ; rd_rq = 0 ; wrt_data = 8'hf0 ;
#10 wrt_rq = 1 ; rd_rq = 0 ; wrt_data = 8'haa ;
#10 wrt_rq = 0 ; rd_rq = 1 ;
#10 rd_rq = 0 ;
#10 $finish ;
end
endmodule

```

Check the code on the previous page by using a test bench in this page.


```

always @ ( rd_rq or wrt_rq or rst_n ) begin
  if ( rst_n==1'b0 ) full = 0 ;
  else begin
    case ( { rd_rq, wrt_rq } )
      2'b00 : begin end // no-operation
      2'b01 : if ( ~full ) begin
                d_bfrr = wrt_data ;
                full = 1 ;
              end
      2'b10 : if ( full ) begin
                rd_data = d_bfrr ;
                full = 0 ;
              end
      2'b11 : if ( full ) begin
                rd_data = d_bfrr ;
                full = 0 ;
              end
            else begin
                d_bfrr = wrt_data ;
                full = 1 ;
            end
          endcase
        end
      end
    end
  end
end

```

A simulation result may look correct, but the code has serious problem.

No edge signal written, therefore combinational logic or latch may be created by this always construct.

No assignment to b_full, d_bfrr, rd_data in this path.



No assignment to rd_data in this path.

No assignment to d_bfrr in this path.

Latches will be created for b_full, d_bfrr, and rd_data.



The gate signals are not explicitly written in the RTL code.

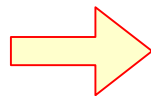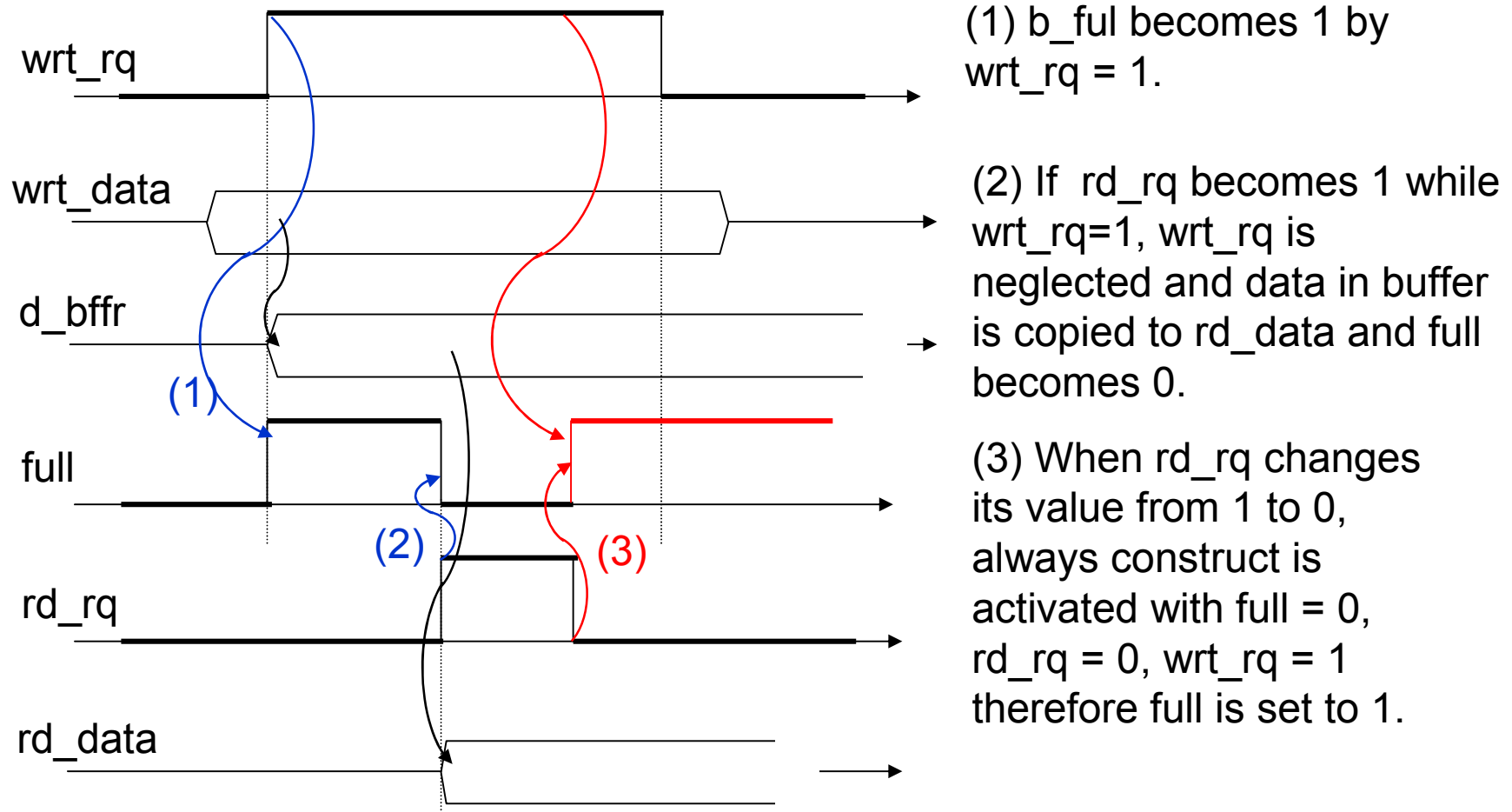Problem1: In the following situation, buffer may become full even if it is read by rd_rq signal.




Once buffer becomes empty, but it is filled with previous write request and becomes full again.

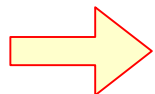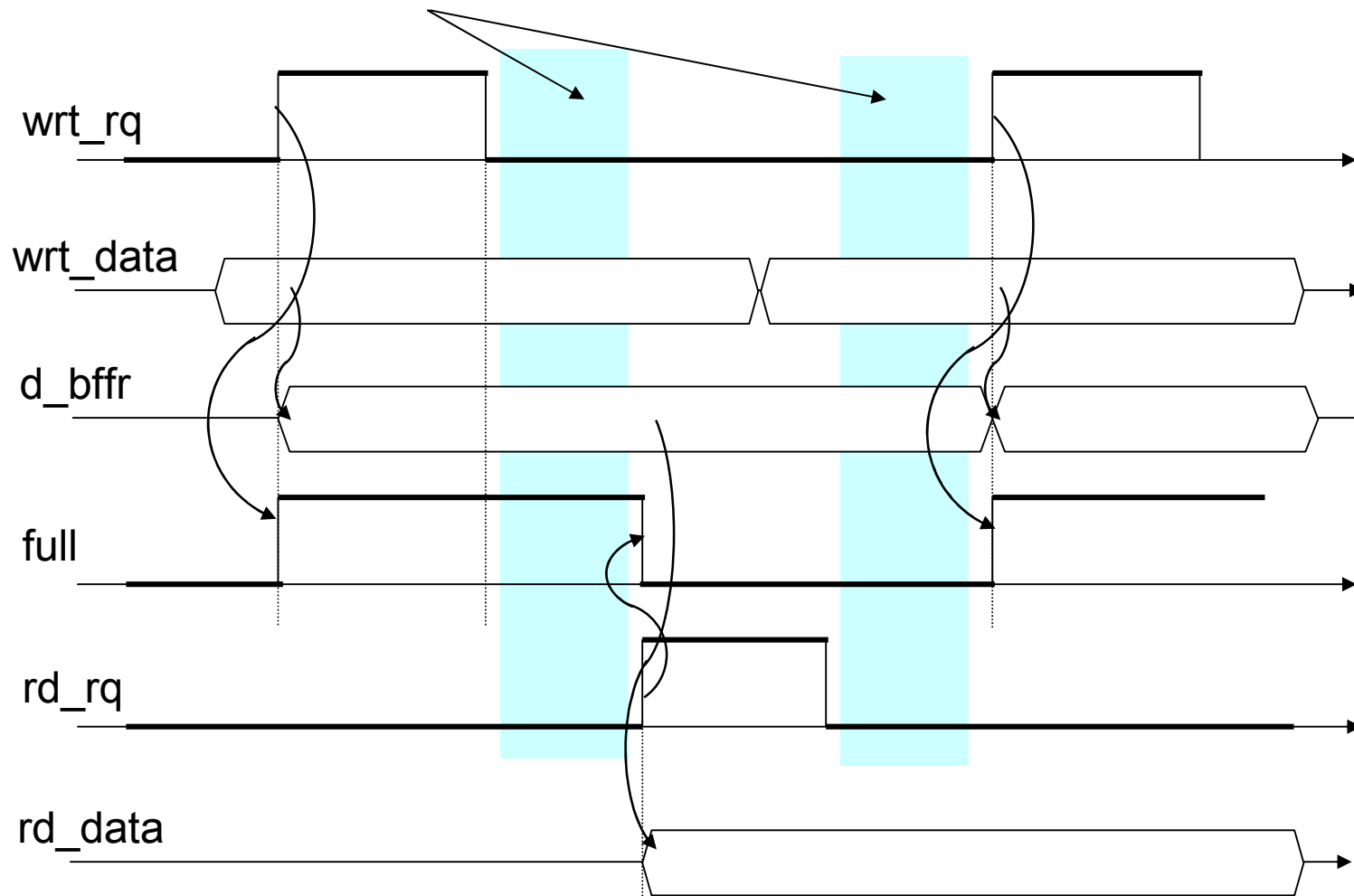The problem in the previous page may be solved by making wrt_rq and rd_rq never become on at the same time.



The RTL simulation may run successfully if above constraint are followed. However, created circuit may still have problems.

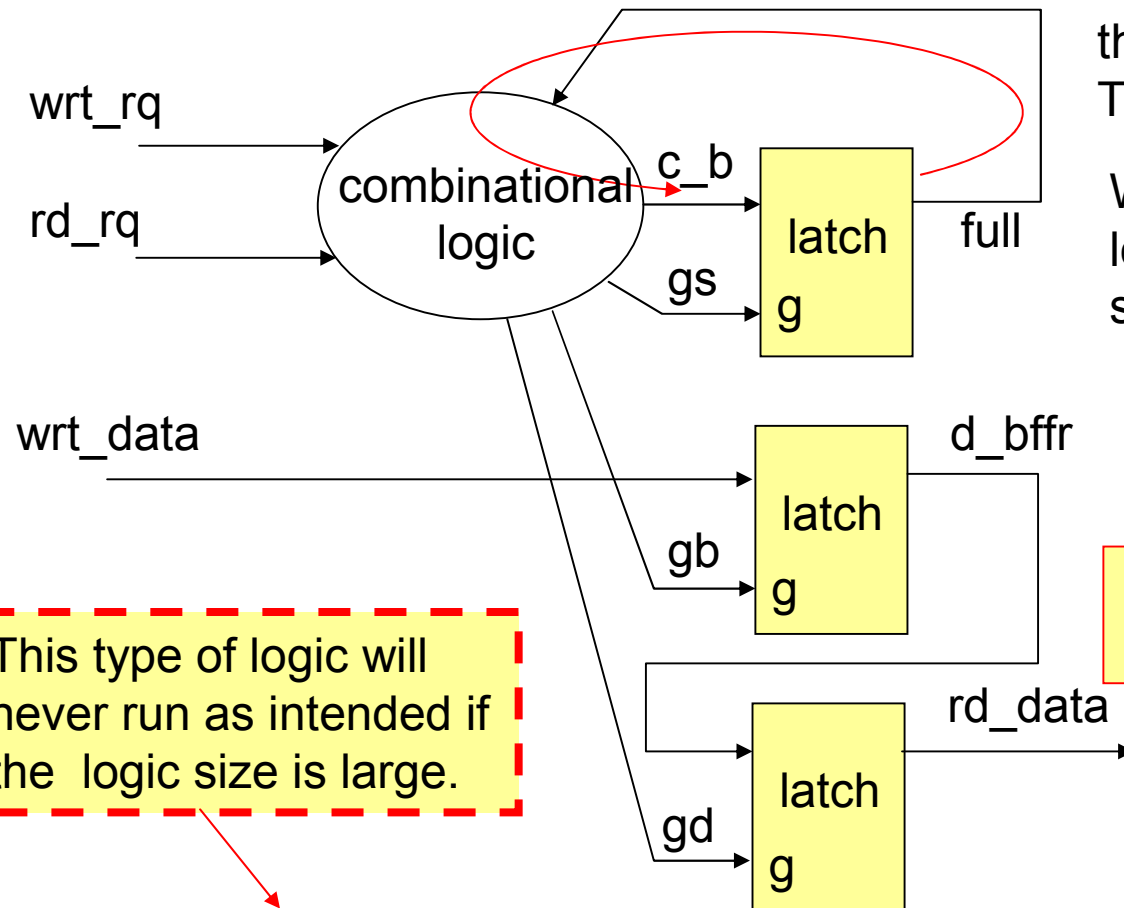Problem2: A gate diagram given by a synthesis tool may look like below. This circuit will never work correctly.



There is a closed loop among D-type transparent latch and the combinational logic.

Therefore, `c_b` may oscillate.

We can not estimate what logic is used to create gate signals from the RTL code,


This type of logic will never run as intended if the logic size is large.

Can not predict on/off timing of the gate of latches.

Critical

Because STA is not applicable to this kind of logic. Note that there is no clock signal. Therefore, we do not have any tools that assure the timing issues.

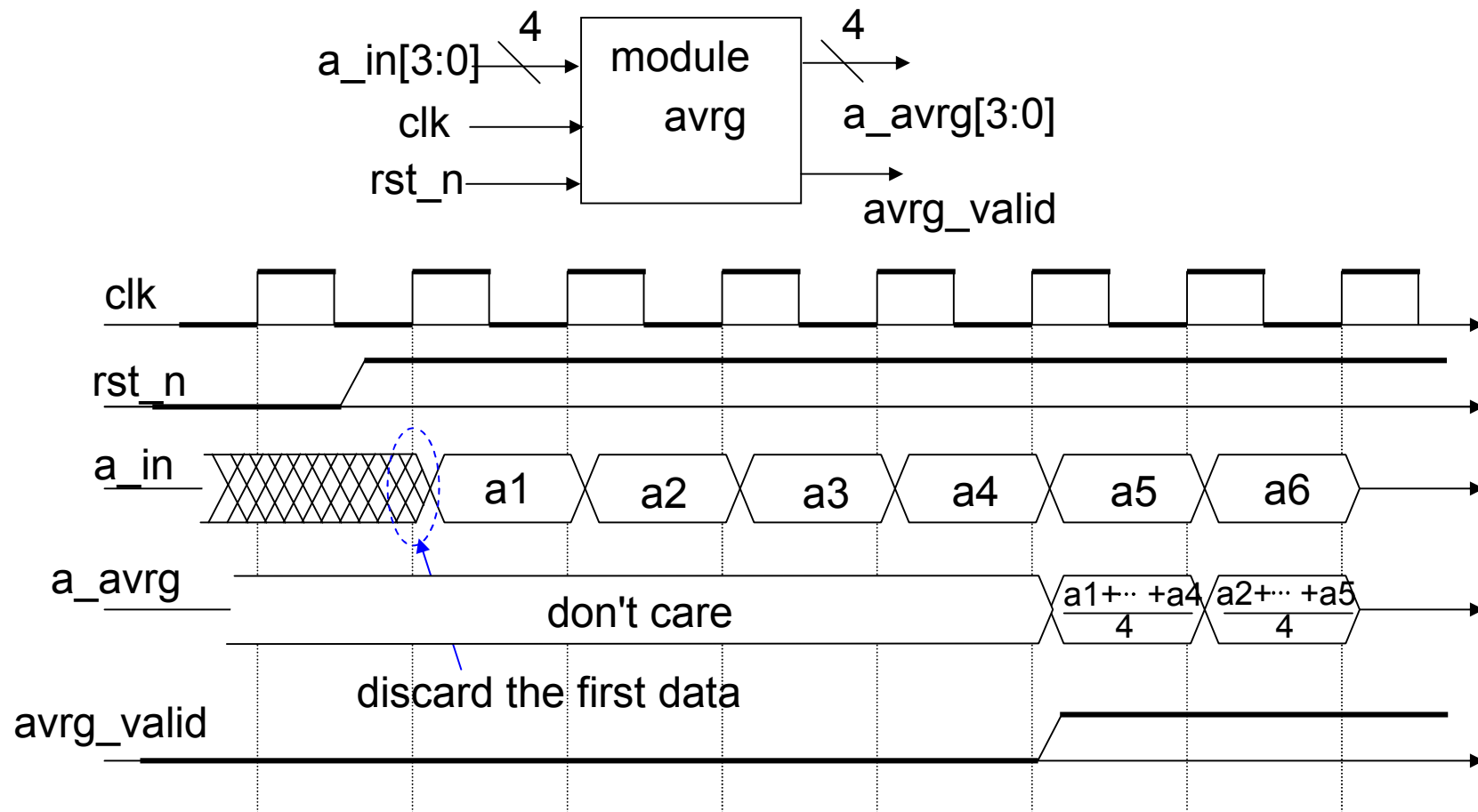
Ex 4-9. Average of sequential four 4-bit data: Write a module which output the average of latest four data coming from input a_in each time the clock clk rises. The result must be rounded, that is, 7.5 must be 8, 3.25 must be 3. avrg_valid signal must be off while output a_avrg is not an average of the latest four data.



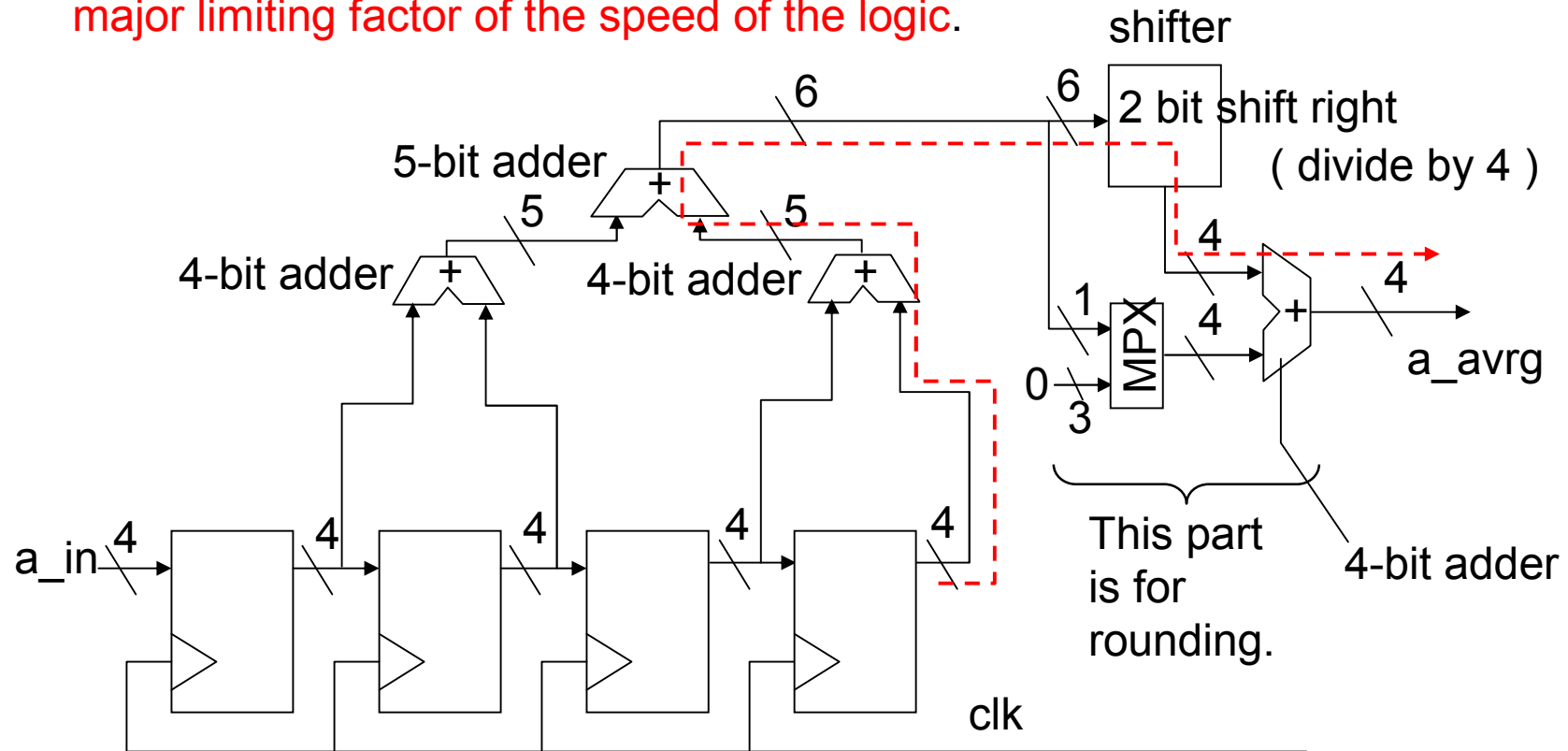(1) How to calculate the average?


The following may be the most straight forward simple structure. However, it has 3 adders serially in the path indicated by the red dashed line.

In synchronous design, **time needed between FFs, or FF to output, is major limiting factor of the speed of the logic.**




Therefore, the structure show on the next page may be better because the length from FF to FF, the red dashed line, is short.

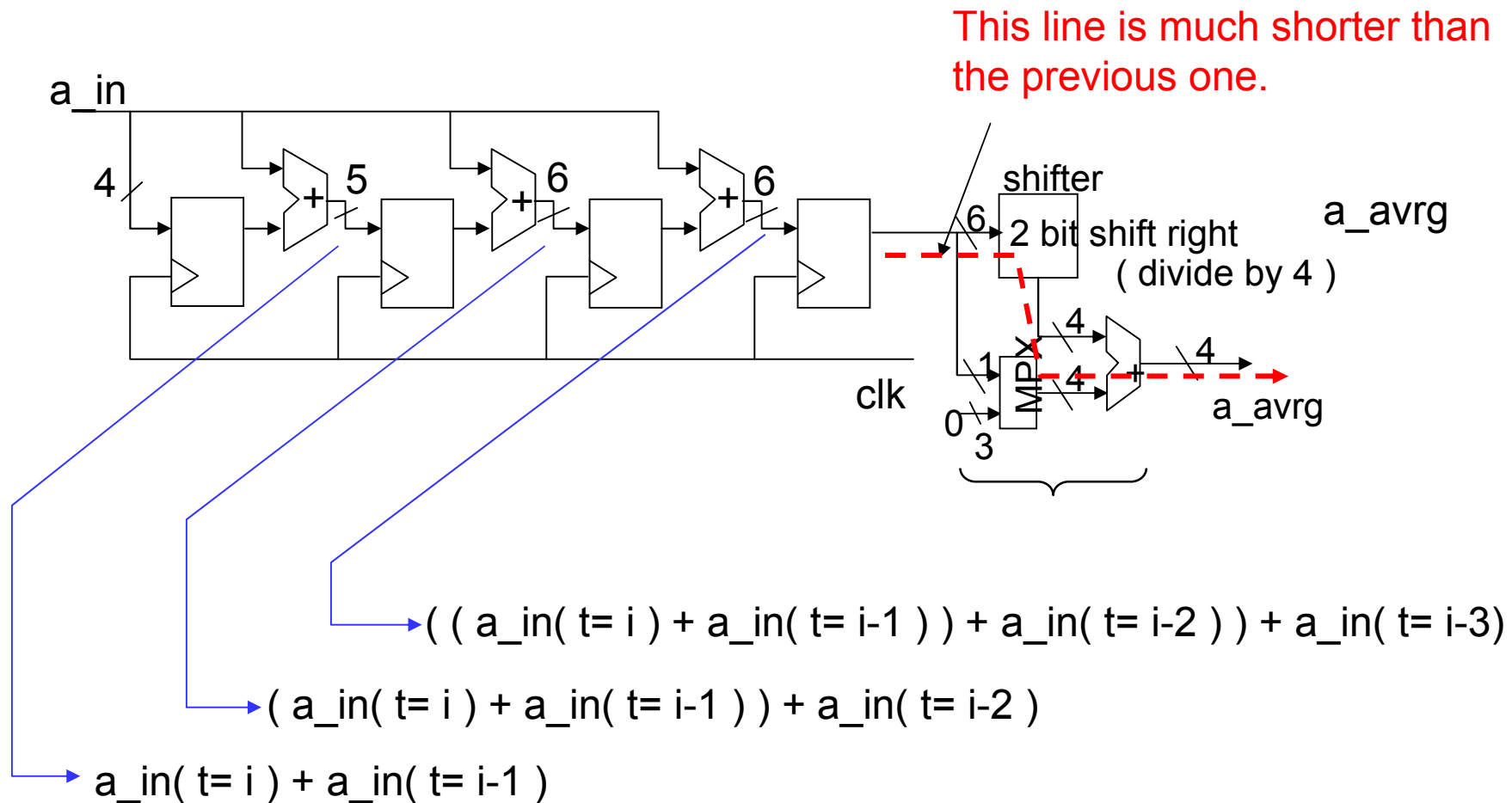In the design below, we only have one adder in the red dashed path.
Therefore, this design may be better from the view point of speed.



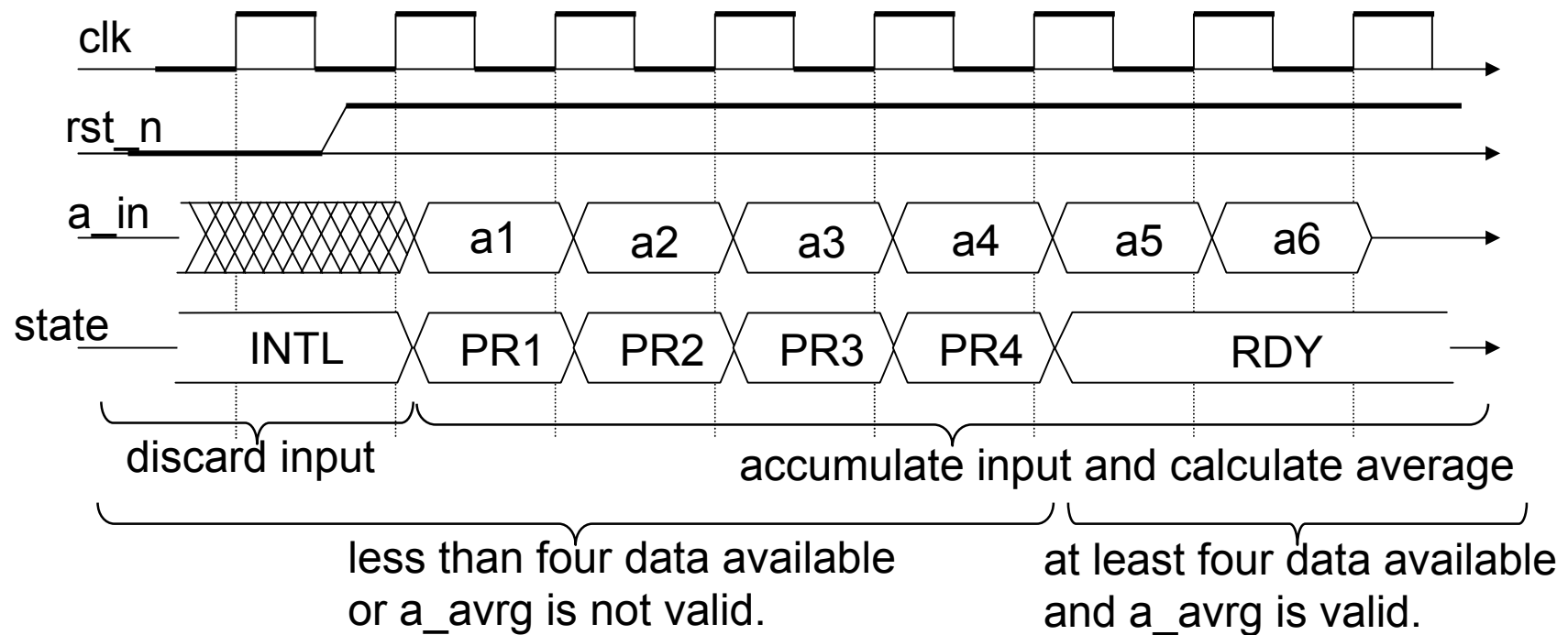(2) How to control state?

This logic needs a state to discard the first data. To simplify the logic, four states, PR1 to PR4, are introduced beside INTL(initial) and RDY(ready).




State control logic:

state		INTL	PR1	PR2	PR3	PR4	RDY
rst_n	clk						
0	x	⇒ INTL	⇒ INTL	⇒ INTL	⇒ INTL	⇒ INTL	⇒ INTL
1		⇒ PR1	⇒ PR2	⇒ PR3	⇒ PR4	⇒ RDY	no operation
	else	no operation					

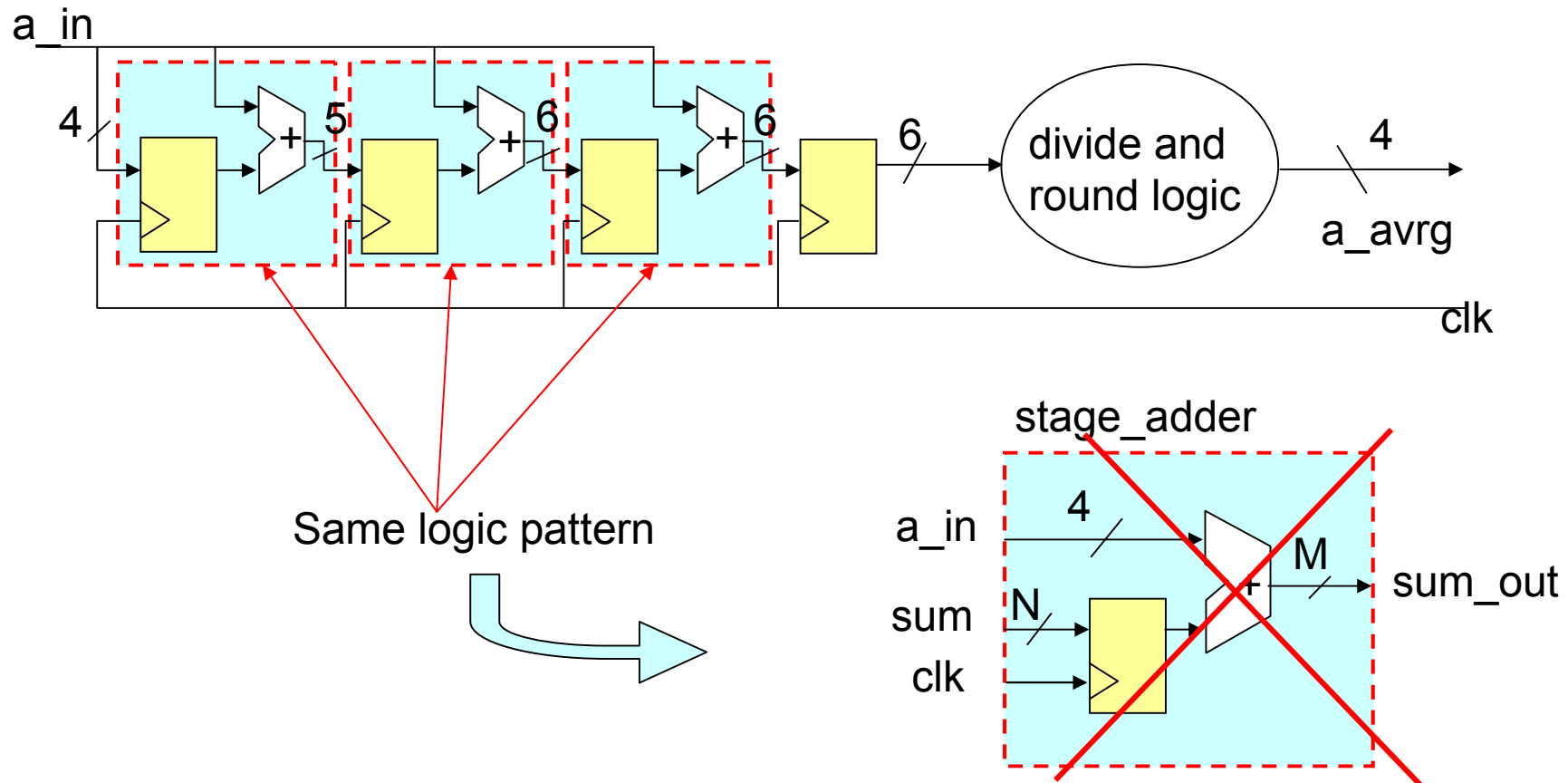(3) Extract common logic block


Extract common process pattern and make it a basic module.



However, this module structure is not a recommended style:


Direct path from input to output and FF path co-exist.

Output does not come directly from FF.

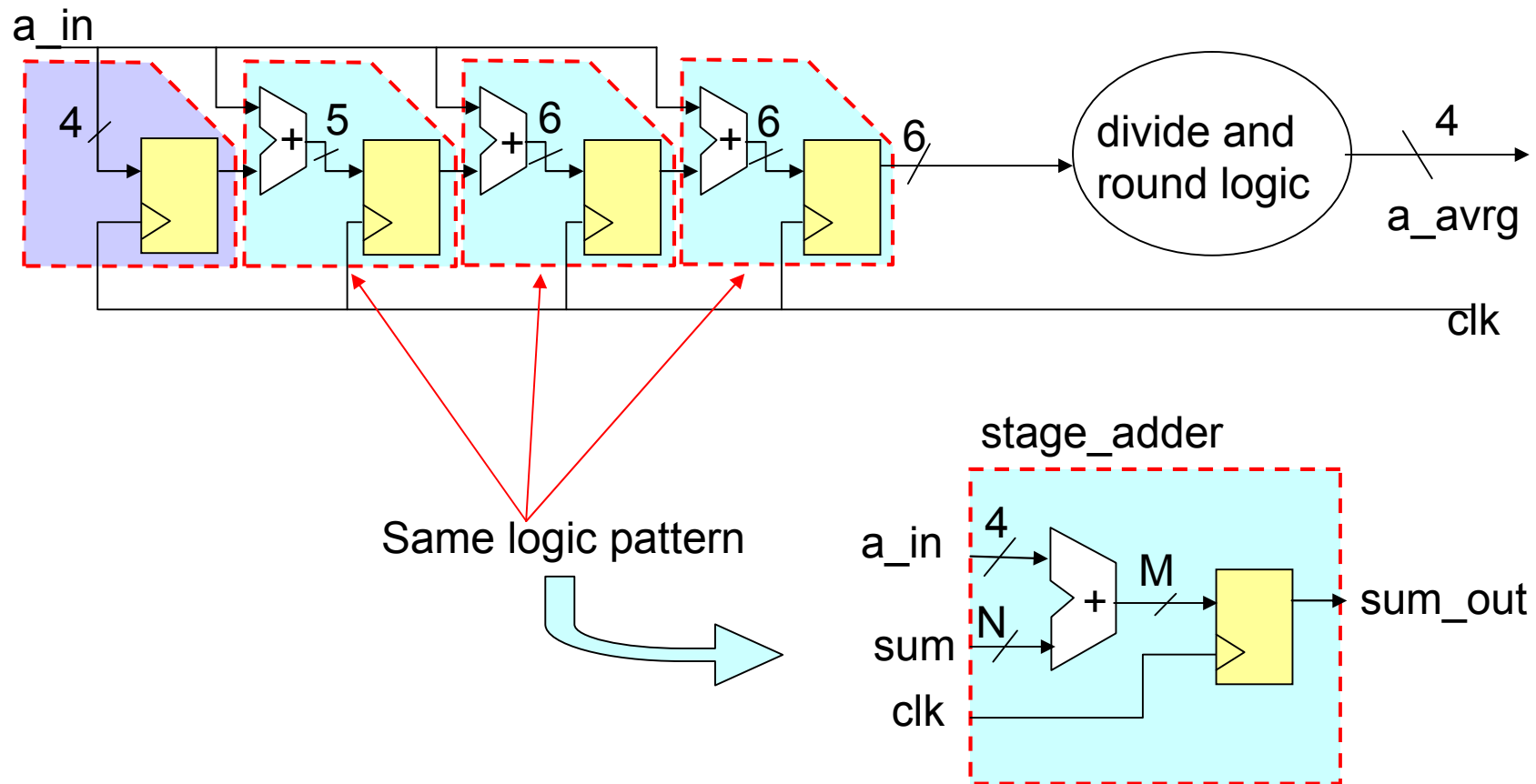


This sub-module structure is better because **output comes from FF directly** and **all the signals go through almost equal logic stages**.

RTL code of stage_adder

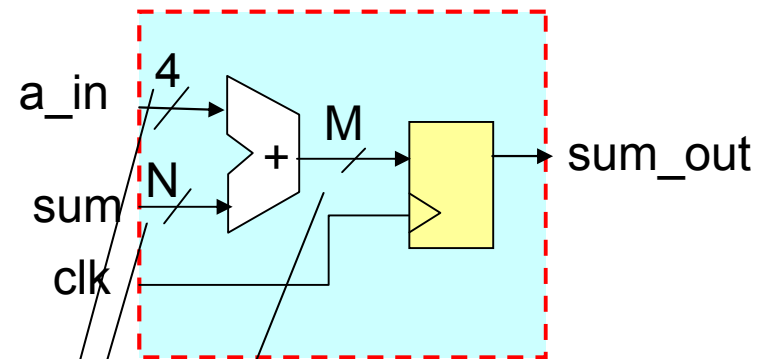


```
//
module stage_adder ( clk, rst_n, a_in, sum, sum_out ) ;
//

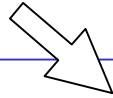parameter A_IN_BW = 4 ; // a_in bit size
parameter SUM_IN_BW = 4 ; // sum bit size
parameter SUM_OUT_BW = 5 ; // sum_out bit size,
//          SUM_OUT_BW can be as large as SUM_IN_BW + 1
//
input clk, rst_n ;
input [A_IN_BW-1:0] a_in ;
input [SUM_IN_BW-1:0] sum ;
output [SUM_OUT_BW-1:0] sum_out ;
//
```





```
wire clk, rst_n ;
wire [A_IN_BW-1:0] a_in ;
wire [SUM_BW-1:0] sum ;
reg [SUM_OUT_BW-1:0] sum_out ; // FF
// internal variables
wire [SUM_OUT_BW-1:0] sum_out ;
//
// max bit size can be as large as SUM_IN_BW + 1
// LHS bit size must be larger than that of RHS to hold carry bit
assign next_sum_out = sum + a_in ;
//
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n==1'b0 ) begin
        sum_out <= 0 ;
    end
    else begin
        sum_out <= next_sum_out ;
    end
end
//
endmodule
```

(4) rounding operation

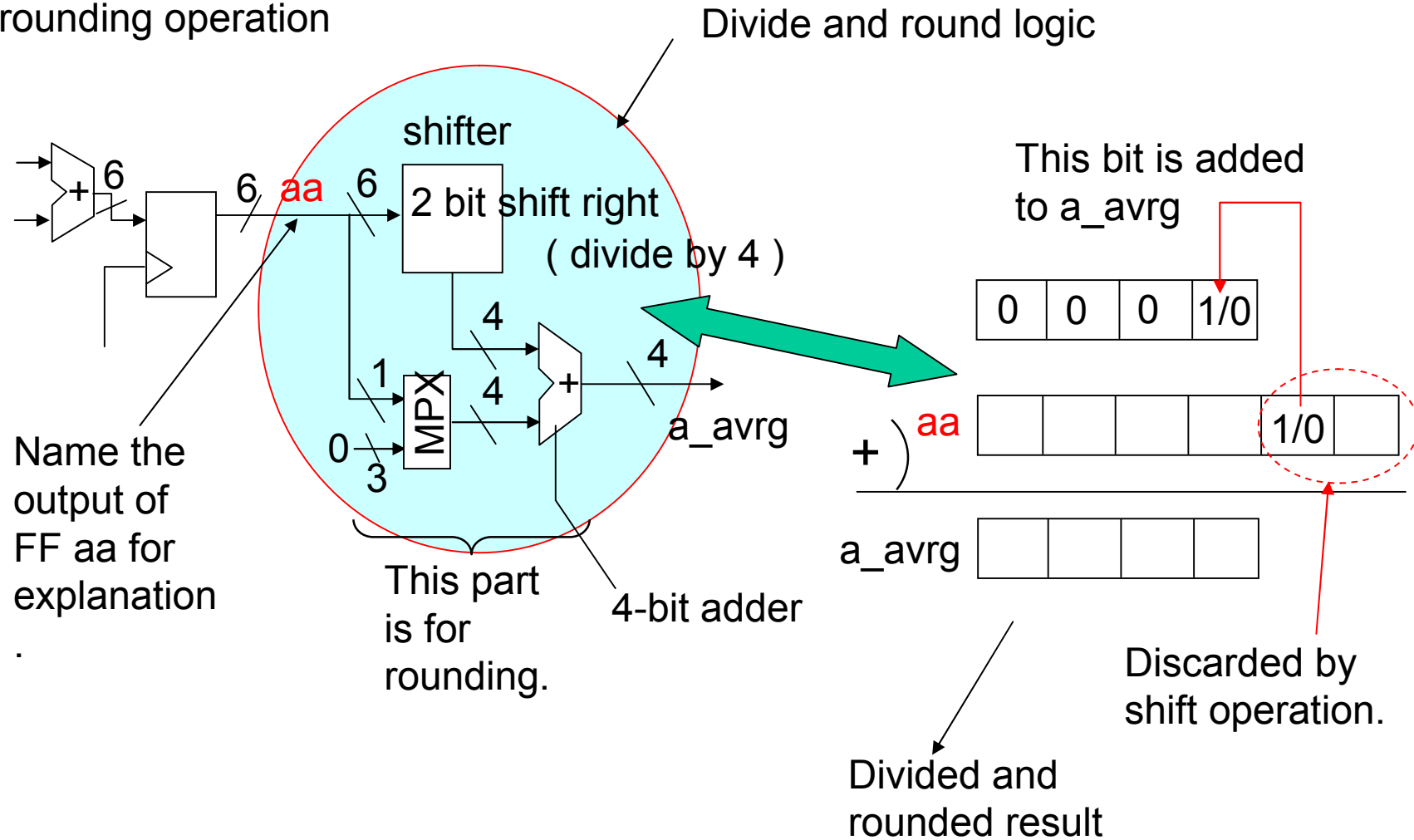


Can't this logic be much simpler?

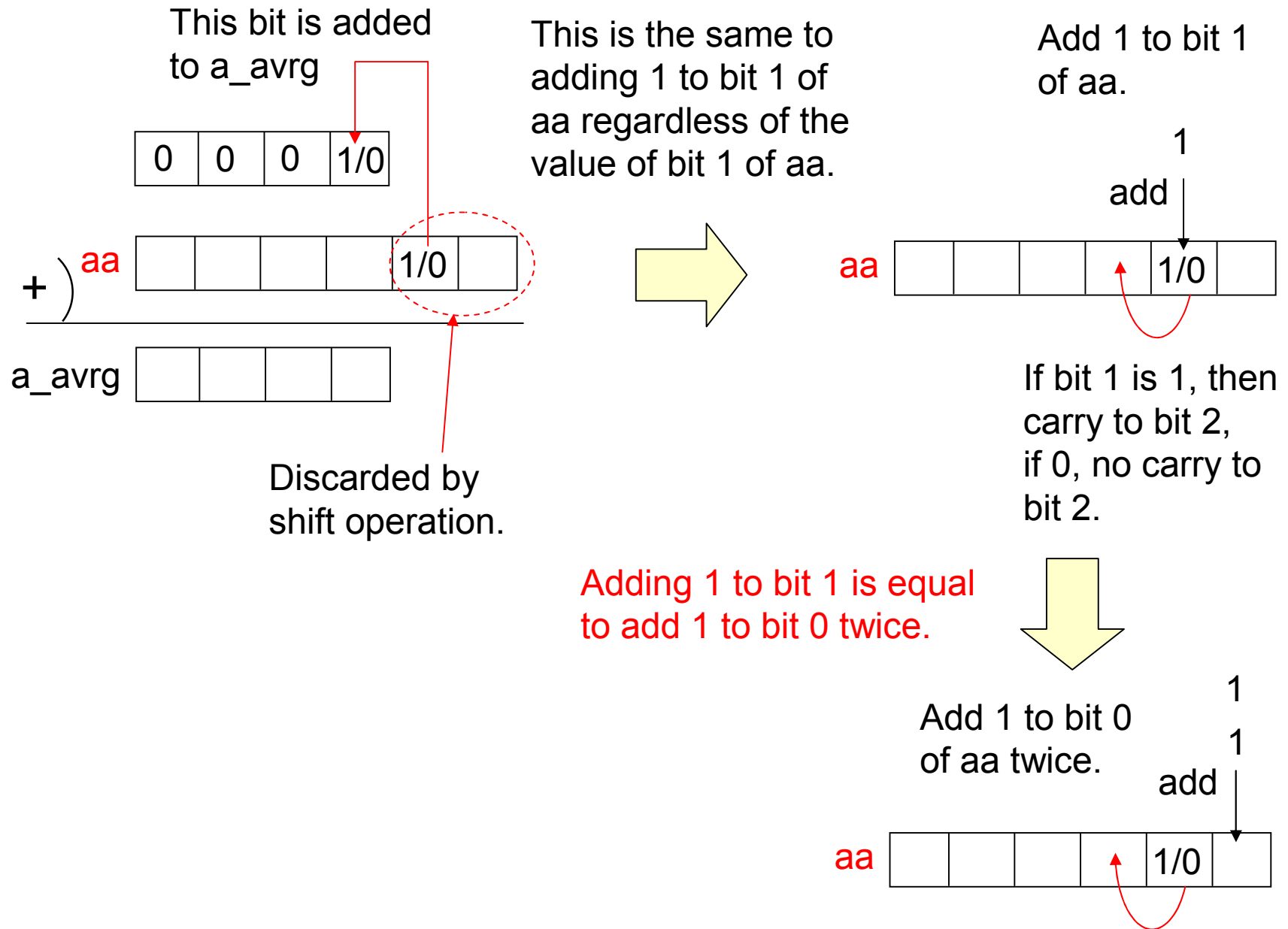

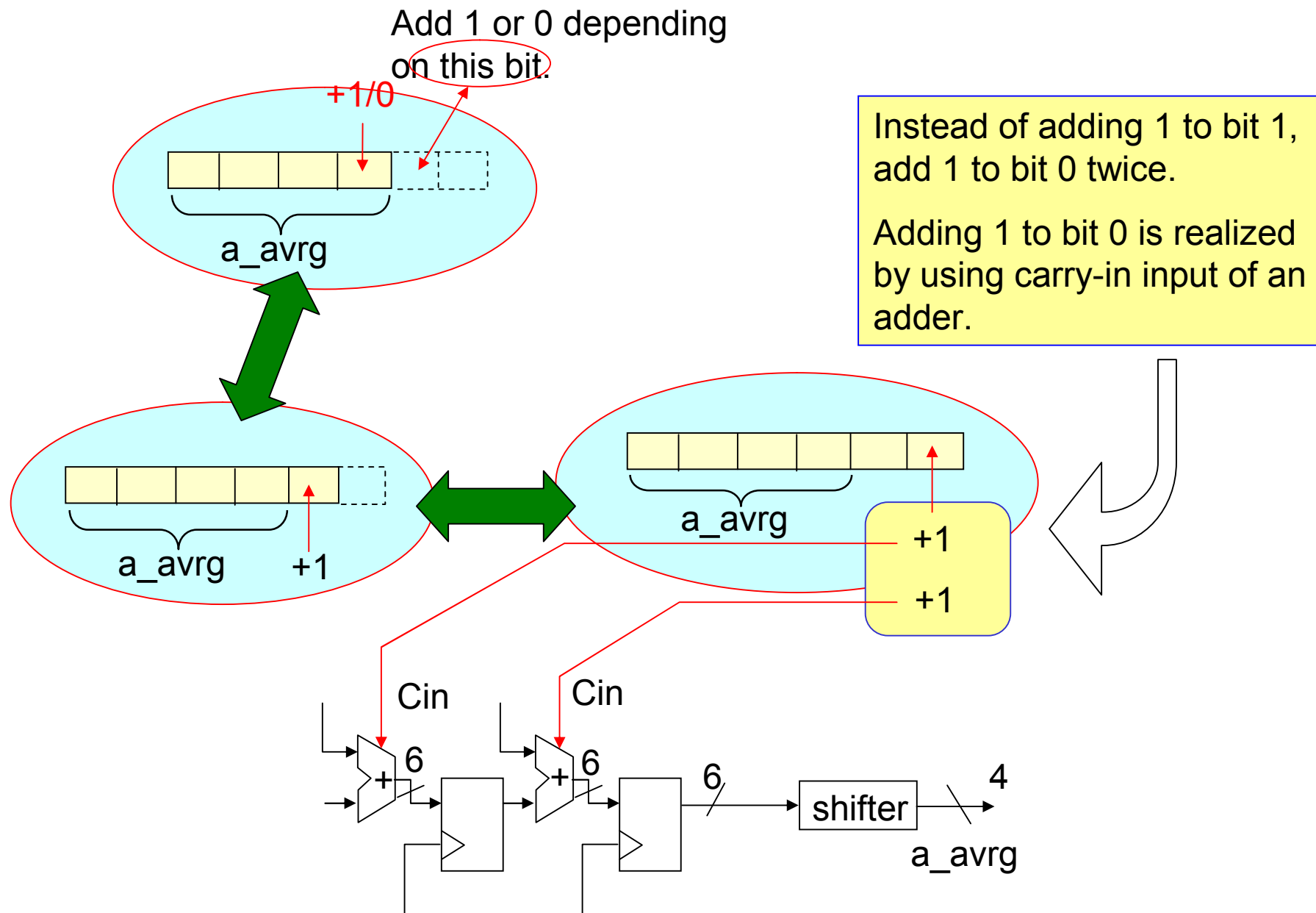


RTL code of stage_adder updated

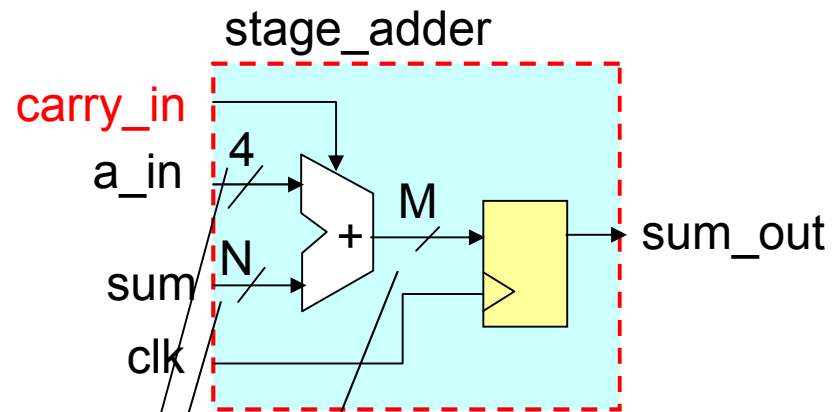




```
//
module stage_adder ( clk, rst_n, a_in, sum, carry_in, sum_out ) ;
//

parameter A_IN_BW = 4 ; // a_in bit size
parameter SUM_IN_BW = 4 ; // sum input bit size
parameter SUM_OUT_BW = 5 ; // sum_out bit size,
//      SUM_OUT_BW can be as large as SUM_IN_BW + 1
//
input clk, rst_n ;
input [A_IN_BW-1:0] a_in ;
input [SUM_IN_BW-1:0] sum ;
input carry_in ;
output [SUM_OUT_BW-1:0] sum_out ;
//
```

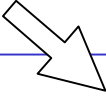
```
wire clk, rst_n ;
wire [A_IN_BW-1:0] a_in ;
wire [SUM_BW-1:0] sum ;
wire carry_in ;
reg [SUM_OUT_BW-1:0] sum_out ; // FF
//
// internal variables
wire [SUM_OUT_BW-1:0] sum_out ;
//
// max bit size can be as large as SUM_IN_BW+1
// LHS bit size must be larger than that of RHS to hold carry bit
assign next_sum_out = sum + a_in + carry_in ;
//
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n==1'b0 ) begin
        sum_out <= 0 ;
    end
    else begin
        sum_out <= next_sum_out ;
    end
end
//
endmodule
```

(5) Decrease bit size of the last FF

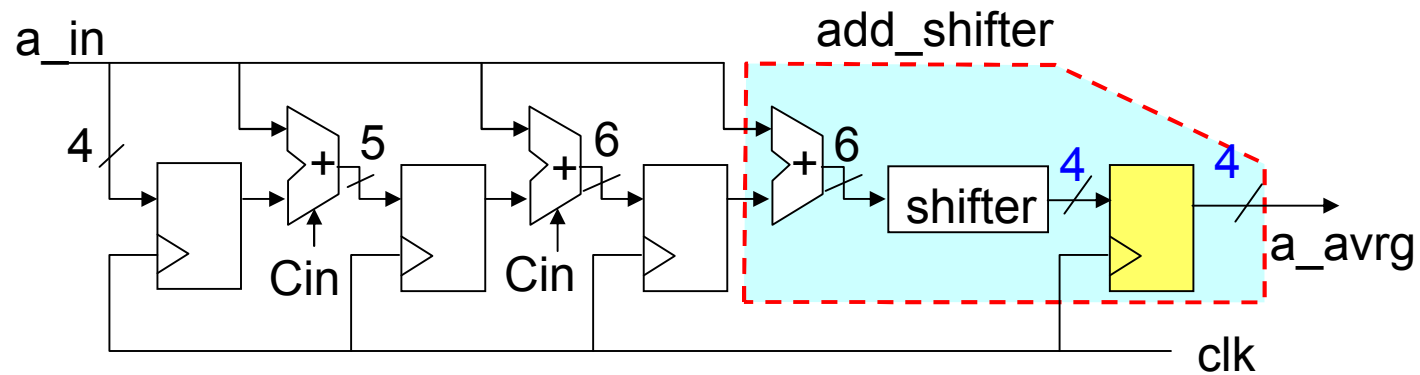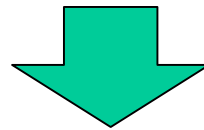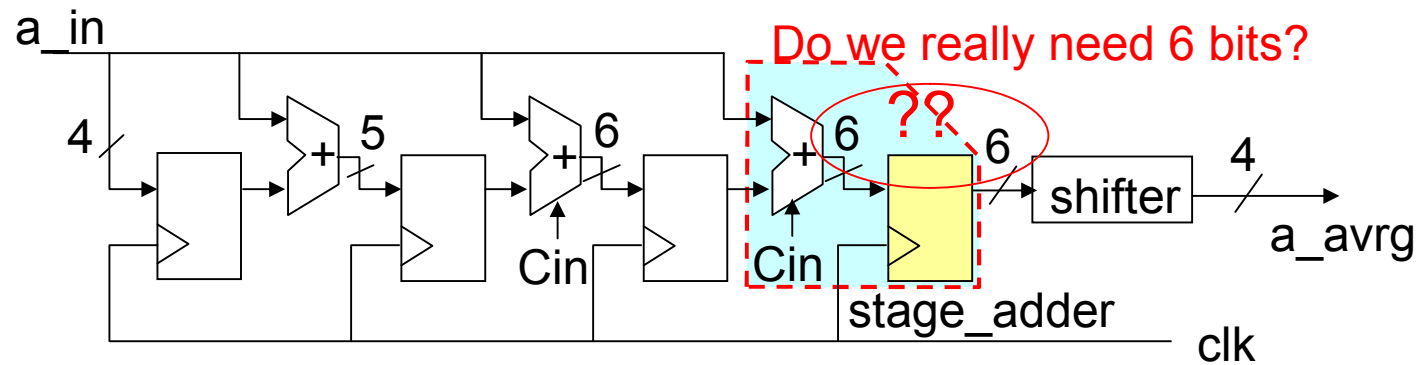

(6) state control implementation


State transition table

state		INTL	PR1	PR2	PR3	PR4	RDY
rst_n	clk						
0	x	FF1,2,3,4 = 0 avrg_valid=0 ⇒ INTL					
1		no operation	*1	*1	*1	*1 avrg_valid=1	*1
	else	⇒ PR1	⇒ PR2	⇒ PR3	⇒ PR4	⇒ RDY	⇒ RDY
		no operation					


Instead of using state PR1, PR2,, etc., introduce a counter (st_cntr) and count up it by 1 at every clock rise time.

st_cntr = 0 ⇒ 1 ⇒ 2 ⇒ 3 ⇒ 4 ⇒ 5
INTL RDY


valid signal creation logic

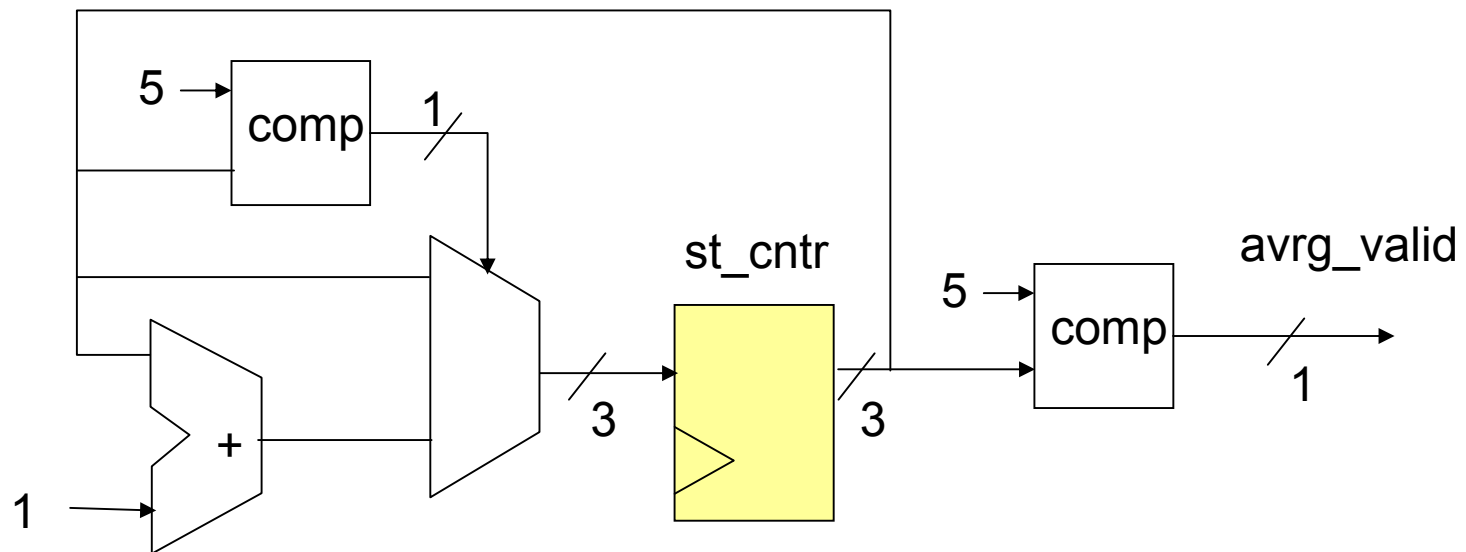


(7) Data path structure and RTL code

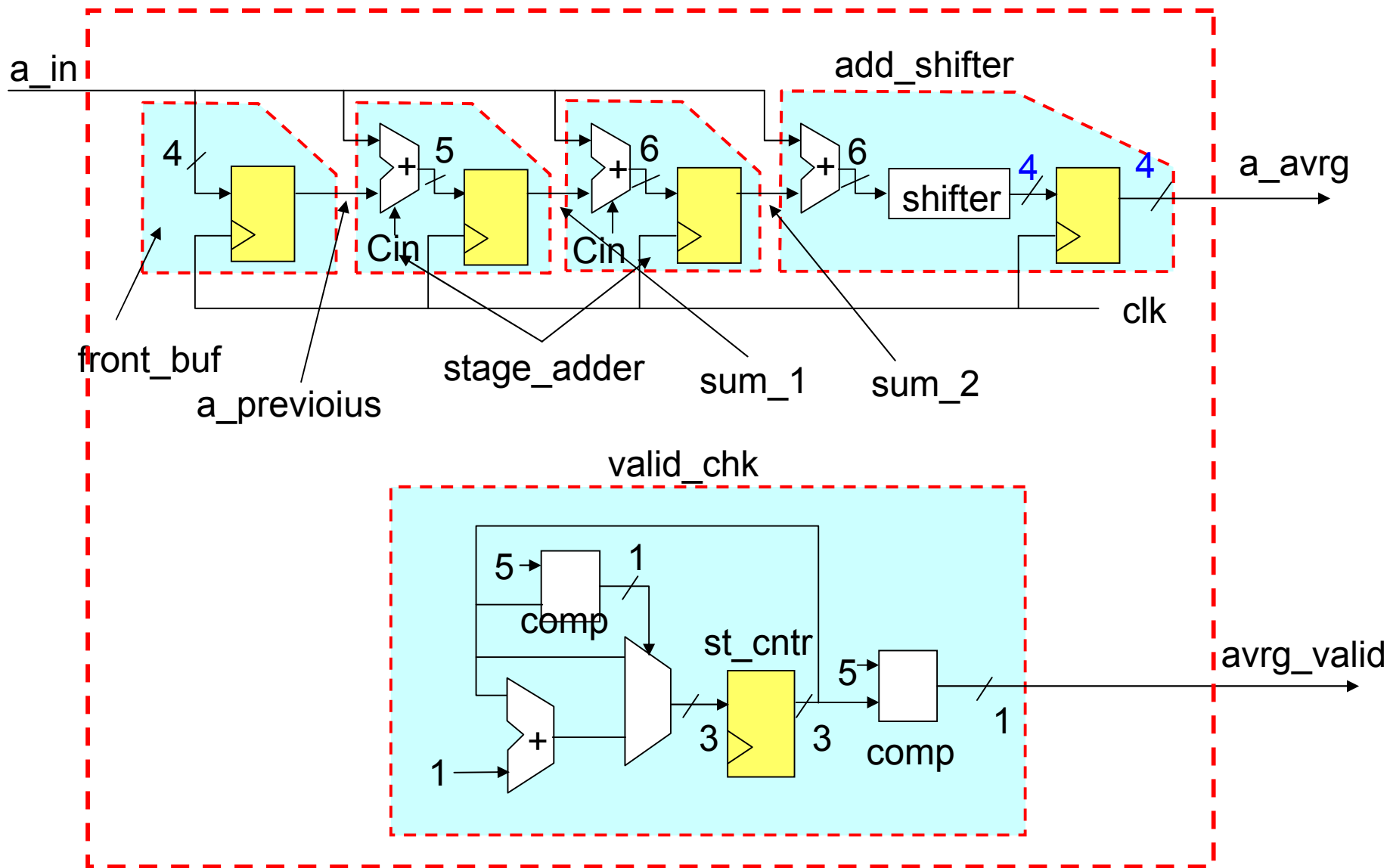


```
//-----
// Project Name : RVC design training
//           : average of four four-bit numbers
// Module Name : avrg
// Function   : this logic out put average of input a_in,
//           : it assume that input is valid at ever clock rise time,
//           : but discard the first data after reset negated.
// note : divide by 4 is implemented by shift operetaion in add_shifter
//       : module, and the shift count is controlled by bit size of a_in and
//       : bit size of sum input for add_shifter module
//       : that is, shift count = SUM_IN_BW - A_IN_BW,
//       : therefore if this relation is not applicable, the divide logic
//       : in add_shifter module must be modified.
// Author    : K. Hayashi (idxxxx)
//----- modification history -----
// Version   Date      Author    Description
// ver.1.0   2010.xx.xx K. Hayashi first release
//-----
//
module avrg ( clk, rst_n, a_in, a_avrg, avrg_valid );
//
parameter A_IN_BW = 4 ; // a_in bit size
```

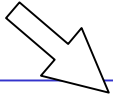



```
//  
parameter SUM_1_BW = A_IN_BW + 1 ; // 1 bit extended for overflow  
parameter SUM_2_BW = SUM_1_BW + 1 ; // another 1 bit extended  
//  
defparam front_buf_01.A_IN_BW = A_IN_BW ;  
//  
defparam stage_adder_01.A_IN_BW = A_IN_BW ;  
defparam stage_adder_01.SUM_IN_BW = A_IN_BW ;  
defparam stage_adder_01.SUM_OUT_BW = SUM_1_BW ;  
//  
defparam stage_adder_02.A_IN_BW = A_IN_BW ;  
defparam stage_adder_02.SUM_IN_BW = SUM_1_BW ;  
defparam stage_adder_02.SUM_OUT_BW = SUM_2_BW ;  
//  
defparam add_shifter_01.A_IN_BW = A_IN_BW ;  
defparam add_shifter_01.SUM_IN_BW = SUM_2_BW ;  
//  
input clk, rst_n ;  
input [A_IN_BW-1:0] a_in ;  
output [A_IN_BW-1:0] a_avg ;  
output avg_valid ;  
//
```

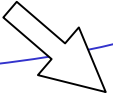

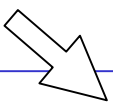



```
wire clk, rst_n ;
wire [A_IN_BW-1:0] a_in ;
wire [A_IN_BW-1:0] a_avg ; // average of four a_in
wire avg_valid ;
//
wire [A_IN_BW-1:0] a_previous ;
wire [SUM_1_BW-1:0] sum_1 ;
wire [SUM_2_BW-1:0] sum_2 ;
//
// connection of stage adders
valid_chk valid_chk_01 ( .clk(clk), .rst_n(rst_n),
                        .valid_out(avg_valid) ) ;
front_buf front_buf_01 ( .clk(clk), .rst_n(rst_n),
                        .a_in(a_in), .a_previous(a_previous) ) ;
stage_adder stage_adder_01 ( .clk(clk), .rst_n(rst_n),
                            .a_in(a_in), .sum(a_previous), .carry_in ( 1'b1 ), .sum_out(sum_1) ) ;
stage_adder stage_adder_02 ( .clk(clk), .rst_n(rst_n),
                            .a_in(a_in), .sum(sum_1), .carry_in( 1'b1 ), .sum_out(sum_2) ) ;
add_shifter add_shifter_01 ( .clk(clk), .rst_n(rst_n),
                            .a_in(a_in), .sum(sum_2), .avg_out(a_avg) ) ;
//
endmodule
```

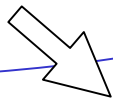






```
module valid_chk ( clk, rst_n, valid_out ) ;  
parameter VALID_CNT_MAX = 5 ; // state counter limiter  
//  
input clk, rst_n ;  
output valid_out ;  
//  
wire clk, rst_n ;  
wire valid_out ;  
//  
// internal variables  
reg [2:0] st_cntr ; // FF, counter to count up to 5  
reg [2:0] next_st_cntr ; // non-FF  
// logic for valid signal  
// define FF for state counter  
always @ ( posedge clk or negedge rst_n ) begin  
    if ( rst_n == 1'b0 ) begin  
        st_cntr <= 0 ;  
    end  
    else begin  
        st_cntr <= next_st_cntr ;  
    end  
end  
end
```

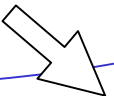

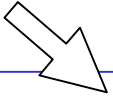

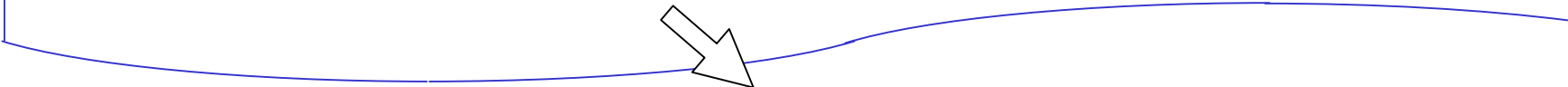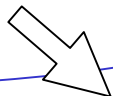

```
// define next_st_cntr
always @ ( st_cntr ) begin
    if ( st_cntr == VALID_CNT_MAX ) begin
        next_st_cntr = st_cntr ; // if counted up to 5, stop update
    end
    else begin
        next_st_cntr = st_cntr + 1 ; // update counter by 1
    end
end
// valid=1 if cntr = VALID_CNT_MAX
assign valid_out = ( st_cntr == VALID_CNT_MAX ) ;
//
endmodule
```








```
module front_buf ( clk, rst_n, a_in, a_previous ) ;  
//  
parameter A_IN_BW = 4 ; // a_in bit size  
//  
input clk, rst_n ;  
input [A_IN_BW-1:0] a_in ;  
output [A_IN_BW-1:0] a_previous ;  
//  
wire clk, rst_n ;  
wire [A_IN_BW-1:0] a_in ;  
reg [A_IN_BW-1:0] a_previous ; // FF  
//  
always @ ( posedge clk or negedge rst_n ) begin  
    if ( rst_n==1'b0 ) begin  
        a_previous <= 0 ;  
    end  
    else begin  
        a_previous <= a_in ;  
    end  
end  
//  
endmodule
```








```
module stage_adder ( clk, rst_n, a_in, sum, carry_in, sum_out ) ;  
//  
parameter A_IN_BW = 4 ; // a_in bit size  
parameter SUM_IN_BW = 4 ; // sum input bit size  
parameter SUM_OUT_BW = 5 ; // sum_out bit size,  
//          SUM_OUT_BW can be as large as SUM_IN_BW + 1  
//  
input clk, rst_n ;  
input [A_IN_BW-1:0] a_in ;  
input [SUM_IN_BW-1:0] sum ;  
input carry_in ;  
output [SUM_OUT_BW-1:0] sum_out ;  
//  
wire clk, rst_n ;  
wire [A_IN_BW-1:0] a_in ;  
wire [SUM_IN_BW-1:0] sum ;  
wire carry_in ;  
reg [SUM_OUT_BW-1:0] sum_out ; // FF  
//  
wire [SUM_OUT_BW-1:0] next_sum_out ;  
//
```

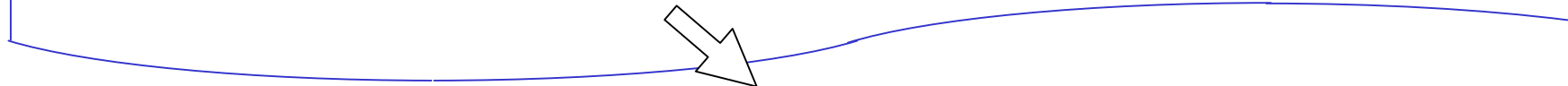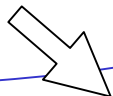




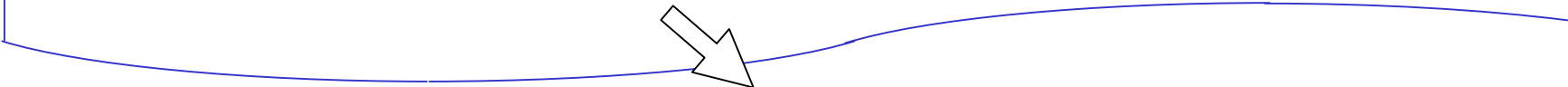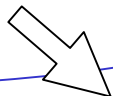
```
// max bit size can be as large as SUM_IN_BW +1
// LHS bit size must be larger than that of RHS to hold carry bit
assign next_sum_out = sum + a_in + carry_in ;
//
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n==1'b0 ) begin
        sum_out <= 0 ;
    end
    else begin
        sum_out <= next_sum_out ;
    end
end
//
endmodule
```





```
module add_shifter ( clk, rst_n, a_in, sum, avrg_out ) ;  
//  
parameter A_IN_BW = 4 ; // a_in bit size  
parameter SUM_IN_BW = 6 ; // sum bit size  
parameter SUM_OUT_BW = A_IN_BW ; // sum_out bit size,  
//          SUM_OUT_BW is equal to A_IN_BW because  
//          lower (SUM_IN_BW - A_IN_BW) is shifted out  
parameter SHIFT_CNT = SUM_IN_BW - A_IN_BW ;  
//  
input clk, rst_n ;  
input [A_IN_BW-1:0] a_in ;  
input [SUM_IN_BW-1:0] sum ;  
output [A_IN_BW-1:0] avrg_out ;  
//  
wire clk, rst_n ;  
wire [A_IN_BW-1:0] a_in ;  
wire [SUM_IN_BW-1:0] sum ;  
reg [A_IN_BW-1:0] avrg_out ; // FF  
// internal variables  
wire [SUM_IN_BW:0] temp_add ; // 1 bit extended for future safty.  
wire [A_IN_BW-1:0] next_avrg_out ;
```

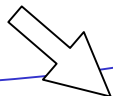

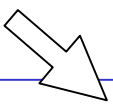

```
//  
// add operation will not result in more than SUM_IN_BW  
// LHS bit size must be larger than that of RHS to hold carry bit  
assign temp_add = sum + a_in ;  
assign next_avrg_out = temp_add >> SHIFT_CNT ; // divide by 4  
//  
always @ ( posedge clk or negedge rst_n ) begin  
    if ( rst_n==1'b0 ) begin  
        avrg_out <= 0 ;  
    end  
    else begin  
        avrg_out <= next_avrg_out ;  
    end  
end  
//  
endmodule
```

file name: avrg.v

(8) test bench


```

module test_avrg ;
parameter HF_CYCL=10 ;
parameter CYCL = HF_CYCL *2 ;
parameter A_IN_BW = 8 ; // note bit size is not 4, modify avrg module to work correctly
event sig_chng_timing ; // this is a event synchtonized to clock, half cycle after clock rise.
reg rst_n, clk ;
reg [A_IN_BW-1:0] a ;
wire[A_IN_BW-1:0] a_avrg ;
wire valid ;
// connect signals to game
avrg avrg_01 ( .rst_n( rst_n ), .clk( clk ),
               .a_in( a ),
               .a_avrg( a_avrg ),
               .avrg_valid( valid )
             ) ;
// connection end
always begin
  clk = 0 ; #HF_CYCL ;
  clk = 1 ; #HF_CYCL ;
end

always @ ( negedge clk ) begin
  -> sig_chng_timing ;
end

always @ ( posedge clk ) begin // clock generator
  #2 $strobe("t=%d, rst=%b, clk=%b, a= %d, ff=%d, %d, %d, temp_add=%d, a_avrg=%d, v=%b",
    $stime, rst_n, clk, a,
    avrg_01.a_previous,
    avrg_01.sum_1,
    avrg_01.sum_2,
    avrg_01.add_shifter_01.temp_add,
    a_avrg, valid
  ) ;
end
end

```




```

initial begin
  a= 0 ;
  #1 ;
  while ( rst_n == 1'b0 ) begin
    #1 ;
  end;
  @ ( sig_chng_timing ) a= 8 ;
  @ ( sig_chng_timing ) a= 16 ;
  @ ( sig_chng_timing ) a= 32 ;
  @ ( sig_chng_timing ) a= 64 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 128 ;
  @ ( sig_chng_timing ) a= 128 ;
  @ ( sig_chng_timing ) a= 128 ;
  @ ( sig_chng_timing ) a= 128 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( sig_chng_timing ) a= 0 ;
  @ ( posedge clk ) #HF_CYCL $finish ;
end
initial begin // give value to control variable
  rst_n = 1'b0 ;
  #(CYCL*2) rst_n = 1'b1 ;
  #(CYCL * 50) $finish ;
end
endmodule

```

file name: test_avrg.v

(9) Bit size extension.

Extend the bit size to 8, not 4, by modifying the code as shown below and test the logic if it works correctly for 8-bit data.

```
module avrg ( clk, rst_n, a_in, a_avrg, avrg_valid );
//
parameter A_IN_BW = 8 ; // a_in bit size
```


```

•
•
•


```

```
module test_avrg ;
parameter HF_CYCL=10 ;
parameter CYCL = HF_CYCL *2 ;
parameter A_IN_BW = 8 ;
defparam avrg_01.A_IN_BW=A_IN_BW ;
    ”
    ”
    ”
    ”
wire[A_IN_BW-1:0] a_avrg ;
wire valid ;
// connect signals to game
avrg avrg_01 ( .rst_n( rst_n ), .clk( clk ),
```

Ex 4-10. 6-stage bund flasher: Write a module named `six_stage_flash`, which outputs 13-bit signal `lp` as shown below. Right after asynchronous active low reset signal, `rst_n`, is negated, `lp` must be 0. When input signal `flick` becomes 1, `lp[0]` must be turned on. After that at each clock rise time, on-bit position must shift toward MSB. The input signal `flick` is valid only when `lp` is 0. On-bit position must go up and down as shown below.

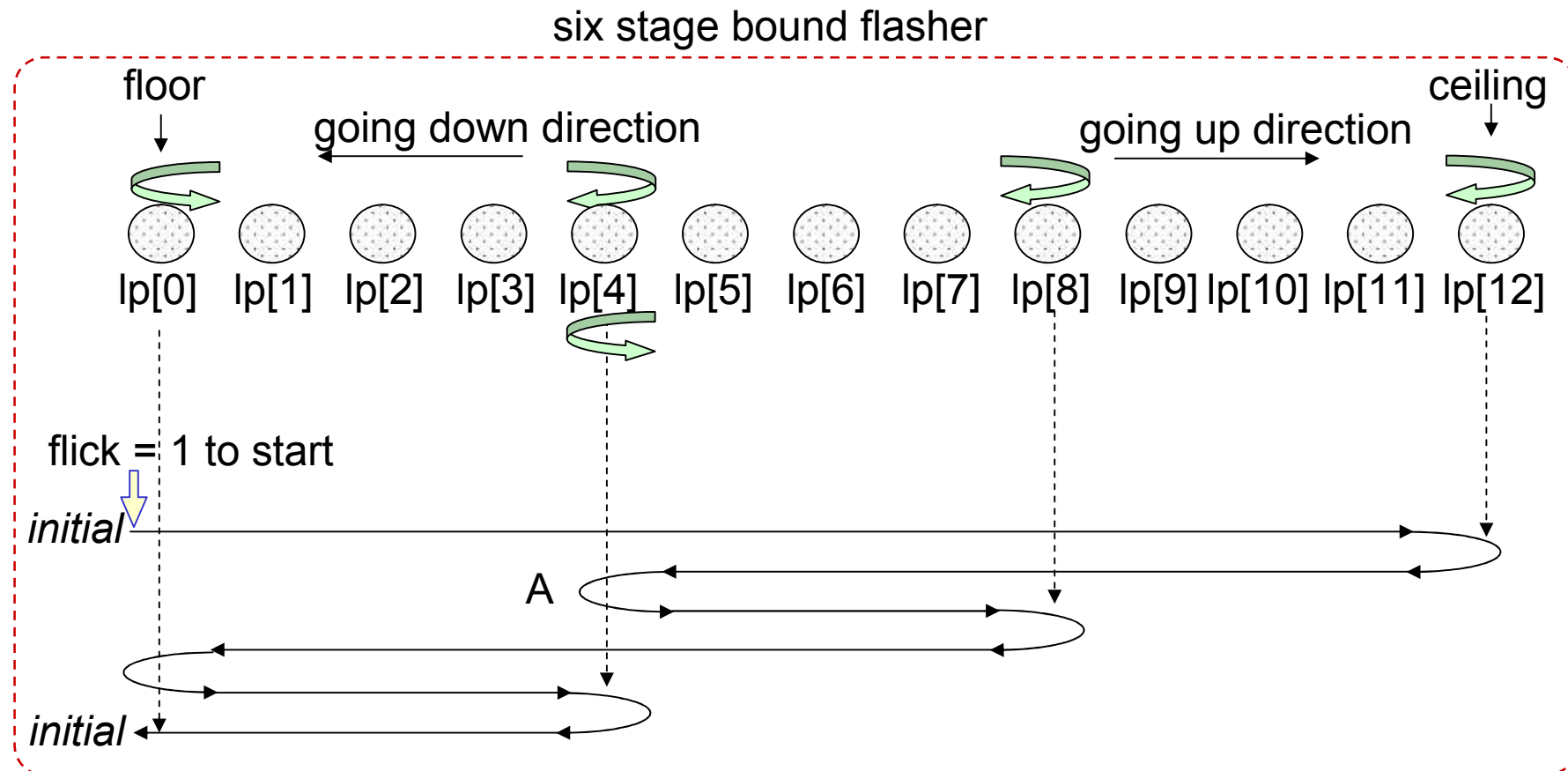

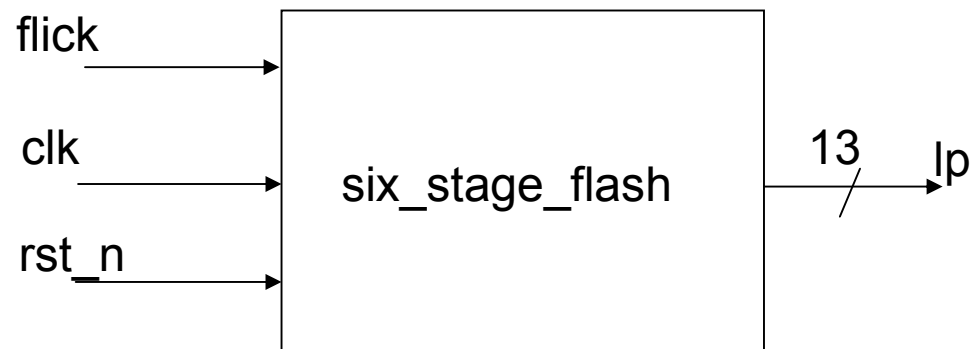In your code, you must use parameters for bit size of *lp*, turning points, initial values, etc. Your logic must work correctly by changing these parameters when the specification changes such as the second turning point, *A*, is not bit 4, but bit 2. Use meaningful and easy to understand names for those parameters.



No sample code is given for this exercise.

Chapter 5. RTL coding style suitable for optimization

In general synthesis tools are getting more intelligent and becomes capable of generating optimized net list from RTL code which may not be written in recommended styles.

However, there still are weak points in synthesis tools therefore knowing what style result in less optimized gate net list and what style result in more optimized one will help writing good RTL code.


In this chapter, we will see several examples which result in easy to optimize gate diagram and hard to optimize gate diagram.

However, do not think today's weak point of synthesis tools is still their tomorrow's weak point.


Ex 5-1. For-loop and if statement: Write a module which counts the number of on bit in a given 32-bit input signal sig_in and output the count onto an 6-bit output signal on_cnt.


To count on-bit in a signal aa, we can apply the logic below. The code below is synthesizable.
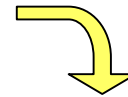
```
integer k ;
cnt = 0 ;
for ( k = 0 ; k < 32 ; k = k +1 ) begin
  if ( aa[k] == 1'b1 ) begin
    cnt = cnt +1 ;
  end
end
```



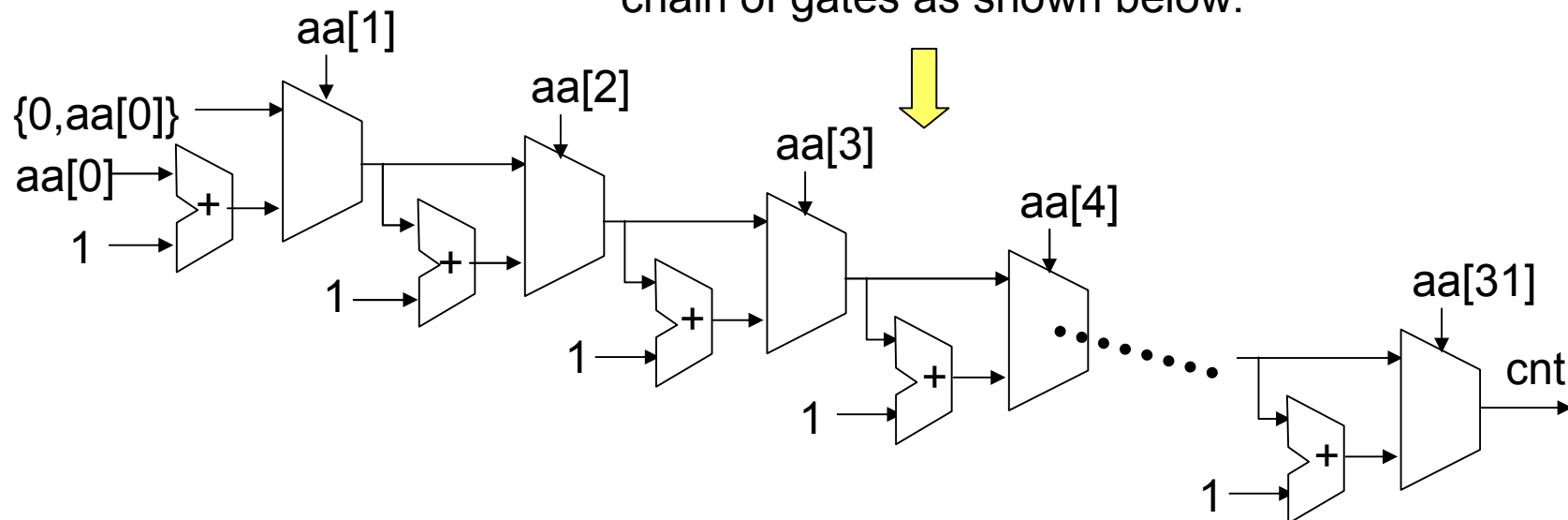However, when synthesized, the code result in a very long serial chain of gates as shown below.



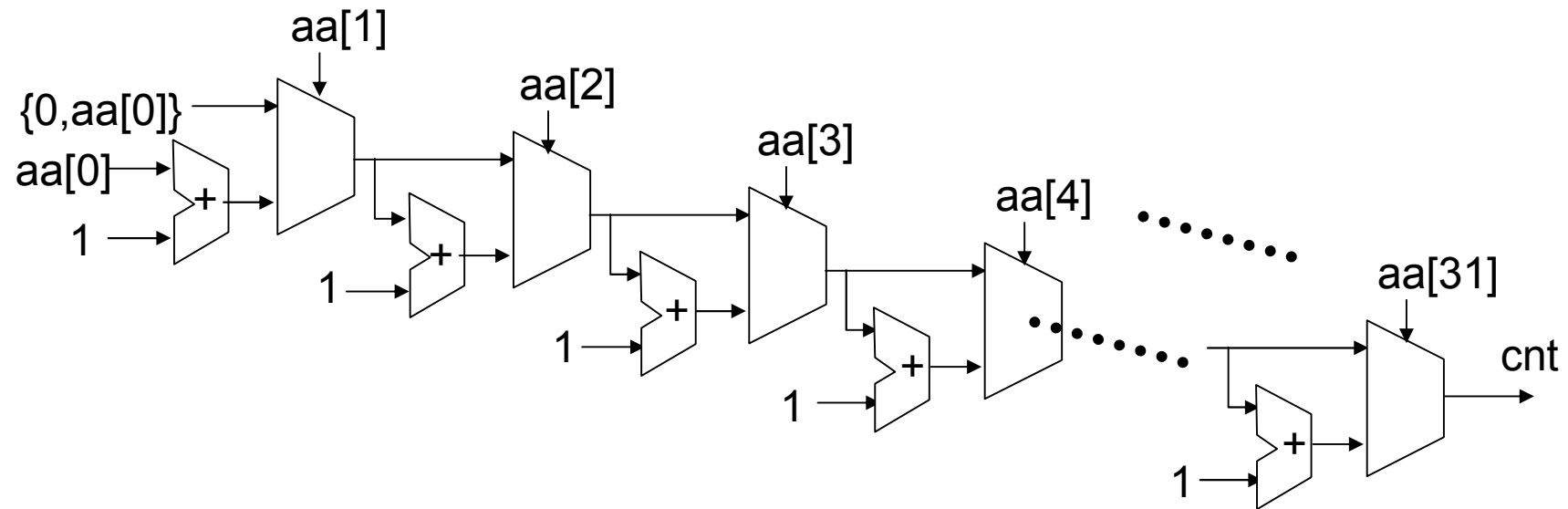

This gate diagram can not be minimized very much even if we apply optimization.

	Before optimization	After optimization		
		min area	min delay	min both
Area	1	0.77	0.66	0.63
Delay	1	0.77	0.32	0.32

The values are normalized to 1.

This shows that the coding style on the previous page is not suitable for synthesis and optimization.

Next, let's think logic to count on-bit without using for loop.

Divide 32-bit data into 8 4-bit data and apply a counting logic to each of 8 4-bit data and sum up them to calculate on-bit count for a given 32-bit data as shown below.

```
function [2:0] on_in_4 ;
input [3:0] aa ;
begin
  on_in_4 = aa[3] + aa[2] + aa[1] + aa[0] ;
end
endfunction
```

```
assign temp_31_24 = on_in_4(sig_in[31:28]) + on_in_4(sig_in[27:24]) ;
assign temp_23_16 = on_in_4(sig_in[23:20]) + on_in_4(sig_in[19:16]) ;
assign temp_15_8 = on_in_4(sig_in[15:12]) + on_in_4(sig_in[11:8]) ;
assign temp_7_0 = on_in_4(sig_in[7:4]) + on_in_4(sig_in[3:0]) ;
```

```
assign temp_31_16 = temp_31_24 + temp_23_16 ;
assign temp_15_0 = temp_15_8 + temp_7_0 ;
assign on_cnt = temp_31_16 + temp_15_0 ;
```


The coding style in the previous page is suitable for optimization, and we can get good result as shown below.

		Before	After optimization		
			min area	min delay	min both
<pre>for (k=0; k<32; K=k+1) if (a[k]) cnt=cnt+1</pre>	Area	1	0.77	0.66	0.63
	Delay	1	0.77	0.32	0.32
<pre>function cnt = a[3]+a[2]+a[1]+a[0]; endfunction</pre>	Area	0.22	0.20	0.46	0.43
	Delay	0.17	0.16	0.11	0.11

The values are normalized to 1.

Next, let's take a different method to count on-bit. Again 32-bit data is divided into 8 4-bit data, but counting uses a different method as shown below.

```
function [2:0] on_in_4 ;
input [3:0] aa ;
begin
case ( aa[3:0] )
4'b0000 : begin on_in_4 = 0 ; end
4'b1000, 4'b0100, 4'b0010,
4'b0001 : begin on_in_4 = 1 ; end
4'b1100, 4'b1010, 4'b1001, 4'b0110, 4'b0101,
4'b0011 : begin on_in_4 = 2 ; end
4'b1110, 4'b1101, 4'b1011,
4'b0111 : begin on_in_4 = 3 ; end
4'b1111 : begin on_in_4 = 4 ; end
endcase
end
endfunction
```

This looks like huge logic and a little bit complicated, but it is not a big problem for synthesis tools. They can handle this style very well and generate compact gate diagram as small and as fast as $on_in_4 = aa[3] + aa[2] + aa[1] + aa[0]$.

The code in the previous page result in the bottom lines of the table below. It is known that the style can get good gate diagram after optimization. We can see that even if a source code looks huge, if the style is suitable for optimization, we can get compact gate diagram from such large code.

		Before	After optimization		
			min area	min delay	min both
for (k=0; k<32; K=k+1) if (a[k]) cnt=cnt+1	Area	1	0.77	0.64	0.62
	Delay	1	0.77	0.32	0.32
function cnt = a[3]+a[2]+a[1]+a[0]; endfunction	Area	0.22	0.20	0.46	0.43
	Delay	0.17	0.16	0.11	0.11
function case (a) 4'b0000 : cnt=o ; 4'b1000, ,,	Area	1.34	0.24	0.50	0.49
	Delay	0.17	0.16	0.10	0.16

The values are normalized to 1.

By the way,

```
begin
  cnt = a[3]+a[2]+a[1]+a[0] ;
end
```

can be extended to the following expression.

```
begin
  cnt = a[31]+ a[30]+ a[29]+ a[28]+ a[27]+ ,,,,,,,+ a[2]+a[1]+a[0] ;
end
```

The above code can be mapped into the following for loop.

```
integer k ;
cnt = 0 ;
for ( k = 0 ; k < 32 ; k = k +1 ) begin
  cnt = cnt + a[k] ;
end
```

Now, let's see what the synthesis result of this code shall be.

The code in the previous page result in the bottom lines of the table below.

```

    cnt = 0 ;
    for ( k = 0 ; k < 32 ; k = k +1 ) begin
        cnt = cnt + a[k] ;
    end


```

		Before	After optimization			
			min area	min delay	min both	
for (k=0; k<32; K=k+1) if (a[k]) cnt=cnt+1	Area	1	0.77	0.64	0.62	Not good!!
	Delay	1	0.77	0.32	0.32	
function cnt = a[3]+a[2]+a[1]+a[0]; endfunction	Area	0.22	0.20	0.46	0.43	Better, same level
	Delay	0.17	0.16	0.11	0.11	
function case (a) 4'b0000 : cnt=o ; 4'b1000, ,,	Area	1.34	0.24	0.50	0.49	
	Delay	0.17	0.16	0.10	0.16	
for (k=0; k<32; K=k+1) cnt=cnt+1	Area	0.18	0.19	0.50	0.48	
	Delay	0.16	0.16	0.10	0.10	

The values are normalized to 1.

Coding example.

```
module cnt_on_bit ( sig_in, on_cnt ) ;  
input [31:0] sig_in ;  
output [5:0] on_cnt ;  
wire [31:0] sig_in ;  
wire [5:0] on_cnt ;  
wire [3:0] temp_31_24, temp_23_16, temp_15_8, temp_7_0 ;  
wire [4:0] temp_31_16, temp_15_0 ;  
  
assign temp_31_24 = cnt(sig_in[31:28]) + cnt(sig_in[27:24]) ;  
assign temp_23_16 = cnt(sig_in[23:20]) + cnt(sig_in[19:16]) ;  
assign temp_15_8 = cnt(sig_in[15:12]) + cnt(sig_in[11:8]) ;  
assign temp_7_0 = cnt(sig_in[7:4]) + cnt(sig_in[3:0]) ;  
  
assign temp_31_16 = temp_31_24 + temp_23_16 ;  
assign temp_15_0 = temp_15_8 + temp_7_0 ;  
assign on_cnt = temp_31_16 + temp_15_0 ;
```



Note that LHS has one bit larger bit width than that of RHS to catch carry bit.

Case style is taken for this example.



```
function [2:0] cnt ;  
input [3:0] aa;  
begin  
  case ( aa )  
    4'b0000 : begin cnt = 0 ; end  
    4'b1000, 4'b0100, 4'b0010,  
    4'b0001 : begin cnt = 1 ; end  
    4'b1100, 4'b1010, 4'b1001,  
    4'b0110, 4'b0101,  
    4'b0011 : begin cnt = 2 ; end  
    4'b1110, 4'b1101, 4'b1011,  
    4'b0111 : begin cnt = 3 ; end  
    4'b1111 : begin cnt = 4 ; end  
    default : begin cnt = 3'bxxx ; end  
  endcase  
end  
endfunction  
  
endmodule
```

file name: cnt_on_bit.v

Ex 5-2. On-bit-block counter: Write a module which counts a number of on-bit blocks in a given 32-bit input signal sig_in and output the count onto a 6-bit output signal on_cnt.

Continuously-on-bits are counted as one block. An isolated on-bit whose adjacent bit is 0 must not be counted as one block.

If 32-bit input is 32'b1100_0101_0101_1101_1111_0000_1010_1110 then the output must be 4 (a block 11, another block 1_11, another block 1_1111, and the other block 111, total 4 blocks.).

If the input is 32'hffff_ffff_0000_0000 then the output must be 1.

To build up your RTL programming power, "think and try oneself" is the best. However "Simulation result OK does not mean the code is OK."

Therefore, you must show or submit your code to elder generation engineers or supporters to see if your code is really OK or not.

No sample answer is given for this exercise.

Chapter 6. Advanced exercises

There are many solutions for these exercises. Depending on what criteria, power consumption, speed, or area size, we think important, the best implementation is different.


For the exercises in this chapter, first try to write a code without looking into sample answers.

Work flow for solutions

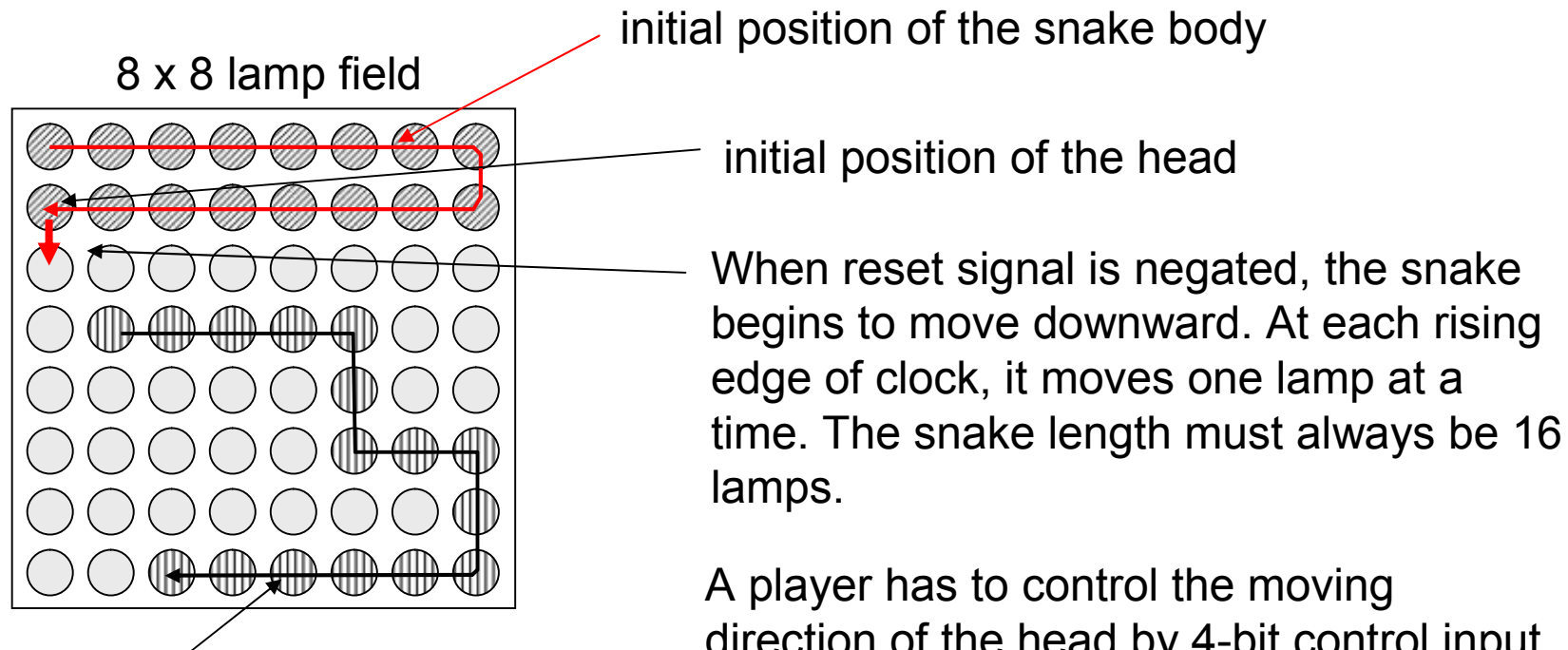- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document including a state transition table,
- (4) Write a RTL code for the target module,
- (5) Write a test bench to test the target module, and
- (6) Run the test bench with the target module to check the logic,
- (7) Study a sample code and run it.

Some exercises has sample test benches. **Your code is not OK if it is rejected by the sample test bench.**

Ex 6-1. Snake game : Design a module to control a snake moving around in 8x8 lamp field. Moving direction is controlled by 4-bit `ctl_dir` input. Game shall stop when the snake hits a wall or its body.




This snake is just for example. There shall be only one snake in the lamp field.


A player has to control the moving direction of the head by 4-bit control input `ctl_dir`.

The game ends if the head can not move any more. The head can neither go out of the lamp field nor cross its body.


An example of the movement is shown below.

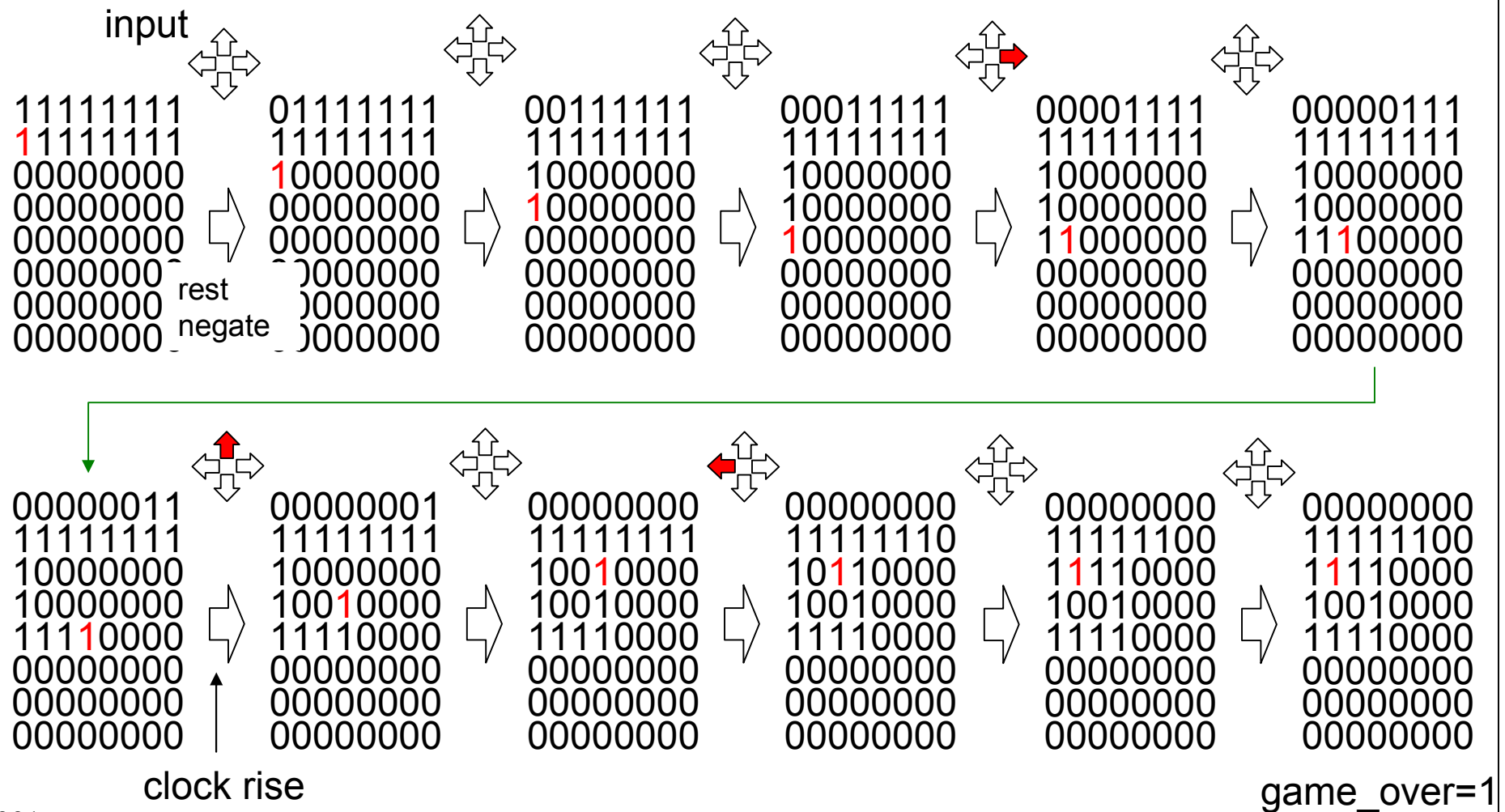1 means lamp on, and 0 means off. The on lamps represent shake body.
It moves one lamp at clock rise time as shown below.



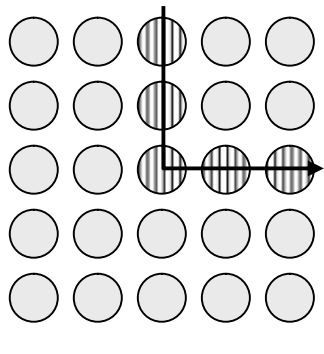


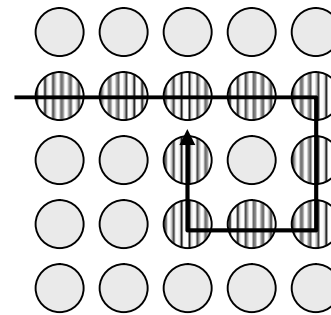game ends unless
the head is
controlled to go
up or down.




game end unless
the head is
controlled to go
left or right.

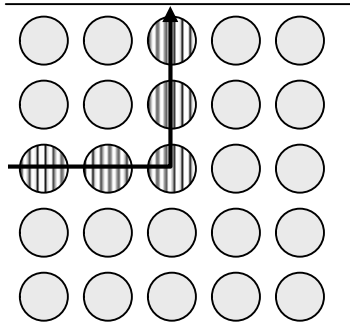(go_right will end
up "game over" in
the next clock cycle
in this case.)




game ends
unless the head
is controlled to
go right or left.

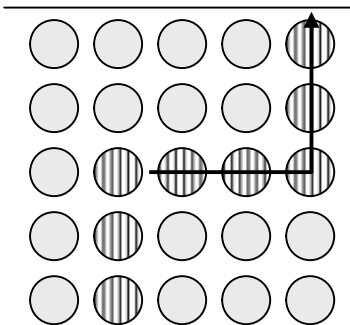
The head can move at most three directions
as shown below. It can not go back. If go
backward input given, the game is over.



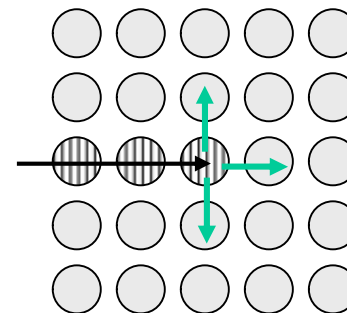game end unless
the head is
controlled to go
left.



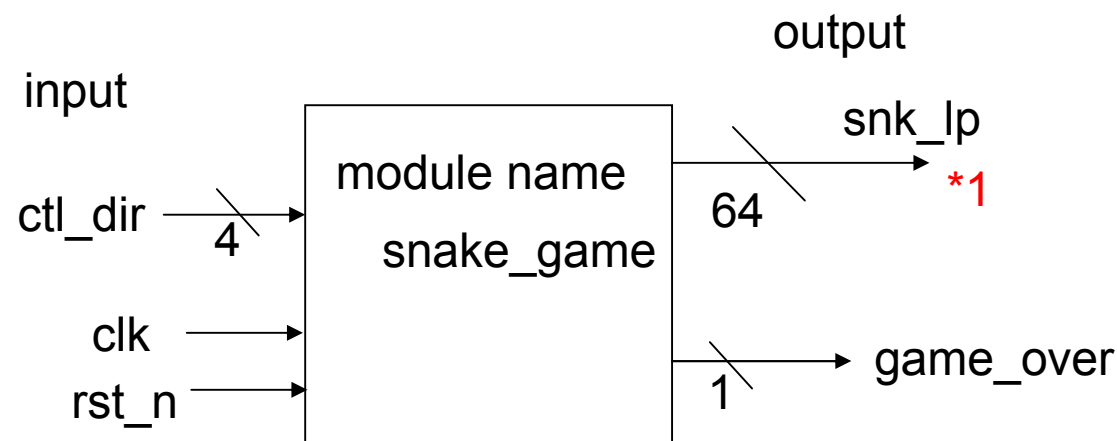
—————→ : snake's current moving direction
—————→ : movable direction



When game_over is asserted, the snake must stop moving and keep its position until reset asserted.

game_over does not become 0 once it is asserted unless reset asserted.

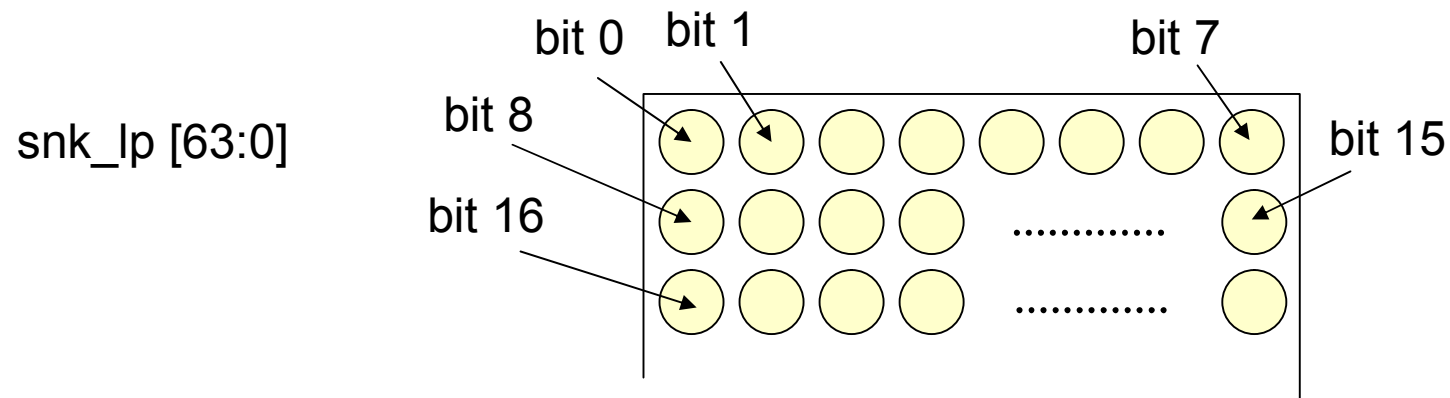*1: In Verilog1995, array can not be used as a port. Therefore, output is defined as 8x8=64-bit length vector data. Each bit represents one lamp in the lamp field. Bit 0 corresponds to upper right corner lamp, bit 7 to upper left corner, bit 56 to bottom right corner, and bit 63 to bottom left corner lamp as shown below.



Detailed specification

(1) The initial position of the snake is: its head at bit-8 (`snk_lp[8]`), neck at bit-9 (`snk_lp[9]`), and the rest of the body at bit-10, bit-11, bit-12, bit-13, bit-14, bit-15, and bit-7, bit-6, bit-5, bit-4, bit-3, bit-2, bit-1, and end at the tail bit-0 (`snk_lp[0]`).

(2) When moving, the head can move only in one direction at a time, it is up, down, left or right. The rest of the body must go through the point where its head passed. It can not slide aside. All the body parts must follow the path which the preceding body part passed. All the body move one lamp at clock rise time.

(3) If there is a field edge or its body ahead and moving into the current direction will cause the head out of the field or collide into its body, `game_over` shall be asserted and the snake must stop at current position. Once asserted, `game_over` can be reset only by reset signal, `rst_n`.

Detailed specification (continued)

(4) While reset asserted, the snake must be at the initial position and `game_over` shall be 0. At the first rise edge of the clock after reset negated, the snake must start moving automatically.

(5) The moving direction is controlled by the 4-bit input `ctl_dir`. Bit-3 of `ctl_dir` represents up direction, bit-2 down, bit-1 left, and bit-0 right, respectively. When all bits are 0, the moving direction in the previous clock cycle is used. If any one bit of `ctl_dir` is 1, the moving direction is a direction represented by the bit. No more than 1 bit of `ctl_dir` shall be on at the same time.

(6) Right after reset negated, the moving direction must be down, unless directed by `ctl_dir`. (Note, that if `ctl_dir` is not 4'b0000 nor 4'b0100, `game_over` will be asserted, because the snake can not move in the direction other than down.)


clk : 1-bit input signal, clock

rst_n : 1-bit input signal, asynchronous reset, active low

ctl_dir : 4-bit input signal, active high, synchronous to the clock

game_over : 1-bit output signal, active high, synchronous to the clock

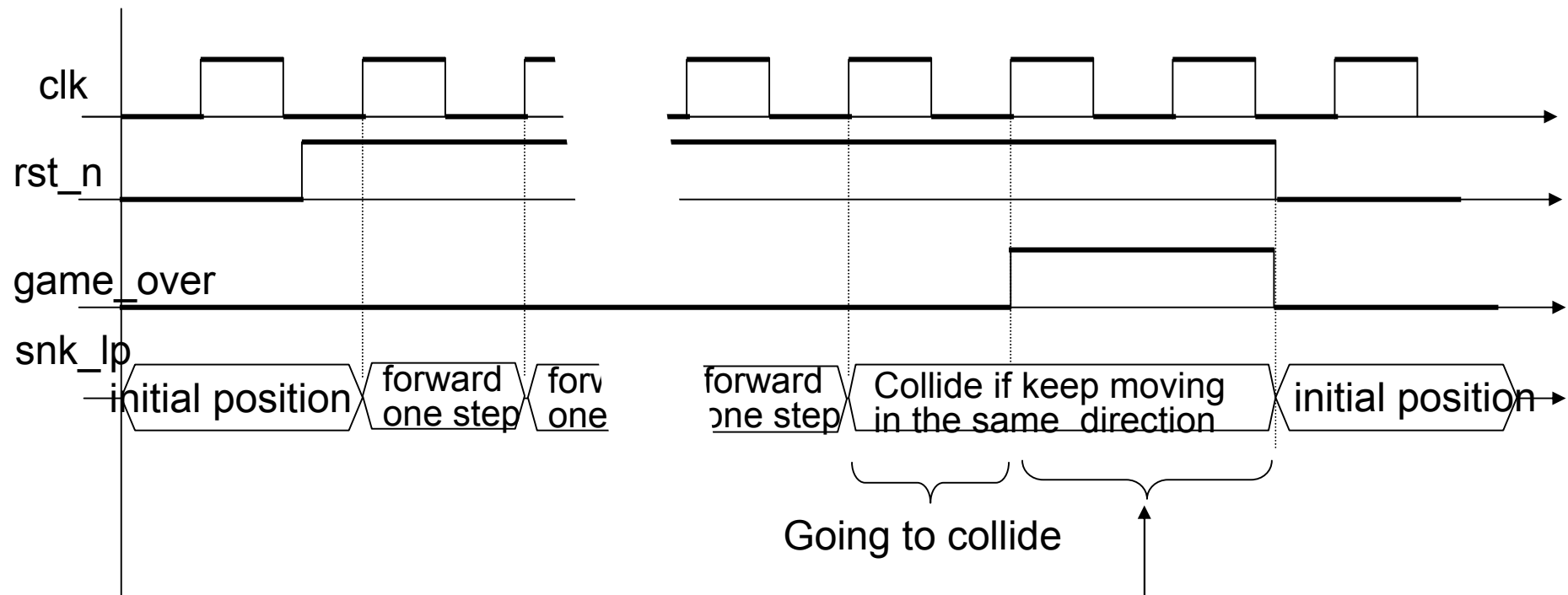snk_lp : 64-bit output signal, active high, synchronous to the clock



If keep moving into the current direction, the snake will collide its body or go out of the field. However, it is stopped with `game_over` asserted.

Note on the implementation

There are many ways on implementation. You can choose whichever you like.

However, `game_over` and `snk_lp` must be FF direct output. You must not make `game_over` nor `snk_lp` as output of combinational logic.

Work flow for solutions

- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document including a state transition table,
- (4) Write a RTL code for the target module,
- (5) Run **the automatic test bench** on the next pages with the target module you created.

If your code is rejected, correct your code.

Copy and paste the test bench module on the next pages into you PC and run it with your snake_game module to see if your code is OK or Not.

If your code is OK, it will output the following message on to your terminal screen.

```
pass test13,  
hit body from left  
test end no error detected
```

A sample test bench, automatic tester

```

`timescale 1ns/100ps
module test_snake_game ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL * 2 ;
parameter FLD_BW = 8 ;
parameter NUM_LP = FLD_BW * FLD_BW ;
parameter DIR_BW = 4 ;
reg rst_n, clk ;
reg [DIR_BW-1:0] ctl_dir ;
wire game_over ;
wire [NUM_LP-1:0] snk_lamp ;
wire [FLD_BW-1:0] tmp_lp_0, tmp_lp_1, tmp_lp_2, tmp_lp_3,
                    tmp_lp_4, tmp_lp_5, tmp_lp_6, tmp_lp_7 ;
wire [FLD_BW-1:0] lp_0, lp_1, lp_2, lp_3, lp_4, lp_5, lp_6, lp_7 ;
reg show_lamp ; // control flag to show lamp on screen, if 0 lamps are not
                // displayed on the screen at each clock rise time
integer kk ; // for loop counter
//
assign { tmp_lp_7, tmp_lp_6, tmp_lp_5, tmp_lp_4,
        tmp_lp_3, tmp_lp_2, tmp_lp_1, tmp_lp_0 } = snk_lamp ;
function [FLD_BW-1:0] bit_swap;
input [FLD_BW-1:0] in_a ;
reg [FLD_BW-1:0] temp ;
begin
    for ( kk = 0; kk <= FLD_BW-1; kk = kk+1 ) begin
        temp[kk] = in_a[FLD_BW-kk-1] ;
    end
    bit_swap = temp ;
end
endfunction


```


Do not change this part.

temporary work for bit swap

Disintegrate 64-bit signal into 8 8-bit signals

bit swap function





```

assign lp_7 = bit_swap(tmp_lp_7);
assign lp_6 = bit_swap(tmp_lp_6);
assign lp_5 = bit_swap(tmp_lp_5);
assign lp_4 = bit_swap(tmp_lp_4);
assign lp_3 = bit_swap(tmp_lp_3);
assign lp_2 = bit_swap(tmp_lp_2);
assign lp_1 = bit_swap(tmp_lp_1);
assign lp_0 = bit_swap(tmp_lp_0);
//

```

bit swap operation

```

// connect signals to game
snake_game snake_game_01 ( .clk( clk ), .rst_n( rst_n ),
    .ctl_dir(ctl_dir),
    .game_over(game_over), .snk_lp(snk_lp)
);

```

connect target module

```

// connection end

```

```

always @ ( posedge clk ) begin

```

```

#1.1 ;

```

```

if ( show_lamp == 1 ) begin

```

```

    $strobe (

```

```

        "t=%0d, r=%b, ctl_dir=%b, game_ovr=%b¥n 0=%b ¥n 1=%b ¥n 2=%b ¥n 3=%b ¥n 4=%b ¥n 5=%b
        ¥n 6=%b ¥n 7=%b ¥n ",

```

```

        $stime, rst_n, ctl_dir, game_over,
        lp_0, lp_1, lp_2, lp_3, lp_4, lp_5, lp_6, lp_7 );

```

```

    end
end

```

```

always begin // clock generator

```

```

    clk = 1'b0 ; # HF_CYCL ;

```

```

    clk = 1'b1 ; # HF_CYCL ;

```

```

end

```

clock
generator

Control display or not, by show_lamp flag


This must be written in one line.

`initial begin`
`show_lamp = 1 ;`
`// test1, run into wall at start`
`ctl_dir = 4'b0010 ; // run to left wall to cause game over`
`rst_n = 0 ;`
`$display("start test1,¥n run into wall at start") ;`
`#(CYCL * 2) ;`
`#CYCL rst_n = 1 ;`
`@(posedge clk) #1.2 ;`
`chcker (1'b1, 64'h00_00_00_00_00_00_ff_ff) ;`
`$display("pass test1,¥n run into wall at start") ;`

`// test2, go back at start`
`ctl_dir = 4'b0010 ; // go to left to cause game over`
`rst_n = 0 ;`
`$display("start test2,¥n go back at start") ;`
`#CYCL rst_n = 1 ;`
`@(posedge clk) #1.2 ;`
`chcker (1'b1, 64'h00_00_00_00_00_00_ff_ff) ;`
`$display("pass test2,¥n go back at start") ;`


test1

game over

 

test2

game over

 


↙

```
// test3, game over running into right wall
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test3, game over running into right wall");
#CYCL rst_n = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_ff_fe ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_01_ff_fc ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_01_01_01_ff_f8 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_01_01_01_01_ff_f0 ) ;
ctl_dir = 4'b0001 ; // go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_03_01_01_01_ff_e0 ) ;
ctl_dir = 4'b0000 ; // keep go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_07_01_01_01_ff_c0 ) ;
ctl_dir = 4'b0000 ; // keep go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_0f_01_01_01_ff_80 ) ;
ctl_dir = 4'b0000 ; // keep go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_1f_01_01_01_ff_00 ) ;
ctl_dir = 4'b0000 ; // keep go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_3f_01_01_01_7f_00 ) ;
ctl_dir = 4'b0000 ; // keep go right to hit wall
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_7f_01_01_01_3f_00 ) ;
```

↘

test3

 


game over

```

    ctl_dir = 4'b0000 ; // keep go right to hit wall
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_00_ff_01_01_01_1f_00 ) ;
    ctl_dir = 4'b0000 ; // keep go right to hit wall
    @( posedge clk ) #1.2 ;
    chcker ( 1'b1, 64'h00_00_ff_01_01_01_1f_00 ) ;
    ctl_dir = 4'b0000 ; // keep go right to hit wall
    $display("pass test3,¥n game over running into right wall");

// test4, game over running into bottom wall
    @( posedge clk ) #1.2 ;
    ctl_dir = 4'b0000 ;
    rst_n = 0 ;
    $display("start test4,¥n game over running into bottom wall");
    #CYCL rst_n = 1 ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_00_00_00_00_01_ff_fe ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_00_00_00_01_01_ff_fc ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_00_00_01_01_01_ff_f8 ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_00_01_01_01_01_ff_f0 ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h00_01_01_01_01_01_ff_e0 ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b0, 64'h01_01_01_01_01_01_ff_c0 ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b1, 64'h01_01_01_01_01_01_ff_c0 ) ;
    @( posedge clk ) #1.2 ;
    chcker ( 1'b1, 64'h01_01_01_01_01_01_ff_c0 ) ;
    $display("pass test4,¥n game over running into bottom wall");

```

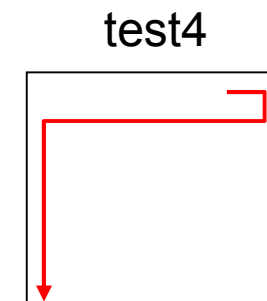


game over

```

// test5, down and left and go into bottom wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test5,¥n down and right and go into bottom wall") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_ff_fe ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_01_ff_fc ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_01_01_01_ff_f8 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_01_01_01_01_ff_f0 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_01_01_01_01_01_ff_e0 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h01_01_01_01_01_01_ff_c0 ) ;
show_lamp = 1 ;
#3 ctl_dir = 4'b0001 ; // go right
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h03_01_01_01_01_01_ff_80 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h07_01_01_01_01_01_ff_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h0f_01_01_01_01_01_7f_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h1f_01_01_01_01_01_3f_00 ) ;
#3 ctl_dir = 4'b0100 ; // go down to hit bottom wall
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h1f_01_01_01_01_01_3f_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h1f_01_01_01_01_01_3f_00 ) ;
$display("pass test5,¥n down and left and go into bottom wall")


```

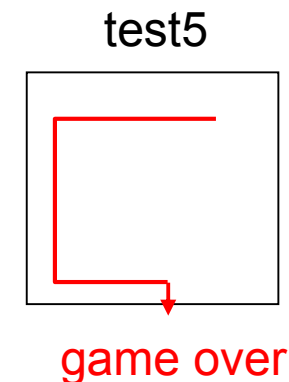

↙

```
// test6, down and left and go into left wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test6,¥n down and run into left wall") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_ff_fe ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_00_01_01_ff_fc ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_01_01_01_ff_f8 ) ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_01_01_01_01_ff_f0 ) ;
#3 ctl_dir = 4'b0010 ; // go left
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_00_01_01_01_01_ff_f0 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_00_01_01_01_01_ff_f0 ) ;
$display("pass test6,¥n down and run into left wall") ;
```

↘

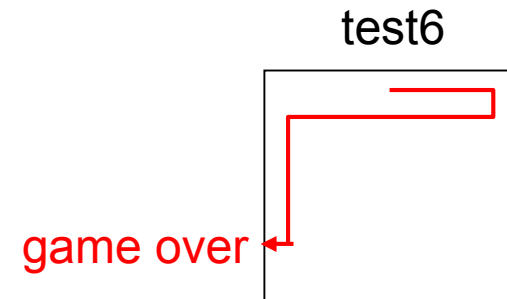


↙

```
// test7, down and left and up and go into left wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test7,¥n down and right and run into upt wall") ;
show_lamp = 1 ;
#CYCL rst_n = 1 ;
#( CYCL * 6 ) ctl_dir = 4'b0001 ;
#( CYCL * 7 ) ctl_dir = 4'b1000 ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_01_01_01_01_03_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_01_01_01_01_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_81_01_01_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_81_81_00_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_81_80_80_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_80_80_80_80_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_80_80_80_80_80_80 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'hff_81_80_80_80_80_80_80 ) ;
$display("pass test7,¥n down and right and run into up wall") ;
```

↘


test7 game over

 

↓

```
// test8, down and left and up and into top wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test8,¥n down and rigth and up and run into right wall") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
#( CYCL * 6 ) #1.2 ctl_dir = 4'b0001 ;
#( CYCL * 7 ) #1.2 ctl_dir = 4'b1000 ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_01_01_01_01_03_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_01_01_01_01_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_81_01_01_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'hff_81_81_81_81_00_00_00 ) ;
#3 ctl_dir = 4'b0001 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'hff_81_81_81_81_00_00_00 ) ;
$display("pass test8,¥n down and left and up and into top wall") ;
```

↓

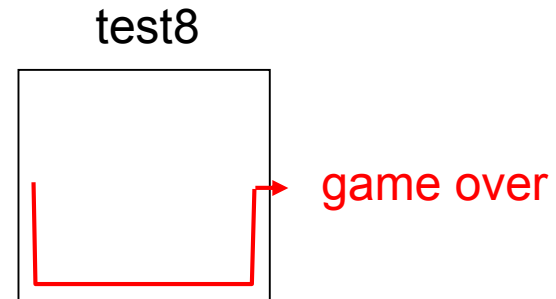




```
// test9, down and left and up and right and go into top wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test9,¥n down and right and up and left and hit body") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
#( CYCL * 5 ) ctl_dir = 4'b0001 ;
#( CYCL * 4 ) ctl_dir = 4'b1000 ;
#( CYCL * 3 ) ctl_dir = 4'b0010 ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_1f_11_11_19_01_07_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_1f_11_11_1d_01_03_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_1f_11_11_1f_01_01_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_1f_11_11_1f_01_01_00 ) ;
$display("pass test9,¥n down and left and up and right and go into top wall") ;
```



test9


game over

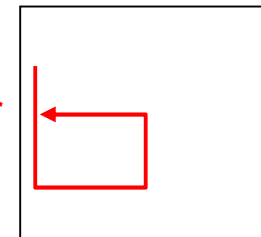

↓

```
// test10, down and left and up and right into right wall
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test10,¥n down and right and up and left and down and through tail and runinto bottom wall") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
#( CYCL * 4 ) ctl_dir = 4'b0001 ;
#( CYCL * 6 ) ctl_dir = 4'b1000 ;
#( CYCL * 5 ) ctl_dir = 4'b0010 ;
#( CYCL * 3 ) ctl_dir = 4'b0100 ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_7f_40_40_40_48_78 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_7e_40_40_48_48_78 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_7c_40_48_48_48_78 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_78_48_48_48_48_78 ) ; // through tail
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_78_48_48_48_48_78 ) ; // head into tail
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_08_68_48_48_48_48_78 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h08_08_48_48_48_48_48_78 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h08_08_48_48_48_48_48_78 ) ;
$display("pass test10,¥n down and right and up and left and down and through tail and runinto bottom wall") ;
```

↓

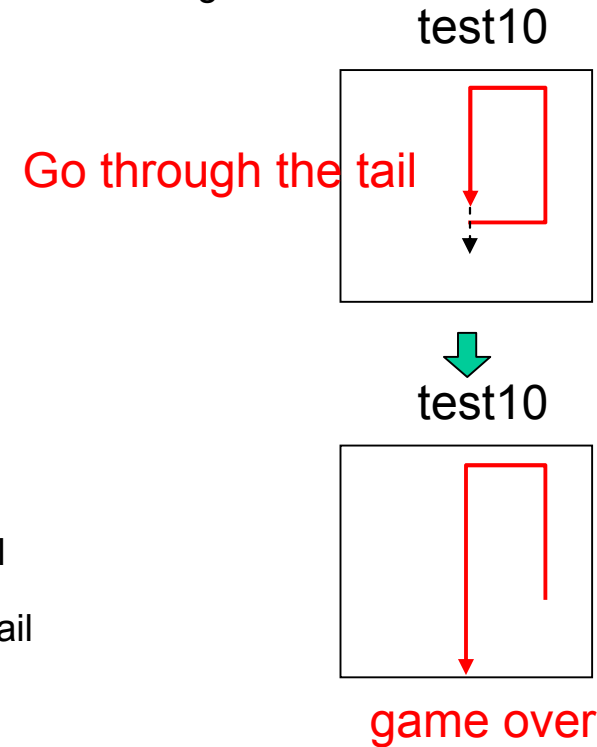


↘

```
// test11, through tail from down and hit body from up
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test11,¥n through tail from down and hit body from up") ;
show_lamp = 0 ;
#CYCL rst_n = 1 ;
#( CYCL * 1 ) ctl_dir = 4'b0001 ;
#( CYCL * 6 ) ctl_dir = 4'b0100 ;
#( CYCL * 2 ) ctl_dir = 4'b0010 ;
#( CYCL * 4 ) ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7e_40_7f_03_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_40_7f_01_00 ) ;
#3 ctl_dir = 4'b1000 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_7f_00_00 ) ; // hit tail from down
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_7f_00_00 ) ; // through tail
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_7d_01_00 ) ;
```


↘

Go through the tail

test11

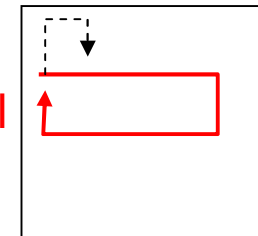

test11

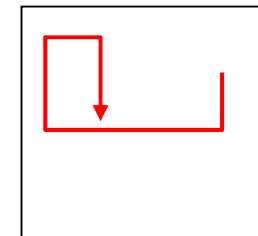

game over

↓


```

#3 ctl_dir = 4'b0001 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_79_03_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_71_07_00 ) ;
#3 ctl_dir = 4'b0100 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_41_65_07_00 ) ;
#3 ctl_dir = 4'b0000 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_00_00_7f_45_45_07_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_00_00_7f_45_45_07_00 ) ; // hit body from up
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_00_00_7f_45_45_07_00 ) ;
$display("pass test11,¥n hrough tail from down and hit body from up") ;

```

↓


test11

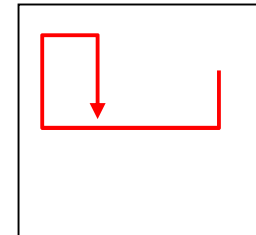

game over

// test12, through tail from left, right and hit body from down
 @(posedge clk) #1.2;
 ctl_dir = 4'b0000;
 rst_n = 0;
 \$display("start test12,¥n through tail from left, right and hit body from down");
 #CYCL rst_n = 1;
 show_lamp = 0;
 #(CYCL * 1) ctl_dir = 4'b0001;
 #(CYCL * 6) ctl_dir = 4'b0100;
 #(CYCL * 5) ctl_dir = 4'b0010;
 #(CYCL * 5) ctl_dir = 4'b1000;
 #(CYCL * 3) ctl_dir = 4'b0001;
 #(CYCL * 2);
 show_lamp = 1;
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h7e_42_42_5e_40_00_00_00);
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h7e_42_42_7e_00_00_00_00); // hit tail from left
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h7e_42_42_7e_00_00_00_00); // through tail
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h7e_42_02_fe_00_00_00_00);
 show_lamp = 0;
 #3 ctl_dir = 4'b0100;
 #(CYCL * 2) ctl_dir = 4'b0010;
 #(CYCL * 3);
 show_lamp = 1;
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h02_fa_82_fe_00_00_00_00);
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h00_fe_82_fe_00_00_00_00); // hit tail from right
 @(posedge clk) #1.2;
 chcker (1'b0, 64'h00_fe_82_fe_00_00_00_00); // through tail


test12

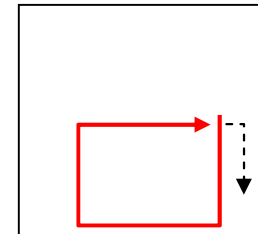

through tail




test12

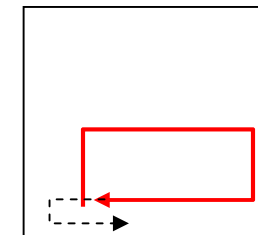

through tail






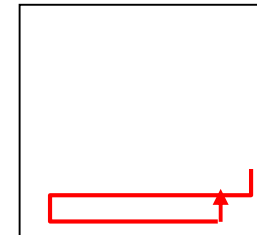
```

@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_ff_80_fe_00_00_00_00 ) ;
#3 ctl_dir = 4'b0100 ;
show_lamp = 0 ;
#( CYCL * 1 ) ctl_dir = 4'b0001 ;
#( CYCL * 3 ) ctl_dir = 4'b0000 ;
show_lamp = 1 ;
#( CYCL * 1 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h3f_ff_80_80_00_00_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h7f_ff_80_00_00_00_00_00 ) ;
#3 ctl_dir = 4'b1000 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h7f_ff_80_00_00_00_00_00 ) ;
$display("pass test12,¥n through tail from left, right and hit body from down") ;

```




test12



game over


```

// test13, hit body from left
@( posedge clk ) #1.2 ;
  ctl_dir = 4'b0000 ;
  rst_n = 0 ;
$display("start test13,¥n hit body from left") ;
#CYCL rst_n = 1 ;
show_lamp = 0 ;
#( CYCL * 1 ) ctl_dir = 4'b0001 ;
#( CYCL * 5 ) ctl_dir = 4'b0100 ;
#( CYCL * 4 ) ctl_dir = 4'b0010 ;
#( CYCL * 4 ) ctl_dir = 4'b1000 ;
#( CYCL * 2 ) ctl_dir = 4'b0001 ;
#( CYCL * 1 ) ;
show_lamp = 1 ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_3e_22_2e_20_3c_00_00 ) ;
@( posedge clk ) #1.2 ;
chcker ( 1'b0, 64'h00_3e_22_3e_20_38_00_00 ) ; // hit body from left
@( posedge clk ) #1.2 ;
chcker ( 1'b1, 64'h00_3e_22_3e_20_38_00_00 ) ; // game over
$display("pass test13,¥n hit body from left") ;

$display("test end no error detected") ;
#1 $finish ;
end

```

test13

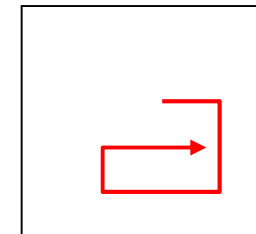

game over



This task compares the output of the target module and the expected values.

```
task chcker ;
input st ; // compare to game over
input [NUM_LP-1:0] pattn ; // compare to snk_lp

begin
  if( snk_lamp != pattn ) begin
    $display("bug stop, at t=%0d,¥n game_over=%b, snk_lamp=%h,¥n expected =%b, snk_lamp=%h¥n",
      $stime, game_over, snk_lamp, st, pattn ) ;
    #1 $finish ;
  end
  else begin
    if( st != game_over ) begin
      $display("bug stop, at t=%0d,¥n game_over=%b, snk_lamp=%h,¥n expected =%b, snk_lamp=%h¥n",
        $stime, game_over, snk_lamp, st, pattn ) ;
      #1 $finish ;
    end
  end
end
endtask


endmodule


`include "snake_game.v"
```

file name: test_snake_game.v


A sample target code

(1) How to describe the snake body

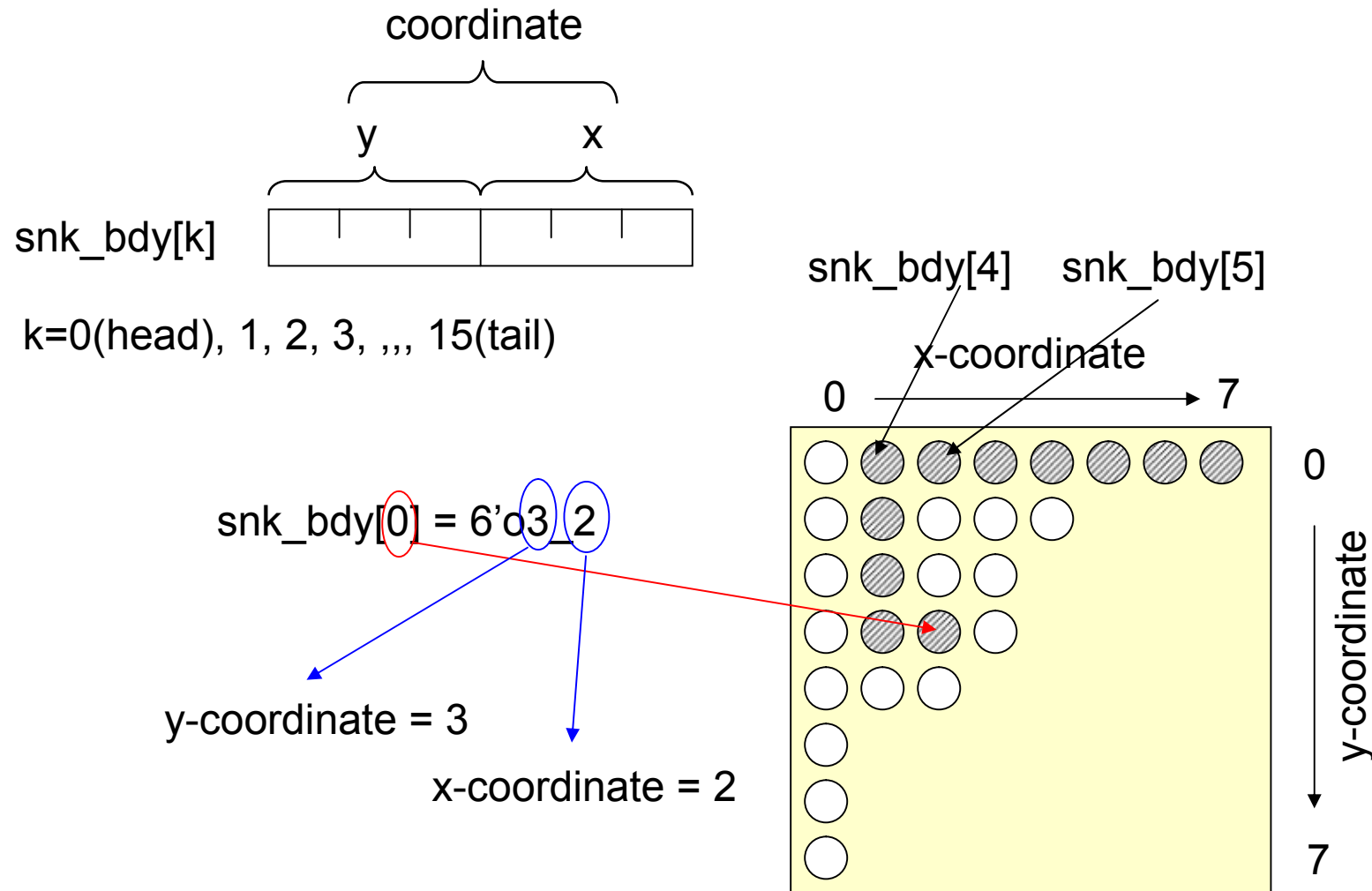

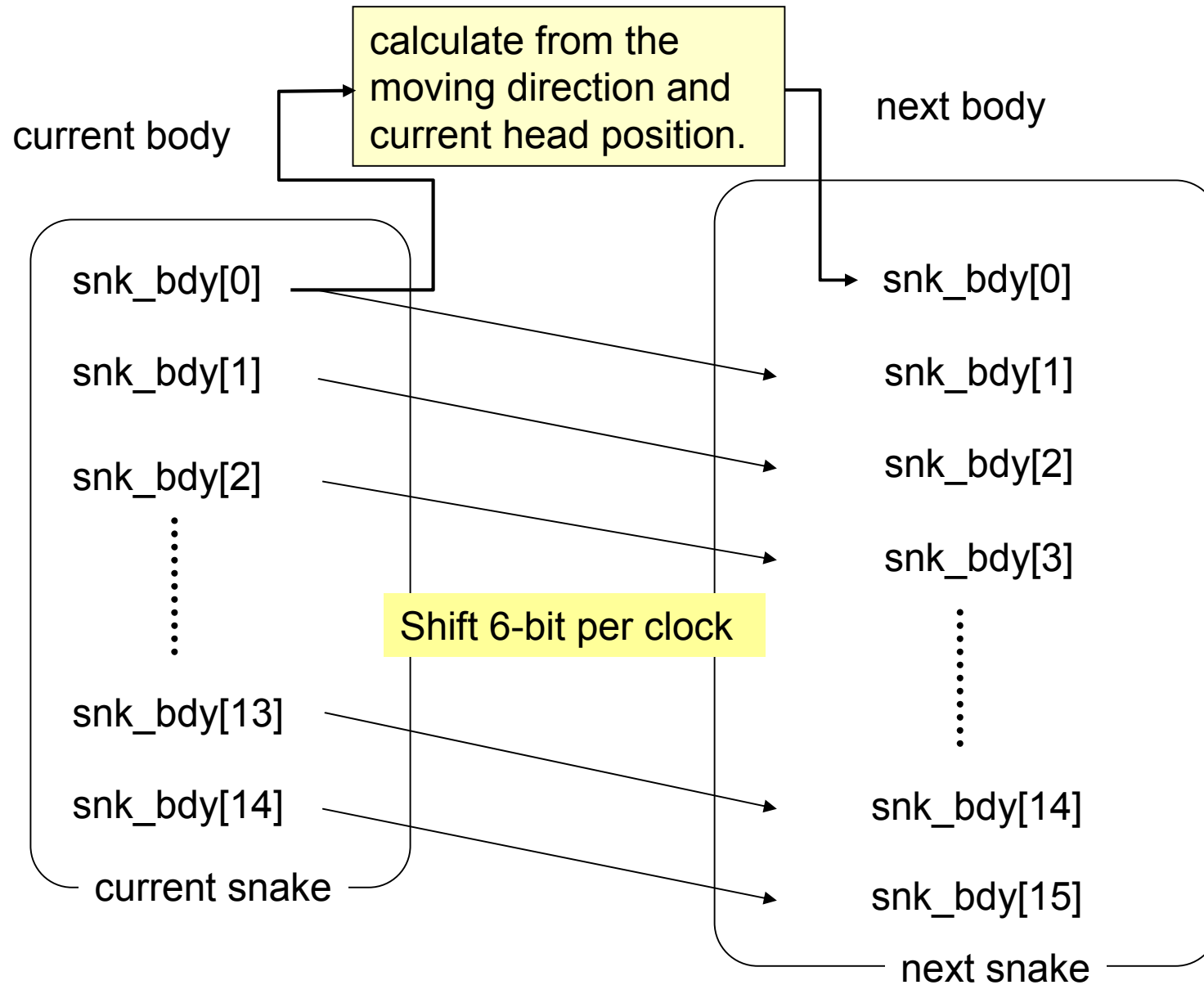


(2) How to control on/off of lamps

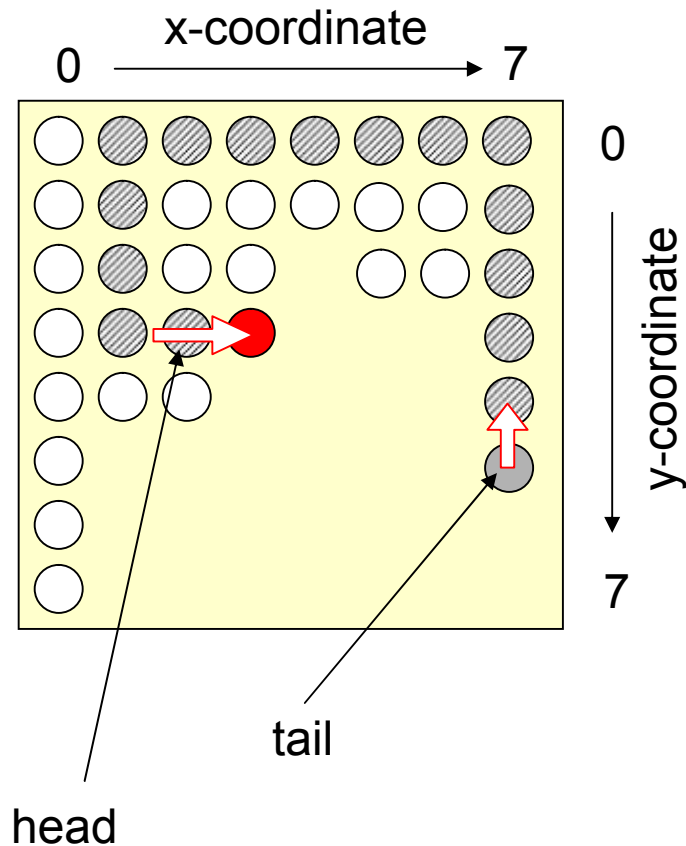

- (a) Turn on one lamp in the direction of head movement.
- (b) Turn off the lamp at the tail.
- (c) If the tail is in the direction of head movement, then keep it on.
- (d) Keep other lamps on and off as they are.

(3) How to check collision

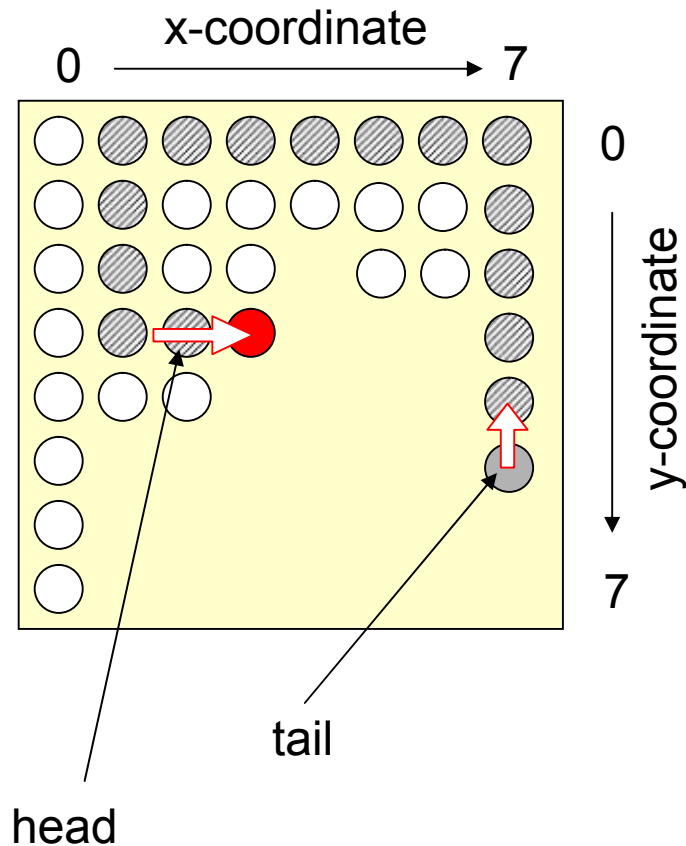



(a) Head goes out of bound.

- moving up → y-coordinate is 0
- moving down → y-coordinate is 7
- moving right → y-coordinate is 7
- moving left → x-coordinate is 0

(b) Head hit the body except the tail.


A lamp in the head moving direction is already on. If it is a tail then it is not a collision because the tail will move to another position at the next clock cycle.

(4) lamp field FF representation

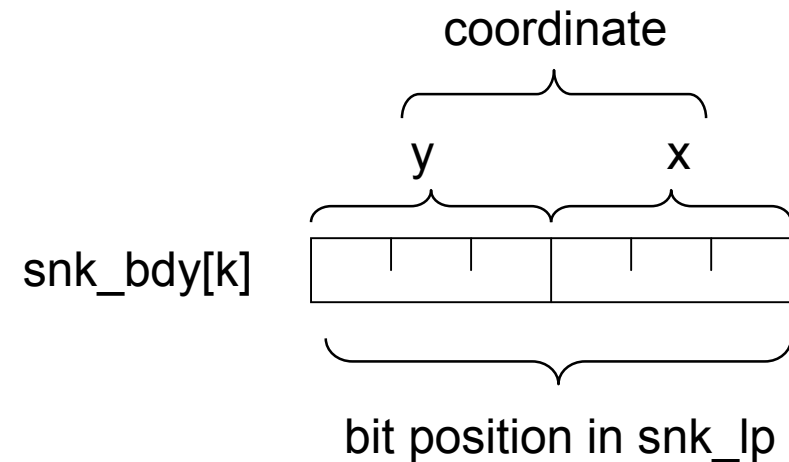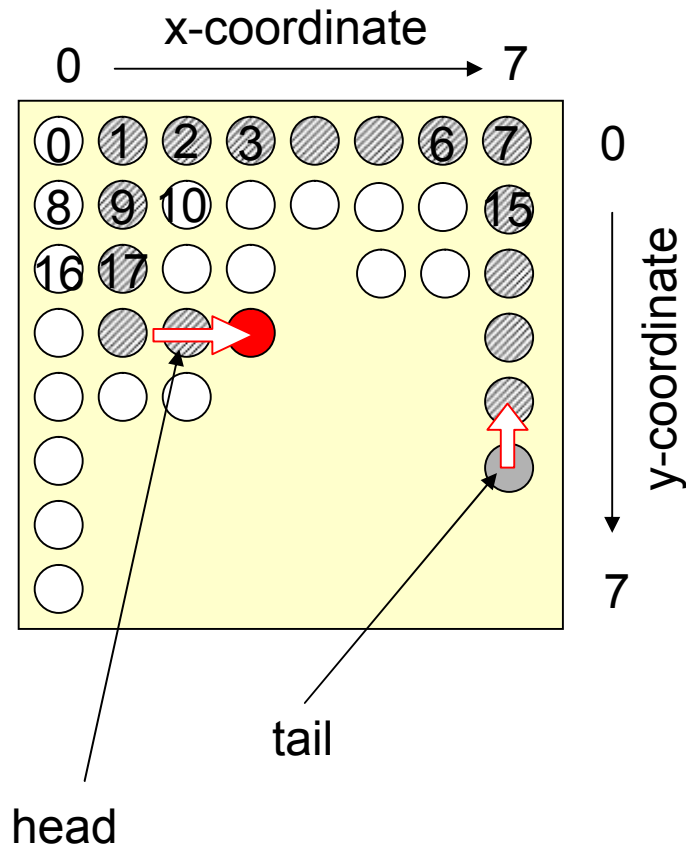

`snk_lp[snk_bdy[0]]` is a FF corresponding the snake head. And `snk_lp[snk_bdy[15]]` is a FF corresponding the snake tail.


The target module structure

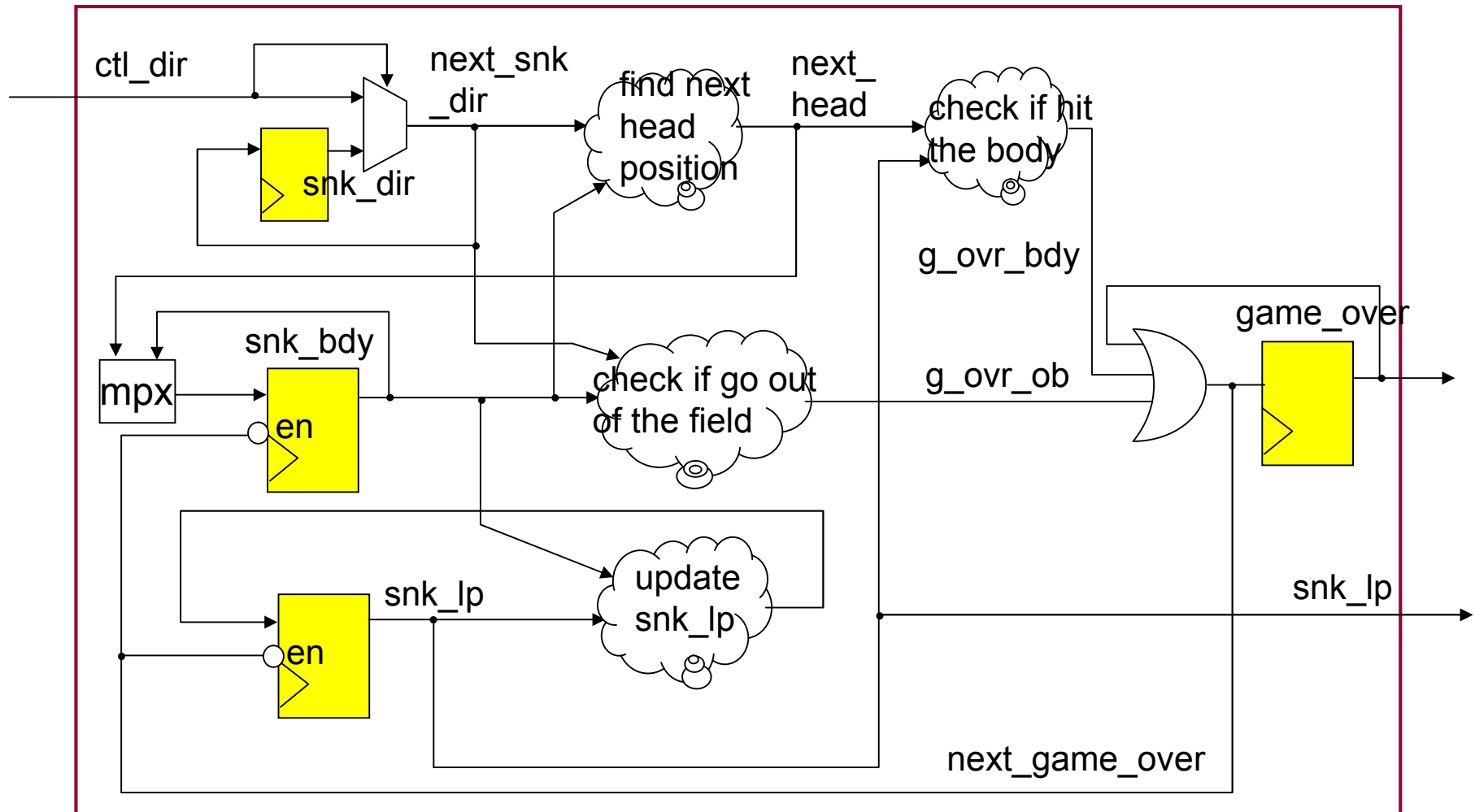


A sample target code

```
// snake game module
// (c) K. Hayashi, 2010
//
module snake_game ( clk, rst_n, ctl_dir, game_over, snk_lp ) ;
//
parameter FLD_BW = 8 ;
parameter LP_BW = FLD_BW * FLD_BW ;
parameter POSI_BW = 3 ;
parameter SNK_LNG = 16 ;
parameter SNK_BDY_BW = POSI_BW * 2 * SNK_LNG ;
parameter DIR_BW = 4 ;
parameter INTL_MV_DIR = 4'b0100 ; // first move down
//
input clk, rst_n ;
input [DIR_BW-1:0] ctl_dir ; // game input, head move direction
output game_over ;
output [LP_BW-1:0] snk_lp ;
//
wire clk, rst_n ;
wire [DIR_BW-1:0] ctl_dir ;
reg game_over ; // FF, game over flag output
reg [LP_BW-1:0] snk_lp ; // FF, on lamp means snake body
//
```





```
// internal variable
reg [DIR_BW-1:0] mv_dir ; // FF, memorized moving direction
wire[DIR_BW-1:0] next_mv_dir ; // next moving direction
wire mv_up, mv_dwn, mv_lft, mv_rgt ;
reg [POS_BW * 2 -1:0] snk_bdy [0:SNK_LNG-1] ; // FF, array for snake body
reg [POS_BW * 2 -1:0] next_head ; // non-FF for next head position
wire [POS_BW -1:0] y_head, x_head ;
reg g_ovr_ob, g_ovr_bdy ; // game over by hit body and hit wall
wire next_game_over ;
wire en ; // enable for lamp FF and snake FF
integer k ; // for-loop counter
```



```

// FF for body
always @ ( posedge clk ) begin
  if ( rst_n == 1'b0 ) begin
    snk_bdy[0] <= 6'o10 ;
    snk_bdy[1] <= 6'o11 ;
    snk_bdy[2] <= 6'o12 ;
    snk_bdy[3] <= 6'o13 ;
    snk_bdy[4] <= 6'o14 ;
    snk_bdy[5] <= 6'o15 ;
    snk_bdy[6] <= 6'o16 ;
    snk_bdy[7] <= 6'o17 ;
    snk_bdy[8] <= 6'o07 ;
    snk_bdy[9] <= 6'o06 ;
    snk_bdy[10] <= 6'o05 ;
    snk_bdy[11] <= 6'o04 ;
    snk_bdy[12] <= 6'o03 ;
    snk_bdy[13] <= 6'o02 ;
    snk_bdy[14] <= 6'o01 ;
    snk_bdy[15] <= 6'o00 ;
  end
  else begin
    if ( en == 1'b1 ) begin
      snk_bdy[0] <= next_head; // head
      for ( k = 0; k < 15; k = k+1 ) begin
        // body follow the head
        snk_bdy[k+1] <= snk_bdy[k] ;
      end
    end
  end
end
end
end

```

Set initial position of
body

If not game over, move snk_body
6-bit. Next head position is
evaluated in another always.

// next head position

assign { mv_up, mv_dwn, mv_lft, mv_rgt } = next_mv_dir ;

assign { y_head, x_head } = snk_bdy[0] ;

always @ (y_head or x_head or mv_up or mv_dwn or mv_lft or mv_rgt) begin

case (1'b1)

mv_up : begin next_head = { {y_head-1'b1} , {x_head} } ; end

mv_dwn : begin next_head = { {y_head+1'b1} , {x_head} } ; end

mv_lft : begin next_head = { {y_head} , {x_head-1'b1} } ; end

mv_rgt : begin next_head = { {y_head} , {x_head+1'b1} } ; end

default: begin next_head = {(POS1_BW * 2 -1){1'bx}} ; end

endcase

end

//

// moving direction FF

always @ (posedge clk or negedge rst_n) begin

if (rst_n == 1'b0) begin

mv_dir <= INTL_MV_DIR ; // initial direction

end

else begin

mv_dir <= next_mv_dir ;

end

end

//

assign next_mv_dir = (ctl_dir)? ctl_dir : mv_dir ;

//

calculate next
head position

FF for memorizing the
moving direction. If
ctl_dir=0, then keep
the previous direction.

// out of bound check 

```
always @ ( y_head or x_head or mv_up or mv_dwn or mv_lft or mv_rgt ) begin
```

```
  g_ovr_ob = 1'b0 ;
```

```
  case ( 1'b1 )
```

```
    mv_up : begin if ( y_head == 3'o0 ) g_ovr_ob = 1'b1 ; end
```

```
    mv_dwn : begin if ( y_head == 3'o7 ) g_ovr_ob = 1'b1 ; end
```

```
    mv_lft : begin if ( x_head == 3'o0 ) g_ovr_ob = 1'b1 ; end
```

```
    mv_rgt : begin if ( x_head == 3'o7 ) g_ovr_ob = 1'b1 ; end
```

```
    default : begin g_ovr_ob = 1'bx ; end
```

```
  endcase
```

```
end
```

// hit body check

```
always @ ( g_ovr_ob or next_head or
          snk_bdy[SNK_LNG-1] or snk_lp[next_head] ) begin
```

```
  g_ovr_bdy = 1'b0 ;
```

```
  if ( g_ovr_ob == 1'b0 ) begin
```

```
    if ( next_head != snk_bdy[SNK_LNG-1] ) begin
```

```
      // next head is not current tail
```

```
      if ( snk_lp[next_head] == 1'b1 ) begin
```

```
        g_ovr_bdy = 1'b1 ; // head hit body
```

```
      end
```

```
    end
```

```
  end
```

```
end
```



check if go out
of field.
If go out, place
1 to g_ovr_ob.

check if run into
the body.
If next_head hit
the tail, then
OK.
Otherwise,
check if hit the
body. If run into
the body, place
1 to g_ovr_bdy.

```

// game over signal
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        game_over <= 1'b0 ;
    end
    else begin
        game_over <= next_game_over ;
    end
end
//
assign next_game_over = g_ovr_bdy | g_ovr_ob | game_over ;
assign en = ~next_game_over ;
//
// field lamps
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        snk_lp <= { {(LP_BW-SNK_LNG){1'b0}}, {SNK_LNG{1'b1}} } ;
    end
    else begin
        if ( en == 1'b1 ) begin
            snk_lp[next_head] <= 1'b1 ;
            if ( next_head != snk_bdy[SNK_LNG-1] ) begin
                snk_lp[snk_bdy[SNK_LNG-1]] <= 1'b0 ;
            end
        end
    end
end
//
endmodule

```

FF for game over flag


update game over.

FF for snk_lp. update it if not game over. Turn on next head lamp, and turn off the tail lamp.

file name: snake_game


Ex 6-2. LRU algorithm: Create a module that finds out the Least Recently Used entry in the four entries specified below.

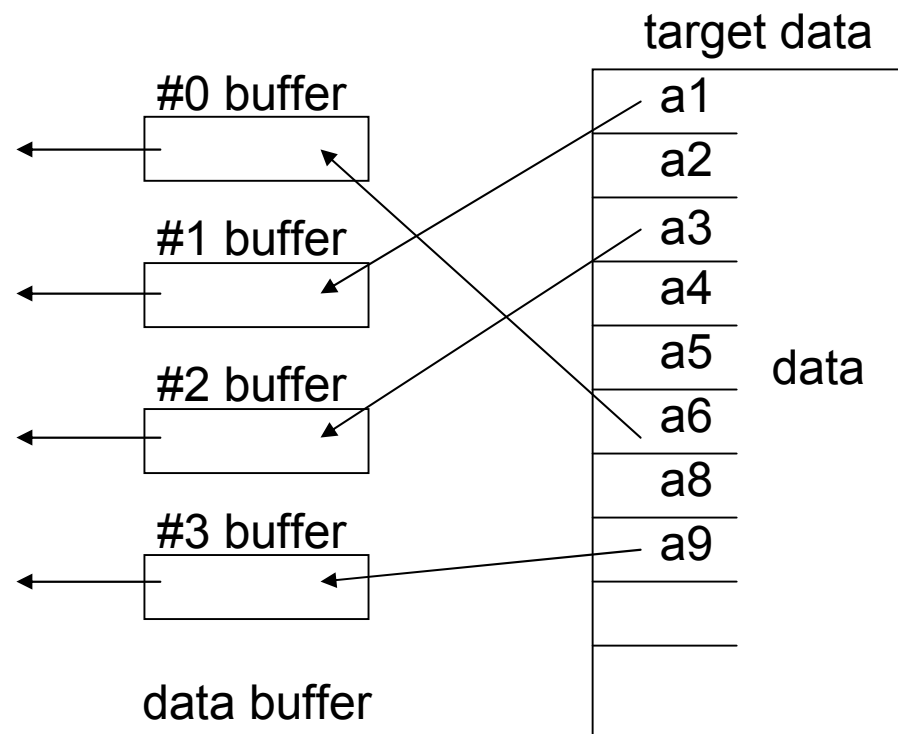The target data are accessible only through data buffers named: #0 buffer, #1 buffer, #2 buffer, and #3 buffer. The following figure shows that data a1 using #1 buffer, a3 using #2 buffer, a6 using #0 buffer, and a9 using #3 buffer. Now, if data a2 is requested, one of the buffers must be replaced for a2. To select the buffer to be replaced for the new request, apply LRU strategy.



Objective:

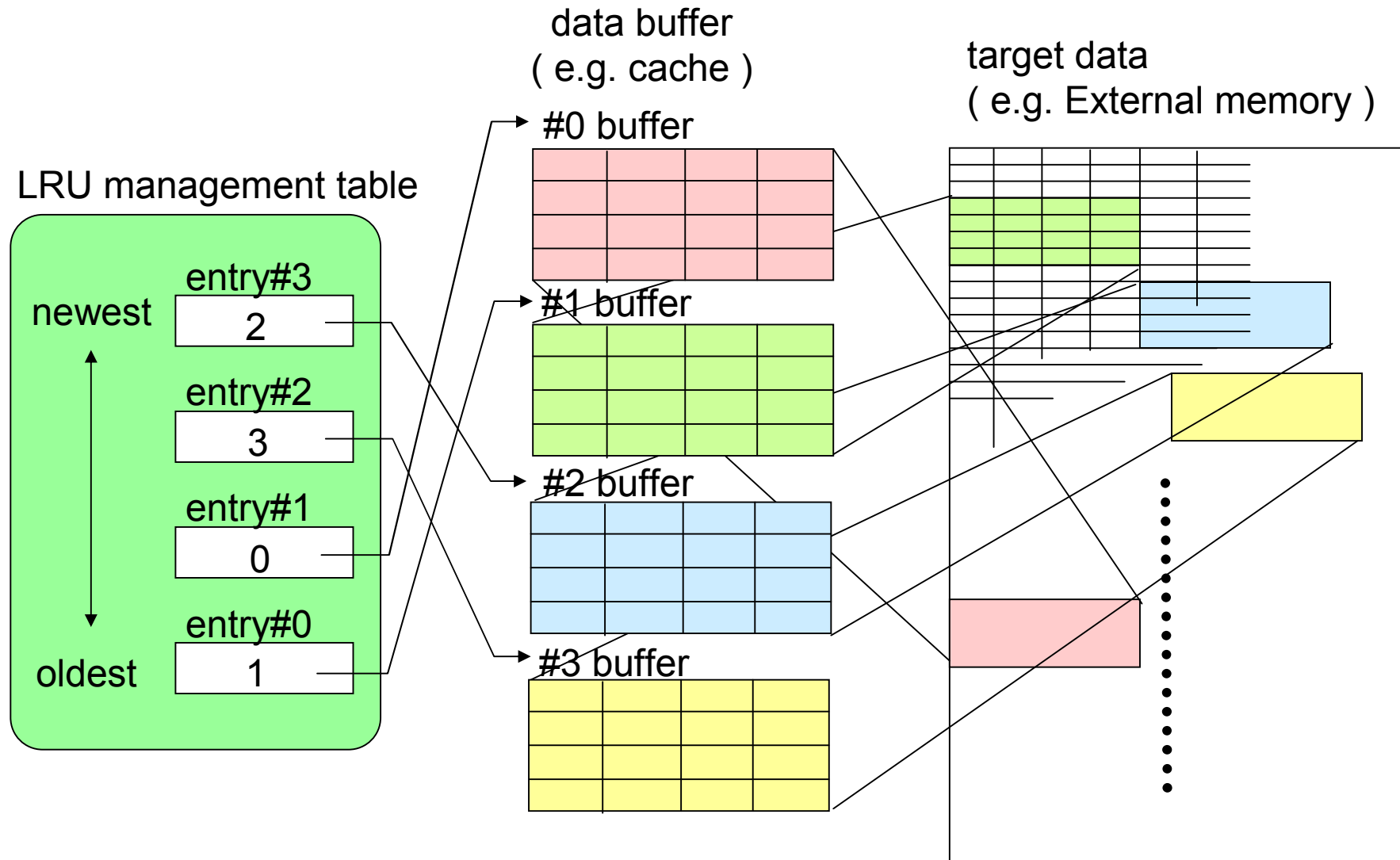
Suppose the target data are randomly accessed, create a module which can output the buffer number to be replaced based on LRU algorithm.




ref_buf_numbr = 2 means data in cache #2 buffer is referenced.

buf_num_replc = 1 means cache #1 buffer shall be replaced (saved back to External memory and shall be filled in with new data).

Operation example:

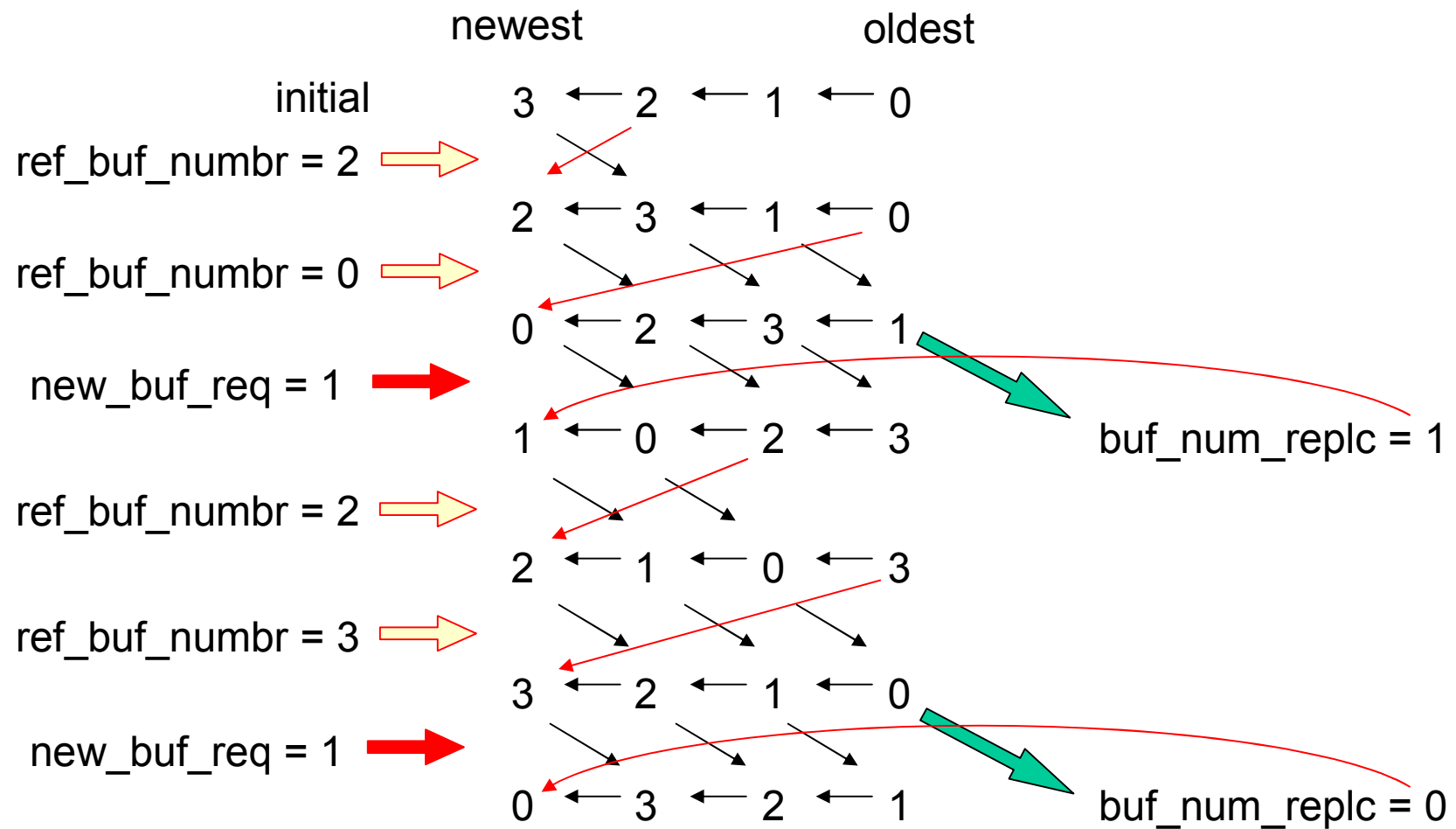

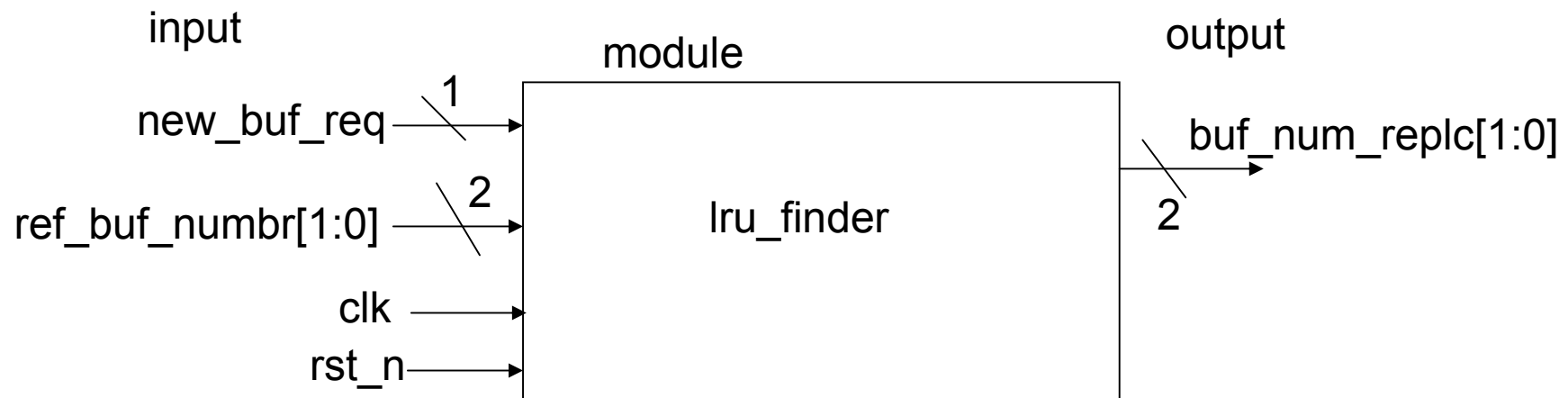Create your own algorithm to find out buf_num_replc.



`new_buf_req` : 0 if no need to replace a buffer. 1 if a buffer must be replaced.


`ref_buf_numbr` : The number of the buffer accessed. This signal is valid only when `new_buf_req` = 0.

`buf_num_replc` : The number of the buffer to be replaced. This signal is valid only during a clock CYCL right after `new_buf_req` is set to 1. The buffer defined by this signal must be treated to be most recently referenced.

At the initial condition, the sequence of filling up the buffers is #0, #1, #2, and then #3, that is #3 is newest and #0 is oldest. The LRU logic in this exercise is only applicable after all entries are filled up.

Timing issue

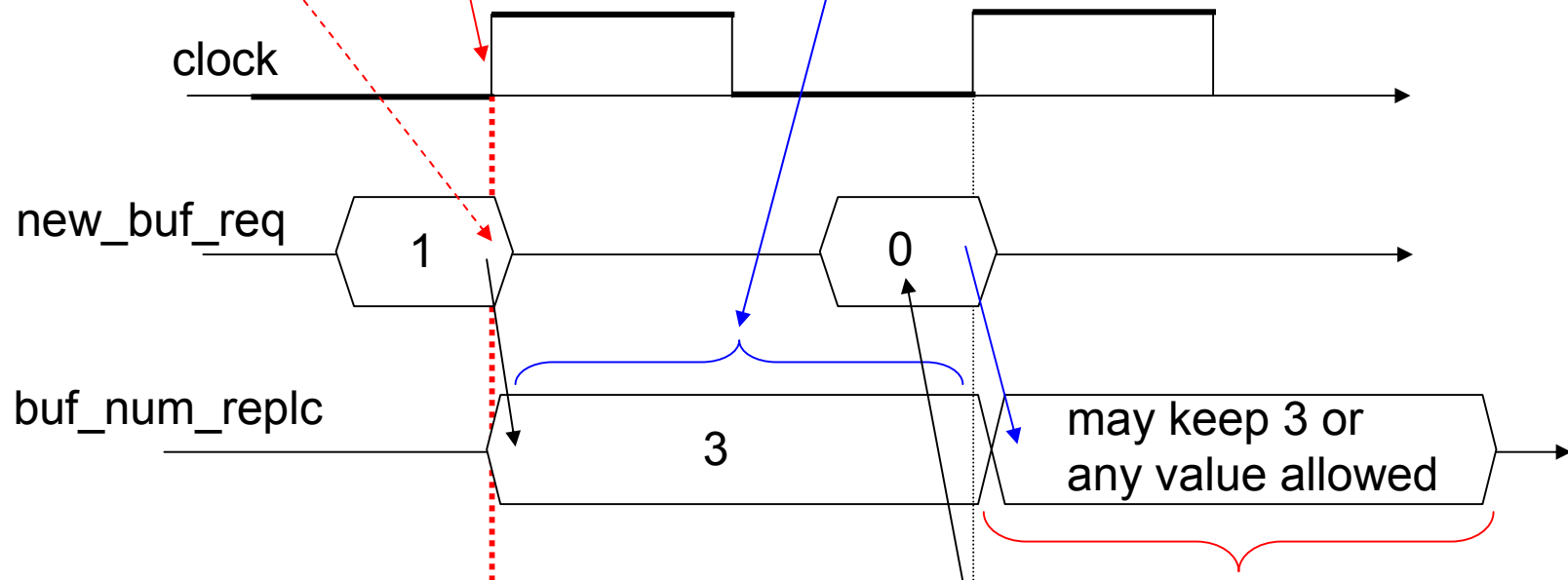The output `buf_num_replc` must become available right after the rise edge of the clock if `new_buf_req` is 1 at that rise edge of the clock.



`buf_num_replc` can be any number in this time period because no new buffer requested. Keeping the previous value (3) may be a good idea.

Note on code efficiency

Because the target of this exercise is to get accustomed to RTL programming, it is acceptable if your logic memorizes all the referenced sequence and use it to select the LRU entry.

Work flow for solutions

- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document,
- (4) Write a RTL code for the target module,
- (5) Run **the automatic test bench** on the next pages with the target module you created.

If your code is rejected, correct your code.

Copy and paste the test bench module on the next pages into you PC and run it with your lru_finder module to see if it is OK or Not.

A sample test bench, automatic tester

```

module test_lru_finder ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL*2 ;
//
reg clk, rst_n ;
reg b_rq ;
reg [1:0] ref ;
wire [1:0] rplc ;
//
// connect signals to game
lru_finder lru_finder_01( .clk( clk ), .rst_n( rst_n ),
                        .new_buf_req( b_rq ), .ref_buf_numbr( ref ),
                        .buf_num_replc( rplc )
                        );
always begin // clock generator
    clk = 1'b0 ; #HF_CYCL ;
    clk = 1'b1 ; #HF_CYCL ;
end
initial begin // give value to control variable
    rst_n = 1'b0 ;
    #1 rst_n = 1'b1 ;
    #(CYCL * 35 ) $display("test end with no error");
    #1 $finish ;
end

```

Copy and paste this module into you PC and run it with your lru_finder module to see if it is OK or Not.

} target module connection

} clock generator


} Termination timer



```

always @ ( posedge clk ) begin
    # 2 $strobe("t=%d, rst=%b, rq=%b, ref= %d, rplc=%b",
        $stime, rst_n, b_rq, ref, rplc
    );
end
//
task chk_and_stop ; // check target result and stop if error
input [7:0] seq ; // buffer sequence
reg [1:0] w_seq [0:3] ;
integer k ;
begin
    { w_seq[0], w_seq[1], w_seq[2], w_seq[3] } = seq[7:0] ;
    for ( k = 0 ; k <= 3 ; k = k+1 ) begin
        @(posedge clk) begin
            #2 if ( rplc != w_seq[k] ) begin
                $strobe("error at t=%d, buf_num_rplc shall be %d, but was %d",
                    $stime, w_seq[k], rplc ) ;
                #5 $finish;
            end
        end
    end
end
endtask


```


 } show result at each clock rise time

Show lamps at each clock rise time

} Divide input to be used in for loop

} compare at clock rise time. If different, display error message and stop simulation.



initial begin

 b_rq = 1'b0 ;

 ref = 2'd0 ;

 #CYCL ref = 2'd1 ;

 #CYCL ref = 2'd0 ;

 #CYCL ref = 2'd3 ;

 #CYCL ref = 2'd2 ;

 #CYCL b_rq = 1'b1 ;

 ref = 2'dx ;

 chk_and_stop(8'b01_00_11_10) ;

 @(negedge clk) b_rq = 1'b0 ;

 ref = 2'd0 ;

 #CYCL b_rq = 1'b1 ;

 ref = 2'dx ;

 chk_and_stop(8'b01_11_10_00) ; // 1320

 @(negedge clk) b_rq = 1'b0 ;

 ref = 2'd2 ;

 #CYCL b_rq = 1'b1 ;


 ref = 2'dx ;

 chk_and_stop(8'b01_11_00_10) ;//1302

buffer shall be
1->0->3->2

buffer shall be
1->3->2->0

buffer shall be
1->3->0->2



```

@(negedge clk) b_rq = 1'b0 ;
    ref = 2'd1 ;
#CYCL b_rq = 1'b1 ;
    ref = 2'dx ;
chk_and_stop( 8'b11_00_10_01 ) ; //3021
@(negedge clk) b_rq = 1'b0 ;
    ref = 2'd1 ;
#CYCL b_rq = 1'b1 ;
    ref = 2'dx ;
chk_and_stop( 8'b11_00_10_01 ) ; //3021
@(negedge clk) b_rq = 1'b0 ;
    ref = 2'd3 ;
#CYCL b_rq = 1'b1 ;
    ref = 2'dx ;
chk_and_stop( 8'b00_10_01_11 ) ; // 0213
@(negedge clk) b_rq = 1'b0 ;
    ref = 2'd0 ;
#10 b_rq = 1'b1 ;
    ref = 2'dx ;
chk_and_stop( 8'b10_01_11_00 ) ; // 2130
end
//
endmodule

```

buffer shall be
3->0->2->1

buffer shall be
3->0->2->1

buffer shall be
0->2->1->3

buffer shall be
2->1->3->0

file name: test_lru_finder

A sample target code

```

//*****
// RTL programming exercise training sample answer
// (c) RVC, 2010
//*****
module lru_finder ( clk, rst_n, new_buf_req,
                    ref_buf_numbr, buf_num_replc );
input clk, rst_n;
input new_buf_req;
input [1:0] ref_buf_numbr;
output [1:0] buf_num_replc;


wire clk, rst_n;
wire new_buf_req;
wire [1:0] ref_buf_numbr;
wire [1:0] buf_num_replc;

// internal signals
reg [7:0] ref_seq; // FF
reg [7:0] next_ref_seq; // non-FF
wire [1:0] ref_numbr;

//***** logics start *****
// This logic works for buffer full state
// assume buffers are used in sequence
// of #0, #1, #2, and #3 sequence
//

//***** select buffer *****
assign buf_num_replc = ref_seq[1:0];
assign ref_numbr = ( new_buf_req == 1'b1 )?
                    ref_seq[7:6] : ref_buf_numbr;

```



```

//***** reference sequence *****
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n == 1'b0 ) begin
        // initialize reference sequence
        // #0(old), #1, #2, and #3(new) order
        ref_seq <= 8'b00_01_10_11;
    end
    else begin
        ref_seq <= next_ref_seq;
    end
end

always @ ( ref_seq[7:0] or ref_numbr ) begin
    case ( ref_numbr[1:0] )
        ref_seq[7:6] : begin
            new_ref_seq = { ref_seq[5:0], ref_seq[7:6] };
        end
        ref_seq[5:4] : begin
            new_ref_seq = { ref_seq[7:6], ref_seq[3:0], ref_seq[5:4] };
        end
        ref_seq[3:2] : begin
            new_ref_seq = { ref_seq[7:4], ref_seq[1:0], ref_seq[3:2] };
        end
        ref_seq[1:0] : begin
            new_ref_seq = { ref_seq[7:2], ref_seq[1:0] };
        end
        default : begin
            new_ref_seq = 8'bxx_xx_xx_xx;
        end
    endcase
end
endmodule

```

file name: lru_finder.v

Another solution

This solution is used in actual products.


The code shown next is based on the following algorithm.

if the pattern is 111xxx then replace #0 and change the pattern by 000xxx

if the pattern is 0xx11x then replace #1 and change the pattern by 1xx00x

if the pattern is x0x0x1 then replace #2 and change the pattern by x1x1x0

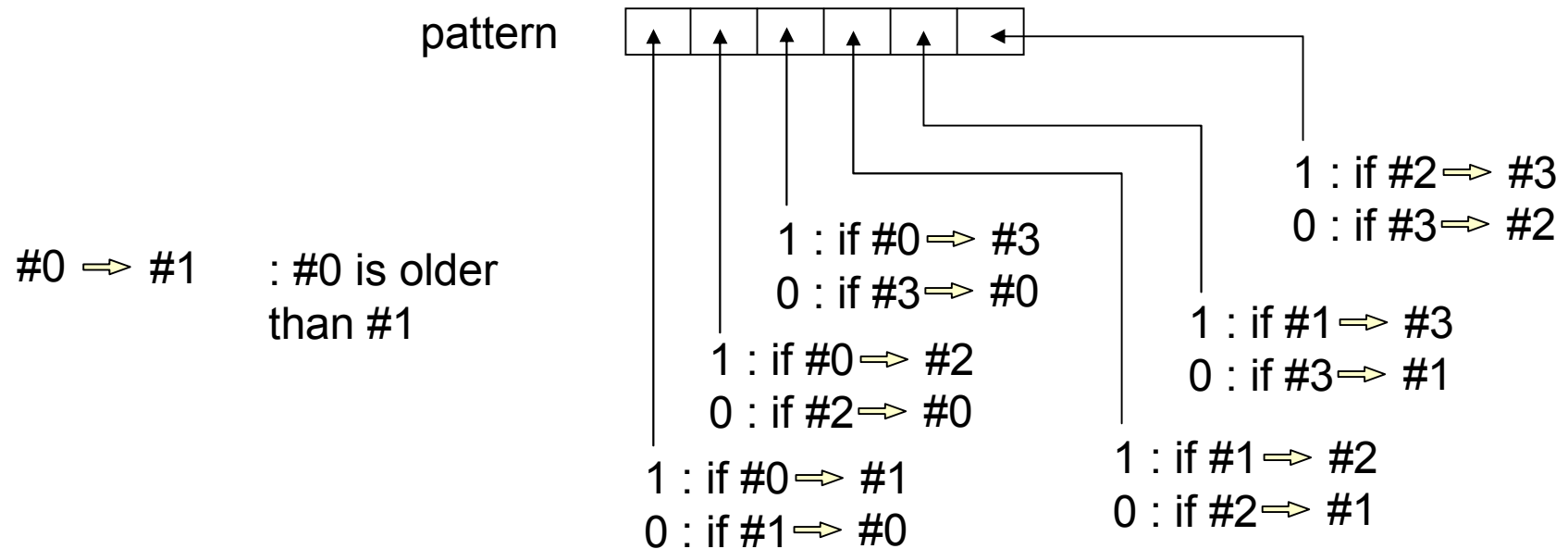if the pattern is xx0x00 then replace #3 and change the pattern by xx1x11



Another sample code

```
module lru_finder ( clk, rst_n,
                  new_buf_req, ref_buf_numbr,
                  buf_num_replc
                );
```

```
input clk, rst_n ;
input new_buf_req ;
input [1:0] ref_buf_numbr ;
output [1:0] buf_num_replc ;
```

```
wire clk, rst_n ;
wire new_buf_req ;
wire [1:0] ref_buf_numbr ;
reg [1:0] buf_num_replc ;
```

```
// internal signals
reg [5:0] ref_seq ; // FF
reg [5:0] next_seq ; // non-FF
reg [1:0] oldest_buf ; // non-FF
wire [1:0] ref_numbr ;
```

```
// ===== find the oldest entry =====
always @ ( ref_seq[5:0] ) begin
  casez ( ref_seq[5:0] )
    6'b111??? : begin
                        oldest_buf[1:0] = 2'b00 ;
                    end
    6'b0???11? : begin
                        oldest_buf[1:0] = 2'b01 ;
                    end
    6'b?0?0?1 : begin
                        oldest_buf[1:0] = 2'b10 ;
                    end
    6'b???0?00 : begin
                        oldest_buf[1:0] = 2'b11 ;
                    end
    default : begin
                        oldest_buf[1:0] = 2'bxx ;
                    end
  end
endcase
end
```

```
//***** select buffer to be replaced *****
always @ ( posedge clk ) begin
  if ( new_buf_req == 1'b1 ) begin
    buf_num_replc[1:0] <= oldest_buf[1:0] ;
  end
end

assign ref_numbr[1:0] = ( new_buf_req == 1'b1 )?
                        oldest_buf[1:0] : ref_buf_numbr[1:0] ;

//***** reference sequence *****
always @ ( posedge clk or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin // initialize reference sequence
    ref_seq[5:0] <= 6'b111_11_1 ; // #0(old), #1, #2, and #3(new) order
  end
  else begin
    ref_seq[5:0] <= next_seq[5:0] ;
  end
end
```

```
always @ ( ref_seq[5:0] or ref_numbr[1:0] ) begin
  case ( ref_numbr[1:0] )
    2'b00 : begin          // update pattern 000xxx
      next_seq[5:0] = { 3'b000, ref_seq[2:0] } ;
    end
    2'b01 : begin          // update pattern 1xx00x
      next_seq[5:0] = { 1'b1, ref_seq[4:3], 2'b0, ref_seq[0] } ;
    end
    2'b10 : begin          // update pattern x1x1x0
      next_seq[5:0] = { ref_seq[5], 1'b1, ref_seq[3], 1'b1, ref_seq[1], 1'b0 } ;
    end
    2'b11 : begin          // update pattern xx1x11
      next_seq[5:0] = { ref_seq[5:4], 1'b1, ref_seq[2], 2'b11 } ;
    end
    default : begin
      next_seq[5:0] = 6'bxxxxxx ;
    end
  endcase
end
endmodule
```



file name: lru_finder_v2.v

The background of the another solution

First , let's study several cases how LRU shall work.

(1) Two entries case


This case is obvious.

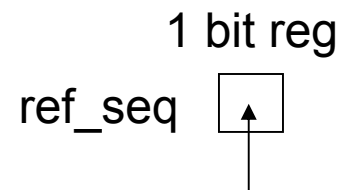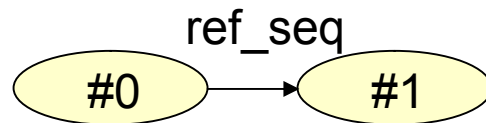


1 : if #0 \Rightarrow #1
0 : if #1 \Rightarrow #0

#0 \Rightarrow #1

This means #0
is older than
#1.

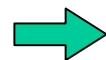

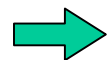There is only one path from #0 to #1, and this one bit information can show which one of two entries is newly referenced.




By checking 1-bit ref_seq, we can determine which one of #0 or #1 shall be replaced.

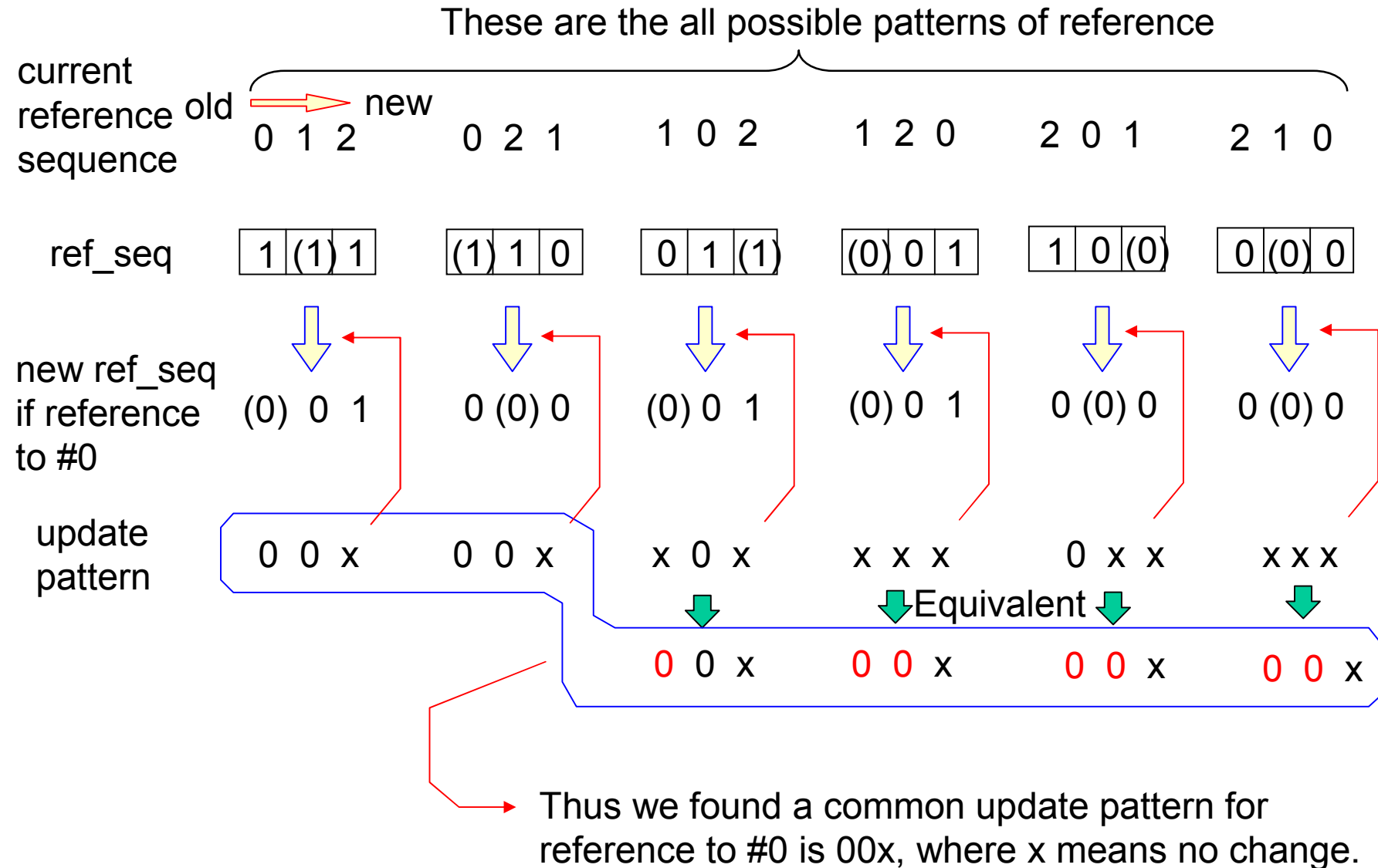(2) Three entries case




➡ There are three paths: from #0 to #1, from #0 to #2, and from #1 to #2. Using old or new relation between the pairs we can define the referenced sequence for all three entries.

However there is some redundancy for this information. For example, if `ref_seq[2] = 1` and `ref_seq[0] = 1`, then `ref_seq[1]` must be 1. This means that we can determine the referenced sequence is #0, #1 and then #3, by checking if `ref_seq`'s bit pattern is 1x1 (x: don't care) or not. The don't care bit position is different depending on the referenced sequence.



() denotes a redundant bit.

(3) for four entries

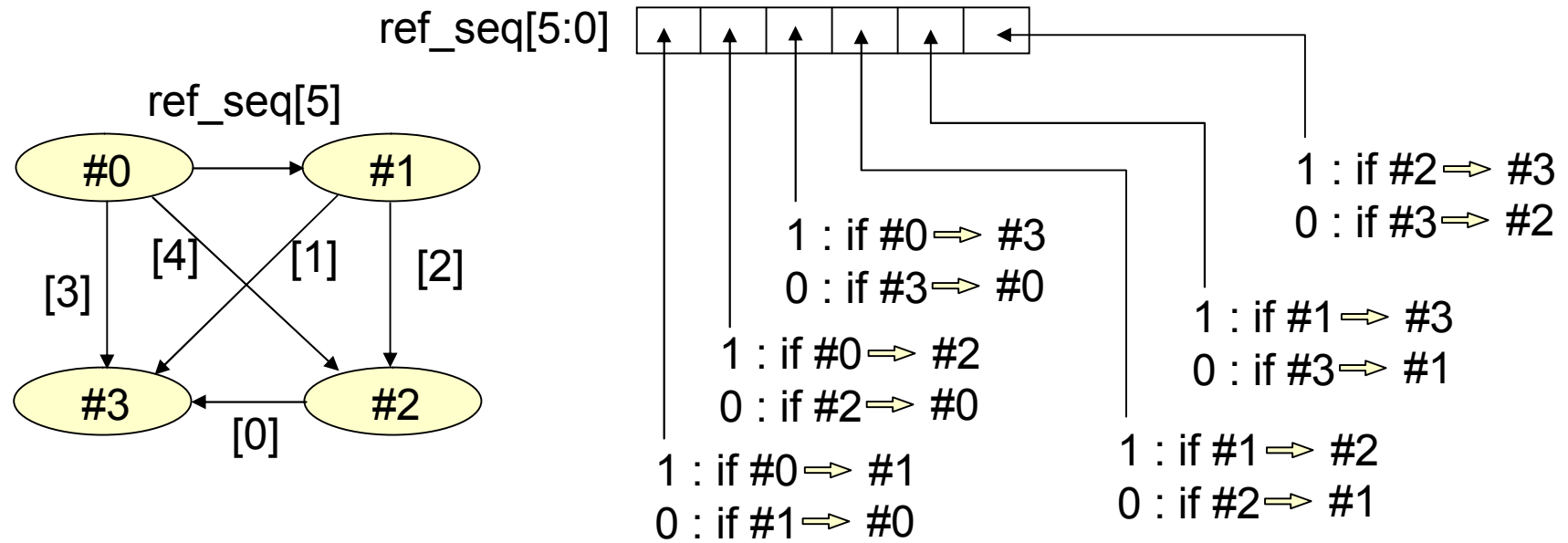

First look for the bit pattern of ref_seq so that we can tell what entry# to replace.

reference sequence	ref_seq pattern
0 1 2 3 →	1 (1)(1) 1 (1) 1
0 1 3 2 →	1 (1)(1)(1) 1 0
0 2 1 3 →	(1) 1 (1) 0 1 (1)
0 2 3 1 →	(1) 1 (1)(0) 0 1
0 3 1 2 →	(1)(1) 1 1 0 (0)
0 3 2 1 →	(1)(1) 1 0 (0) 0

111xxx then replace #0

2 0 1 3 →	1 0 (1)(0) 1 (1)
2 0 3 1 →	(1) 0 1 (0) 0 (1)
2 1 0 3 →	0 (0) 1 0 (1)(1)
2 1 3 0 →	(0)(0) 0 0 1 (1)
2 3 0 1 →	1 (0) 0 (0)(0) 1
2 3 1 0 →	0 (0)(0)(0) 0 1

x0x0x1 then replace #2

reference sequence	ref_seq pattern
1 0 2 3 →	0 1 (1)(1)(1) 1
1 0 3 2 →	0 (1) 1 (1)(1) 0
1 2 0 3 →	(0) 0 1 1 (1)(1)
1 2 3 0 →	(0)(0) 0 1 (1) 1
1 3 0 2 →	(0) 1 0 (1) 1 (0)
1 3 2 0 →	(0) 0 (0)(1) 1 0

0xx11x then replace #1

3 0 2 1 →	(1) 1 0 0 (0)(0)
3 0 1 2 →	1 (1) 0 1 (0)(0)
3 1 0 2 →	0 1 (0)(1) 0 (0)
3 1 2 0 →	(0) 0 (0) 1 0 (0)
3 2 0 1 →	1 0 (0)(0)(0) 0
3 2 1 0 →	0 (0)(0) 0 (0) 0

xx0x00 then replace #3

Next, look for the update pattern

reference sequence	ref_seq	pattern	new pattern if reference to #0	update pattern
-----------------------	---------	---------	--------------------------------	----------------

0 1 2 3	→	1 (1)(1) 1 (1) 1	⇒	1 2 3 0 : (0)(0) 0 1 (1) 1	→	000xxx
---------	---	------------------	---	----------------------------	---	--------

0 1 3 2	→	1 (1)(1)(1) 1 0	⇒	1 3 2 0 : (0) 0 (0)(1) 1 0	→	000xxx
---------	---	-----------------	---	----------------------------	---	--------

0 2 1 3	→	(1) 1 (1) 0 1 (1)	⇒	2 1 3 0 : (0)(0) 0 0 1 (1)	→	000xxx
---------	---	-------------------	---	----------------------------	---	--------

0 2 3 1	→	(1) 1 (1)(0) 0 1	⇒	2 3 1 0 : 0 (0)(0)(0) 0 1	→	000xxx
---------	---	------------------	---	---------------------------	---	--------

0 3 1 2	→	(1)(1) 1 1 0 (0)	⇒	3 1 2 0 : (0)(0) 0 1 0 (0)	→	000xxx
---------	---	------------------	---	----------------------------	---	--------

0 3 2 1	→	(1)(1) 1 0 (0) 0	⇒	3 2 1 0 : 0 (0)(0) 0 (0) 0	→	000xxx
---------	---	------------------	---	----------------------------	---	--------

1 0 2 3	→	0 1 (1)(1)(1) 1	⇒	1 2 3 0 : (0)(0) 0 1 (1) 1	→	x00xxx
---------	---	-----------------	---	----------------------------	---	--------

1 0 3 2	→	0 (1) 1 (1)(1) 0	⇒	1 3 2 0 : (0) 0 (0)(1) 1 0	→	x00xxx
---------	---	------------------	---	----------------------------	---	--------

1 2 0 3	→	(0) 0 1 1 (1)(1)	⇒	1 2 3 0 : (0)(0) 0 1 (1) 1	→	xx0xxx
---------	---	------------------	---	----------------------------	---	--------

1 2 3 0	→	(0)(0) 0 1 (1) 1	⇒	1 2 3 0 : (0)(0) 0 1 (1) 1	→	xxxxxx
---------	---	------------------	---	----------------------------	---	--------

1 3 0 2	→	(0) 1 0 (1) 1 (0)	⇒	1 3 2 0 : (0) 0 (0)(1) 1 0	→	x0xxxx
---------	---	-------------------	---	----------------------------	---	--------

1 3 2 0	→	(0) 0 (0)(1) 1 0	⇒	1 3 2 0 : (0) 0 (0)(1) 1 0	→	xxxxxx
---------	---	------------------	---	----------------------------	---	--------

→ 000xxx

2 0 1 3	→	1 0 (1)(0) 1 (1)	⇒	2 1 3 0 : (0)(0) 0 0 1 (1)	→	0x0xxx
---------	---	------------------	---	----------------------------	---	--------

2 0 3 1	→	(1) 0 1 (0) 0 (1)	⇒	2 3 1 0 : 0 (0)(0)(0) 0 1	→	0x0xxx
---------	---	-------------------	---	---------------------------	---	--------

2 1 0 3	→	0 (0) 1 0 (1)(1)	⇒	2 1 3 0 : (0)(0) 0 0 1 (1)	→	xx0xxx
---------	---	------------------	---	----------------------------	---	--------

2 1 3 0	→	(0)(0) 0 0 1 (1)	⇒	2 1 3 0 : (0)(0) 0 0 1 (1)	→	xxxxxx
---------	---	------------------	---	----------------------------	---	--------


2 3 0 1	→	1 (0) 0 (0)(0) 1	⇒	2 3 1 0 : 0 (0)(0)(0) 0 1	→	0xxxxx
---------	---	------------------	---	---------------------------	---	--------

2 3 1 0	→	0 (0)(0)(0) 0 1	⇒	2 3 1 0 : 0 (0)(0)(0) 0 1	→	xxxxxx
---------	---	-----------------	---	---------------------------	---	--------

→ 000xxx

reference sequence	ref_seq	pattern	new pattern if reference to #0	update pattern
3 0 2 1	→	(1) 1 0 0 (0)(0)	⇒ 3 2 1 0 :	0 (0)(0) 0 (0) 0 → 00xxxx
3 0 1 2	→	1 (1) 0 1 (0)(0)	⇒ 3 1 2 0 :	(0) 0 (0) 1 0 (0) → 00xxxx
3 1 0 2	→	0 1 (0)(1) 0 (0)	⇒ 3 1 2 0 :	(0) 0 (0) 1 0 (0) → x0xxxx
3 1 2 0	→	(0) 0 (0) 1 0 (0)	⇒ 3 1 2 0 :	(0) 0 (0) 1 0 (0) → xxxxxx
3 2 0 1	→	1 0 (0)(0)(0) 0	⇒ 3 2 1 0 :	0 (0)(0) 0 (0) 0 → 0xxxxx
3 2 1 0	→	0 (0)(0) 0 (0) 0	⇒ 3 2 1 0 :	0 (0)(0) 0 (0) 0 → xxxxxx

} → 000xxx

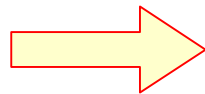

Thus we get 000xxx for #0 update pattern

reference sequence	ref_seq	pattern	new pattern if reference to #1	update pattern
0 1 2 3	→	1 (1)(1) 1 (1) 1	⇒ 0 2 3 1 :	(1) 1 (1)(0) 0 1 → xxx00x
0 1 3 2	→	1 (1)(1)(1) 1 0	⇒ 0 3 2 1 :	(1)(1) 1 0 (0) 0 → xxx00x
0 2 1 3	→	(1) 1 (1) 0 1 (1)	⇒ 0 2 3 1 :	(1) 1 (1)(0) 0 1 → xxxx0x
0 2 3 1	→	(1) 1 (1)(0) 0 1	⇒ 0 2 3 1 :	(1) 1 (1)(0) 0 1 → xxxxxx
0 3 1 2	→	(1)(1) 1 1 0 (0)	⇒ 0 3 2 1 :	(1)(1) 1 0 (0) 0 → xxx0xx
0 3 2 1	→	(1)(1) 1 0 (0) 0	⇒ 0 3 2 1 :	(1)(1) 1 0 (0) 0 → xxxxxx

} → 1xx00x

reference sequence	ref_seq	pattern	new pattern if reference to #1	update pattern
1 0 2 3	→	0 1 (1)(1)(1) 1	⇒ 0 2 3 1 : (1) 1 (1)(0) 0 1	→ 1xx00x
1 0 3 2	→	0 (1) 1 (1)(1) 0	⇒ 0 3 2 1 : (1)(1) 1 0 (0) 0	→ 1xx00x
1 2 0 3	→	(0) 0 1 1 (1)(1)	⇒ 2 0 3 1 : (1) 0 1 (0) 0 (1)	→ 1xx00x
1 2 3 0	→	(0)(0) 0 1 (1) 1	⇒ 2 3 0 1 : 1 (0) 0 (0)(0) 1	→ 1xx00x
1 3 0 2	→	(0) 1 0 (1) 1 (0)	⇒ 3 0 2 1 : (1) 1 0 0 (0)(0)	→ 1xx00x
1 3 2 0	→	(0) 0 (0)(1) 1 0	⇒ 3 2 0 1 : 1 0 (0)(0)(0) 0	→ 1xx00x
<hr/>				
2 0 1 3	→	1 0 (1)(0) 1 (1)	⇒ 2 0 3 1 : (1) 0 1 (0) 0 (1)	→ xxxx0x
2 0 3 1	→	(1) 0 1 (0) 0 (1)	⇒ 2 0 3 1 : (1) 0 1 (0) 0 (1)	→ xxxxxx
2 1 0 3	→	0 (0) 1 0 (1)(1)	⇒ 2 0 3 1 : (1) 0 1 (0) 0 (1)	→ 1xxx0x
2 1 3 0	→	(0)(0) 0 0 1 (1)	⇒ 2 3 0 1 : 1 (0) 0 (0)(0) 1	→ 1xxx0x
2 3 0 1	→	1 (0) 0 (0)(0) 1	⇒ 2 3 0 1 : 1 (0) 0 (0)(0) 1	→ xxxxxx
2 3 1 0	→	0 (0)(0)(0) 0 1	⇒ 2 3 0 1 : 1 (0) 0 (0)(0) 1	→ 1xxxxx
<hr/>				
3 0 2 1	→	(1) 1 0 0 (0)(0)	⇒ 3 0 2 1 : (1) 1 0 0 (0)(0)	→ xxxxxx
3 0 1 2	→	1 (1) 0 1 (0)(0)	⇒ 3 0 2 1 : (1) 1 0 0 (0)(0)	→ xxx0xx
3 1 0 2	→	0 1 (0)(1) 0 (0)	⇒ 3 0 2 1 : (1) 1 0 0 (0)(0)	→ 1xx0xx
3 1 2 0	→	(0) 0 (0) 1 0 (0)	⇒ 3 2 0 1 : 1 0 (0)(0)(0) 0	→ 1xx0xx
3 2 0 1	→	1 0 (0)(0)(0) 0	⇒ 3 2 0 1 : 1 0 (0)(0)(0) 0	→ xxxxxx
3 2 1 0	→	0 (0)(0) 0 (0) 0	⇒ 3 2 0 1 : 1 0 (0)(0)(0) 0	→ 1xxxxx


→ 1xx00x

→ 1xx00x




Thus we get 1xx00x for #1 update pattern

reference sequence	ref_seq	pattern	new pattern if reference to #2	update pattern
2 0 1 3	→	1 0 (1)(0) 1 (1)	⇒ 0 1 3 2 : 1 (1)(1)(1) 1 0	→ x1x1x0
2 0 3 1	→	(1) 0 1 (0) 0 (1)	⇒ 0 3 1 2 : (1)(1) 1 1 0 (0)	→ x1x1x0
2 1 0 3	→	0 (0) 1 0 (1)(1)	⇒ 1 0 3 2 : 0 (1) 1 (1)(1) 0	→ x1x1x0
2 1 3 0	→	(0)(0) 0 0 1 (1)	⇒ 1 3 0 2 : (0) 1 0 (1) 1 (0)	→ x1x1x0
2 3 0 1	→	1 (0) 0 (0)(0) 1	⇒ 3 0 1 2 : 1 (1) 0 1 (0)(0)	→ x1x1x0
2 3 1 0	→	0 (0)(0)(0) 0 1	⇒ 3 1 0 2 : 0 1 (0)(1) 0 (0)	→ x1x1x0

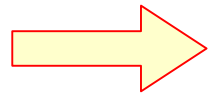

For other current patterns we can find that
x1x1x0 is the update pattern for #2


reference sequence	ref_seq	pattern	new pattern if reference to #3	update pattern
3 0 2 1	→	(1) 1 0 0 (0)(0)	⇒ 0 2 1 3 : (1) 1 (1) 0 1 (1)	→ xx1x11
3 0 1 2	→	1 (1) 0 1 (0)(0)	⇒ 0 1 2 3 : 1 (1)(1) 1 (1) 1	→ xx1x11
3 1 0 2	→	0 1 (0)(1) 0 (0)	⇒ 1 0 2 3 : 0 1 (1)(1)(1) 1	→ xx1x11
3 1 2 0	→	(0) 0 (0) 1 0 (0)	⇒ 1 2 0 3 : (0) 0 1 1 (1)(1)	→ xx1x11
3 2 0 1	→	1 0 (0)(0)(0) 0	⇒ 2 0 1 3 : 1 0 (1)(0) 1 (1)	→ xx1x11
3 2 1 0	→	0 (0)(0) 0 (0) 0	⇒ 2 1 0 3 : 0 (0) 1 0 (1)(1)	→ xx1x11

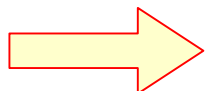


For other current patterns we can find that
xx1x11 is the update pattern for #3

Ex 6-3. Two ring flasher : Write a module for a two ring flasher of which movement is given in the figure below. $a[n]$ represents a lamp in ring A, 0/1 of $a[n]$ corresponds to off/on of #n lamp in ring A. $b[m]$ represents a lamp in ring B, 0/1 of $b[m]$ corresponds to off/on of #m lamp in ring B.

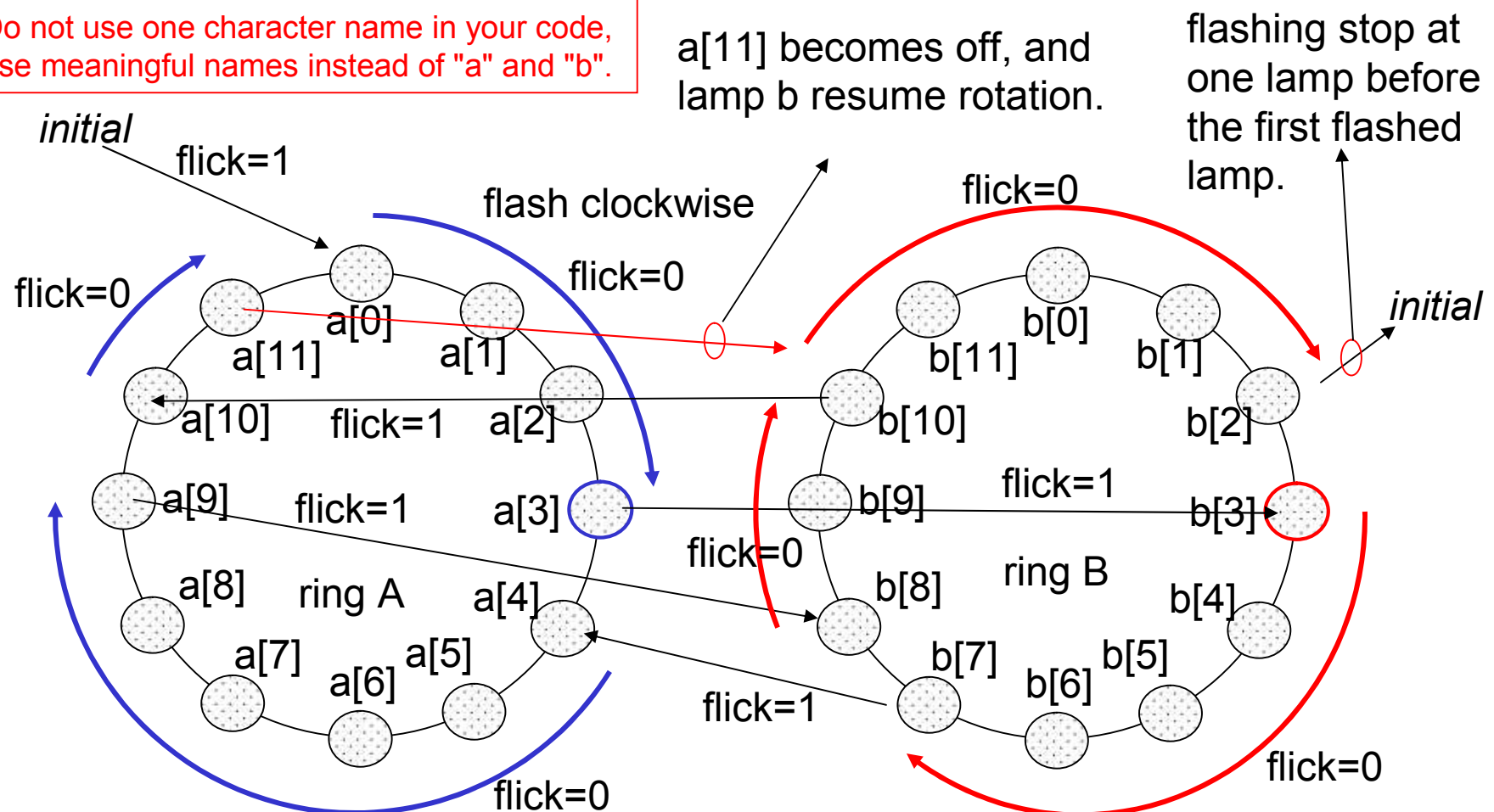Do not use one character name in your code, use meaningful names instead of "a" and "b".



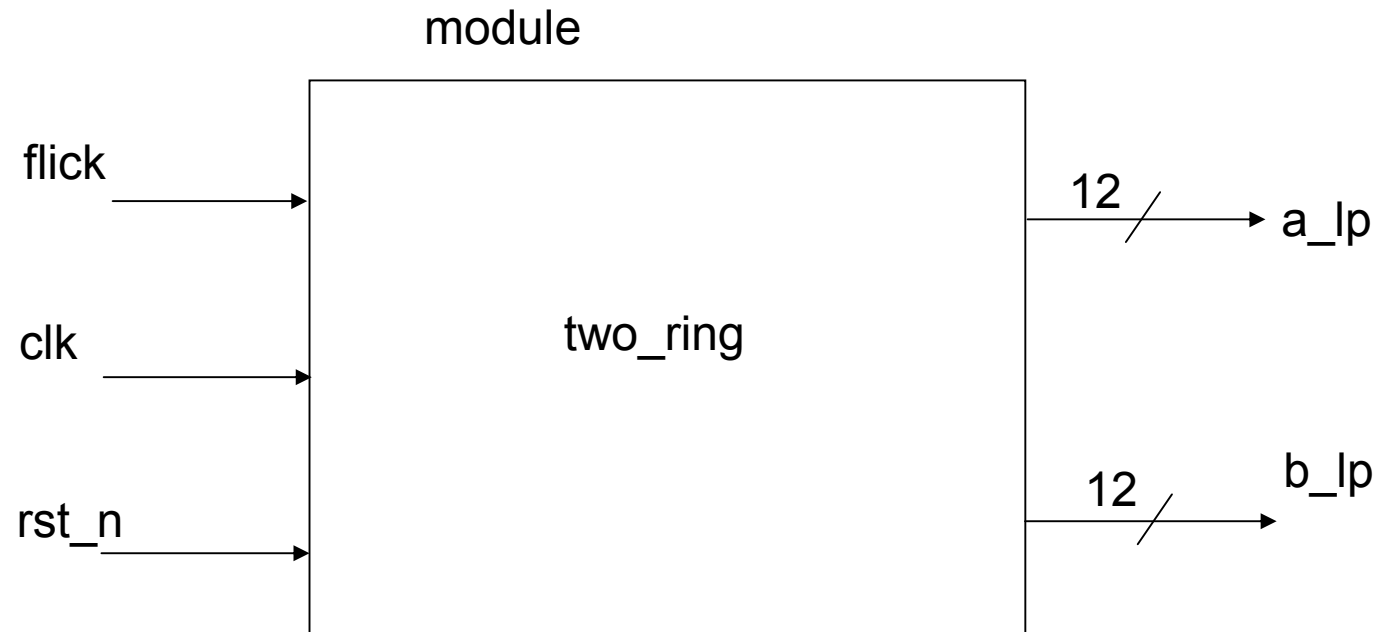

A sample test bench is prepared for this exercise.
Your code is not OK if it is rejected by the sample test bench.

Detailed specification

1. State definition

(1) *ring-on state* and *ring-off state*:

Ring A and ring B can be in either *ring-on state* or *ring-off state*.

Ring-on state means one lamp of the ring is on.

Ring-off state means all lamps of the ring is off.

(2) *Sys-initial state* and *sys-run state*:

The total system can be in either *sys-initial state* or *sys-run state*.

Sys-initial state means the both ring A and B are in *ring-off state*.

Sys-run state means either or both of ring A and B are in *ring-on state*.

2. *First-lamp* and *last-lamp* definition

(1) *First-lamp* is a lamp which turns on first when a ring becomes *ring_on* state from *ring-off* state.

(2) *Last-lamp* is a lamp next to the *first-lamp* in the counterclockwise direction.

(3) ring A's *first-lamp* is always #0.

(4) ring B's *first-lamp* can be either one of the flowing (A) or (B) depending on the flick signal when ring B becomes *ring-on* state from *ring-off* state.

2. *First-lamp and last-lamp* definition (continued)

- (A) If flick is 0, then #0 is the *first lamp* of ring B.
- (B) Otherwise, flick is 1, the lamp at the same position of the ring A's on lamp is the *first lamp* of ring B.

3. Operation of rings; *rotate operation* and *hold operation*.

Ring A and ring B must do *rotate operation* or *hold operation* at every clock rise time.

Rotate operation means the following 4 operations, (1) to (4).

- (1) Turn on the first lamp of a ring which has not been in *ring-on* state after the most recent *sys_initial* state.
- (2) Keep *ring-off* state of a ring which had been in *ring-on* state after the most recent *sys_initial* state and is currently in *ring-off* state.
- (3) Turn off current on-lamp of the ring and at the same time turn on the next lamp in a clockwise direction if other than the *last_lamp* of the ring is on.
- (4) Turn off current on-lamp of the ring if the *last_lamp* of the ring is on.

3. Operation of rings; *rotate operation* and *hold operation*. (*continued*)

Hold operation means the following operation (5).

(5) Neither on lamp position nor off lamp position of the ring change.

4. System's behavior definition (input flick is evaluated at clock rise time)

In *sys_initial* state, depending on flick input, either <1> or <2> must occur.

<1> If flick=0, the system must keep *sys_initial* state.

<2> If flick=1, ring A must do *rotate operation* and ring B must do *hold operation*.

In *sys_run* state, depending on flick input, either <3> or <4> must occur.

<3> If flick=0, both ring must do the same operation as the most recent operation.

<4> If flick=1, ring A must do the same operation of the most recent ring B's operation, and ring B must do the same operation of the most recent ring A's operation. (Both ring exchange their most recent operation.)

5. Exceptional cases


<5> If the *rotate operation* caused by <3> or <4> has to be applied to the *last-lamp* turned on or it has to be applied to the ring which became *ring-off* state after the most recent *sys-initial* state, then the other ring has to do *rotate operation* at the same time. That is, both rings must do *rotate operation* at the same time in such cases..

6. Reset

<6> When reset asserted, the system must become *sys_initial* state regardless of the current state. While reset is asserted, flick signal is invalid.


Additional explanation

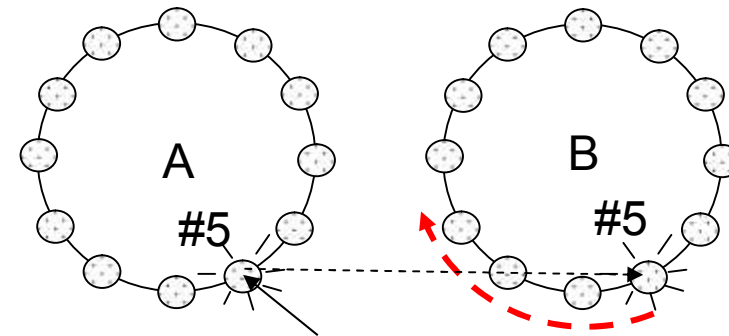When B off and a[5] on and flick is set to 1, then b[5] becomes the *first-lamp*.




If flick becomes on at a[5] lamp, B starts from b[5] lamp.

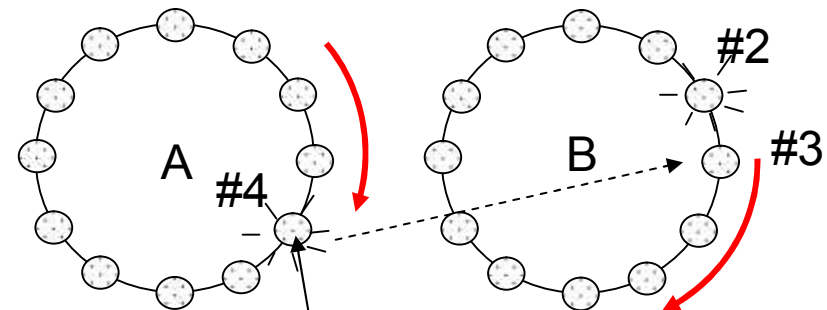When the rotating ring switches from ring A/B to B/A, ring A/B's lamp will stop rotation but keeps illuminating.




lamp stop moving but keep illuminating.

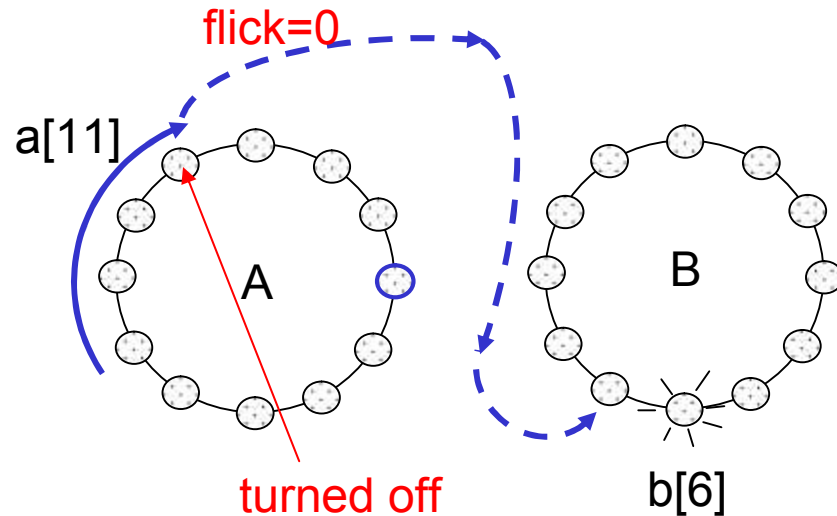When a ring completed its one turn, all its lamps must become off as explained below.




ring A is rotating. If flick is kept off, it will complete one turn. Therefore, a[11] and b[6] becomes off and b[7] becomes on at the same time.

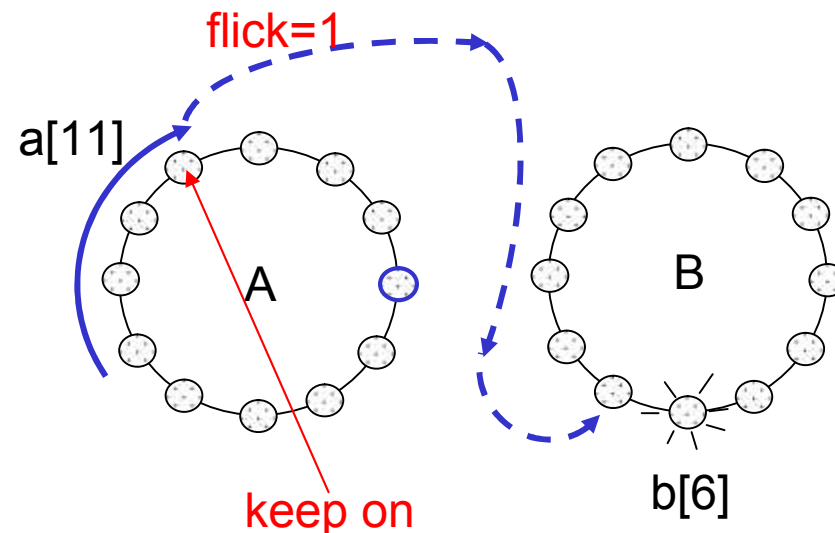However, if the switching is caused by flick signal at a[11], a[11] must not be turned off as shown on the right. b[6] becomes off and b[7] becomes on while a[11] is kept on.




There are very special cases as below.

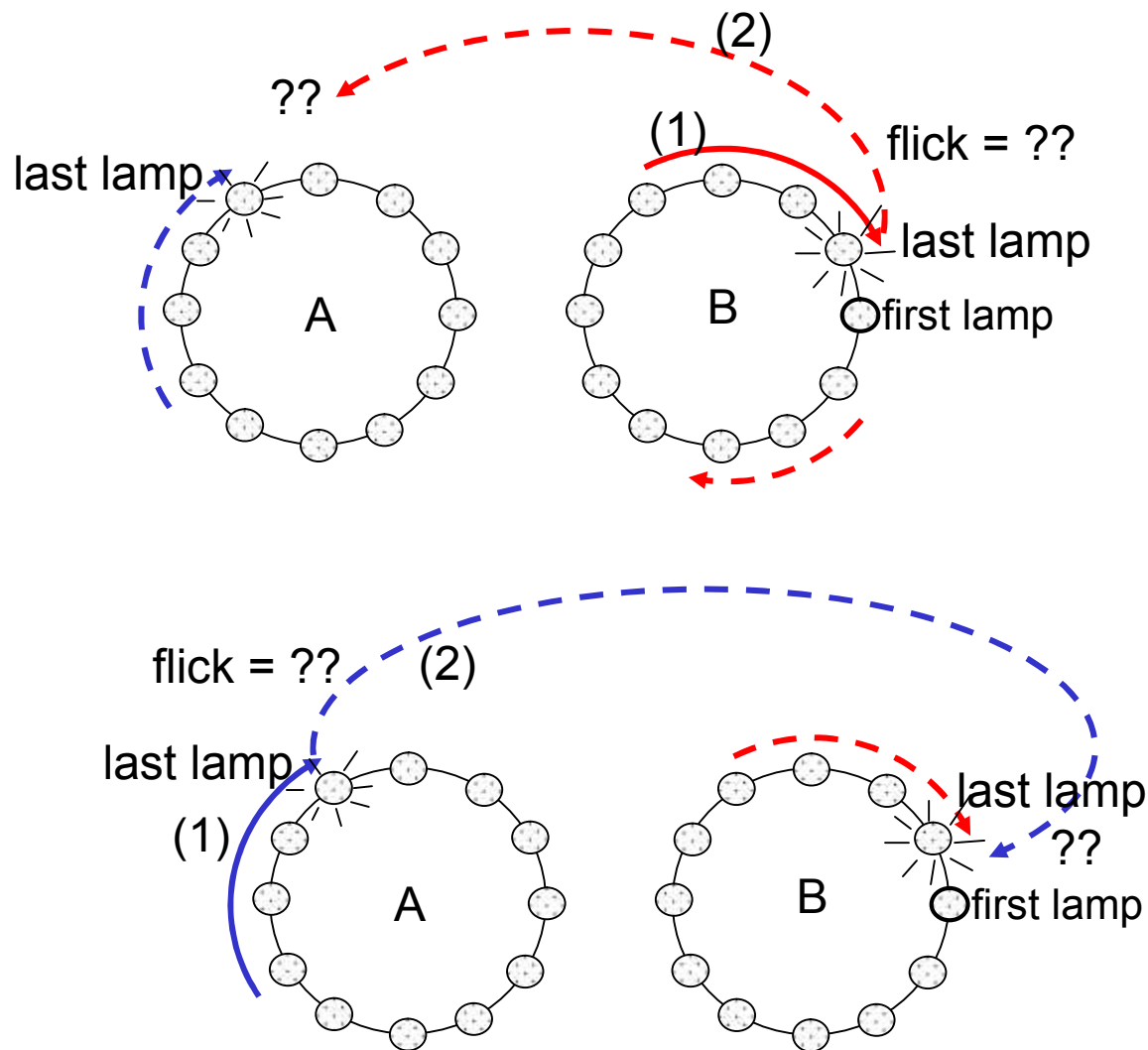

In both cases, on switching to another ring, the last lamps are already on, therefore switching means completion of the other ring's one turn. And because the completed ring can not rotate any more, original ring must resume rotation at once. This means the original ring must also complete the turn.

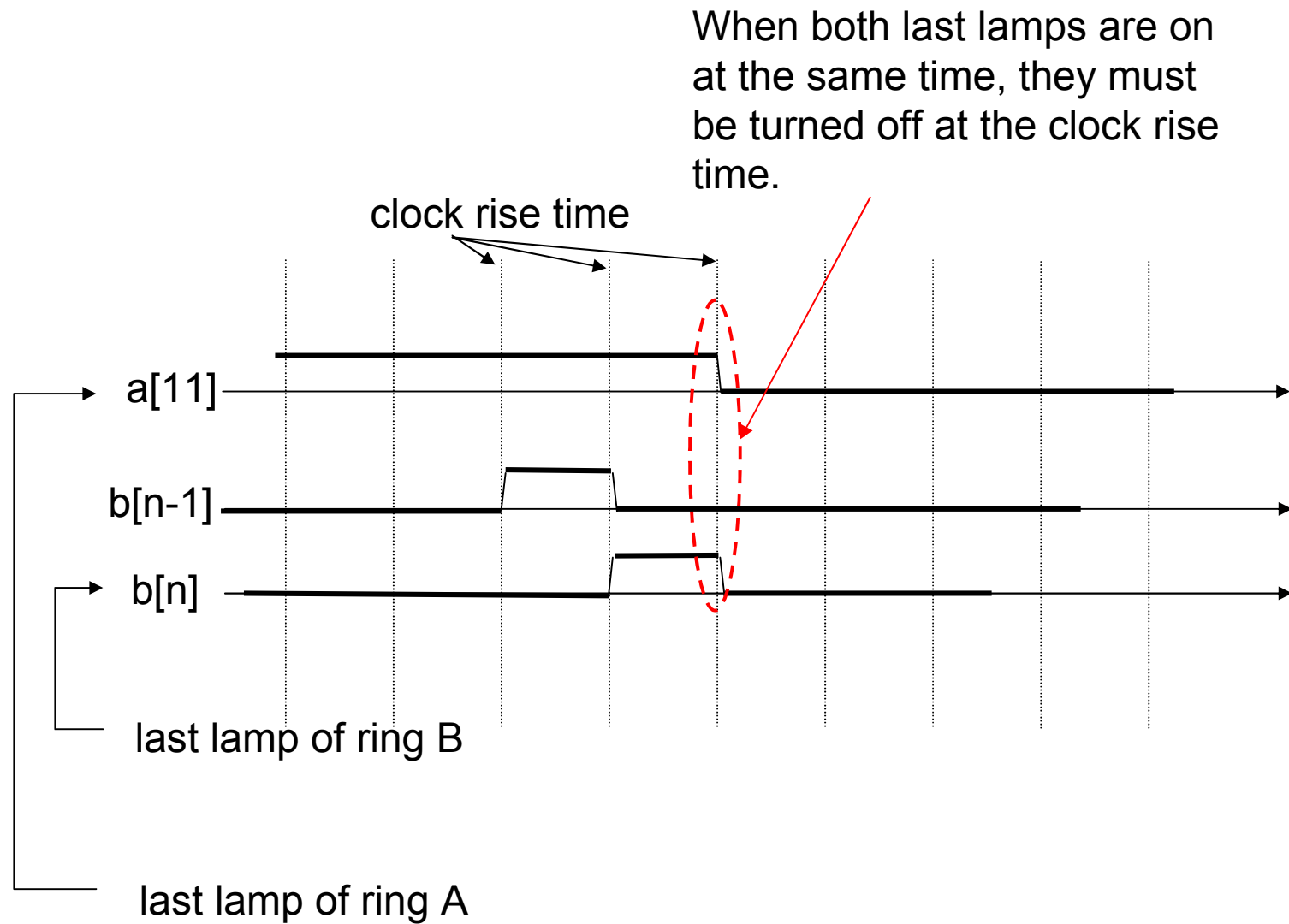So, for these special cases, make your logic to turn off both lamps and go to initial state as shown on the time chart on the next page.



Work flow for solutions

- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document including a state transition table,
- (4) Write a RTL code for the target module,
- (5) Run **a sample test bench** on the next pages with the target module you created.

If your code is rejected, correct your code.

Copy and paste the test bench module on the next pages into you PC and run it with your two_ting module to see if your code is OK or Not.

A sample test bench, automatic tester

Copy and paste this module into you PC and run it with your two_ting module to see if it is OK or Not.

```
module test_two_ring ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL*2 ;
```

```
reg rst_n, clk, flick ;
wire [11:0] a_lp, b_lp ;
reg [11:0] g_a_lp, g_b_lp ;
```

When using a sample target code in the latter pages, change this part to multi_ring multi_ring_01.

```
// module connection
two_ring two_ring_01 ( .clk(clk), .rst_n(rst_n), .flick(flick),
                      .a_lp(a_lp), .b_lp(b_lp) );
```

target module connection

```
// display the movements
always @ ( posedge clk ) begin
#2 $display("t=%d,r=%b,f=%b,a=%b,b=%b",
           $stime, rst_n, flick,
           a_lp, b_lp );
```


Change this to
.lamp_1(a_lp), .lamp_2(b_lp)

Show lamps at each clock rise time

```
end
initial begin
# (CYCL * 800 ) $finish;
end
```

Termination timer

This must be larger than FF_DLY if delay is used in FF design.



```

/// test data and monitor
// clk and reset
always begin
  clk = 0 ; #HF_CYCL ;
  clk = 1 ; #HF_CYCL ;
end

```

} clock generator

```

initial begin
  rst_n=0 ; #(CYCL*3 + 3 ) ;
  rst_n=1 ;
end

```

} reset control

```

event timng ; // timing event
always @ ( posedge clk ) begin
  #HF_CYCL -> timng ;
end



```

} generate event "timng"
at clock fall time

```


// invoke golden model and compare
always begin
  @(posedge clk) golden_ring(g_a_lp, g_b_lp) ;
  #2 cmp_chk ( g_a_lp, g_b_lp, a_lp, b_lp ) ;
end

```

} Invoke golden model
and compare at each
clock rise time


This must be larger than FF_DLY if delay is used in FF design.



```


task golden_ring ;
output [11:0] a_lp, b_lp ;
integer a_cnt, b_cnt, b_pos ;
reg a_flg ; // non-FF
reg [11:0] temp ; // non-FF. work for B bit position
begin
  if ( rst_n == 0 ) begin
    a_cnt = 0 ; // A lamp position counter
    b_cnt = 0 ; // B lamp position counter
    b_pos = 0 ; // B start position
  end
  else begin
    if ( a_cnt == 0 ) begin // not started
      if ( flick ) begin
        a_cnt = 1 ; // first lamp on
        a_flg = 1 ; // ring A rotate
      end
    end
  end
end

```



initialize if reset is active


a_cnt==0 means no lamp is on.
 Therefore, if flick==1, start rotating A



```

else begin // already started
  if ( flick ) begin
    if ( a_flg ) begin
      a_flg = 0 ; // rign B rotate
      b_pos = ( b_cnt == 0 )? a_cnt-1 : b_pos ;
      b_cnt = b_cnt+1 ;
      if ( b_cnt > 12 ) begin
        a_flg = 1 ;
        a_cnt = a_cnt + 1 ;
      end
    end
  end
  else begin
    a_flg = 1 ; // rign A rotate
    a_cnt = a_cnt+1 ;
    if ( a_cnt > 12 ) begin
      a_flg = 0 ;
      b_cnt = b_cnt + 1 ;
    end
  end
end
end

```




This logic does have to care if
counter becomes larger than 12.


The golden model task will run well
with the counter larger than 12.

Rotate B, if B complete
one turn, then rotate A.
If B not started, set
start position of B.


Rotate A, if A complete
one turn, then rotate B.




```
else begin // flick is 0
  if ( a_flg ) begin
    a_cnt = a_cnt+1 ;
    if ( a_cnt > 12 ) begin
      a_flg = 0 ;
      b_cnt = b_cnt + 1 ;
    end
  end
end
else begin
  b_cnt = b_cnt+1 ;
  if ( b_cnt > 12 ) begin
    a_flg = 1 ;
    a_cnt = a_cnt + 1 ;
  end
end
end
end
end
```




Rotate A, if A complete
one turn, then rotate B.



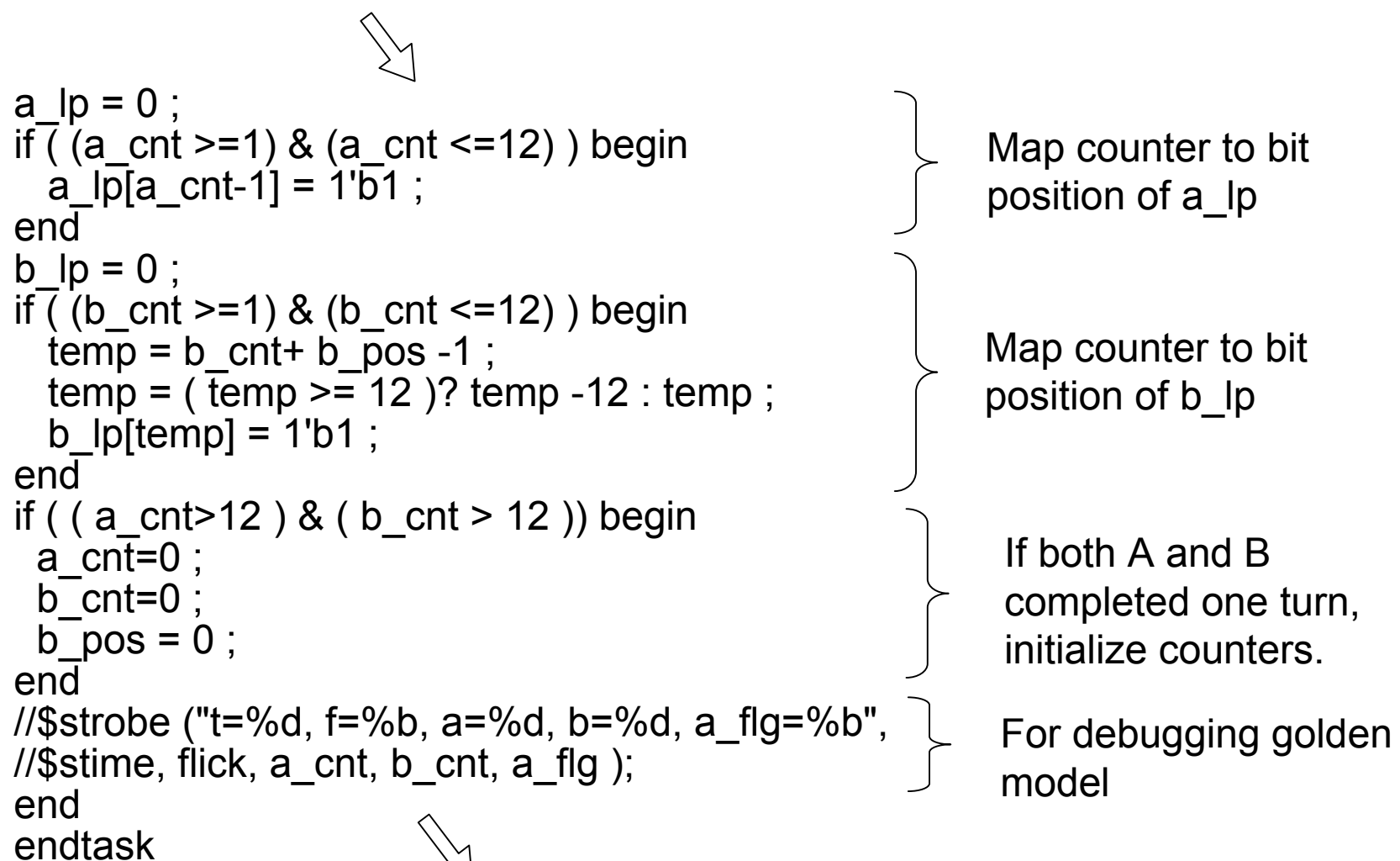Rotate B, if B complete
one turn, then rotate A.





```

a_lp = 0 ;
if ( (a_cnt >=1) & (a_cnt <=12) ) begin
    a_lp[a_cnt-1] = 1'b1 ;
end
b_lp = 0 ;
if ( (b_cnt >=1) & (b_cnt <=12) ) begin
    temp = b_cnt+ b_pos -1 ;
    temp = ( temp >= 12 )? temp -12 : temp ;
    b_lp[temp] = 1'b1 ;
end
if ( ( a_cnt>12 ) & ( b_cnt > 12 )) begin
    a_cnt=0 ;
    b_cnt=0 ;
    b_pos = 0 ;
end
//$strobe ("t=%d, f=%b, a=%d, b=%d, a_flg=%b",
//$stime, flick, a_cnt, b_cnt, a_flg );
end
endtask


```

Map counter to bit position of a_lp

Map counter to bit position of b_lp


If both A and B completed one turn, initialize counters.

For debugging golden model



```
task cmp_chk ;
input [11:0] g_a_lp, g_b_lp ;
input [11:0] a_lp, b_lp ;
begin
  if ( g_a_lp != a_lp ) begin
    $display("at t=%d, error in a_lp  golden=%b, target=%b",
             $stime, g_a_lp, a_lp ) ;
    #10 $finish ;
  end
  else begin
    if ( g_b_lp != b_lp ) begin
      $display("at t=%d, error in b_lp  golden=%b, target=%b",
               $stime, g_b_lp, b_lp ) ;
      #10 $finish ;
    end
  end
end
end


endtask
```



This task check if the output of the golden model and the target model are the same or not.

} Check ring A

} Check ring B



```
initial begin
flick = 0 ;
while ( ~rst_n ) begin
    # 1 ;
end
```


} Wait for reset negated.


```
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_b_lp[11] == 1 ) ;
#CYCL $display("single turn check end");
```

} simple test.
First A finish and then B

```
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_a_lp[11] == 1 ) #CYCL ;
@ ( timng ) flick = 1 ; // check if flick don't care
wait ( g_b_lp[11] == 1 ) ;
@ ( timng ) ;
@ ( timng ) flick = 0 ;
@ ( timng ) $display("single turn flick dont care check end");
```

} First A finish and then B.
flick does not care after
A finished.






```
@ ( timng ) flick=1 ;
wait ( g_a_lp[11] == 1 ) ;
wait ( g_b_lp[11] == 1 ) ;
wait ( g_a_lp == 0 & g_b_lp ==0 ) ;
@ ( timng ) flick = 0 ;
#CYCL $display ("flick always 1 test end") ;
```

flick is always 1

```
@ ( timng ) flick = 1 ;
#(CYCL) flick = 0 ;
wait ( g_a_lp[11]==1 ) ;
@ ( timng ) flick=1 ;
#(CYCL) flick = 0 ;
wait ( g_b_lp[10] == 1 ) ;
#(CYCL*2) ;
#CYCL $display("a0->a11->b11->b0->Brot->b10->A/B off check end") ;
```

First A stop at a11
and then B.
A and B finish at
the same time.





```
@ ( timng ) flick = 1 ;
#(CYCL*2) flick = 0 ;
wait ( g_b_lp[11]==1 ) #CYCL ;
@ ( timng ) flick = 1 ; // dont care check
wait ( g_a_lp[11] == 1 ) ;
@ ( timng ) #CYCL flick = 0 ;
#CYCL $display("a0->b0->Brot->b11->Boff/Arot check end") ;
```

B start at #0 and finish and then A

```
@ ( timng ) flick = 1 ;
#(CYCL*2) flick = 0 ;
wait ( g_b_lp[11]==1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_a_lp[11] == 1 ) ;
@ ( timng ) #CYCL ;
#CYCL $display("a0->b0->Brot->b11->a1->Arot->a11->A/Boff check end") ;
```

B start at #0 and at #11 B resume rotation and A/B finish at the same time.





```
@ ( timng ) flick = 1 ;
#(CYCL*2) flick = 0 ;
wait ( g_b_lp[11]==1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_a_lp[11] == 1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
#CYCL $display("flick = 1 at last A, last B check end") ;
```


Same to the previous case, but flick applied at the last lamp.

```
@ ( timng ) flick = 1 ;
#(CYCL*3) flick = 0 ;
wait ( g_b_lp[11] == 1 ) #CYCL ;
#CYCL $display("a0->b0->a1->Arot->a11->Aoff/b1->Brot->b11 check end") ;
```


See the message

```
@ ( timng ) flick = 1 ;
#(CYCL*3) flick = 0 ;
wait ( g_a_lp[11] == 1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_b_lp[11] == 1 ) #CYCL ;
#CYCL $display("a0->b0->a1->Arot->a11->b1->Brot->b11->A/B off check end") ;
```


See the message




```
@ ( timng ) flick = 1 ;  
#(CYCL*3) flick = 0 ;  
wait ( g_a_lp[11] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp[6] == 1 ) ;  
@ ( timng ) flick = 1 ;  
wait ( g_b_lp[11] == 1 ) ;  
@ ( timng ) #CYCL flick = 0 ;  
#CYCL $display(  
    "a0->b0->a1->Arot->a11->b1->Brot->b[6]/A off->Brot check end"  
);
```




} See the message




```
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[4] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp [7] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[6] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#(CYCL*3) flick = 0 ;  
wait ( g_b_lp[11] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp[3] == 1 ) #CYCL;  
#CYCL $display("random turn A finich first check end") ;
```




```
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[4] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp [7] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[6] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#(CYCL*3) flick = 0 ;  
wait ( g_b_lp[11] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[11]== 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp[3] == 1 ) #CYCL;  
#CYCL $display(  
    "random turn A finish first and flick on last A lamp check end"  
);
```

```
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[2] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_b_lp [9] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[6] == 1 ) ;  
@ ( timng ) flick = 1 ;  
#CYCL flick = 0 ;  
wait ( g_a_lp[11] == 1 ) #CYCL;  
#CYCL $display("random turn B finich first check end") ;
```





```

@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_a_lp[2] == 1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_b_lp [9] == 1 );
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_a_lp[6] == 1 );
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
wait ( g_b_lp[1] == 1 ) ;
@ ( timng ) flick = 1 ;
#CYCL flick = 0 ;
@ ( g_a_lp[11] == 1 ) #CYCL;
#CYCL $display(
    "random turn B finich first and flick at last B lamp check end"
);
#(CYCL*2) ;
$display("test OK, No error in the target module") ;
#5;
$finish;
end
//
endmodule

```

} No bug if this sentence executed.

A sample answer

If the number of lamps in the ring is infinite, then rotating ring is toggled from A to B or from B to A every time flick becomes 1. Very simple logic is applicable to the system.

However, because of the limited number of lamps, the rings can not rotate forever. This makes the system complex.






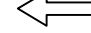
Taking into the fact that if the last lamp is on, the ring can not keep rotating, we can chose "the last lamp on" as one of major events to determine the behavior of the system.

And we can draw a state transition table on the next page.

This table can be mapped into RTL code less than 300 lines.

However, the code is not applicable for systems having more than 2 rings. Now, let's think of the architecture applicable to more than 2 rings system.

A state transition table for 2-ring system

last A is on	last B is on	state flick	INTL	A_ROT_ B_NYS_	A_PAU_ B_ROT_	A_ROT_ B_PAU_	A_FIN_ B_ROT_	A_ROT_ B_FIN_
0	0	0	nop	rot_a=1	rot_b=1	rot_a=1	rot_b=1	rot_a=1
		1	rot_a=1 → AR_BN	rot_b=1 → AP_BR	rot_a=1 → AR_BP	rot_b=1 → AP_BR		
	1	0			rot_a,b=1 → AR_BF	rot_a=1	rot_b=1 → INTL	
		1			rot_a=1 → AR_BP	rot_a,b=1 → AR_BF		
1	0	0		rot_a,b=1 → AF_BR	rot_b=1	rot_a,b=1 → AF_BR		rot_a=1 → INTL
		1		rot_b=1 → AP_BR	rot_a,b=1 → AF_BR	rot_b=1 → AP_BR		
	1		rot_a,b=1 → INTL					

NYS: not started yet

ROT: rotate

Pau: pause

FIN: completed



This can be mapped into
RTL in about 200 to 250
code lines of RTL.

A sample answer extendable to many rings

Let's focus on what is essential to this system.

Essential operation

Make up for exceptional cases

Rotating ring changes with the flick signal.


⇒ Only a rotating ring receives flick, and it send "rotate request" to another ring. Then, when a ring finishes one turn, it also send "rotate request" to another ring, this time, not initiated by flick.

What makes essential operation inapplicable?

⇒ The next ring already finished or at the last lamp, so it can not start/resume rotation.






⇒ Such ring pass "rotate request" to another ring.

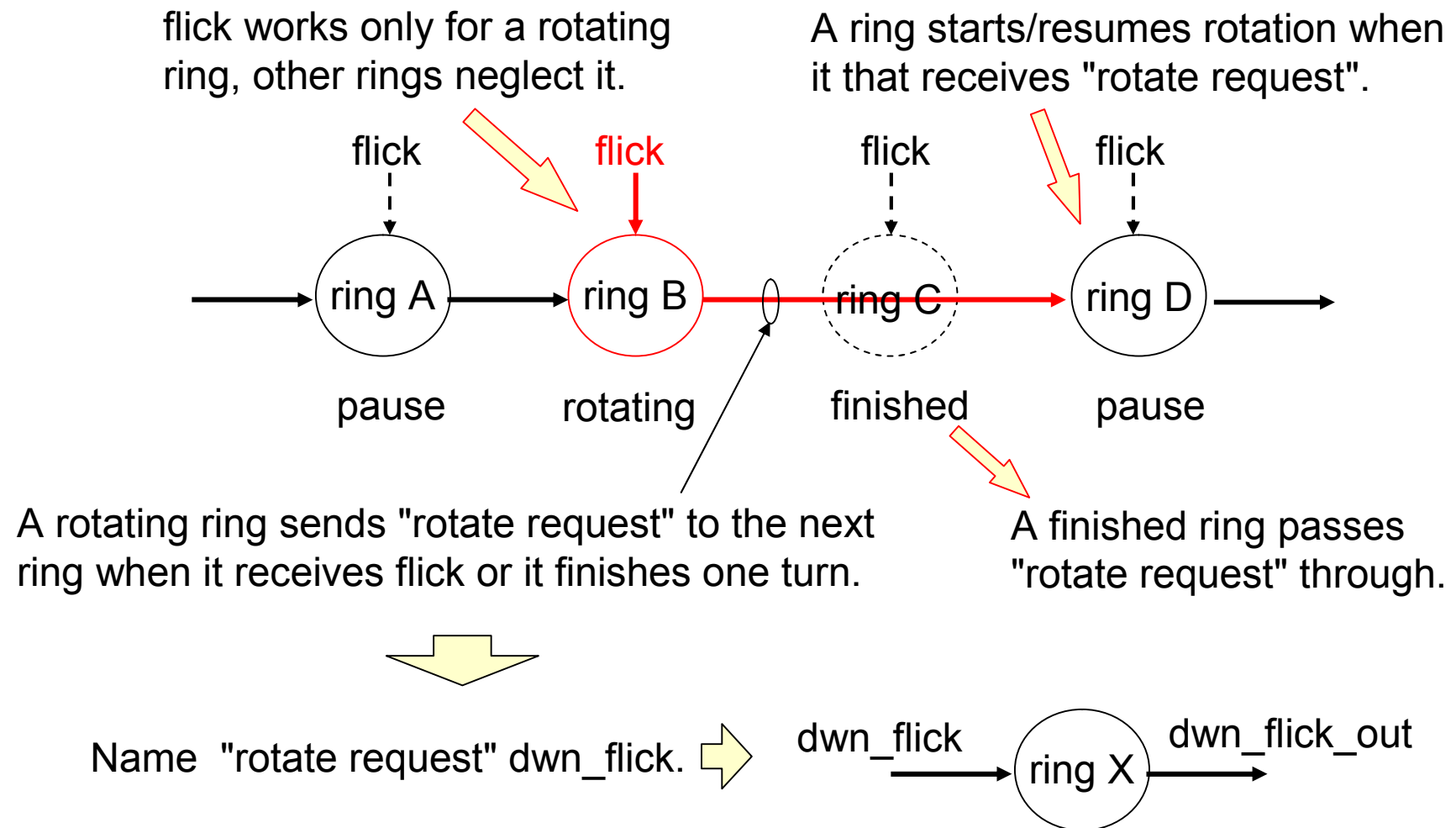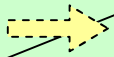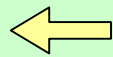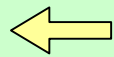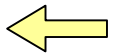The idea on the previous page can be illustrated as below.




goto_intl become on when
all ring finished one turn.

State transition table of a ring

event			Not started yet	Rotating	Pause	One turn complete
flick	dwn_flick	goto_intl	INTL	ROT	STP	FIN
x	x	1		dwn_flick_out=0 → INTL		
0	0	0	dwn_flick_out =0	if last lamp dwn_flick_out=1 → FIN else dwn_flick_out =0	dwn_flick_out =0	
1	0	0	dwn_flick_out =0	dwn_flick_out =1 → STP		
0	1	0	turn on initial lamp dwn_flick_out =0	 (same to goto_intl=1)	if last lamp dwn_flick_out=1 → FIN else dwn_flick_out =0	dwn_flick_out =1
1	1	0	→ ROT	dwn_flick_out =1 → ROT	→ ROT	

 
In the all boxes above, fin is calculated by (last lamp on or state is FIN)? 1:0 ;




For all green boxes, lamp shall newly start, rotate, or all lamps become off.

Total system structure

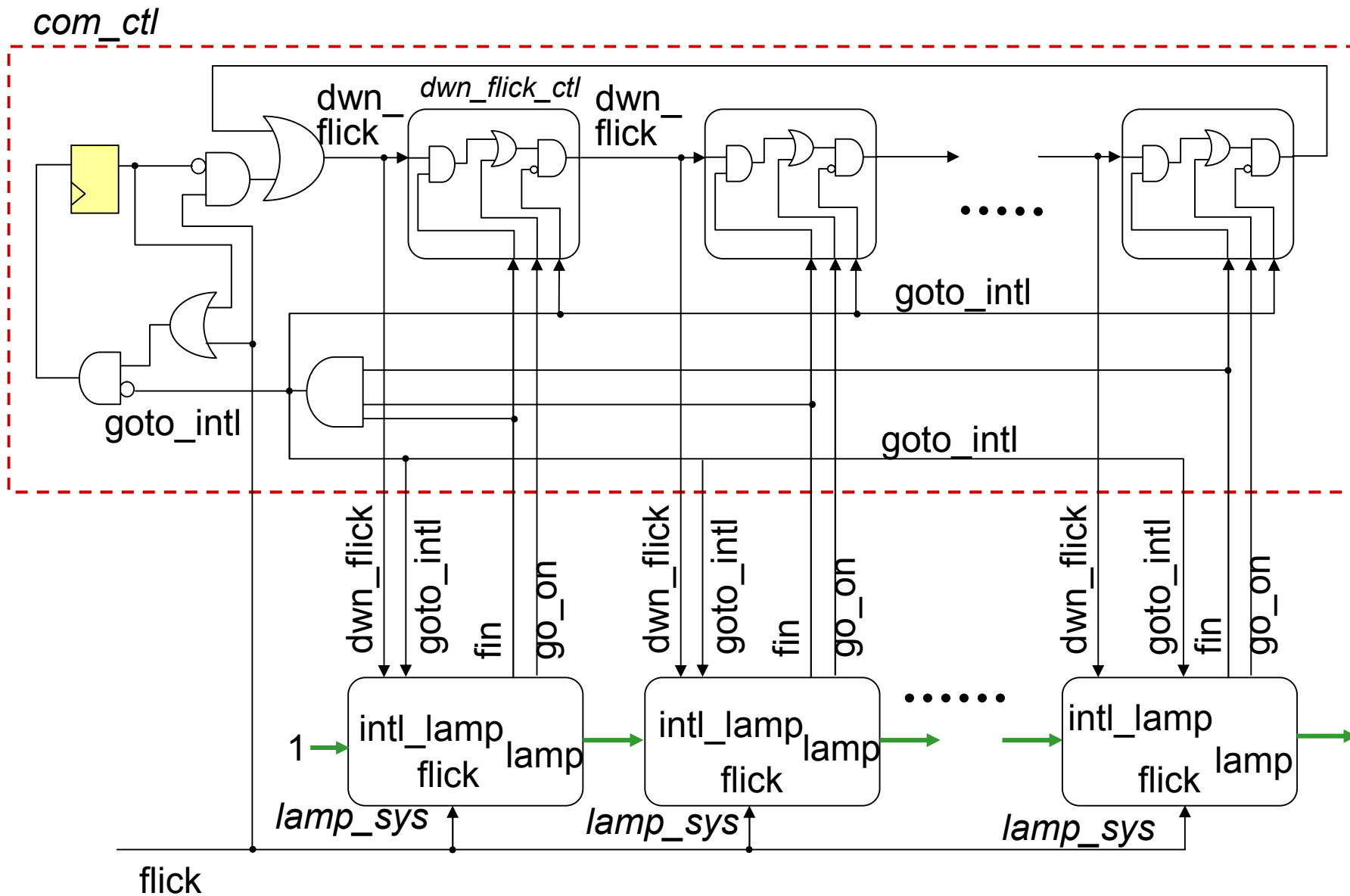The logic uses counters to keep on-lamp position of rings.



The structure of lamp_sys

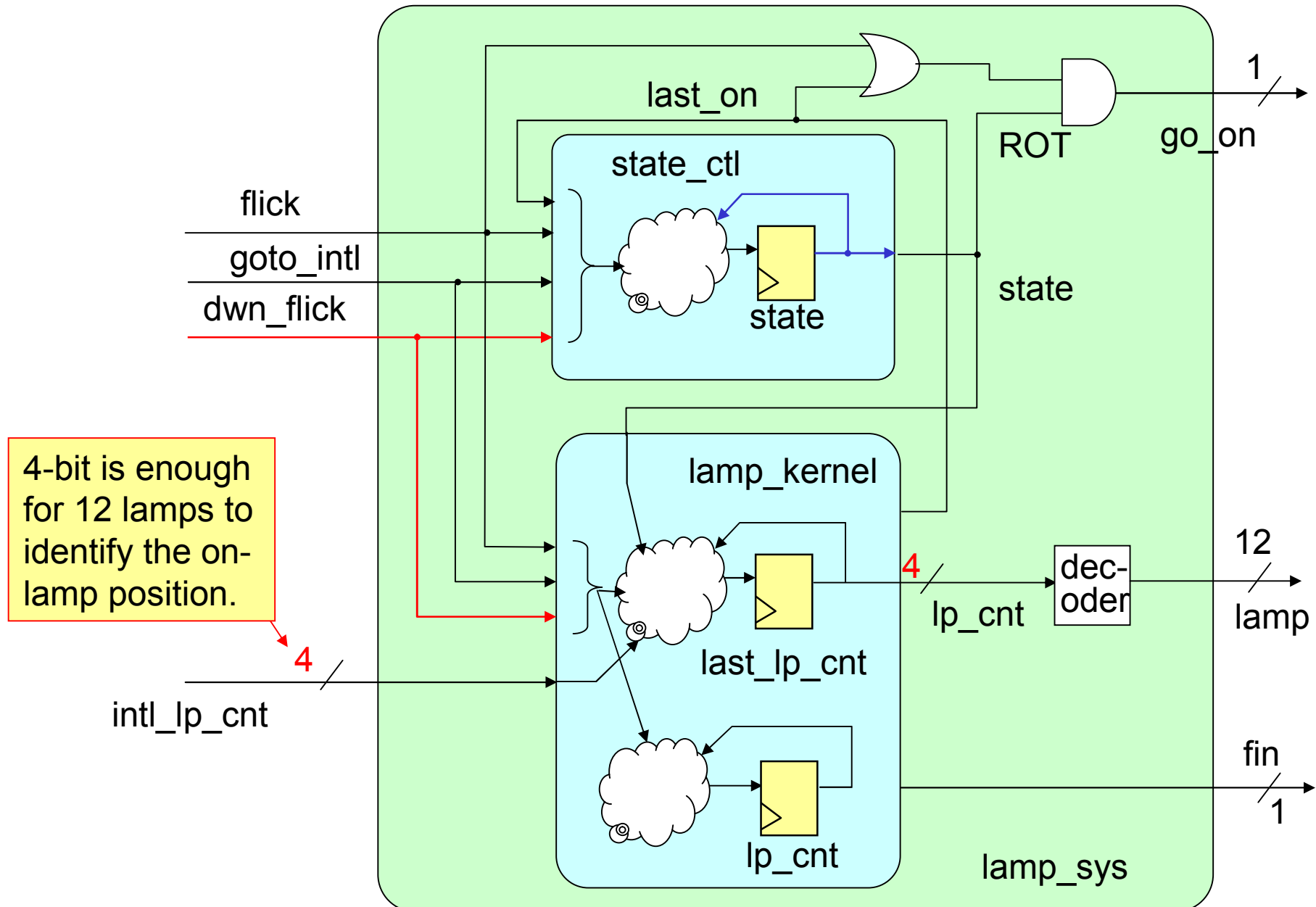

A sample target code

For two rings, define
is commented out.

```
//`define R4
module multi_ring( clk, rst_n, flick,
    lamp_1, lamp_2
`ifdef R4
    , lamp_3, lamp_4
`endif
);
parameter NUM_LMP = 12 ;
parameter BW_LP_CNT = 4 ;
// first ring start count
parameter [BW_LP_CNT-1:0] INTL_CNT = 1
; //
input clk, rst_n ;
input flick ;
output [NUM_LMP-1:0]
    lamp_1, lamp_2
`ifdef R4
    , lamp_3, lamp_4
`endif
;

wire clk, rst_n ;
wire flick ;
wire [NUM_LMP-1:0]
    lamp_1, lamp_2
`ifdef R4
    , lamp_3, lamp_4
`endif
;
```


This code is ready for 4 rings. By defining R4, it works
for 4 rings, otherwise it works for 2 rings.

```
// common control signals
wire fin_1, fin_2
`ifdef R4
    , fin_3, fin_4
`endif
;
wire goto_intl ;

// internal variables
wire [BW_LP_CNT-1:0]
    lp_1_cnt, lp_2_cnt
`ifdef R4
    , lp_3_cnt, lp_4_cnt
`endif
;
wire dwn_flick_1, dwn_flick_2
`ifdef R4
    , dwn_flick_3, dwn_flick_4
`endif
;

// lamp position logic
assign lamp_1 = cnt_to_bit_posi(lp_1_cnt) ;
assign lamp_2 = cnt_to_bit_posi(lp_2_cnt) ;
`ifdef R4
assign lamp_3 = cnt_to_bit_posi(lp_3_cnt) ;
assign lamp_4 = cnt_to_bit_posi(lp_4_cnt) ;
`endif
```


convert
from
counter
to bit
position



```
// connection
com_ctl com_ctl_01( .clk(clk), .rst_n(rst_n), .flick(flick),
`ifdef R4
    .fin_v( {fin_4, fin_3, fin_2, fin_1 } ),
    .go_on_v( {go_on_4, go_on_3, go_on_2, go_on_1 } ),
    .dwn_flick_v( {dwn_flick_4, dwn_flick_3, dwn_flick_2, dwn_flick_1} ),
`else
    .fin_v( { fin_2, fin_1 } ),
    .go_on_v( { go_on_2, go_on_1 } ),
    .dwn_flick_v( { dwn_flick_2, dwn_flick_1 } ),
`endif
    .goto_intl(goto_intl) );
```

} 4 rings connection

} 2 rings connection




```


//
lamp_sys lamp_sys_01( .clk(clk), .rst_n(rst_n), .goto_intl(goto_intl),
                    .flick(flick), .dwn_flick(dwn_flick_1),
                    .intl_lp_cnt( INTL_CNT ),
                    .lp_cnt(lp_1_cnt),
                    .fin(fin_1), .go_on(go_on_1)
                );
lamp_sys lamp_sys_02( .clk(clk), .rst_n(rst_n), .goto_intl(goto_intl),
                    .flick(flick), .dwn_flick(dwn_flick_2),
                    .intl_lp_cnt( lp_1_cnt ),
                    .lp_cnt(lp_2_cnt),
                    .fin(fin_2), .go_on(go_on_2)
                );
`ifdef R4
lamp_sys lamp_sys_03( .clk(clk), .rst_n(rst_n), .goto_intl(goto_intl),
                    .flick(flick), .dwn_flick(dwn_flick_3),
                    .intl_lp_cnt( lp_2_cnt ),
                    .lp_cnt(lp_3_cnt),
                    .fin(fin_3), .go_on(go_on_3)
                );
lamp_sys lamp_sys_04( .clk(clk), .rst_n(rst_n), .goto_intl(goto_intl),
                    .flick(flick), .dwn_flick(dwn_flick_4),
                    .intl_lp_cnt( lp_3_cnt ),
                    .lp_cnt(lp_4_cnt),
                    .fin(fin_4), .go_on(go_on_4)
                );
`endif
// connection end

```

2 rings connection

4 rings connection

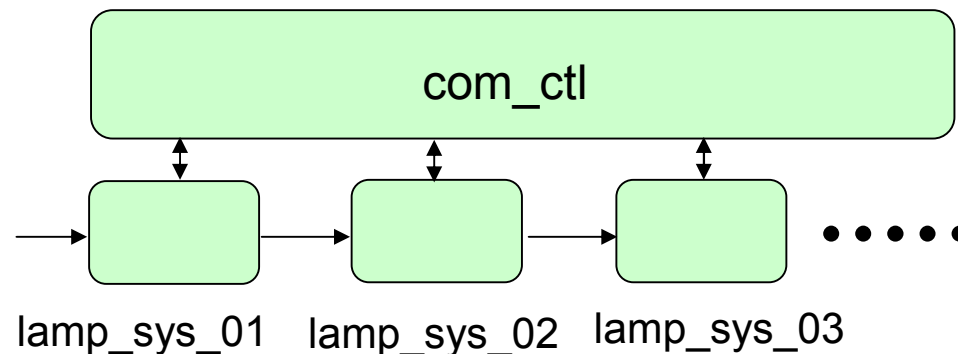




```
function [NUM_LMP-1:0] cnt_to_bit_posi ;  
input [BW_LP_CNT-1:0] lp_cnt ;  
reg [BW_LP_CNT-1:0] bit_ix ;  
//  
begin  
    cnt_to_bit_posi = 0 ;  
    if ( lp_cnt != 0 ) begin  
        bit_ix = lp_cnt -1'b1 ;  
        cnt_to_bit_posi[bit_ix] = 1'b1 ;  
    end  
end  
endfunction  
  
endmodule
```



convert from counter
to bit position



The followings are the lower level modules.



```


module com_ctl ( clk, rst_n, flick, fin_v, go_on_v, dwn_flick_v, goto_intl ) ;
`ifdef R4
parameter NUM_CRCL = 4 ;
`else
parameter NUM_CRCL = 2 ;
`endif
parameter FF_DLY =1 ;
input clk, rst_n ;
input flick ;
input [NUM_CRCL-1:0] fin_v ;
input [NUM_CRCL-1:0] go_on_v ;
output goto_intl ;
output [NUM_CRCL-1:0] dwn_flick_v ;


wire clk, rst_n ;
wire flick ;
wire [NUM_CRCL-1:0] fin_v ;
wire [NUM_CRCL-1:0] go_on_v ;
wire goto_intl ;
wire [NUM_CRCL-1:0] dwn_flick_v ;

// internal variable
reg sys_st ; // 0 in initial state, 1 not in initial state
wire next_sys_st ;
wire dwn_flick_loop ; // dwn_flick_out of the Last circle

//
assign goto_intl = & fin_v[NUM_CRCL-1:0] ;
assign dwn_flick_v[0] = dwn_flick_loop | ( flick & (~sys_st) ) ;


```





```
// FF for sys_st
always @ ( posedge clk or negedge rst_n ) begin
  if ( ~rst_n ) begin
    sys_st <= 1'b0 ;
  end
  else begin
    sys_st <= #FF_DLY next_sys_st ;
  end
end
assign next_sys_st = (~goto_intl) & ( flick | sys_st )
;
```

FF to memorize
"system started"

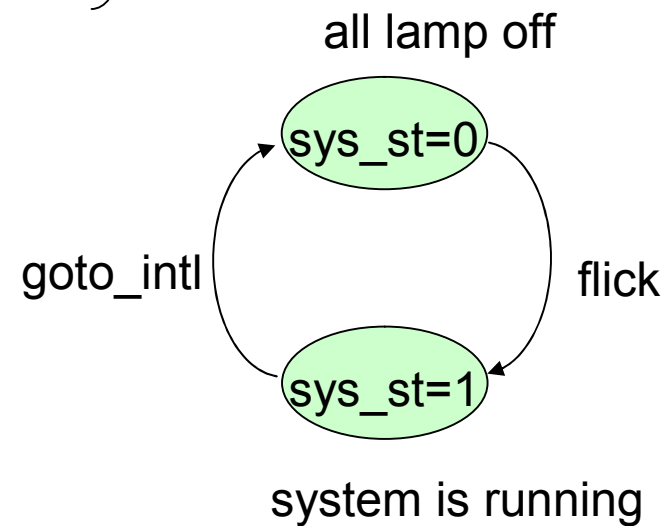

```

// connection
dwn_flick_ctl dwn_flick_ctl_01(
    .goto_intl(goto_intl),
    .dwn_flick(dwn_flick_v[0]),
    .flick(flick),
    .go_on(go_on_v[0]),
    .fin(fin_v[0]),
    .dwn_flick_out(dwn_flick_v[1])
);
dwn_flick_ctl dwn_flick_ctl_02(
    .goto_intl(goto_intl),
    .dwn_flick(dwn_flick_v[1]),
    .flick(flick),
    .go_on(go_on_v[1]),
    .fin(fin_v[1]),
    .dwn_flick_out(dwn_flick_v[2])
);
`ifdef R4
dwn_flick_ctl dwn_flick_ctl_03(
    .goto_intl(goto_intl),
    .dwn_flick(dwn_flick_v[2]),
    .flick(flick),
    .go_on(go_on_v[2]),
    .fin(fin_v[2]),
    .dwn_flick_out(dwn_flick_v[3])
);
dwn_flick_ctl dwn_flick_ctl_04(
    .goto_intl(goto_intl),
    .dwn_flick(dwn_flick_v[3]),
    .flick(flick),
    .go_on(go_on_v[3]),
    .fin(fin_v[3]),
    .dwn_flick_out(dwn_flick_loop)
);
`endif

//
endmodule

```

2 rings connection

4 rings connection

2 rings connection



```
module dwn_flick_ctl( goto_intl, dwn_flick, flick, go_on, fin, dwn_flick_out );
input goto_intl, dwn_flick, flick, go_on, fin ;
output dwn_flick_out ;
```

```
wire goto_intl, dwn_flick, flick, go_on, fin ;
wire dwn_flick_out ;
```

```
//
assign dwn_flick_out = (~goto_intl) & ( go_on | ( fin & dwn_flick ) ) ;
//
```

```
endmodule
```

```
// *****
```

```
module state_ctl ( clk, rst_n, goto_intl, flick, dwn_flick, last_on, state ) ;
```

```
parameter FF_DLY = 1 ;
```

```
parameter INTL = 2'b00 ; // initial, all lamp off
```

```
parameter ROT = 2'b01 ; // rotating
```

```
parameter STP = 2'b10 ; // stop
```

```
parameter FIN = 2'b11 ; // finished one turn, all lamp off
```

```
//
```

```
input clk, rst_n ;
```

```
input goto_intl ;
```

```
input flick, dwn_flick ;
```

```
input last_on ;
```

```
output [1:0] state ;
```

```
//
```

```
wire clk, rst_n ;
```

```
wire goto_intl ;
```

```
wire flick, dwn_flick ;
```

```
wire last_on ;
```

```
reg [1:0] state ; // FF
```

```
//
```

```
reg [1:0] next_state ; // non-FF
```

```
// state transition logic
```

```
always @ ( posedge clk or negedge rst_n ) begin
```


```
if ( ~rst_n ) state <= INTL ;
```

```
else state <=#FF_DLY next_state ;
```

```
end
```




FF for the state

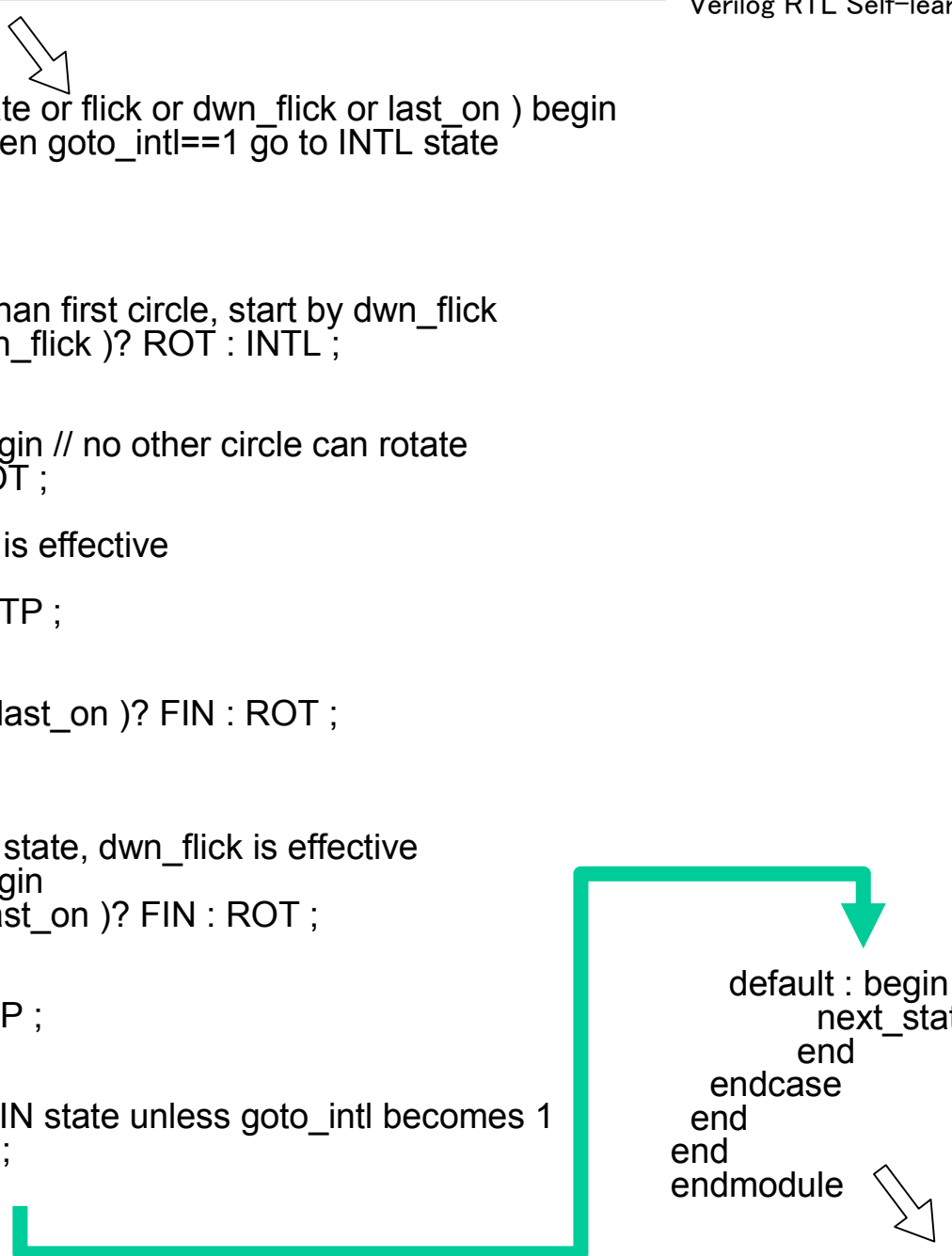

```

always @ ( goto_intl or state or flick or dwn_flick or last_on ) begin
  if ( goto_intl ) begin // when goto_intl==1 go to INTL state
    next_state = INTL ;
  end
  else begin
    case ( state )
      INTL : begin // Other than first circle, start by dwn_flick
        next_state = ( dwn_flick )? ROT : INTL ;
      end
      ROT : begin
        if ( dwn_flick ) begin // no other circle can rotate
          next_state = ROT ;
        end
        else begin // flick is effective
          if ( flick ) begin
            next_state = STP ;
          end
          else begin
            next_state = ( last_on )? FIN : ROT ;
          end
        end
      end
      STP : begin // in STP state, dwn_flick is effective
        if ( dwn_flick ) begin
          next_state = ( last_on )? FIN : ROT ;
        end
        else begin
          next_state = STP ;
        end
      end
      FIN : begin // stay in FIN state unless goto_intl becomes 1
        next_state = FIN ;
      end
      default : begin
        next_state = 2'bxx ;
      end
    endcase
  end
end
endmodule

```





```

module lamp_kernel( clk, rst_n, goto_intl, state, flick, dwn_flick, intl_lp_cnt,
                    lp_cnt, last_on, fin );
parameter FF_DLY = 1;
parameter NUM_LMP = 12;
parameter BW_LP_CNT = 4;
parameter INTL = 2'b00; // initial, all lamp off
parameter ROT = 2'b01; // rotating
parameter STP = 2'b10; // stop
parameter FIN = 2'b11; // finished one turn, all lamp off
//
input clk, rst_n;
input goto_intl;
input [1:0] state;
input flick, dwn_flick;
input [BW_LP_CNT-1:0] intl_lp_cnt; // initial start lamp position
output [BW_LP_CNT-1:0] lp_cnt;
output last_on, fin;
//
wire clk, rst_n;
wire goto_intl;
wire [1:0] state;
wire flick, dwn_flick;
wire [BW_LP_CNT-1:0] intl_lp_cnt;
reg [BW_LP_CNT-1:0] lp_cnt;
wire last_on, fin;
//
reg [BW_LP_CNT-1:0] next_lp_cnt; // non-FF
reg [BW_LP_CNT-1:0] last_lp_cnt; // last lamp position FF
reg [BW_LP_CNT-1:0] next_last_lp_cnt; // non-FF
//
assign last_on = ( ( lp_cnt == last_lp_cnt ) &
                  ( ( state == ROT ) | ( state == STP ) ) );
assign fin = ( last_on | ( state == FIN ) ) ? 1 : 0;

```

} last_on and fin evaluation







```
// lamp FF logic
always @ ( posedge clk or negedge rst_n ) begin
  if( ~rst_n ) begin // clear lamp on reset
    lp_cnt <= 0 ;
  end
  else begin
    lp_cnt <=#FF_DLY next_lp_cnt ;
  end
end
```


} FF for lamp position
counter

```
always @ ( goto_intl or state or flick or dwn_flick or last_on or intl_lp_cnt or
lp_cnt ) begin
  if ( goto_intl ) begin // on go_to_intl clear lamp
    next_lp_cnt = 0 ;
  end
  else begin
    case ( state )
      INTL : begin
        case ( { flick, dwn_flick } )
          2'b01 : begin // start from #0 lamp if flick=0
            next_lp_cnt = 1 ;
          end
          2'b11 : begin // start from intl_lamp if flick=1
            next_lp_cnt = intl_lp_cnt ;
          end
          default : begin // if dwn_flick=0, do not start
            next_lp_cnt = lp_cnt ;
          end
        endcase
      end
    endcase
  end
end
```





```
ROT : begin
    if ( dwn_flick ) begin
        next_lp_cnt = rot_lamp(lp_cnt) ;
    end
    else begin
        if ( flick ) begin // if flick=1 in ROT, stop
            next_lp_cnt = lp_cnt ;
        end
        else begin
            next_lp_cnt = ( last_on )? 0 : rot_lamp(lp_cnt) ;
        end
    end
end
end
STP : begin
    if ( dwn_flick ) begin
        next_lp_cnt = ( last_on )? 0 : rot_lamp(lp_cnt) ;
    end
    else begin
        next_lp_cnt = lp_cnt ;
    end
end
default : begin
    next_lp_cnt = lp_cnt ;
end
endcase
end
end
```



```


// last lamp position logic
always @ ( posedge clk or negedge rst_n ) begin
    if( ~rst_n ) begin // set last lamp position
        last_lp_cnt <= NUM_LMP ;
    end
    else begin
        last_lp_cnt <=#FF_DLY next_last_lp_cnt ;
    end
end
end
reg [BW_LP_CNT-1:0] temp_cnt ;
always @ ( state or flick or dwn_flick or intl_lp_cnt or last_lp_cnt ) begin
    case ( state )
        INTL : begin
            if ( flick & dwn_flick ) begin
                temp_cnt = intl_lp_cnt - 1'b1 ;
                next_last_lp_cnt = (temp_cnt )? temp_cnt : NUM_LMP ;
            end
            else begin
                next_last_lp_cnt = last_lp_cnt ;
            end
        end
        default : begin
            next_last_lp_cnt = last_lp_cnt ;
        end
    endcase
end


function [BW_LP_CNT-1:0] rot_lamp ;
input [BW_LP_CNT-1:0] lp_cnt ;
reg [BW_LP_CNT-1:0] rot_wk ;
begin
    rot_wk = lp_cnt + 1'b1 ;
    rot_lamp = ( rot_wk > NUM_LMP )? (rot_wk - NUM_LMP) : rot_wk ;
end
endfunction

endmodule

```

FF for last lamp
position counter

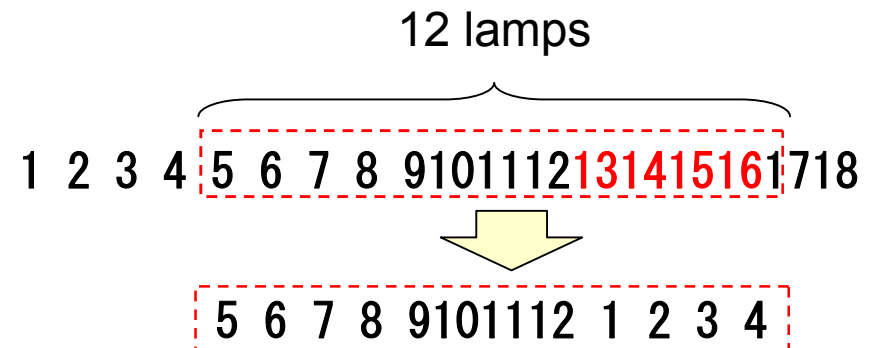



```

module lamp_sys( clk, rst_n, goto_intl, flick, dwn_flick, intl_lp_cnt,
                lp_cnt, fin, go_on );
parameter NUM_LMP = 12 ;
parameter BW_LP_CNT = 4 ;
parameter FF_DLY = 1 ;

parameter INTL = 2'b00 ; // initial, all lamp off
parameter ROT = 2'b01 ; // rotating
parameter STP = 2'b10 ; // stop
parameter FIN = 2'b11 ; // finished one turn, all lamp off


//
input clk, rst_n ;
input goto_intl ; // 1 if go to INTL state
input flick, dwn_flick ;
input [BW_LP_CNT-1:0] intl_lp_cnt ; // initial lamp position

output [BW_LP_CNT-1:0] lp_cnt ; // On lamp position counter
output fin ; // 1 if last lamp on or FIN state, else 0
output go_on ; // 1 if dwn_flick must be given to the next circle
//
wire clk, rst_n ;
wire goto_intl ;
wire flick, dwn_flick ;
wire [BW_LP_CNT-1:0] intl_lp_cnt ;

wire [BW_LP_CNT-1:0] lp_cnt ;
wire fin ;
wire go_on ;

// internal variables
wire last_on ; // 1 if last lamp is on

```



↙


```
// control signals and connection
assign go_on = (state == ROT) & ( flick | last_on );

state_ctl state_ctl_01( .clk(clk), .rst_n(rst_n),
    .goto_intl(goto_intl),
    .flick(flick), .dwn_flick(dwn_flick), .last_on(last_on),
    .state(state)
);
lamp_kernel lamp_kernel_01( .clk(clk), .rst_n(rst_n),
    .goto_intl(goto_intl), .state(state),
    .flick(flick), .dwn_flick(dwn_flick),
    .intl_lp_cnt(intl_lp_cnt),
    .lp_cnt(lp_cnt), .last_on(last_on), .fin(fin)
);


endmodule
```

file name: multi_ring.v

Run this code for 4 rings
system if you have time.

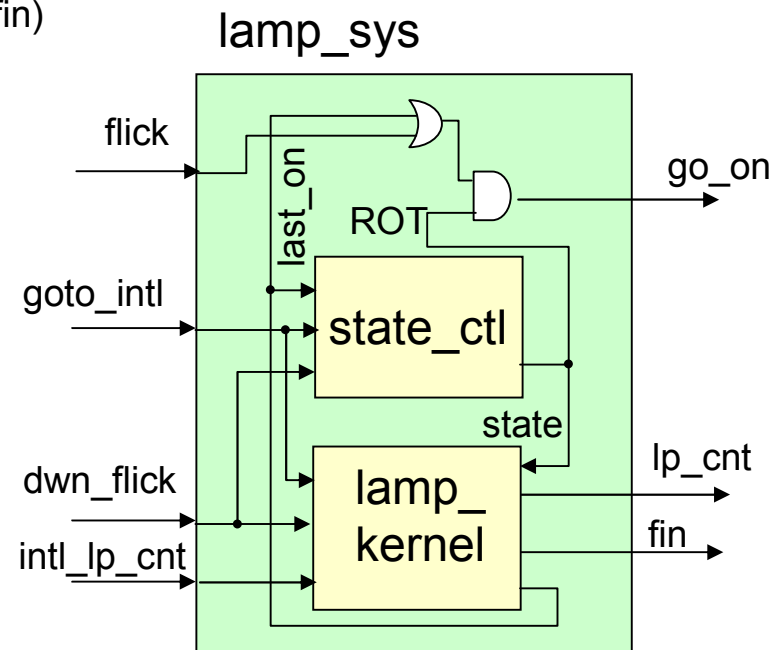


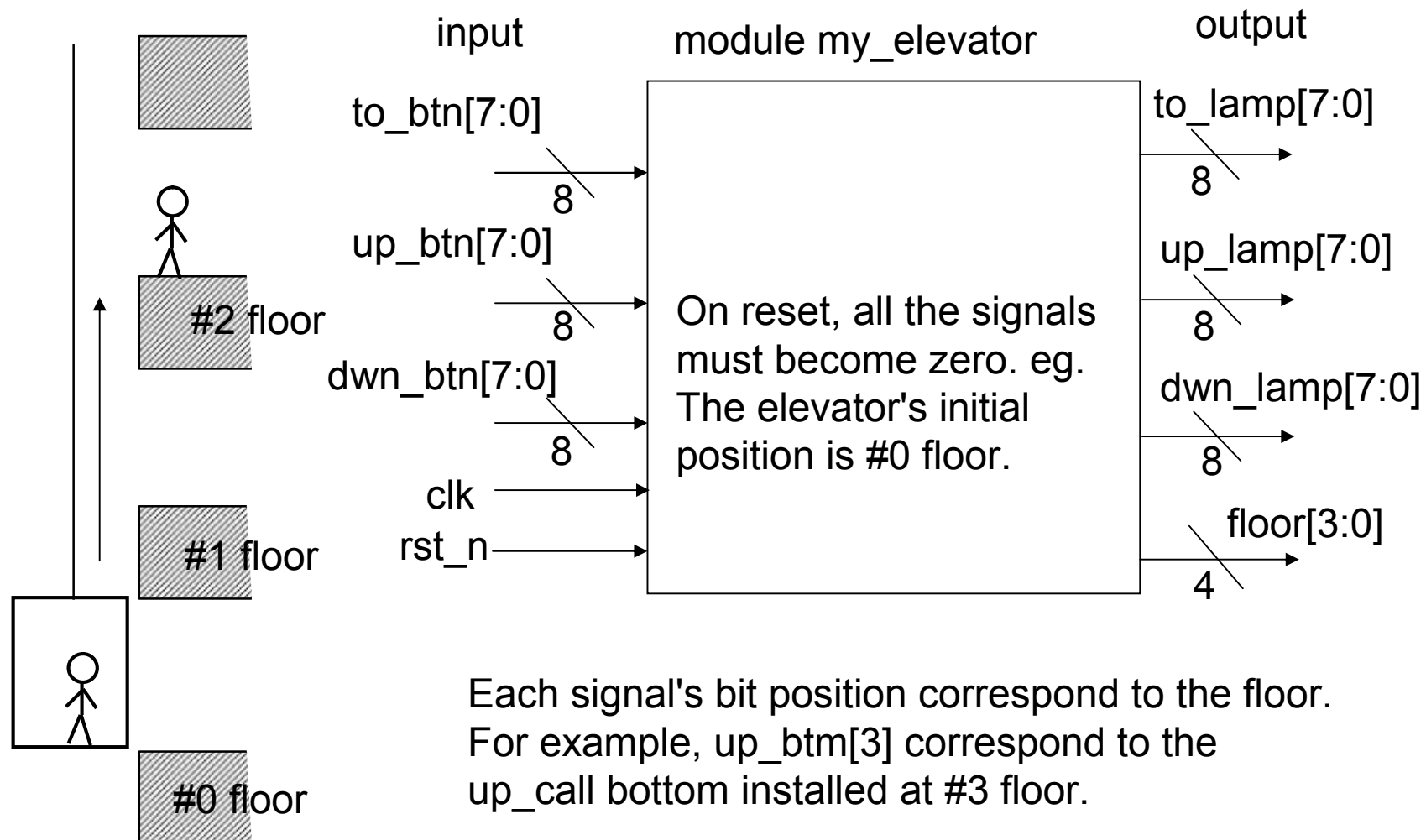
Ex 6-4. Elevator : Design a module to control an elevator cage moving up and down through 8 stories high building.



- to_btn[7:0] : installed in the elevator cage. If pushed, the corresponding to_lamp will become on at the next clock rise time.
- to_lamp[7:0] : installed in the elevator cage. It shows the floor to stop and becomes on when to_btn pushed, and becomes off when the elevator stops at the designated floor.
- up_btn[7:0] : installed on each floor. Bit i is installed on #i floor. Becomes on if up-going elevator is requested.
- dwn_btn[7:0] : installed on each floor. Bit i is installed on #i floor. Becomes on if down-going elevator is requested.
- up_lamp[7:0] : installed on each floor. Bit i is installed on #i floor. Becomes on if up-going elevator request is accepted and becomes off when up_going elevator stops at the floor.
- dwn_lamp[7:0] : installed on each floor. Bit i is installed on #i floor. Becomes on if down-going elevator request is accepted and becomes off when down_going elevator stops at the floor.
- floor[3:0] : shows the position of the elevator in the building. floor = 3 means the elevator is at #3 floor.

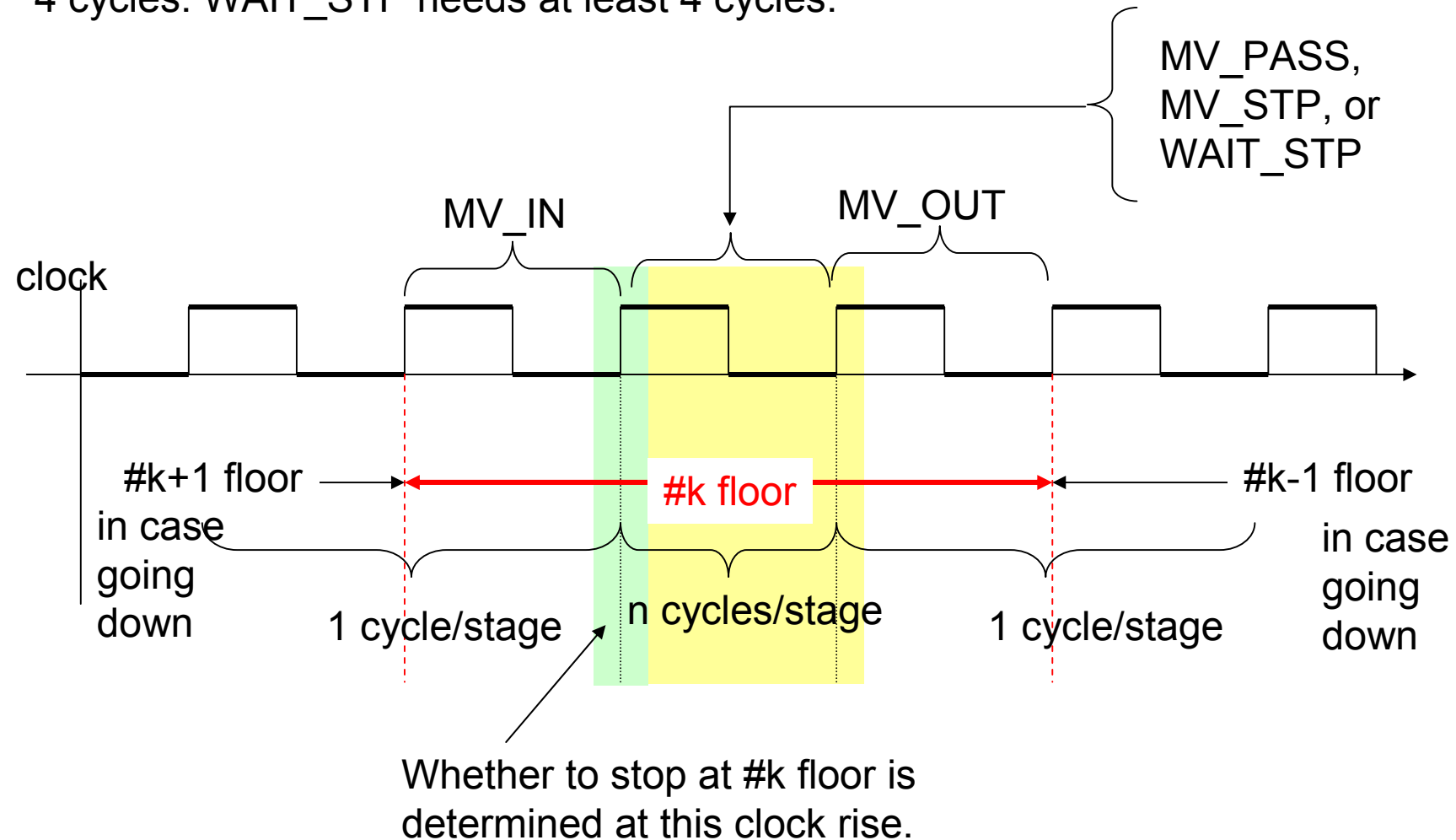The elevator cage needs 3 stages to pass one floor. The first stage is MV_IN, and the middle stage is MV_PASS, MV_STP, or WAIT_STP, and the last stage is MV_OUT. MV_IN, MV_PASS, and MV_OUT need 1 cycle. MV_STP needs 4 cycles. WAIT_STP needs at least 4 cycles.




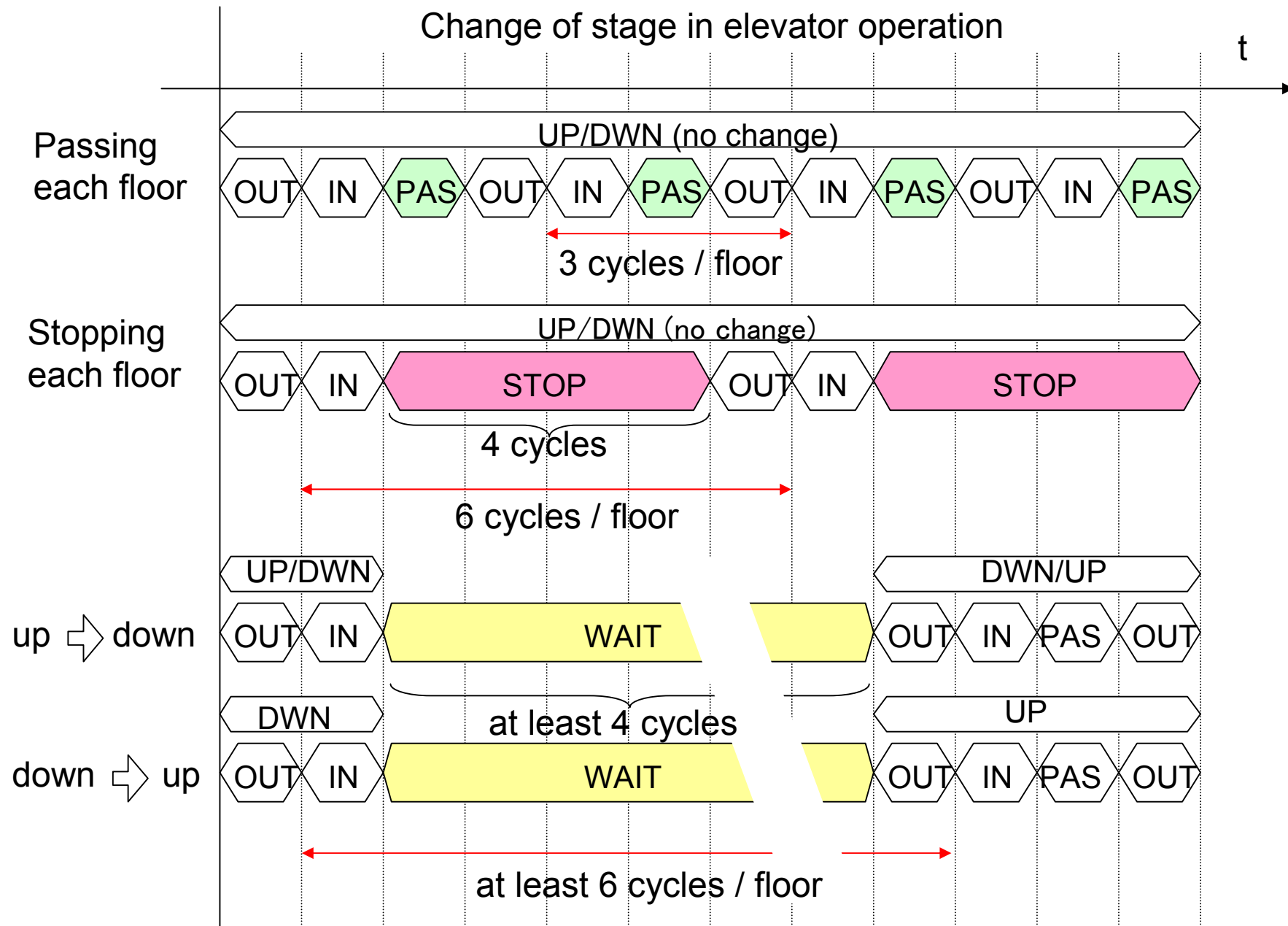

Elevator state

State (stage)			The next state
(1)	UP_ GOING or	MV_OUT	MV_IN of one floor up (incase UP_GOING) or MV_IN of one floor down (incase DWN_GOING). No change of UP/DWN direction.
(2)		MV_IN	(3)MV_IN, (4)MV_STP, or (5)WAIT_STP of the same floor depending on xx_lamp at clock rise time. UP/DWN direction may change.
(3)		MV_PAS	MV_OUT of the same floor. No change of UP/DWN direction.
(4)	DWN_ GOING	MV_STP	Stay in this state 4 cycles, and then go to MV_OUT. No change of UP/DWN direction.
(5)	WAIT_STP		After staying in this state 4 cycles go to (1)MV_OUT of (5)WAIT_STP of the same floor depending on xx_lamp.

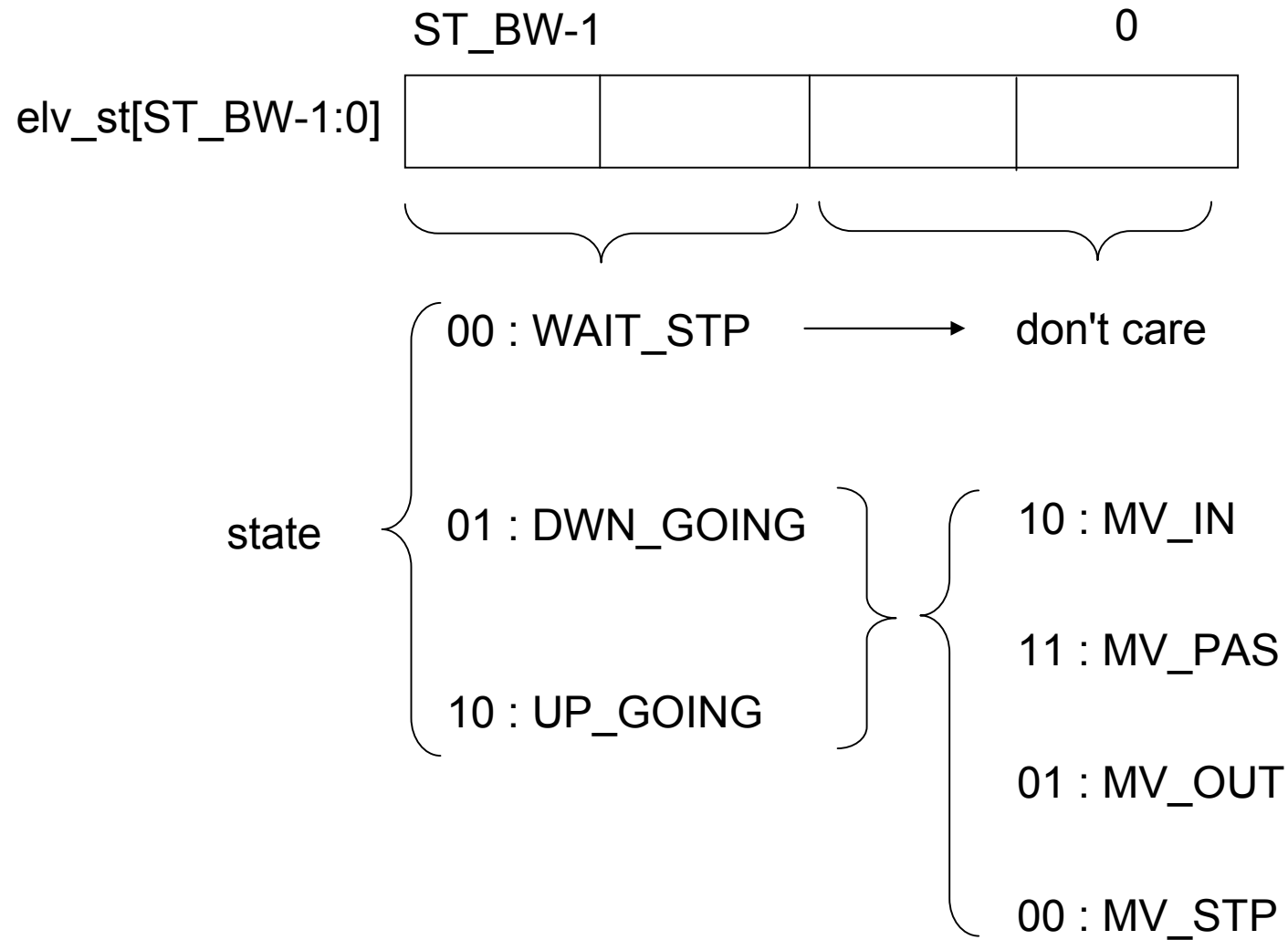Use the following state variable if needed.




Action in each state

State	Operation at clock rise time
(1) MV_OUT	If UP_GOING add 1 to floor, if DWN_GOING subtract 1 from floor. ⇒ (2) MV_IN
(2) MV_IN	Go to $\left\{ \begin{array}{l} \Rightarrow (3) \text{ MV_PAS} \\ \Rightarrow (4) \text{ MV_STP} \\ \Rightarrow (5) \text{ WAIT_STP} \end{array} \right\}$ by following the rule on the next page.
(3) MV_PAS	⇒ (2) MV_OUT
(4) MV_STP	After staying 4 cycles in this state ⇒ (2) MV_OUT
(5) WAIT_STP	After staying 4 cycles in this state, check the flowing at clock rise time. If any call from upper floors ⇒ (1) MV_OUT In case call from upper floors, set UP_GOING. If from lower floors, set DWN_GOING. If both at the same time set UP_GOING. else no call ⇒ (5) WAIT_STP

Call from upper/lower floors can be checked as shown on the next page.

Operation in case of MV_IN (UP_GOING)

lamp state		description
Call from #k+1 or upper	to_lamp[k]=1 or up_lamp[k]=1	⇒ (4) MV_STP
	other than above	⇒ (3) MV_PAS
No call from #k+1 or upper	Call from #k-1 or lower	UP_GOING → DWN_GOING ⇒ (4) MV_STP
	No call from #k-1 or lower	⇒ (5) WAIT_STP

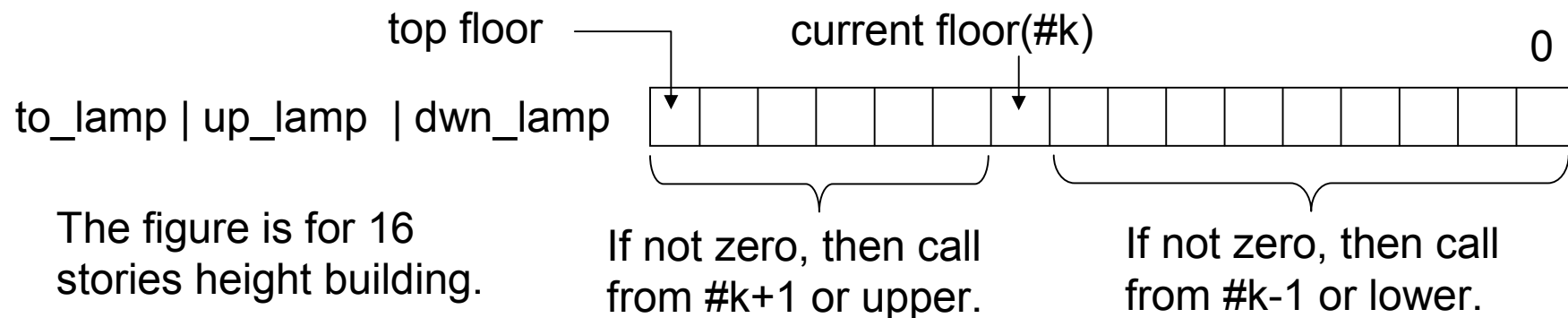

Operation in case of MV_IN (DWN_GOING)

lamp state		description
Call from #k-1 or lower	to_lamp[k]=1 or dwn_lamp[k]=1	⇒ (4) MV_STP
	other than above	⇒ (3) MV_PAS
No call from #k-1 or lower	Call from #k+1 or upper	DWN_GOING → UP_GOING ⇒ (4) MV_STP
	No call from #k+1 or upper	⇒ (5) WAIT_STP

To which state to move from MV_IN and WAIT_STP state is determined by moving up/down direction and to_lamp, up_lamp, and dwn_lamp. These lamps are turned on by to_btn, up_btn, and dwn_btn respectively. However, depending on the state and direction, some of these bottoms are invalid as shown below. They can turn on lamps only when they are valid. Note that, bit n of xx_btn is always valid if n is not a current floor.

validity of bit k of xx_btn when the cage is at #k floor

bottom	state
to_btn	In the states, MV_IN, MV_PAS, MV_STP, or WAIT_STP, the bit k is invalid. In other cases, valid.
up_btn	In case of UP_GOING, invalid if in the state of MV_IN, MV_PAS, MV_STP, or WAIT_STP. In other cases valid.
dwn_btn	In case of DWN_GOING, invalid if in the state of MV_IN, MV_PAS, MV_STP, or WAIT_STP. In other cases valid.

Following the rule of validity of xx_btn, xx_lamp is controlled as below.

Operation applicable to to_lamp

floor	Operation
current floor (#k)	<p>If in the state of MV_IN, MV_PAS, MV_STP, or WAIT_STP, then turn off to_lamp[k].</p> <p>In other states apply the following operation.</p> <p style="padding-left: 40px;">If to_btn[k] = 1, then to_lamp[k] = 1, else keep previous value.</p>
<p>other floor (#n)</p> <p>n is 0 to top floor except current floor.</p>	<p>If to_btn[n] = 1, then to_lamp[n] = 1, else keep previous value.</p>

Actual turn on/off operation must be applied at clock rise time, therefore, xx_lamp shall become 1 in the next clock cycle.

Example; If to_btn[k] is on in MV_OUT state, to_lamp[k] will be on throughout MV_IN state.

Operation applicable to up_lamp

floor	Operation
current floor (#k)	<p>When UP_GOING, and if in the state of MV_IN, MV_PAS, MV_STP, or WAIT_STP, then turn off up_lamp[k].</p> <p>In other states apply the following operation.</p> <p style="padding-left: 40px;">If up_btn[k] = 1, then up_lamp[k] = 1, else keep previous value.</p>
<p>other floor (#n)</p> <p>n is 0 to top floor except current floor.</p>	<p>If up_btn[k] = 1, then up_lamp[k] = 1, else keep previous value.</p>

Operation applicable to dwn_lamp

floor	Operation
current floor (#k)	<p>When DWN_GOING, and if in the state of MV_IN, MV_PAS, MV_STP, or WAIT_STP, then turn off dwn_lamp[k].</p> <p>In other states apply the following operation.</p> <p style="padding-left: 40px;">If dwn_btn[k] = 1, then dwn_lamp[k] = 1, else keep previous value.</p>
<p>other floor (#n)</p> <p>n is 0 to top floor except current floor.</p>	<p>If dwn_btn[k] = 1, then dwn_lamp[k] = 1, else keep previous value.</p>

Now write Verilog RTL code for elevator.

You do not have to use state definition given in the previous pages. You can use your own state variables. However, the elevator cage must operate as described in the previous pages.

When writing the code, you must consider the followings;

The number of floors must be adjustable. Write the code so that you can easily change the number of floors.

Do not write flat code. Create a structured code so that the system can be tested from lower level primitive module to higher level top module.

You must also write a test bench to test your code.

You may use a test bench shown on the next pages besides your own test bench.

Work flow for solutions

- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document including a state transition table,
- (4) Write a RTL code for the target module,
- (5) Run **the automatic test bench** on the next pages with the target module you created.

If your code is rejected, correct your code.

Copy and paste the test bench module on the next pages into you PC and run it with your my_elavator module to see if your code is OK or Not.

A sample test bench, automatic tester

```
// test bench for elevator exercise
//*****
module test_my_elevator ;
parameter FL_NUM = 8 ;
parameter FL_BW = 4 ;
parameter HF_CYCL = 5 ;
parameter CYCL = HF_CYCL * 2 ;
reg rst_n, clk ;
reg[FL_NUM-1:0] to_btn, up_btn, dwn_btn ;
wire[FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ;
wire[FL_BW-1:0] floor ;
// work
reg [400:1] msg ;
reg [2:0] cnt ;

// connect signals to game
my_elevator my_elevator_01 ( .rst_n(rst_n), .clk(clk),
                             .to_btn(to_btn), .up_btn(up_btn), .dwn_btn(dwn_btn),
                             .to_lamp(to_lamp), .up_lamp(up_lamp), .dwn_lamp(dwn_lamp),
                             .floor(floor)
                           ) ;
// connection end

always begin // clock generator
    clk = 1'b0 ; #HF_CYCL ;
    clk = 1'b1 ; #HF_CYCL ;
end
```

target module
connection

clock generator



Display variables 2 units time after clock rise

```
always @ ( posedge clk ) begin
  #2 $strobe("t=%d, rst=%b, clk=%b,¥n tfb=%b, ucb=%b, dcb=%b,¥n tlp=%b, ulp=%b,
  dlp=%b,¥n floor=%d, state=%b, cntr=%d, u_cl=%b, d_cl=%b",
    $time, rst_n, clk, to_btn, up_btn, dwn_btn, to_lamp, up_lamp, dwn_lamp, floor,
    my_elevator_01.elv_st, my_elevator_01.st_ctl_01.sty_cntr,
    my_elevator_01.st_ctl_01.up_call, my_elevator_01.st_ctl_01.dwn_call
  );
```

end

initial begin // give value to control variable

rst_n = 1'b0 ;

#CYCL rst_n = 1'b1 ;

end

Internal signals are observed,
change this part to fit to your
RTL code.

initial begin

to_btn = 8'b0000_0000 ;

up_btn = 8'b0000_0000 ;

dwn_btn = 8'b0000_0000 ;

\$display("***** test 1 start, no movement if there is no request") ;

@(posedge clk) #2 chk_stay(1, "must stay at #0 with no request", 0, 8'h00, 8'h00, 8'h00) ;

// check no move for no request

#(CYCL*9) chk_stay(0, "must stay at #0 with no request", 0, 8'h00, 8'h00, 8'h00) ;

// check no move for no request

\$display("test 1 end¥n¥n") ;

test1: Check keep no operation
if no request.

test2: Check if the cage can go top floor without stopping any floor if up call from the top floor.



```
$display("test 2 start, up call from #7 only and go to #7 and wait") ;
#CYCL up_btn = 8'b1000_0000 ;
#CYCL chk_stay( 1, "up_lamp[7] must turn on", 0, 8'h00, 8'h80, 8'h00 ) ;
    up_btn = 8'b0000_0000 ;
@( posedge clk ) #2 chk_stay( 1, "start going up", 0, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 1, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 2, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 3, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 4, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 5, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 3, "keep going up", 6, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 1, "arrive at #7", 7, 8'h00, 8'h80, 8'h00 ) ;
#CYCL chk_stay( 0, "arrive at #7", 7, 8'h00, 8'h00, 8'h00 ) ;
#(CYCL*5) chk_stay( 1, "stay at #7", 7, 8'h00, 8'h00, 8'h00 ) ;
$display("test 2 end¥n¥n") ;
```




test3: While at top floor, down call from all the floors, and one cycle later up call from all the floors. Check go down stopping at all the floors and go up again stopping at all the floors up to #6 floor.

While at the top floor, xx_btn for the top floor must be neglected.



```
$display("test 3 start, dwn call from all the floor and next up call from all the floor") ;
    dwn_btn = 8'b1111_1111 ;
#CYCL chk_stay( 1, "start #7 to down", 7, 8'h00, 8'h00, 8'h7f ) ;
    dwn_btn = 8'b0000_0000 ;
    up_btn = 8'b1111_1111 ;
#CYCL chk_stay( 1, "start #7 to down", 7, 8'h00, 8'h7f, 8'h7f ) ;
    up_btn = 8'b0000_0000 ;
#CYCL chk_stay( 1, "enter #6 to down", 6, 8'h00, 8'h7f, 8'h7f ) ;
#CYCL chk_stay( 5, "stopping #6",    6, 8'h00, 8'h7f, 8'h3f ) ;
#CYCL chk_stay( 1, "enter #5 to down", 5, 8'h00, 8'h7f, 8'h3f ) ;
#CYCL chk_stay( 5, "stopping #5",    5, 8'h00, 8'h7f, 8'h1f ) ;
```






```

#CYCL chk_stay( 1, "enter #4 to down", 4, 8'h00, 8'h7f, 8'h1f ) ;
#CYCL chk_stay( 5, "stopping #4",    4, 8'h00, 8'h7f, 8'h0f ) ;
#CYCL chk_stay( 1, "enter #3 to down", 3, 8'h00, 8'h7f, 8'h0f ) ;
#CYCL chk_stay( 5, "stopping #3",    3, 8'h00, 8'h7f, 8'h07 ) ;
#CYCL chk_stay( 1, "enter #2 to down", 2, 8'h00, 8'h7f, 8'h07 ) ;
#CYCL chk_stay( 5, "stopping #2",    2, 8'h00, 8'h7f, 8'h03 ) ;
#CYCL chk_stay( 1, "enter #1 to down", 1, 8'h00, 8'h7f, 8'h03 ) ;
#CYCL chk_stay( 5, "stopping #1",    1, 8'h00, 8'h7f, 8'h01 ) ;
#CYCL chk_stay( 1, "enter #0 to down", 0, 8'h00, 8'h7f, 8'h01 ) ;
#CYCL chk_stay( 1, "down to up change", 0, 8'h00, 8'h7f, 8'h00 ) ;
#CYCL chk_stay( 4, "stopping #0",    0, 8'h00, 8'h7e, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #1 to up", 1, 8'h00, 8'h7e, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #1",    1, 8'h00, 8'h7c, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #2 to up", 2, 8'h00, 8'h7c, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #2",    2, 8'h00, 8'h78, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #3 to up", 3, 8'h00, 8'h78, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #3",    3, 8'h00, 8'h70, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #4 to up", 4, 8'h00, 8'h70, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #4",    4, 8'h00, 8'h60, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #5 to up", 5, 8'h00, 8'h60, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #5",    5, 8'h00, 8'h40, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #6 to up", 6, 8'h00, 8'h40, 8'h00 ) ;
#CYCL chk_stay( 5, "stopping #6",    6, 8'h00, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 0, "wait at #6",    6, 8'h00, 8'h00, 8'h00 ) ;
$display("test 3 end¥n¥n") ;

```




test4: While at #6 floor, to_btn for #6, #4, #2, and #0 are on.
Check if pass #5, #3, and #1, and if stop at #4, #2, and #0.



```
$display("test 4 start, to_call#6,#4,#2,#0 and then up call from #0");
@(posedge clk ) #2 to_btn = 8'b0101_0101 ;
#CYCL chk_stay( 1, "start going dwn", 6, 8'h15, 8'h00, 8'h00 ) ;
    to_btn = 8'b0000_0000 ;
#CYCL chk_stay( 1, "leave #6 to dwn", 6, 8'h15, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #5",      5, 8'h15, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 2, "pass #5 to dwn", 5, 8'h15, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #4 to dwn", 4, 8'h15, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 5, "stay #4",      4, 8'h05, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #3 to dwn", 3, 8'h05, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 2, "pass #3",      3, 8'h05, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #2 to dwn", 2, 8'h05, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 5, "stay #2",      2, 8'h01, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #1 to dwn", 1, 8'h01, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 2, "pass #1",      1, 8'h01, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #0 to dwn", 0, 8'h01, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 5, "stay #0",      0, 8'h00, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 0, "wait st #0",    0, 8'h00, 8'h00, 8'h00 ) ;
$display("test 4 end\n\n") ;
```




test5: up down mixed operation




```

$display("test 5 start, random test");
@(posedge clk ) #2 to_btn = 8'b0000_0011 ;
#CYCL chk_stay( 1, "still at #0",    0, 8'h02, 8'h00, 8'h00 ) ;
    to_btn = 8'b0000_0000 ;
#CYCL chk_stay( 1, "start to up",    0, 8'h02, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 1, "enter #1",      1, 8'h02, 8'h00, 8'h00 ) ;
#CYCL chk_stay( 5, "stay at #1",    1, 8'h00, 8'h00, 8'h00 ) ;
    up_btn = 8'b0010_1010 ;
    dwn_btn = 8'b1000_0011 ;
#CYCL chk_stay( 1, "start to up",    1, 8'h00, 8'h28, 8'h81 ) ;
    up_btn = 8'b0000_0000 ;
    dwn_btn = 8'b0000_0000 ;
#CYCL chk_stay( 1, "leave #1",      1, 8'h00, 8'h28, 8'h81 ) ;
#CYCL chk_stay( 3, "passing #2",    2, 8'h00, 8'h28, 8'h81 ) ;
#CYCL chk_stay( 1, "enter #3",      3, 8'h00, 8'h28, 8'h81 ) ;
#CYCL chk_stay( 5, "stay #3",      3, 8'h00, 8'h20, 8'h81 ) ;
#CYCL chk_stay( 3, "passing #4",    4, 8'h00, 8'h20, 8'h81 ) ;
#CYCL chk_stay( 1, "enter #5",      5, 8'h00, 8'h20, 8'h81 ) ;
#CYCL chk_stay( 5, "stay #5",      5, 8'h00, 8'h00, 8'h81 ) ;
#CYCL chk_stay( 3, "passing #6",    6, 8'h00, 8'h00, 8'h81 ) ;

```






```

#CYCL chk_stay( 2, "enter #7",      7, 8'h00, 8'h00, 8'h81 ) ;
#CYCL chk_stay( 4, "stay #7",      7, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 3, "passing #6",   6, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 3, "passing #5",   5, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 3, "passing #4",   4, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 3, "passing #3",   3, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 3, "passing #2",   2, 8'h00, 8'h00, 8'h01 ) ;
    to_btn = 8'b0000_0010 ;
#CYCL chk_stay( 1, "enter #1",     1, 8'h02, 8'h00, 8'h01 ) ;
    to_btn = 8'b0000_0000 ;
#CYCL chk_stay( 5, "stay at #1",   1, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 1, "enter #0",     0, 8'h00, 8'h00, 8'h01 ) ;
#CYCL chk_stay( 0, "stay at #0",   0, 8'h00, 8'h00, 8'h00 ) ;
$display("test 5 end¥n¥n") ;

$display("test complete with no error¥n") ;
$finish ;
end

```



// *****

task chk_stay ; // check if stay cnt cycles, if cnt=0 check 8 cycles

input [2:0] cnt ;

input [400:1] msg ;

input [FL_BW-1:0] flr ;

input [FL_NUM-1:0] to_lp, up_lp, dwn_lp ;

begin : THIS_LOOP

chk_elv(msg, flr, to_lp, up_lp, dwn_lp) ;

if (cnt == 1) begin

disable THIS_LOOP ;

end

else begin

#CYCL chk_elv(msg, flr, to_lp, up_lp, dwn_lp) ;

if (cnt == 2) begin

disable THIS_LOOP ;

end

else begin

#CYCL chk_elv(msg, flr, to_lp, up_lp, dwn_lp) ;

if (cnt == 3) begin

disable THIS_LOOP ;

end

else begin


#CYCL chk_elv(msg, flr, to_lp, up_lp, dwn_lp) ;

if (cnt == 4) begin


disable THIS_LOOP ;

end

Task chk_stay : check if variables are the same to input arguments during cnt cycles. If cnt=0, check for 8 cycles.



```
else begin
    #CYCL chk_elv( msg, flr, to_lp, up_lp, dwn_lp ) ;
    if ( cnt == 5 ) begin
        disable THIS_LOOP ;
    end
    else begin
        #CYCL chk_elv( msg, flr, to_lp, up_lp, dwn_lp ) ;
        if ( cnt == 6 ) begin
            disable THIS_LOOP ;
        end
        else begin
            #CYCL chk_elv( msg, flr, to_lp, up_lp, dwn_lp ) ;
            if ( cnt == 7 ) begin
                disable THIS_LOOP ;
            end
            else begin
                #CYCL chk_elv( msg, flr, to_lp, up_lp, dwn_lp ) ;
            end
        end
    end
end
end
end
end
end
end
endtask
```





```
// *****
task chk_elv ;
input [400:1] msg ;
input [FL_BW-1:0] flr ;
input [FL_NUM-1:0] to_lp, up_lp, dwn_lp ;

begin
  if ( ( flr != floor ) | ( to_lp != to_lamp ) | ( up_lp != up_lamp ) | ( dwn_lp != dwn_lamp ) )
  begin
    $strobe("t=%0d, %s, floor=%0d : expected=%0d", $stime, msg, floor, flr ) ;
    $strobe(" to_lamp=%b : expected=%b, btn=%b\n up_lamp=%b : expected=%b,
btn=%b\n dw_lamp=%b : expected=%b, btn=%b",
    to_lamp, to_lp, to_btn, up_lamp, up_lp, up_btn, dwn_lamp, dwn_lp, dwn_btn ) ;
    $strobe("state=%b", my_elevator_01.elv_st );
    #1 $finish ;
  end
end

endtask

endmodule
```

Task chk_elv : Check if variables are same to the input arguments. If not, then output message and terminate simulation.


file name: test_my_elevator.v

A sample target code

```
// elevator control logic exercise
// top module
// (c) all right reserved, 2010, RVC, Corp.
module my_elevator ( clk, rst_n, to_btn, up_btn, dwn_btn,
                    to_lamp, up_lamp, dwn_lamp, floor    );
parameter FL_NUM = 8 ;
parameter FL_BW = 4 ; // bit width needed for FL_NUM, if FL_NUM=8, FL_BW must be 4.
                      // if FL_NUM=16, FL_BW must be 5. if FL_NUM=32, FL_BW must be 6.
                      // if FL_NUM=20, FL_BW must be 6

//
input clk, rst_n ;
input [FL_NUM-1:0] to_btn, up_btn, dwn_btn ;
output [FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ;
output [FL_BW-1:0] floor ;
// module connection
st_ctl st_ctl_01( .clk(clk), .rst_n(rst_n), .floor(floor),
                 .to_lamp(to_lamp), .up_lamp(up_lamp), .dwn_lamp(dwn_lamp),
                 .elv_st(elv_st)
                 );
elv_ctl elv_ctl_01( .clk(clk), .rst_n(rst_n), .elv_st(elv_st),
                  .floor(floor)
                  );
lamp_ctl lamp_ctl_01( .clk(clk), .rst_n(rst_n), .elv_st(elv_st), .floor(floor),
                    .to_btn(to_btn), .up_btn(up_btn), .dwn_btn(dwn_btn),
                    .to_lamp(to_lamp), .up_lamp(up_lamp), .dwn_lamp(dwn_lamp) );

endmodule
```







```
// elevator state control module
// (c) all right reserved, 2010, RVC, Corp.
module st_ctl ( clk, rst_n, floor,
               to_lamp, up_lamp, dwn_lamp, elv_st );
parameter FF_DLY = 1 ;
parameter FL_NUM = 8 ; // number of floors, one bit for one floor
parameter FL_BW = 4 ; // bit width needed to hold floor number
parameter ST_BW = 4 ; // bit width of state to hold UP_GOING and MV_IN
parameter CNT_BW = 4 ; // bit width of counter to count up to 4,
                      // 4 is the minimum cycle to stay in WAIT_STP state
parameter WAIT_STP = 2'b00 ;
parameter UP_GOING = 2'b10 ;
parameter DWN_GOING = 2'b01 ;
parameter MV_IN = 2'b10 ;
parameter MV_OUT = 2'b01 ;
parameter MV_STP = 2'b00 ;
parameter MV_PAS = 2'b11 ;
//
input clk, rst_n;
input [FL_BW-1:0] floor ;
input [FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ;

output [ST_BW-1:0] elv_st ;
//
wire clk, rst_n;
wire [FL_BW-1:0] floor ;
wire [FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ;
reg [ST_BW-1:0] elv_st ; // FF
```





```
// internal variables
reg [ST_BW:0] next_elv_st ; // non-FF
wire [1:0] mv_dir, mv_st ;
reg [CNT_BW-1:0] sty_cntr ; // FF, counter to stay at least 4 cycles
reg [CNT_BW-1:0] next_sty_cntr ; // non-FF
//
always @ ( posedge clk or negedge rst_n ) begin
    if ( rst_n==1'b0 ) begin
        elv_st <=#FF_DLY { WAIT_STP, 2'b00 } ;
    end
    else begin
        elv_st <=#FF_DLY next_elv_st ;
    end
end
// connect call check module
wire [FL_NUM-1:0] floor_call ;
assign floor_call = to_lamp | up_lamp | dwn_lamp ;
call_chk call_chk_01( .floor(floor), .floor_call(floor_call),
                    .up_call(up_call), .dwn_call(dwn_call) ) ;
//
always @ ( elv_st or floor or to_lamp or up_lamp or dwn_lamp
          or up_call or dwn_call or sty_cntr ) begin
    casez ( elv_st ) // synopsys parallel_case
        { UP_GOING, MV_OUT }, { DWN_GOING, MV_OUT } : begin // MV_OUT to MV_IN
            next_elv_st = { elv_st[ST_BW-1:ST_BW-2], MV_IN } ;
        end
        { UP_GOING, MV_PAS }, { DWN_GOING, MV_PAS } : begin // MV_PAS to MV_OUT
            next_elv_st = { elv_st[ST_BW-1:ST_BW-2], MV_OUT } ;
        end
    end
end
```







```

{ UP_GOING, MV_STP },
{ DWN_GOING, MV_STP } : begin // MV_STP to MV_OUT
    // stay in the same state 0,1,2,3 cycles??
    next_elv_st=( sty_cntr == 3'd3 )? { elv_st[ST_BW-1:ST_BW-2], MV_OUT } : elv_st;
end
{ WAIT_STP, 2'b?? } : begin // WAIT_STP to UP_GOING/DWN MV_OUT
    if ( sty_cntr == 3'd3 ) begin // stay in the same state 0,1,2,3 cycles??
        if ( up_call == 1'b1 ) begin
            next_elv_st = { UP_GOING, MV_OUT } ;
        end
        else begin
            next_elv_st= ( dwn_call == 1'b1 )? { DWN_GOING, MV_OUT } : elv_st ;
        end
    end
    else begin
        next_elv_st = elv_st ;
    end
end
{ UP_GOING, MV_IN } : begin // UP_GOING MV_IN to MV_PAS, MV_STP or WAIT_STP
    if ( up_call == 1'b1 ) begin
        next_elv_st= ( to_lamp[floor] | up_lamp[floor] )? { UP_GOING, MV_STP } :
            { UP_GOING, MV_PAS } ;
    end
    else begin
        // if no up_call, must stop at current floor change direction
        next_elv_st=( dwn_call == 1'b1 )? { DWN_GOING, MV_STP } : { WAIT_STP, 2'b00 }
    end
;
end
end

```



```
{ DWN_GOING, MV_IN }: begin // DWN_GOING MV_IN to MV_PAS, MV_STP or WAIT_STP
    if ( dwn_call == 1'b1 ) begin
        next_elv_st = ( to_lamp[floor] | dwn_lamp[floor] )? { DWN_GOING, MV_STP } :
            { DWN_GOING, MV_PAS };
    end
    else begin // Change direction or Wait if no call from up nor down
        next_elv_st = ( up_call == 1'b1 )? { UP_GOING, MV_STP } : { WAIT_STP, 2'b00 };
    end
end
default : begin
    next_elv_st = 4'bxxxx ;
end
endcase
end
```






```
// stay counter
always @ ( posedge clk or negedge rst_n ) begin
  if ( ~rst_n ) begin
    sty_cntr <=#FF_DLY 3'b000 ;
  end
  else begin
    sty_cntr <=#FF_DLY next_sty_cntr ;
  end
end

always @ ( elv_st or sty_cntr ) begin
  next_sty_cntr = 3'b000 ;
  casez ( elv_st ) // synopsys parallel_case
    { UP_GOING, MV_STP }, { DWN_GOING, MV_STP },
    { WAIT_STP, 2'b?? } : begin // count 4, from 0 to 3, to stay at least 4 cycles
      next_sty_cntr = ( sty_cntr < 3'b011 ) ? sty_cntr + 1'b1 : sty_cntr ;
    end
    default : begin
      next_sty_cntr = 0 ;
    end
  endcase
end

endmodule
```







```
// local module in st_ctl;
// check if there are call from upper floors or from lower floors
// (c) all right reserved, RVC, Corp.
//
module call_chk ( floor, floor_call, up_call, dwn_call ) ;
parameter FL_NUM = 8 ;
parameter FL_BW = 4 ;
//
input [FL_BW-1:0] floor ;
input [FL_NUM-1:0] floor_call ;
output up_call, dwn_call ; // up_call is 1 if there is call from upper floor
//
wire [FL_BW-1:0] floor ;
wire [FL_NUM-1:0] floor_call ;
wire up_call, dwn_call ;


// internal varibale
wire [FL_NUM-1:0] up_wk, dwn_wk ;

// check floor_call[FL_NUM-1:floor+1] and floor_call[floor-1:0]
assign { up_wk, dwn_wk } = { floor_call, {FL_NUM{1'b0}} } >> floor ;
assign up_call = ( up_wk[FL_NUM-1:1] )? 1'b1 : 1'b0 ;
assign dwn_call = ( dwn_wk[FL_NUM-1:0] )? 1'b1 : 1'b0 ;
//
endmodule
```





```
// lamp control moduel, turn on and off lamps
// (c) all right reserved, RVC, Corp.
//
module lamp_ctl ( clk, rst_n, elv_st, floor,
                 to_btn, up_btn, dwn_btn,
                 to_lamp, up_lamp, dwn_lamp ) ;
parameter FF_DLY = 1 ;
parameter FL_NUM = 8 ;
parameter FL_BW = 4 ;
parameter ST_BW = 4 ;
parameter WAIT_STP = 2'b00 ;
parameter UP_GOING = 2'b10 ;
parameter DWN_GOING = 2'b01 ;
parameter MV_IN = 2'b10 ;
parameter MV_OUT = 2'b01 ;
parameter MV_STP = 2'b00 ;
parameter MV_PAS = 2'b11 ;
//
input clk, rst_n;
input [ST_BW-1:0] elv_st ;
input [FL_BW-1:0] floor ;
input [FL_NUM-1:0] to_btn, up_btn, dwn_btn ;
output [FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ;
//
wire clk, rst_n;
wire [ST_BW-1:0] elv_st ;
wire [FL_BW-1:0] floor ;
wire [FL_NUM-1:0] to_btn, up_btn, dwn_btn ;
```






```
reg [FL_NUM-1:0] to_lamp, up_lamp, dwn_lamp ; // FF,

// internal register
reg [FL_NUM-1:0] next_to_lamp, next_up_lamp, next_dwn_lamp ; // non-FF

// internal variables
wire [1:0] mv_dir, mv_st ;
//
assign { mv_dir, mv_st } = elv_st ;
//
//
always @ ( posedge clk or negedge rst_n ) begin
  if ( ~rst_n ) begin
    to_lamp[FL_NUM-1:0] <=#FF_DLY {FL_NUM{1'b0}} ;
    up_lamp[FL_NUM-1:0] <=#FF_DLY {FL_NUM{1'b0}} ;
    dwn_lamp[FL_NUM-1:0] <=#FF_DLY {FL_NUM{1'b0}} ;
  end
  else begin
    to_lamp[FL_NUM-1:0] <=#FF_DLY next_to_lamp ;
    up_lamp[FL_NUM-1:0] <=#FF_DLY next_up_lamp ;
    dwn_lamp[FL_NUM-1:0] <=#FF_DLY next_dwn_lamp ;
  end
end
end
```







```


always @ ( elv_st or floor or to_btn or to_lamp ) begin
    next_to_lamp = to_lamp | to_btn ;
    casez ( elv_st ) // synopsys parallel_case
        { UP_GOING, MV_IN }, { UP_GOING, MV_PAS }, { UP_GOING, MV_STP },
        { DWN_GOING, MV_IN }, { DWN_GOING, MV_PAS }, { DWN_GOING, MV_STP },
        { WAIT_STP, 2'b?? } : begin
            next_to_lamp[floor] = 1'b0 ;
        end
    endcase
end
always @ ( elv_st or floor or up_btn or up_lamp ) begin
    next_up_lamp = up_lamp | up_btn ;
    casez ( elv_st ) // synopsys parallel_case
        { UP_GOING, MV_IN }, { UP_GOING, MV_PAS }, { UP_GOING, MV_STP },
        { WAIT_STP, 2'b?? } : begin
            next_up_lamp[floor] = 1'b0 ;
        end
    endcase
end
always @ ( elv_st or floor or dwn_btn or dwn_lamp ) begin
    next_dwn_lamp = dwn_lamp | dwn_btn ;
    casez ( elv_st ) // synopsys parallel_case
        { DWN_GOING, MV_IN }, { DWN_GOING, MV_PAS }, { DWN_GOING, MV_STP },
        { WAIT_STP, 2'b?? } : begin
            next_dwn_lamp[floor] = 1'b0 ;
        end
    endcase
end
//
endmodule


```





```
// elevator position control moduel, count up or down floor
// (c) all right reserved, RVC, Corp.
//
module elv_ctl ( clk, rst_n, elv_st, floor ) ;
//
parameter FL_BW = 4 ;
parameter ST_BW = 4 ;
parameter FF_DLY = 1 ;
parameter WAIT_STP = 2'b00 ;
parameter UP_GOING = 2'b10 ;
parameter DWN_GOING = 2'b01 ;
parameter MV_IN  = 2'b10 ;
parameter MV_OUT = 2'b01 ;
parameter MV_STP = 2'b00 ;
parameter MV_PAS = 2'b11 ;
//
input clk, rst_n ;
input [ST_BW-1:0] elv_st ;
output [FL_BW-1:0] floor ;
//
wire clk, rst_n ;
wire [ST_BW-1:0] elv_st ;
//
reg [FL_BW-1:0] floor ;
```






```
// internal variables
wire [1:0] mv_dir, mv_st ;
reg [FL_BW-1:0] next_floor ; // non-FF
//
assign { mv_dir, mv_st } = elv_st ;
always @ ( posedge clk or negedge rst_n ) begin
    if ( ~rst_n ) begin
        floor <=#FF_DLY {(FL_BW){1'b0}} ; // initial floor = #0
    end
    else begin // update floor only at MV_OUT stage
        if ( ( mv_dir !=2'b00 ) & ( mv_st == MV_OUT ) ) begin
            floor <=#FF_DLY next_floor ;
        end
    end
end
always @ ( mv_dir or floor ) begin
    case ( mv_dir ) // synopsys parallel_case
        WAIT_STP : begin        next_floor = floor ;        end
        UP_GOING : begin        next_floor = floor + 1'b1 ;    end
        DWN_GOING : begin       next_floor = floor - 1'b1 ;    end
        default : begin         next_floor = {FL_BW{1'bx}} ; end
    endcase
end
//
//
endmodule
```

file name: my_elevator

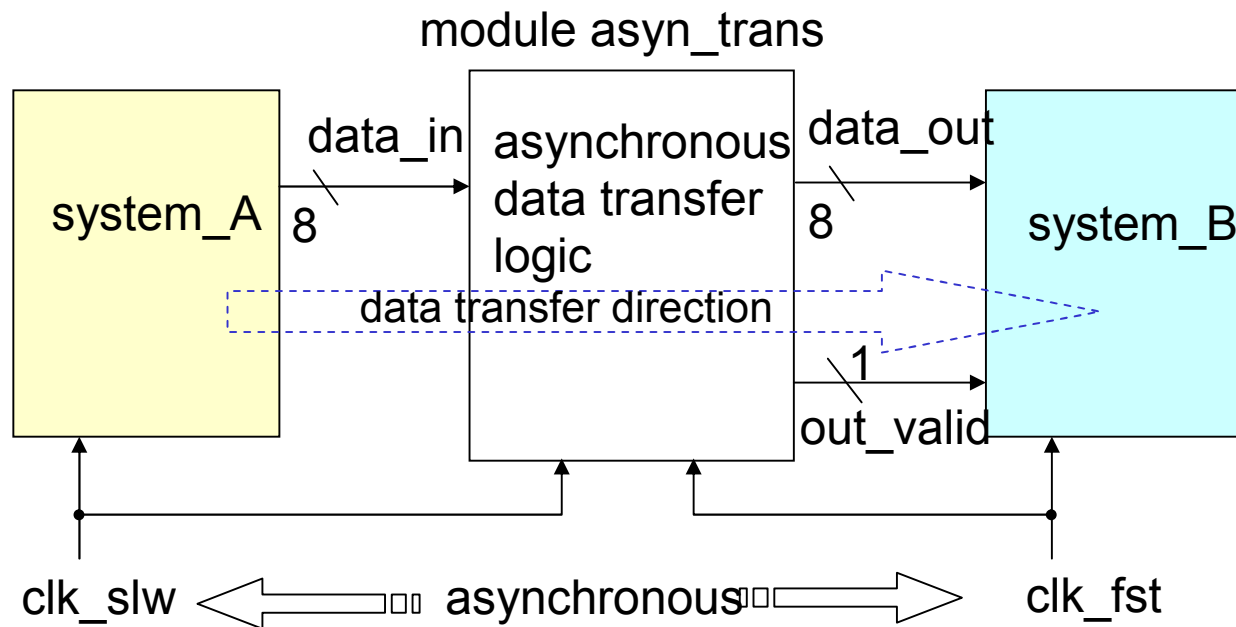
Ex 6-5. Asynchronous data transfer : Design data transfer logic which can transfer data from slow clock system to fast clock system, where two clock are running independently, that is, asynchronous.



- (1) clk_fst is running at least 6 times faster than clk_slw,
- (2) do not use cyclic buffer, use only 8-bit DFFs,
- (3) data_in is directly connected to the output FF of system A.
- (4) hold out_valid to 1 only for one clk_fst cycle while data_out is valid.

Detailed specification:

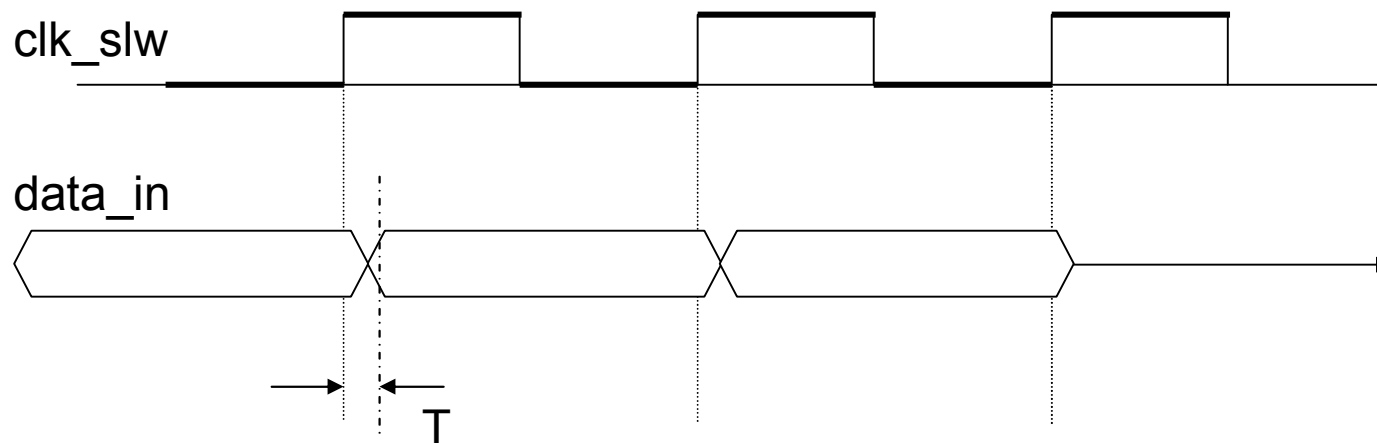- 1) The time chart for data_in must be as shown below.
T + FF's setup/hold time is much shorter than 1 cycle of clk_fst.
- 2) clk_slw's rise time is shorter than clk_fst's half cycle.
- 3) Duty of clk_slw is 50%. (While clk_slw is 1, clk_fst rises at least 4 times.
- 4) out_valid is on for only one cycle of clk_fst.



Work flow for solutions

- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document ,
- (4) Write a RTL code for the target module,
- (5) Run a test bench to see if your code is OK or not.


No sample test module is given for this exercise.
You have to create your own test bench.

See the next pages for further understanding of
the logic you have to implement.


How to know the timing of data_in is correctly received.

clk_fst is 6 times faster than clk_slw, therefore it is assured that at least 5 rise edge of clk_fst during clk_slw is 1.

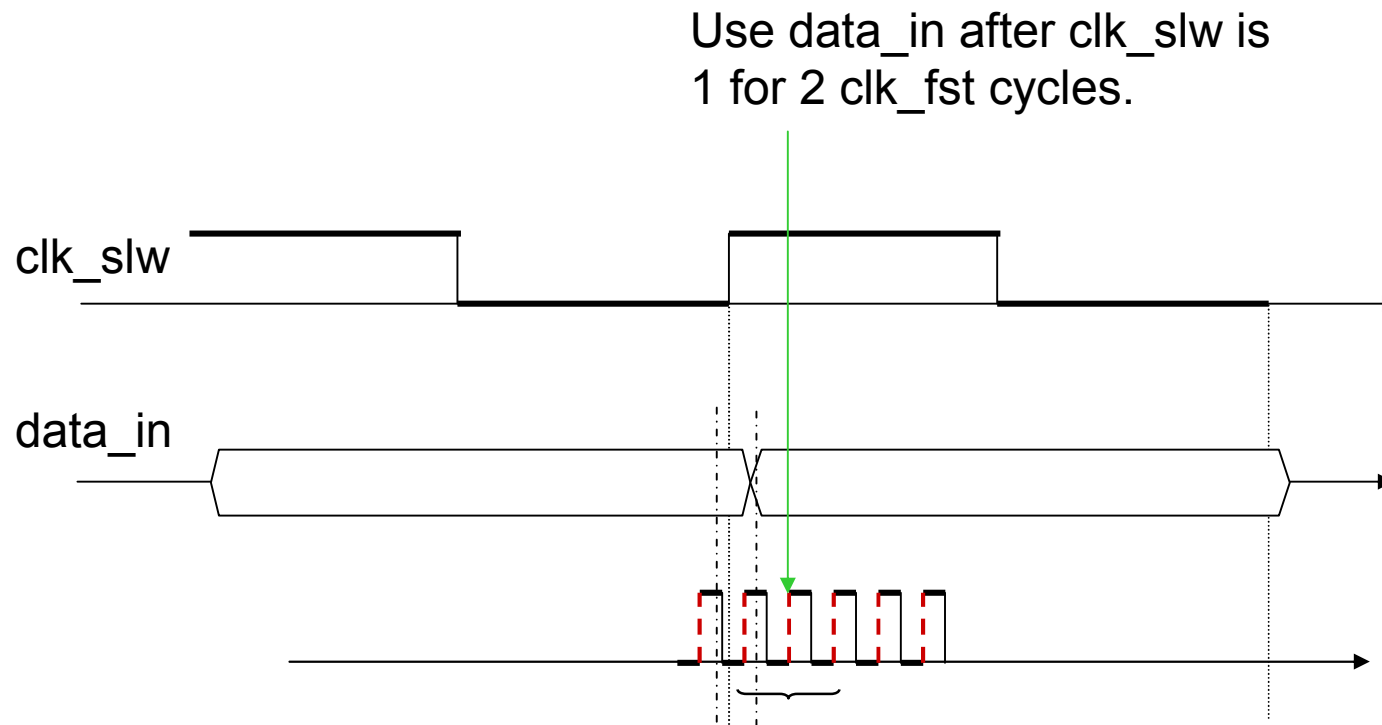
To ensure using data_in after clk_slw rise and stable, use data_in at the timing when sampled clk_slw is continuously 1 for 2 clock cycles.




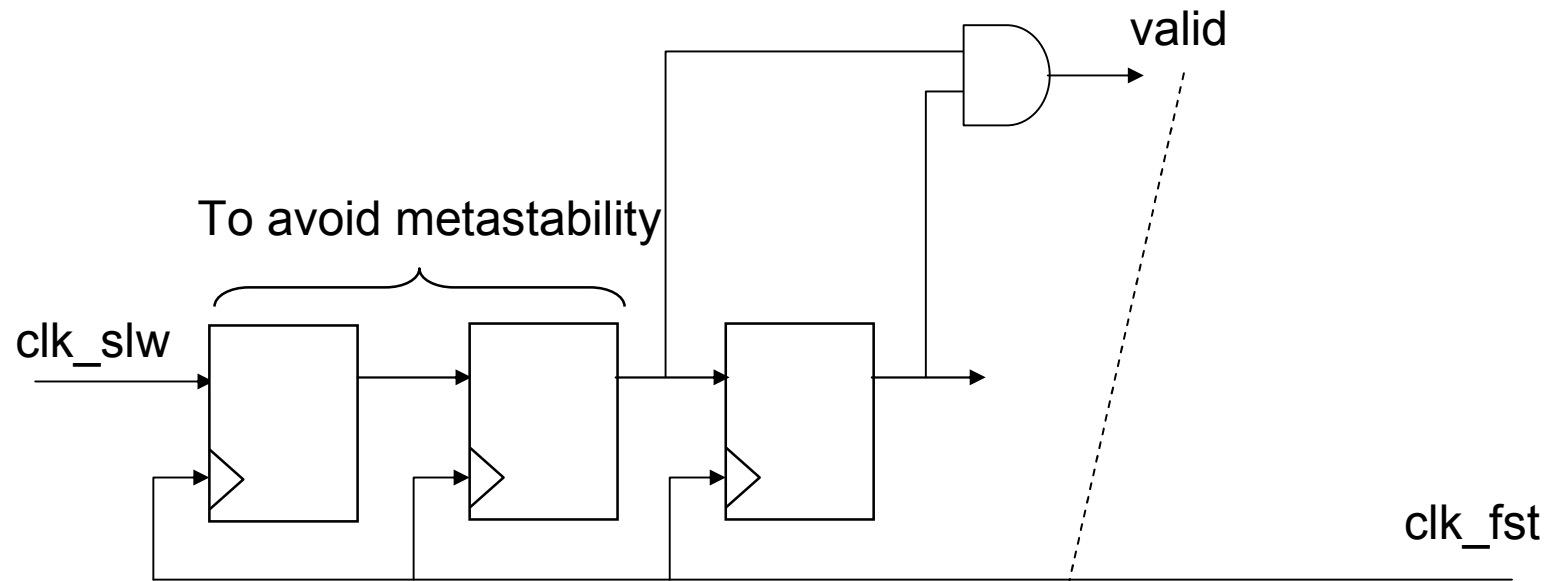The first 1 may be caused by metastability, but using second 1 makes it sure that data_in is stable.




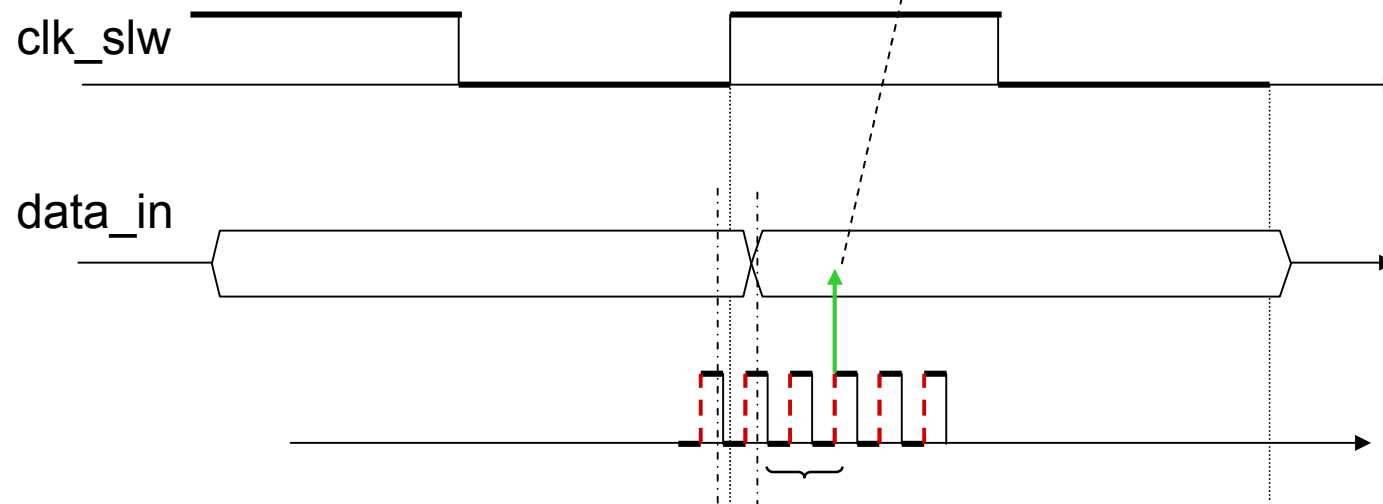We can use this valid signal as enable signal to sample data_in.




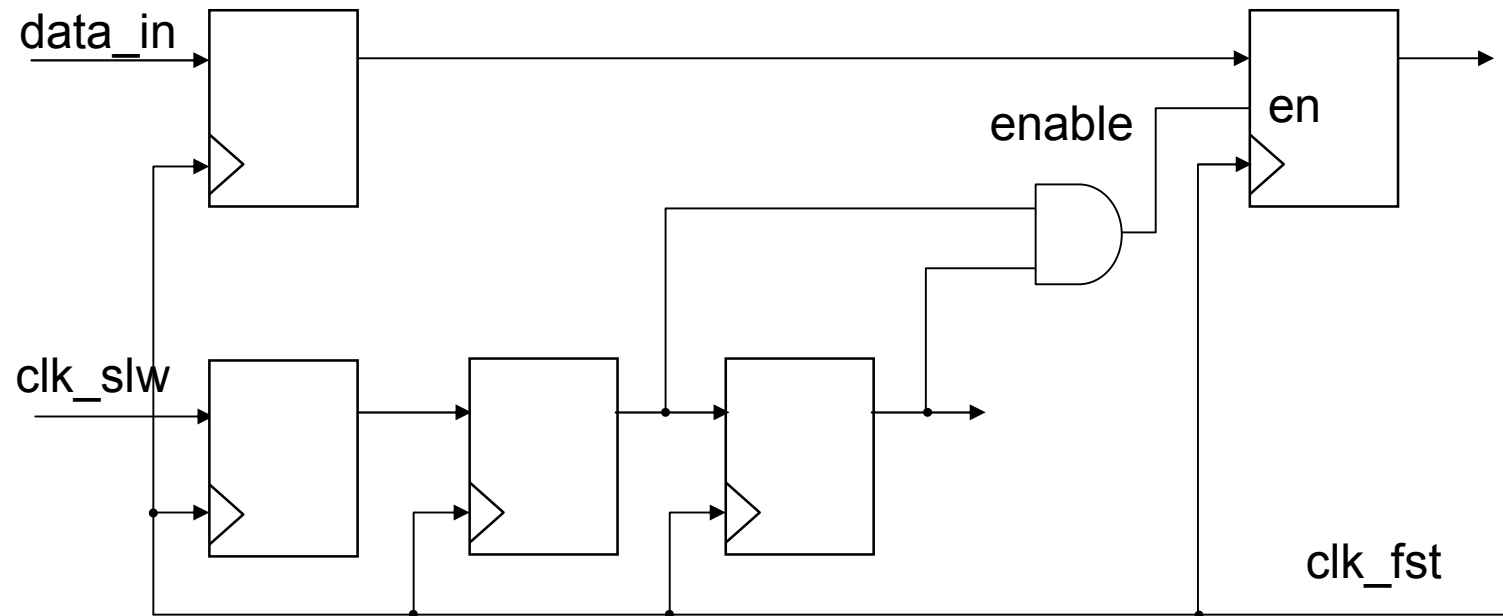

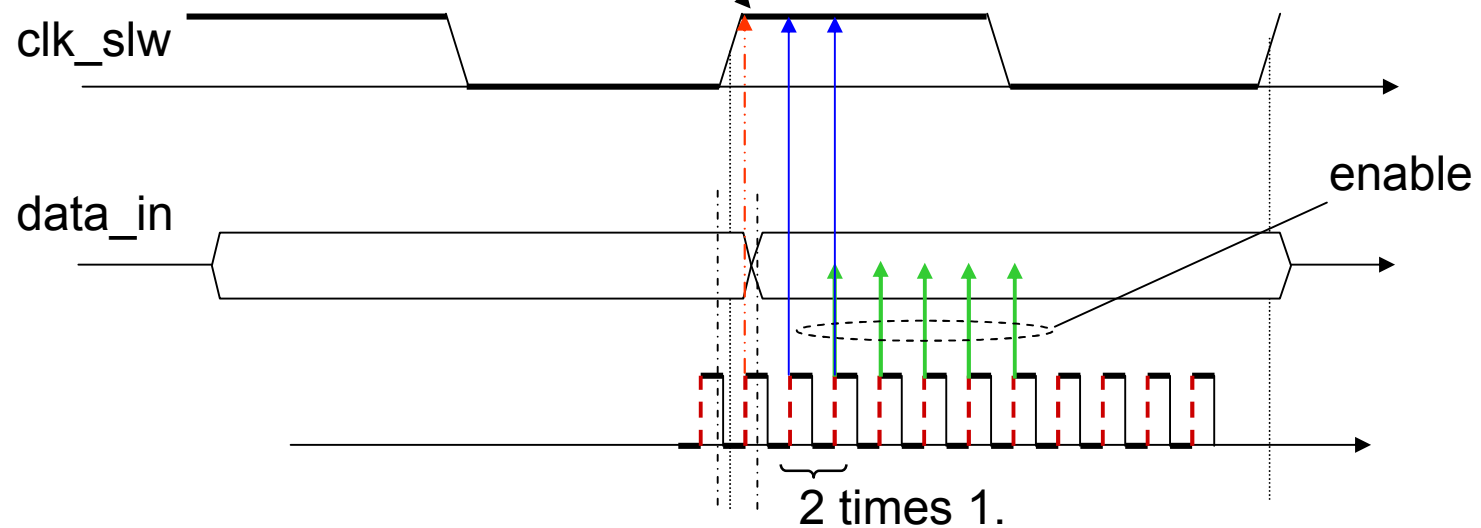This may not be 1 because of metastability




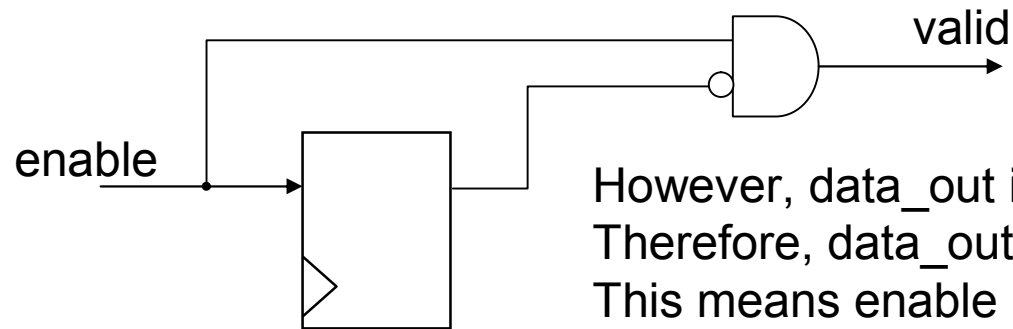To make valid signal 1 only one `clk_fst` cycle, use the following logic.




However, `data_out` is set by `enable` signal. Therefore, `data_out` is delayed one cycle. This means `enable` must be delayed one cycle.


The total logic shall look like below.

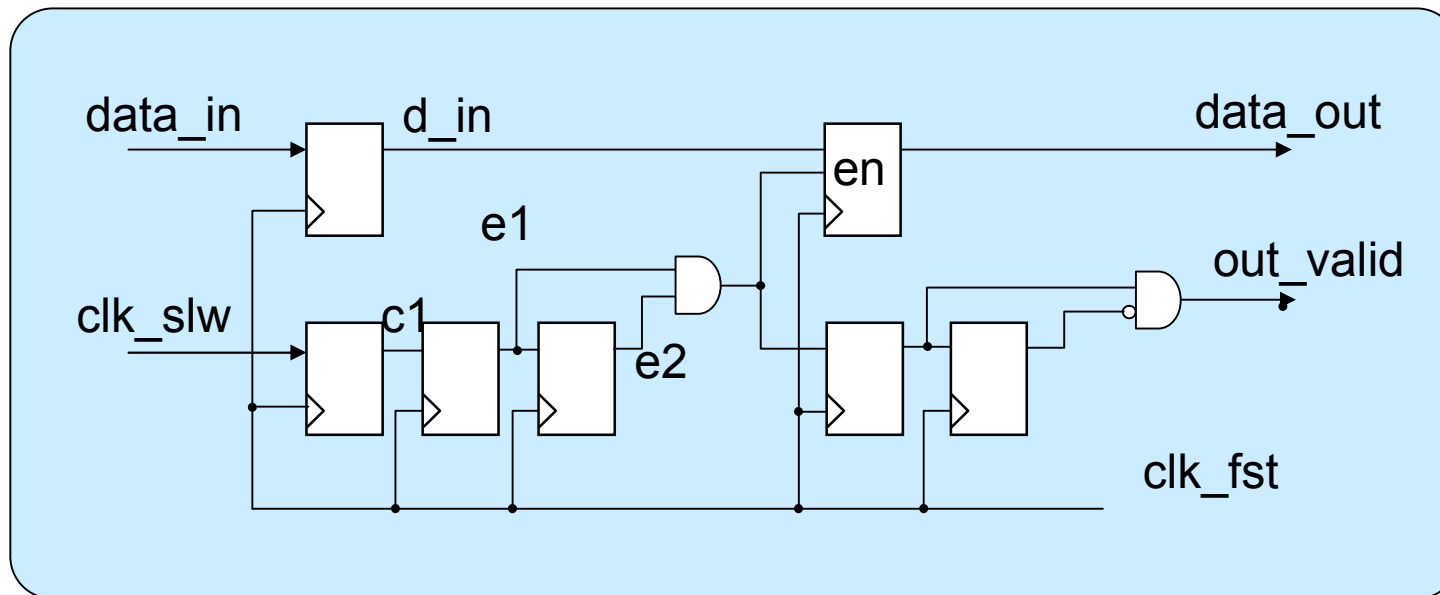


Total time chart

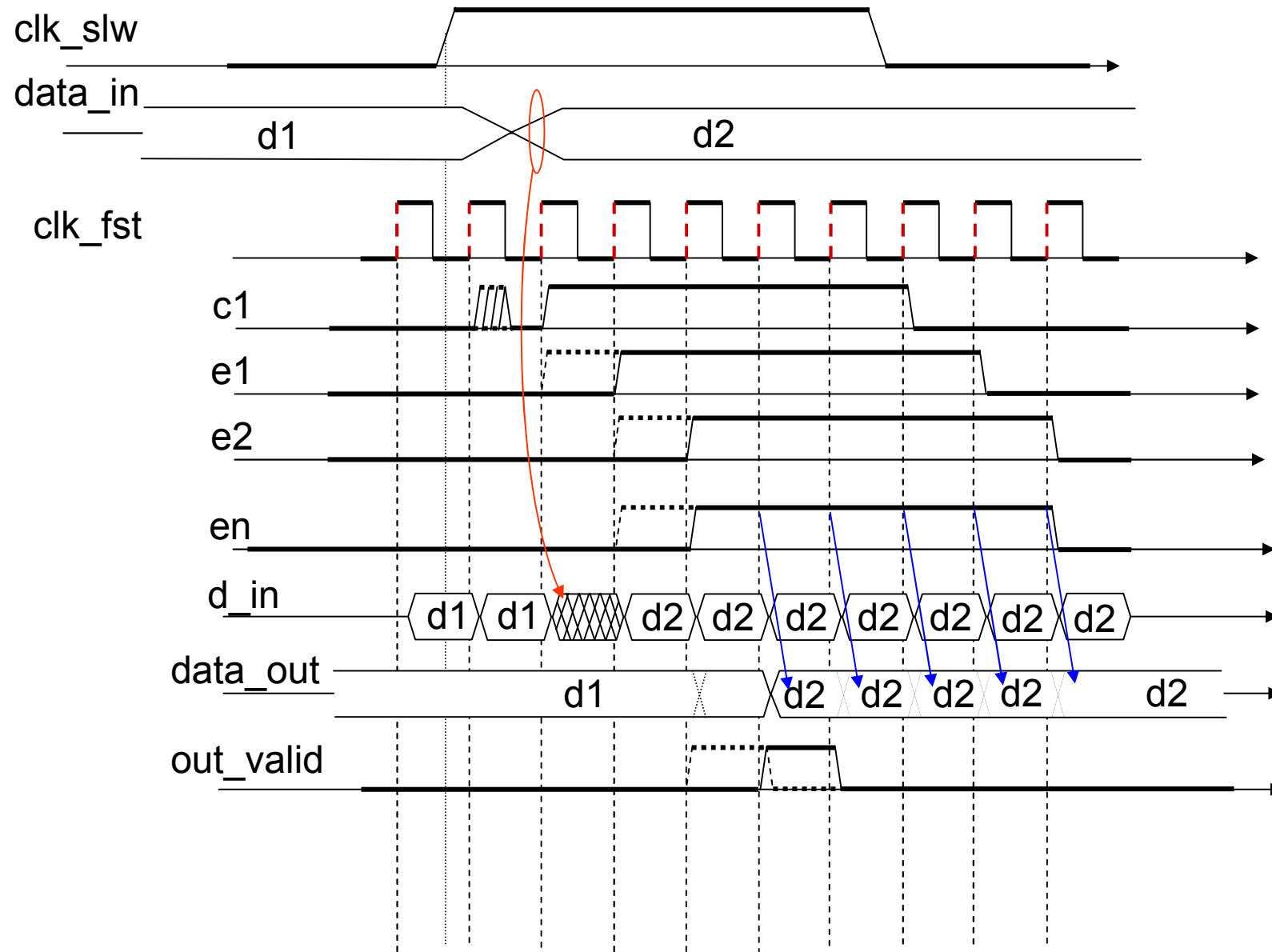

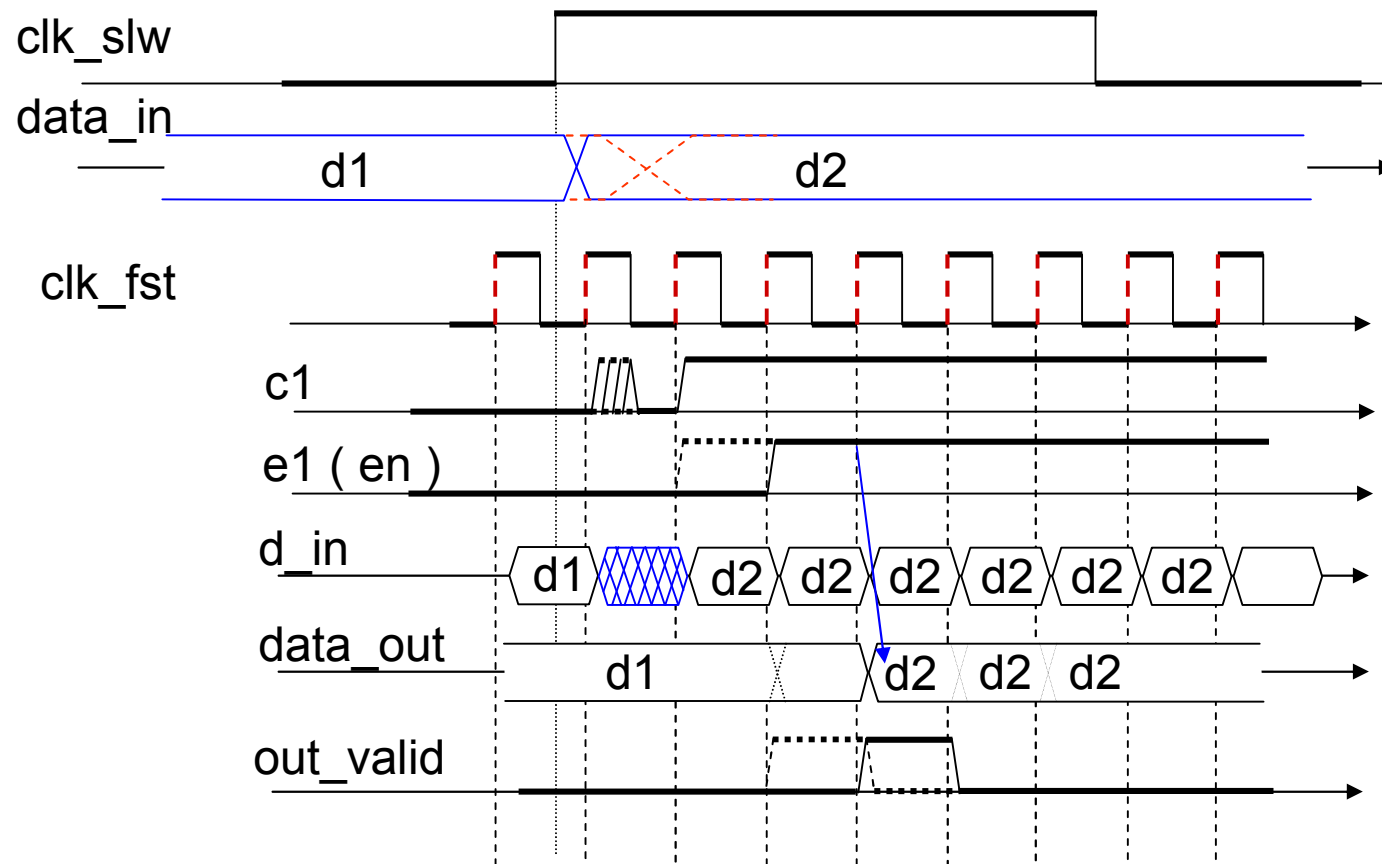From the time chart on the previous page, using 2 continuous 1 of c1 is known to be redundant if the duration of data_in is not stable is short enough compared to clk_fst cycle. In such case we can use e1 as enable signal as shown below.



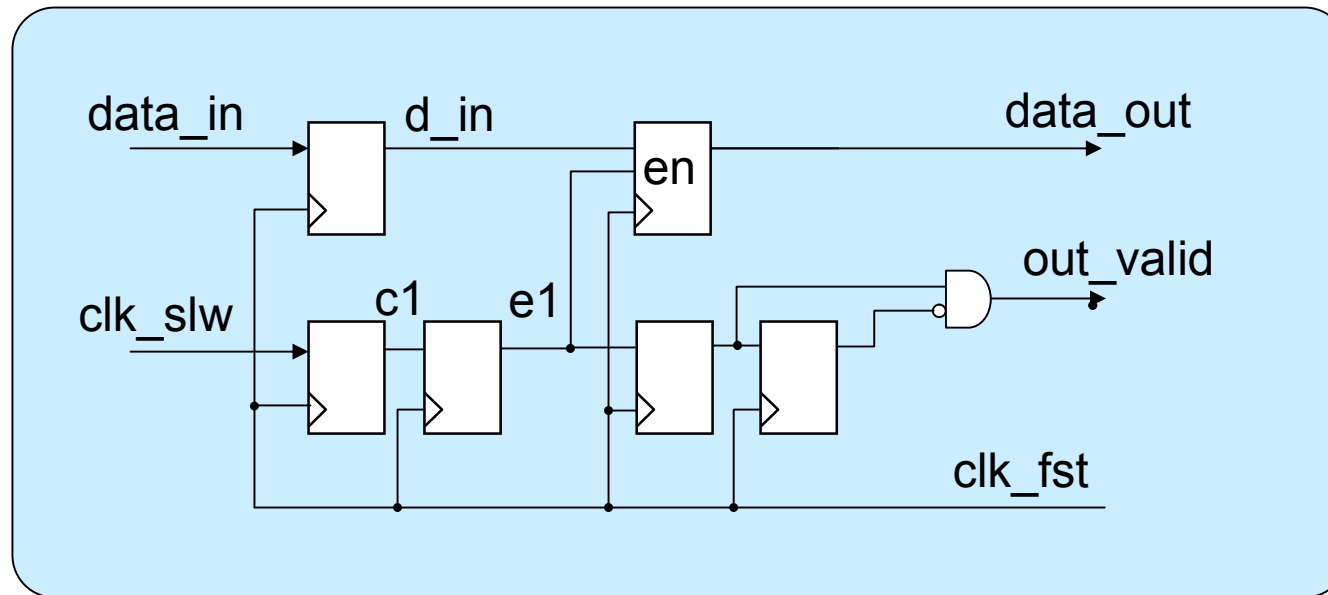Such assumption gives us the following logic diagram.



A sample target code on the next pages uses 2 continuous 1 of e1.

No test bench is shown for this exercise.

A sample target code

```

module async_trans ( clk_slw, clk_fst, rst_n,
                    data_in,
                    data_out, out_valid
                    );
//*****
// RTL programming exercise training sample answer
// (c) RVC, 2010
//*****
// note: this logic is applicable for clk_fst is 6 time faster than clk_slw.
//
input clk_slw, clk_fst ;
input rst_n ;
input [7:0] data_in ;
output [7:0] data_out ;
output out_valid ;
wire clk_slw, clk_fst ;
wire rst_n ;
wire [7:0] data_in ;
reg [7:0] data_out ;
wire out_valid ;
//internal variables
// internal reg
reg    fst_clk_smpl, scnd_clk_smpl ; // FF
reg    smpl_d_1, smpl_d_2 ; // FF
reg [7:0] data_reg_fst ; // FF
reg    reg_for_valid, secnd_reg_for_valid ; // FF
// wires
wire en_reg_set ;



```

```

//***** logic start *****
// create enable and out_valid signal
//
assign en_reg_set = smpl_d_1 & smpl_d_2 ;
assign out_valid = reg_for_valid & ( ~secnd_reg_for_valid ) ;

//***** FF *****
//
always @ ( posedge clk_fst or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    fst_clk_smpl <= 1'b0 ;
    scnd_clk_smpl <= 1'b0 ;
    smpl_d_1 <= 1'b0 ;
    smpl_d_2 <= 1'b0 ;
  end
  else begin
    fst_clk_smpl <= clk_slw ;
    scnd_clk_smpl <= fst_clk_smpl ;
    smpl_d_1 <= scnd_clk_smpl ;
    smpl_d_2 <= smpl_d_1 ;
  end
end
end

```

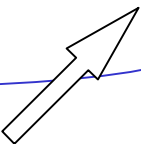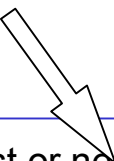



```

always @ ( posedge clk_fst or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    data_reg_fst[7:0] <= 8'b0000_0000 ;
    data_out[7:0] <= 8'b0000_0000 ;
  end
  else begin
    data_reg_fst[7:0] <= data_in[7:0] ;
    if ( en_reg_set == 1'b1 ) data_out[7:0] <= data_reg_fst[7:0] ;
  end
end
always @ ( posedge clk_fst or negedge rst_n ) begin
  if ( rst_n == 1'b0 ) begin
    reg_for_valid <= 1'b0 ;
    secnd_reg_for_valid <= 1'b0 ;
  end
  else begin
    reg_for_valid <= en_reg_set ;
    secnd_reg_for_valid <= reg_for_valid ;
  end
end
end
endmodule

```

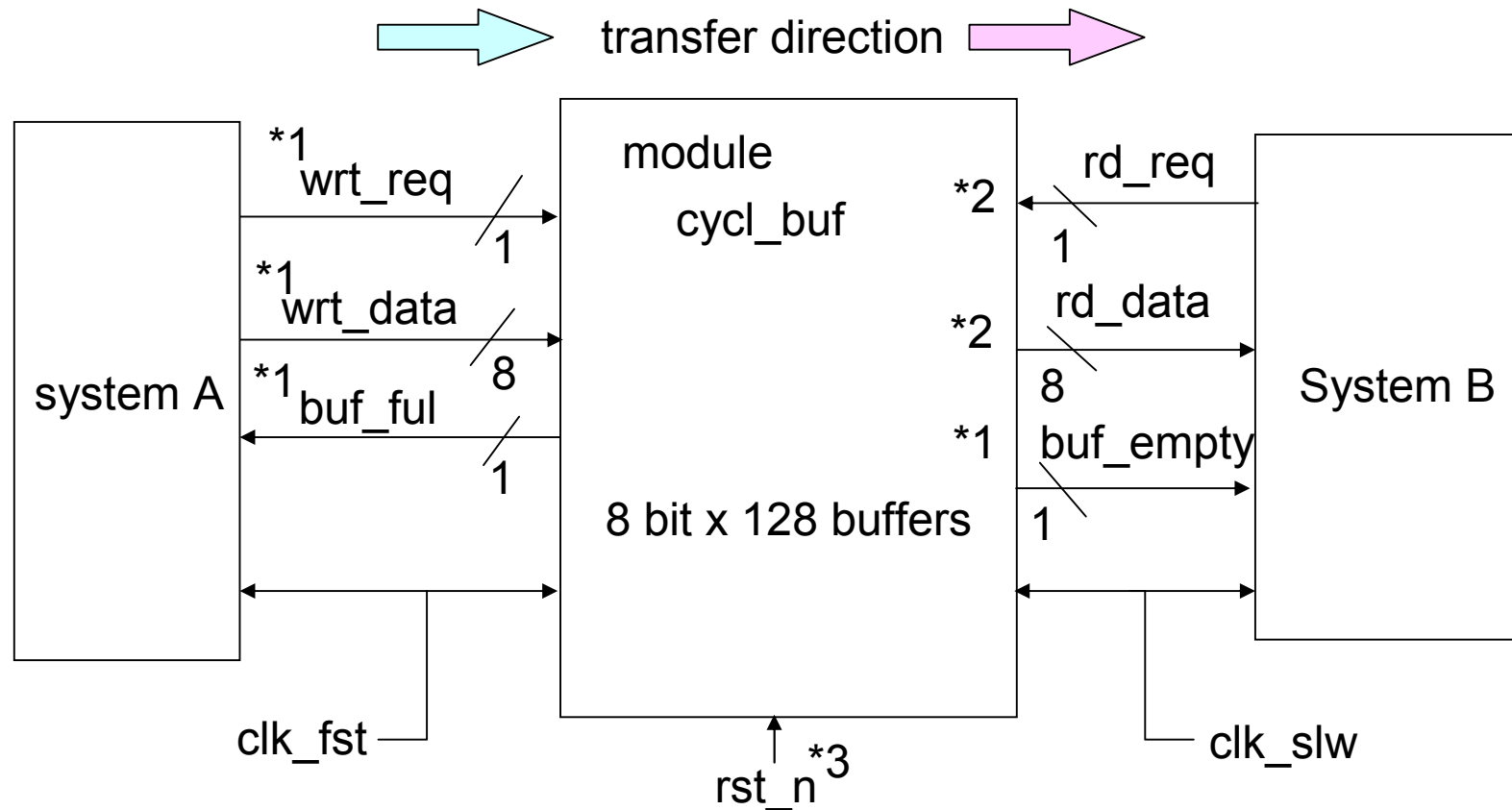Ex 6-6. Cyclic FIFO buffer : Design a module which passes data from fast running system A to slow running system B.





- *1 : synchronous to `clk_fst`
- *2 : synchronous to `clk_slw`
- *3 : asynchronous reset

System A is running 4 times faster than System B and their clocks are synchronized to one another. That is, whenever `clk_slw` rises `clk_fst` rises at the same time.


When buffer size is large, such as several k-byte or larger, we must use SRAM instead of FF. When using SRAM, major design issues are in how to write and read it from slow clock side and fast clock side.

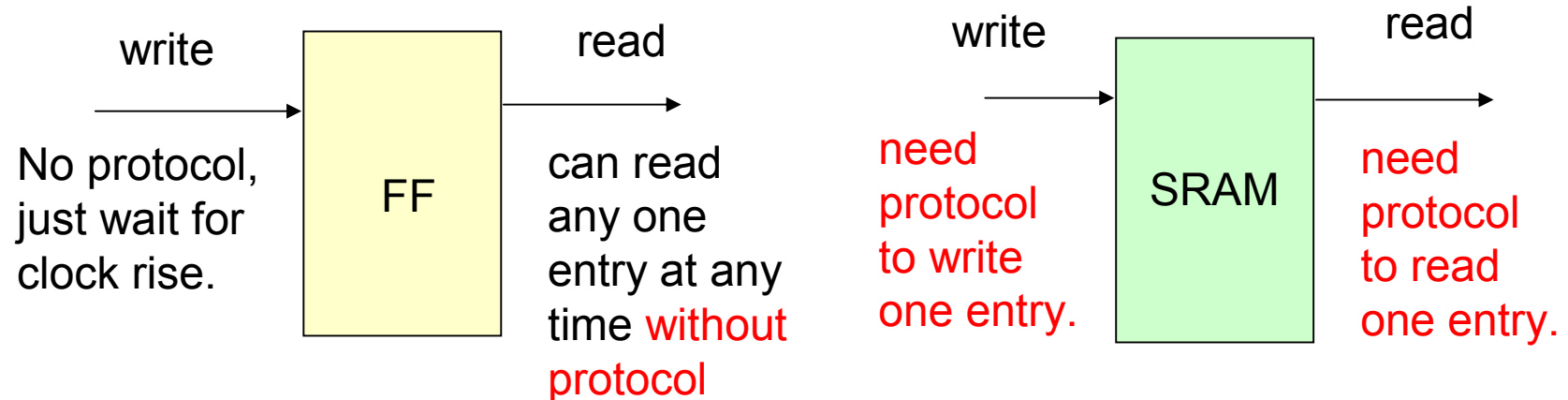In this RTL programming exercise, let's use FFs for buffer.




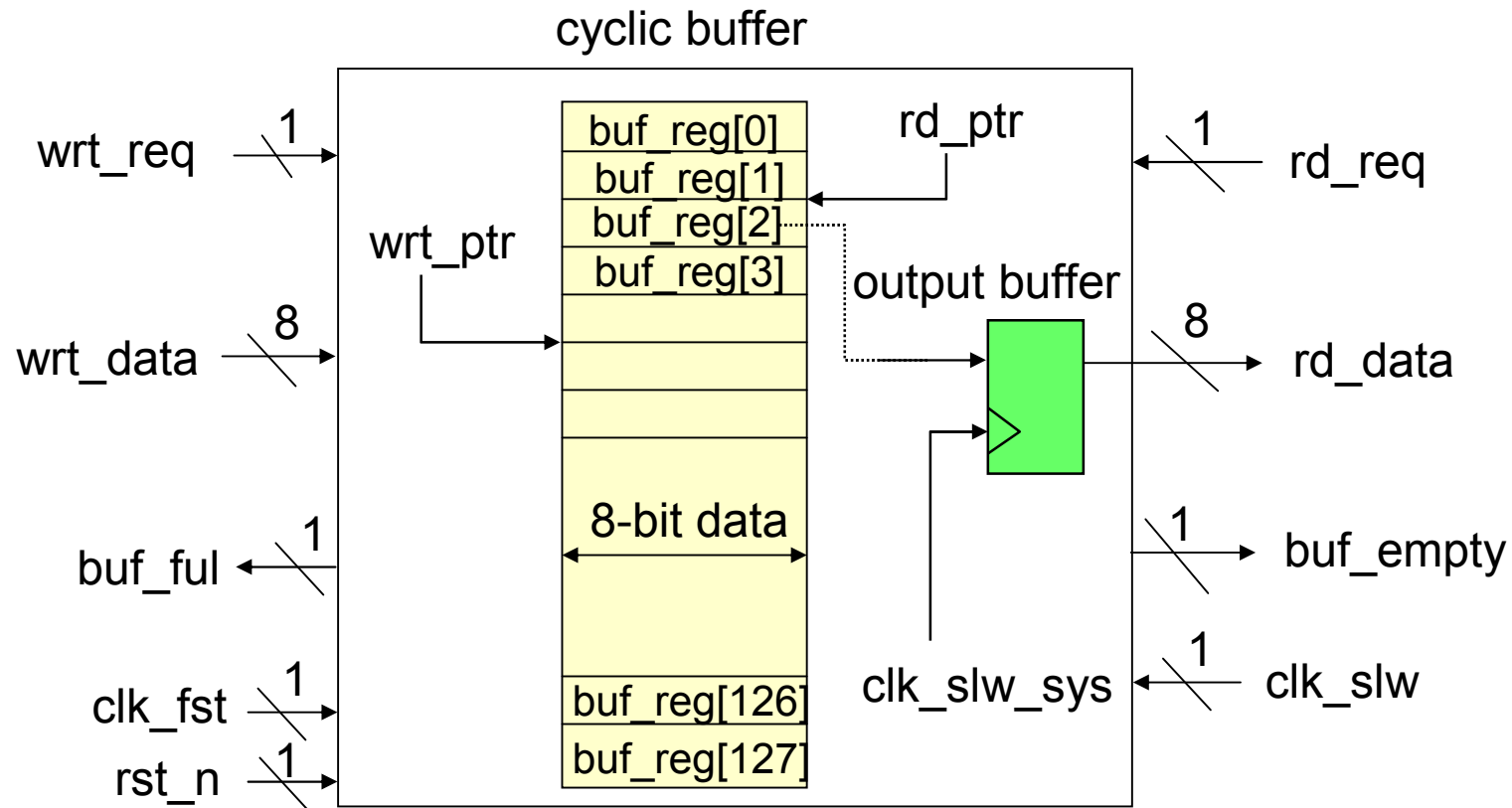

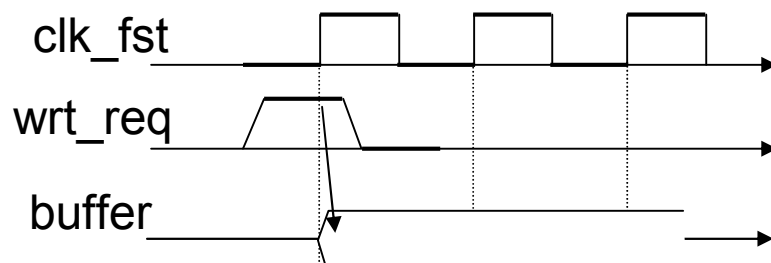When the buffer is not full, `wrt_data` must go into the buffer at the rise edge of the clock if `wrt_req` is asserted.



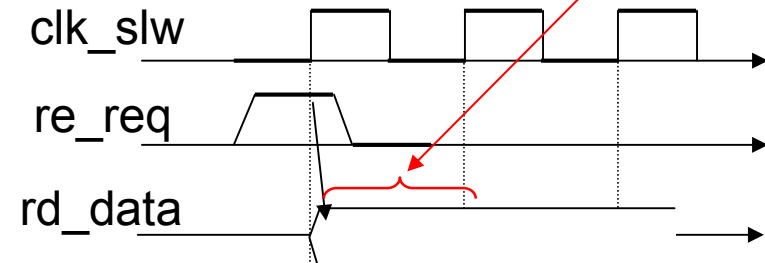When the buffer is not empty, buffer data must appear on `rd_data` in the next clock cycle after `rd_req` is asserted.



Work flow for solutions


- (1) Investigate the function of the system.
- (2) Find what is essential to the function,
- (3) Write a design document including a state transition table,
- (4) Write a RTL code for the target module,
- (5) Run **the automatic bench** on the latter pages with your cycl_buf module to see if it is correct or not.


Use slow clock to update read pointer and output buffer.
Use fast clock to update write pointer and data buffer.
Because fast and slow clocks are synchronized, signals are stable at any rise edge of clocks **except** rd_req.
rd_req is stable only at rise edge of slow clock.

See the next pages for further understanding of the logic you have to implement.


You must use parameter BUF_LEN to make buffer size adjustable for 2^n (where n shall be 2, 3, 4, 5, ..., etc.).

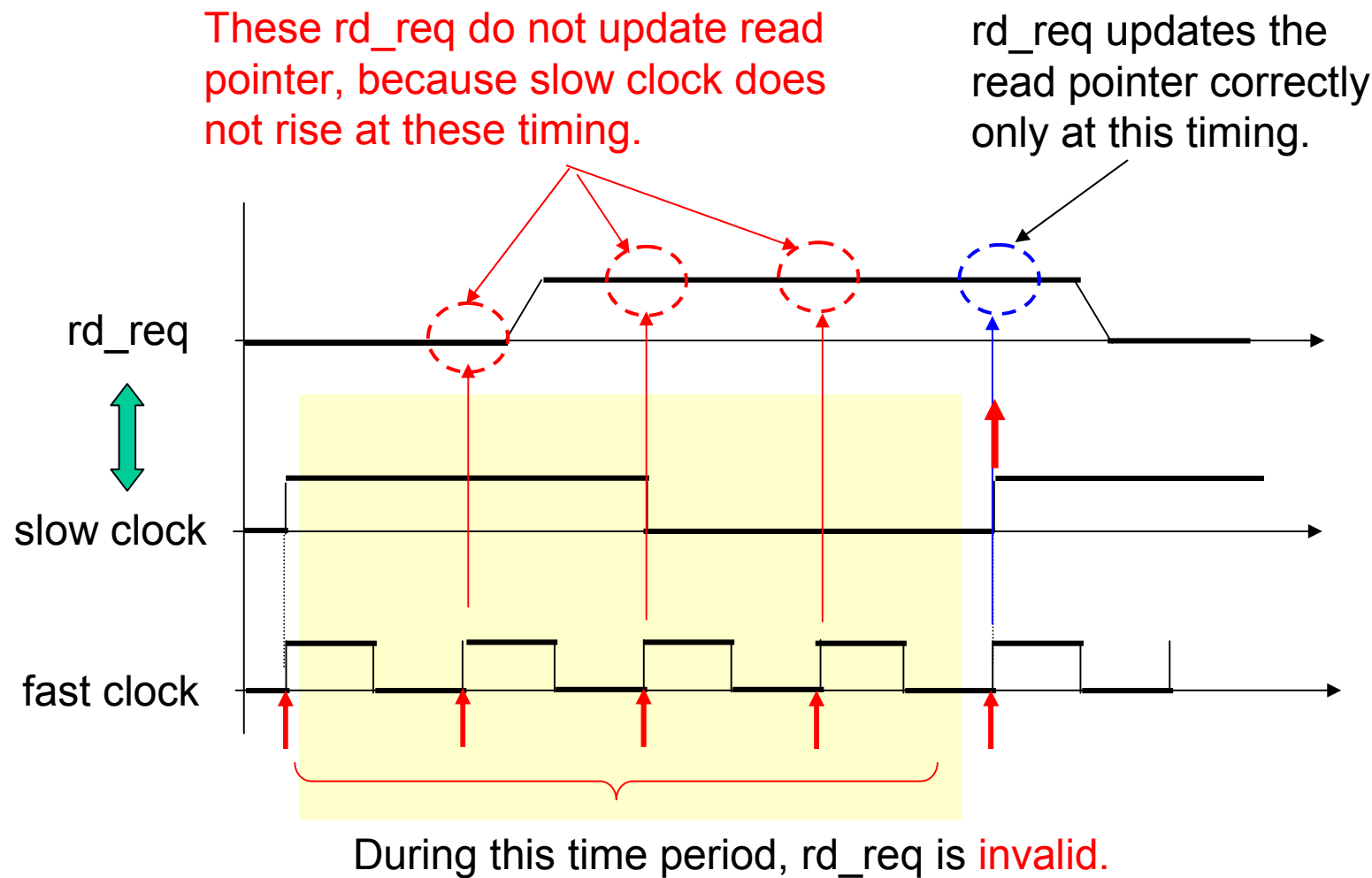When looking for a solution, you must be careful that rd_req and next read pointer evaluated from current read pointer and rd_req **may not be correct**.



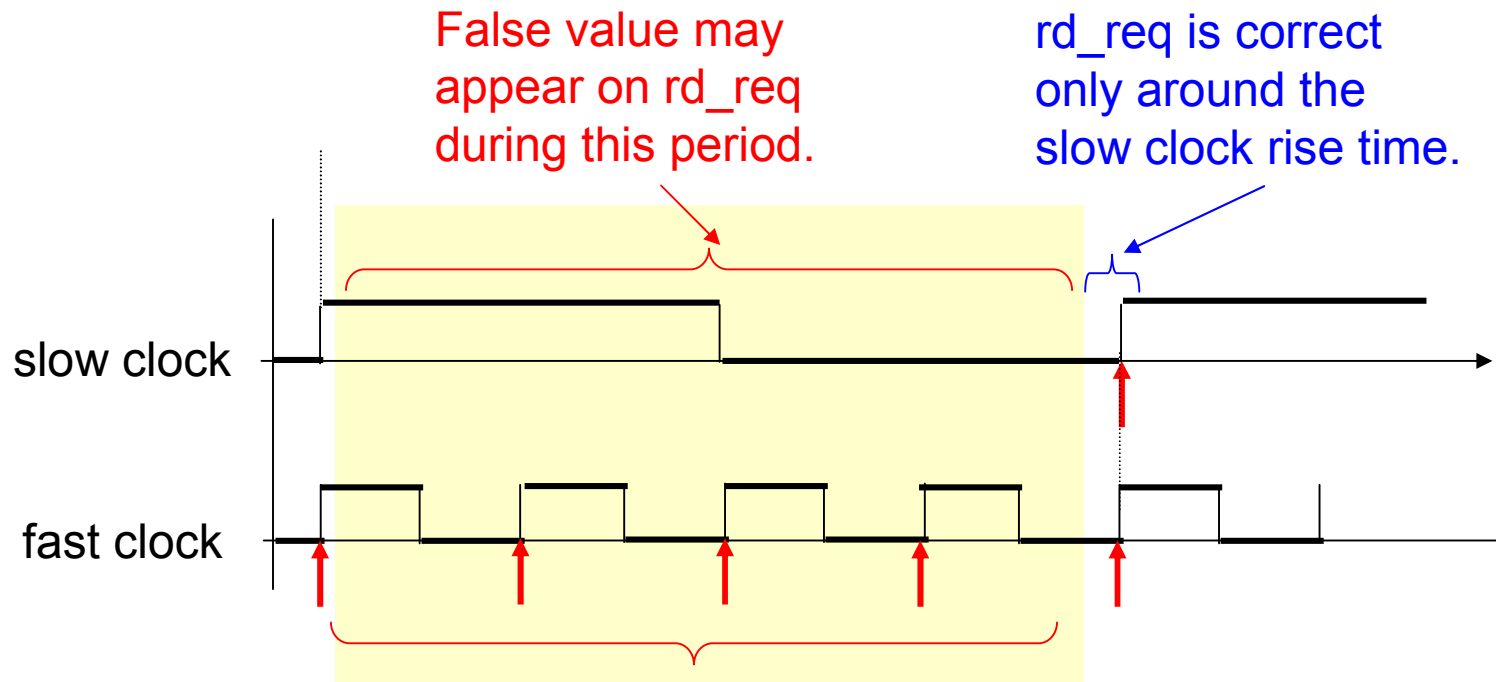

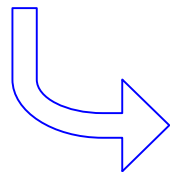Therefore, for this time period, **neither** rd_req **nor** next read pointer calculated based on rd_req can be **used** in evaluating buffer state.





We can not use rd_req to evaluate buffer usage when fast clock rises but slow clock does not rise.
We have to use values updated by clock to evaluate buffer usage.

Introducing bit size extended pointer can be a solution for this problem.


If we use as many bits as necessary for the pointer to avoid its overflow ,
 (1) rdd_ptr will never become larger than wrt_ptr, and
 (2) wrt_ptr will never become larger than rd_ptr + buffer size.

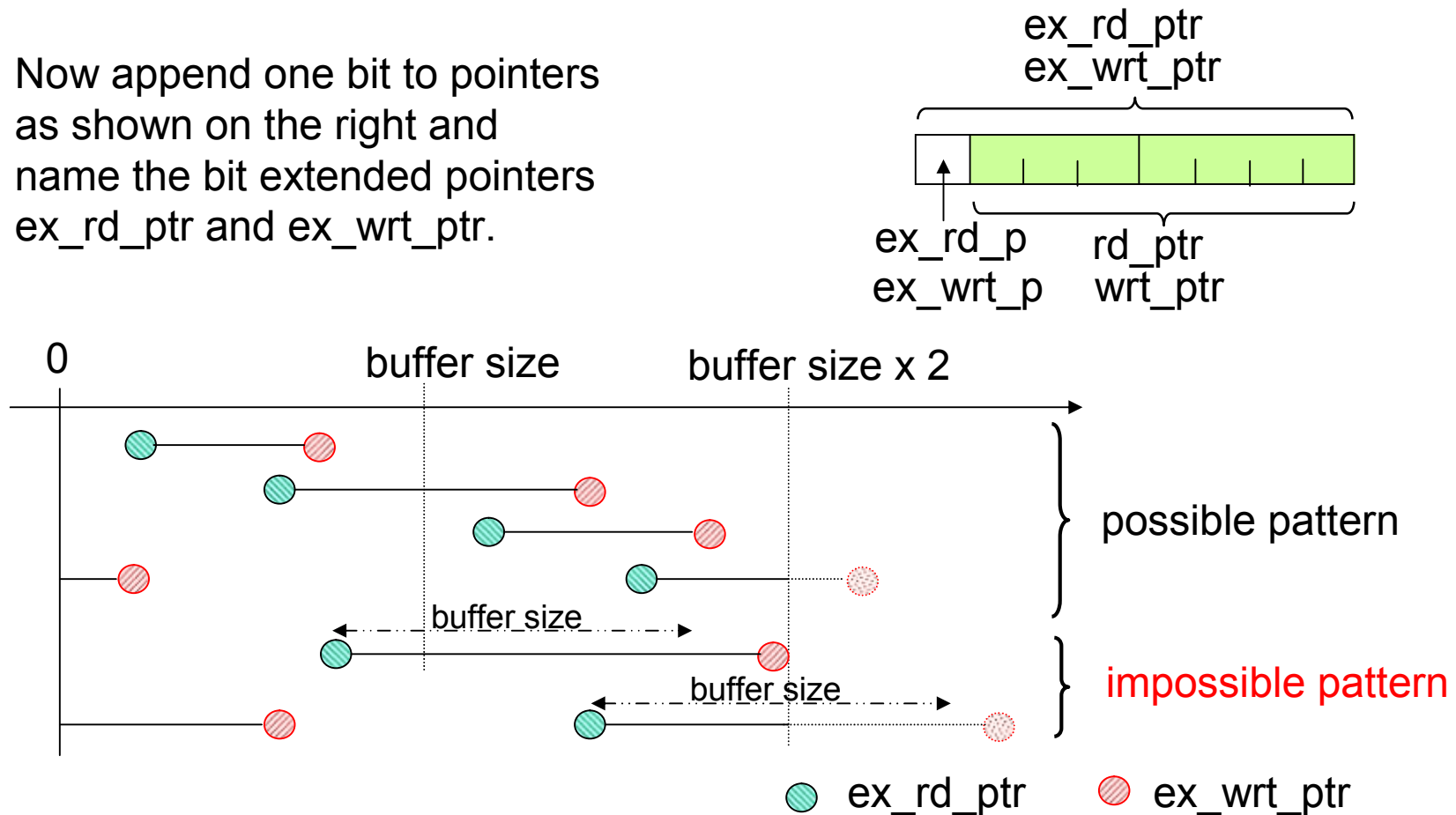Now append one bit to pointers as shown on the right and name the bit extended pointers ex_rd_ptr and ex_wrt_ptr.



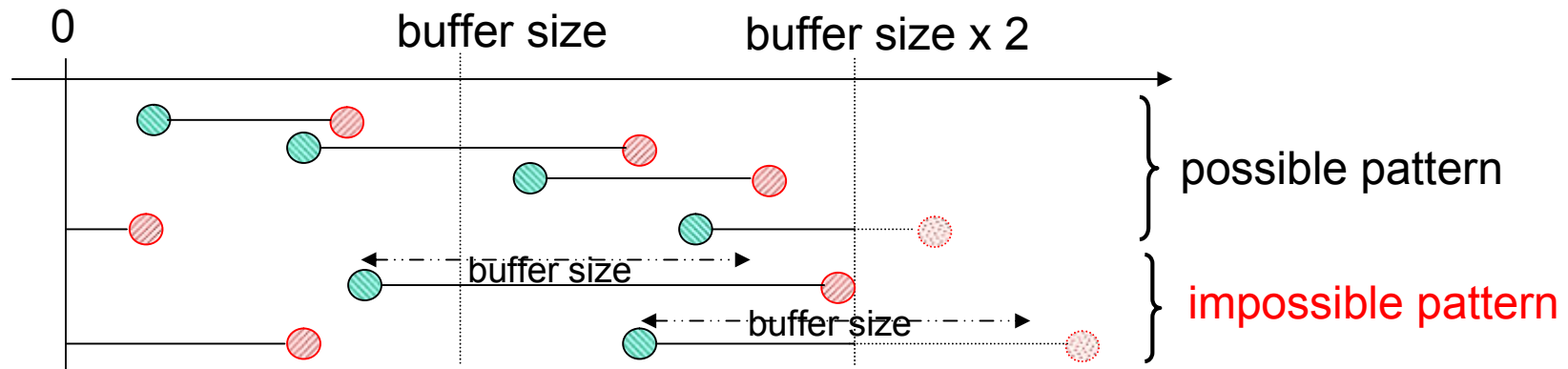

ex_rd_p	ex_wrt_p	rd_ptr	wrt_ptr	buf_empty	buf_ful
0	0	rd_ptr < wrt_ptr		0	0
		rd_ptr = wrt_ptr		1	0
		rd_ptr > wrt_ptr		X	
	1	rd_ptr < wrt_ptr			
		rd_ptr = wrt_ptr		0	1
		rd_ptr > wrt_ptr		0	0
1	1	rd_ptr < wrt_ptr		0	0
		rd_ptr = wrt_ptr		1	0
		rd_ptr > wrt_ptr		X	
	0	rd_ptr < wrt_ptr			
		rd_ptr = wrt_ptr		0	1
		rd_ptr > wrt_ptr		0	0

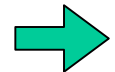

buf_empty = 1 if rd_ptr=wrt_ptr and ex_rd_p=ex_wrt_p


buf_ful = 1 if rd_ptr=wrt_ptr and ex_rd_p=ex_wrt_p

We may get our solution by;

- (1) Updating `ex_rd_ptr` at rise edge of slow clock,
- (2) updating `ex_wrt_ptr` at rise edge of fast clock, and
- (3) using them to evaluate buffer usage as shown on the previous page.

Now write some document yourself, and write a module `cycl_buf` based on your document.
And run it with the automatic test bench shown on the next pages.

A sample test bench, automatic tester

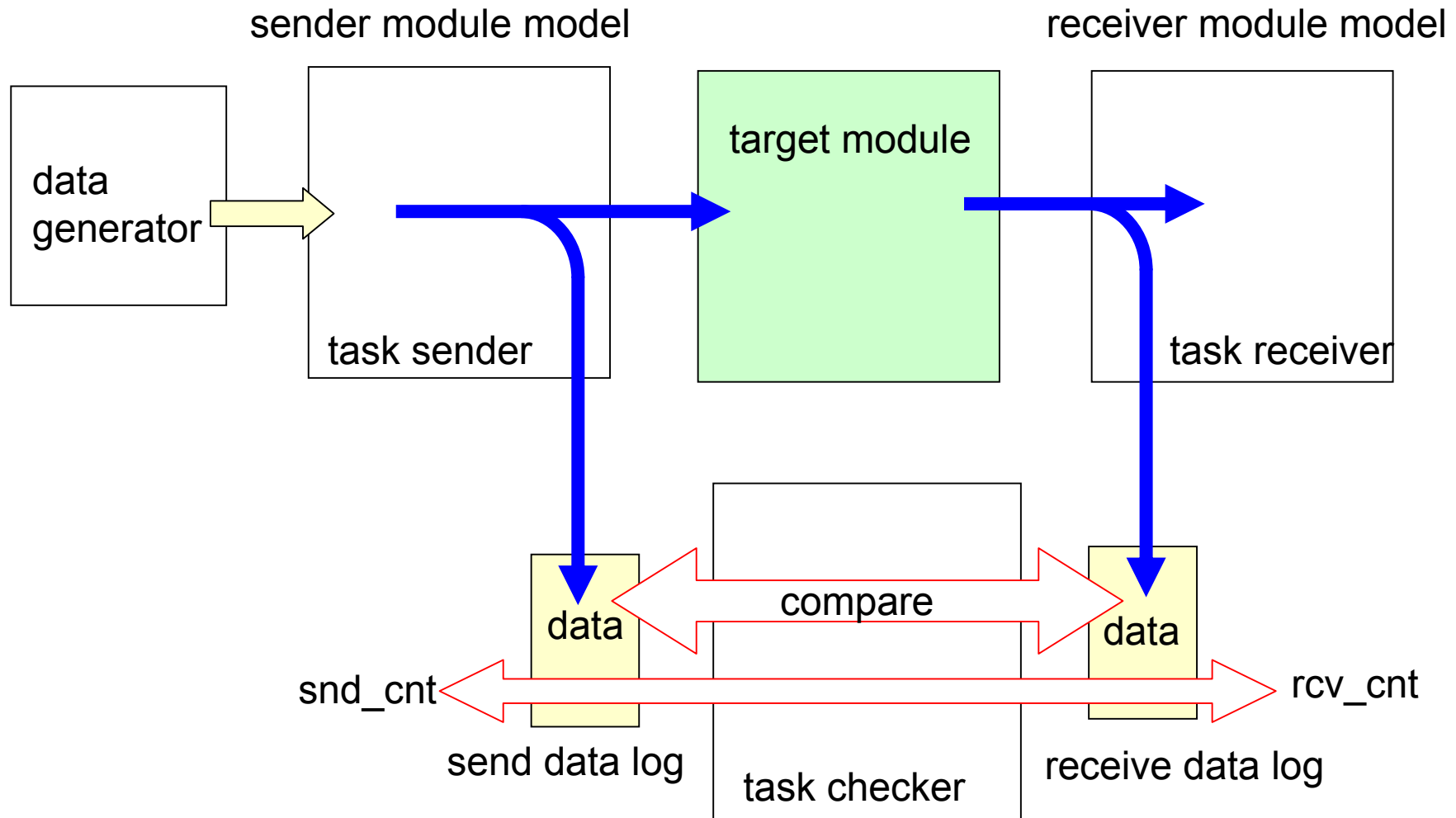

```

// automatic tester for cycl_buf
module test_cycl_buf ;
reg rst_n;
reg clk_fst, clk_slw;
//
parameter BUF_BW = 8 ;
parameter BUF LENG = 8 ;
defparam cycl_buf_01.BUF LENG = BUF LENG ;
defparam cycl_buf_01.PTR_BW = 3 ;
//
reg [BUF_BW-1:0] data_source[0:255] ;
integer snd_cnt, rcv_cnt ;
reg [BUF_BW-1:0] snd_log[0:1023] ; // max data count is 1024
reg [BUF_BW-1:0] rcv_log[0:1023] ;
reg [BUF_BW-1:0] wrt_data ;
reg rd_req, wrt_req;
wire buf_ful, buf_empty ;
//
integer n, i ;
event snd_tming, rcv_tming ;
//
parameter SIM_MX=1000; // test cycles in slow clock
parameter FST_HF_CYCL =5;
parameter FST_CYCL = FST_HF_CYCL*2;
parameter SLW_HF_CYCL =FST_HF_CYCL*4;
parameter SLW_CYCL = SLW_HF_CYCL*2;
//
// module connection
cycl_buf cycl_buf_01(.rst_n(rst_n), .clk_fst(clk_fst), .clk_slw(clk_slw),
                    .wrt_req(wrt_req), .wrt_data(wrt_data),
                    .rd_req(rd_req), .rd_data(rd_data),
                    .buf_ful(buf_ful), .buf_empty(buf_empty) );

```

To make test time short, buffer length is changed to 8.

If your code does not parameterize pointer bit width, remove this line.

module connection


```

// clock generator
always begin // fast clock
  clk_fst=0; #FST_HF_CYCL;
  clk_fst=1; #FST_HF_CYCL;
end

initial begin // slow clock
  clk_slw=0; #FST_HF_CYCL;
  forever begin // synchronized to rise edge of fast clock
    clk_slw=1; #SLW_HF_CYCL;
    clk_slw=0; #SLW_HF_CYCL;
  end
end
//
// send and receive timing
always @ ( negedge clk_fst ) begin
  #(FST_HF_CYCL-1) -> snd_tmng ;
end
always @ ( negedge clk_slw ) begin
  #(SLW_HF_CYCL-1) -> rcv_tmng ;
end
//
initial begin
  rst_n = 0;
  #(SLW_CYCL*2) rst_n = 1;
  #(SLW_CYCL*SIM_MX+20) ;
  $display("Could not complete send or receive, error") ;
  #1 $finish;
end
//


```

clock generator

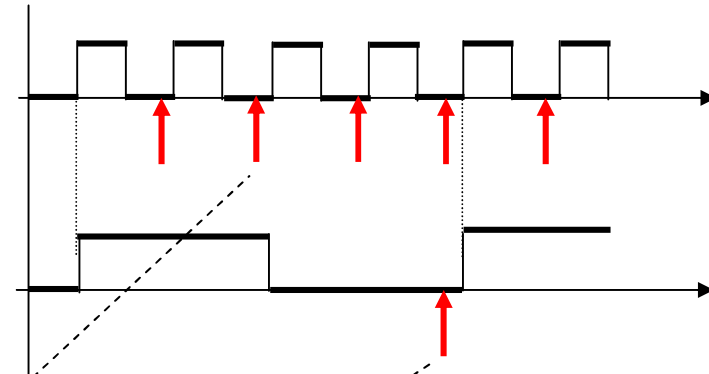

buf_ful/sender and
buf_empty/receiver
evaluate timing.

reset and simulation stopper



```

initial begin // sender
  wait (rst_n == 1'b1 ) ;
  #(FST_CYCL*1);
  #1;
  sender(15);
  #(FST_CYCL*70);
  sender(4);
  #(FST_CYCL*60);
  sender(8);
  #(FST_CYCL*100);
end
//


```

} data send sequence

```


initial begin // receiver
  wait (rst_n == 1'b1 ) ;
  #(SLW_CYCL*3);
  #1;
  receiver(7);
  #(SLW_CYCL*3);
  receiver(7);
  #(SLW_CYCL*5);
  receiver(13) ;
  #(SLW_CYCL*3);
  $display ("ful=%b,emp=%b,r_p=%h, w_p=%h, buf = ¥n  %d %d %d %d %d %d %d %d ",
    buf_ful, buf_empty,
    cycl_buf_01.rd_ptr, cycl_buf_01.wrt_ptr,
    cycl_buf_01.buf_reg[0], cycl_buf_01.buf_reg[1], cycl_buf_01.buf_reg[2], cycl_buf_01.buf_reg[3],
    cycl_buf_01.buf_reg[4], cycl_buf_01.buf_reg[5], cycl_buf_01.buf_reg[6], cycl_buf_01.buf_reg[7]
  );
  #1 ;
  checker ;
end

```



} data receive sequence


} check result



```


initial begin
    snd_cnt = 0;
    rcv_cnt = 0;
    wrt_req = 0;
    rd_req = 0;
end
//
task sender;
input [8:0] cnt ; // send data count
integer k ;
begin
    k = 0;
    //wrt_req = 0;
    while ( k < cnt ) begin
        @( snd_tming ) begin
            if ( buf_ful == 1'b0 ) begin
                k = k + 1;
                wrt_req = 1'b1;
                wrt_data = data_source[snd_cnt] ;
                snd_log[snd_cnt] = wrt_data;
                snd_cnt = snd_cnt + 1;
                #1 $strobe("t=%d, wrt_req=%b, snd_cnt=%d, data=%d",
                    $stime, wrt_req, snd_cnt, wrt_data ) ;
            end
        end
    end
    #2 wrt_req = 0; // rest wrt_req after clock rise
end
endtask

```



} set initial values for counter and request


} sender task :
send requested number
of data into buffer,
loop until all the data
sent into buffer.



```

task receiver;
input [8:0] cnt ; // receive data count
integer j ;
begin
  j=0;
  rd_req=0;
  while ( j < cnt ) begin
    @( rcv_tming ) begin
      if ( buf_empty == 1'b0 ) begin
        j=j+1;
        rd_req =1 ;
        @( posedge clk_slw ) begin
          #1 rcv_log[rcv_cnt] = rd_data;
          rcv_cnt=rcv_cnt+1;
          $strobe("t=%d, rd_req=%b, rcv_cnt=%d, data=%d",
            $stime, rd_req, rcv_cnt, rd_data ) ;
        end
      end
    end
  end
  #2 rd_req =0; // rest rd_req after clock rise
end
endtask
//

```




receiver task:
 receive requested number
 of data from buffer,
 loop until all the data
 come out of buffer.



```
//
task checker; // compare send and receive data
integer m ;
begin
  if ( snd_cnt !== rcv_cnt ) begin
    $display("send and receive data count miss-match, snd=%d, rcv=%d",
      snd_cnt, rcv_cnt );
    #1 $finish;
  end
  else begin
    for ( m=0; m <= snd_cnt; m=m+1 ) begin
      if ( rcv_log[m] !== snd_log[m] ) begin
        $display("data miss-match at %d -th data, snd=%d, rcv=%d",
          m+1, snd_log[m], rcv_log[m] );
        #1 $finish ;
      end
    end
    #1;
    $display("%0d data sent ¥n simulation complete with no error",
      snd_cnt);
    #1 $finish ; end
  end
endtask
```

checker task:
compare sent
and received
data count, and
sent and
received data





```
// sending data creation
integer kk ;
initial begin
  for( kk = 0; kk <=255 ; kk = kk+1 ) begin
    data_source[kk] = kk ;
  end
end
```

Create data to send and receive.
You may replace
data_source[kk] = kk ;
by
data_source[kk] = \$random;.

```
always @ ( posedge clk_fst ) begin
  $strobe("t=%d, r=%b, fst=%b, slw=%b, f=%b, e=%b, w_p=%d, r_p=%d, w_req=%b, r_req=%b",
    $stime, rst_n, clk_fst, clk_slw, buf_ful, buf_empty,
    cycl_buf_01.wrt_ptr, cycl_buf_01.rd_ptr,
    wrt_req, rd_req );
end
//
//
//
endmodule
//
`include "cycl_buf.v"
```

print state, request,
and pointers

file name: test_cycl_buf.v


This tester does not check the
timing automatically, you have
to check with your eyes about
the timing.
if you are interested, improve
the module so that it can check
the timing automatically.


A sample target code

```

module cycl_buf ( rst_n, clk_fst, clk_slw, wrt_req, wrt_data, rd_req,
                  rd_data, buf_ful, buf_empty );
parameter BUF_BW = 8 ;
parameter BUF LENG = 128 ;
parameter PTR_BW = 7 ;
//
input rst_n, clk_fst, clk_slw ;
input wrt_req;
input [BUF_BW-1:0] wrt_data;
input rd_req;
output [BUF_BW-1:0] rd_data;
output buf_ful, buf_empty;
//
wire rst_n, clk_fst, clk_slw ;
wire wrt_req;
wire [BUF_BW-1:0] wrt_data;
wire rd_req;
reg [BUF_BW-1:0] rd_data; // FF
wire buf_ful;
wire buf_empty;
//
wire [PTR_BW-1:0] wrt_ptr;
wire [PTR_BW-1:0] rd_ptr;
wire ex_wrt_p, ex_rd_p ;
reg [PTR_BW:0] ex_wrt_ptr, ex_rd_ptr ;
reg [BUF_BW - 1:0] buf_reg [0:BUF LENG-1 ] ; // buffer array//
//
assign { ex_wrt_p, wrt_ptr } = ex_wrt_ptr ;
assign { ex_rd_p, rd_ptr } = ex_rd_ptr ;
//

```

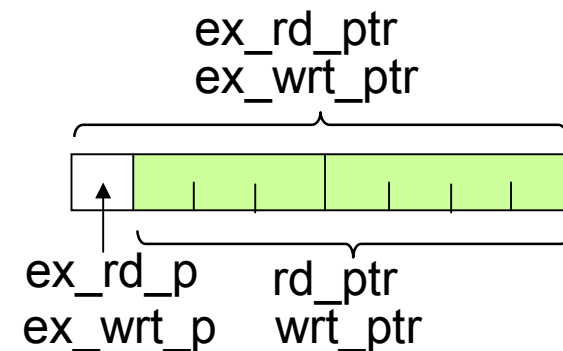

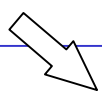

```
//buffer write operation
always @ (posedge clk_fst or negedge rst_n) begin
    if ( rst_n == 1'b0 ) ex_wrt_ptr <= 0 ;
    else begin
        if ( ( wrt_req == 1'b1 ) & ( buf_ful == 1'b0 ) ) begin
            buf_reg[ wrt_ptr ] <= wrt_data ;
            ex_wrt_ptr <= ex_wrt_ptr + 1'b1;
        end
    end
end

//buffer read operation
always @ (posedge clk_slw or negedge rst_n) begin
    if ( rst_n == 1'b0 ) ex_rd_ptr <= 0 ;
    else begin
        if ( ( rd_req == 1'b1 ) & ( buf_empty == 1'b0 ) ) begin
            // rd_data = buf_reg[ rd_ptr ] ;
            ex_rd_ptr <= ex_rd_ptr + 1'b1;
            rd_data <= buf_reg[ rd_ptr ] ;
        end
    end
end

//
assign buf_ful      = ( wrt_ptr == rd_ptr ) & ~( ex_wrt_p == ex_rd_p ) ;
assign buf_empty    = ( wrt_ptr == rd_ptr ) &  ( ex_wrt_p == ex_rd_p ) ;
//
endmodule
```

file name: cycl_buf.v

Concluding remarks

Engineering has always several solutions.
A good engineer can find multiple solutions and choose the best one for the purpose of the design.

Do not be satisfied when you got one solution for an exercise. Always try to find better solutions.

End of the text material